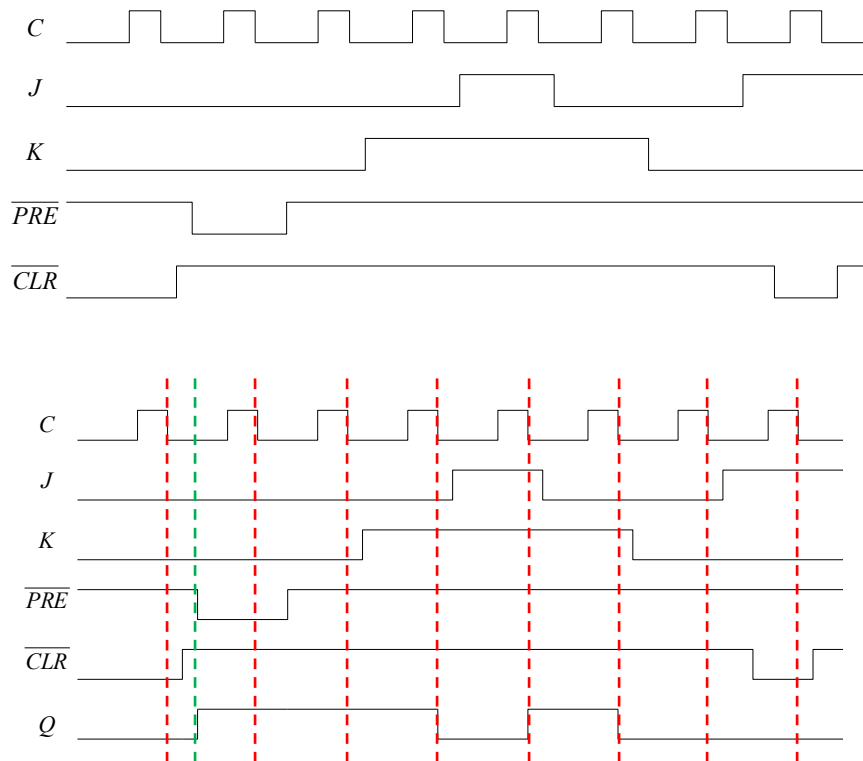



EE 2000 Logic Circuit Design
Semester A 2024/25

Tutorial 7




1. The waveforms are applied to the inputs of an SN7476 *JK* flip-flop (negative-edge triggered). Complete the timing diagram by drawing the waveforms of flip-flop output *Q*.




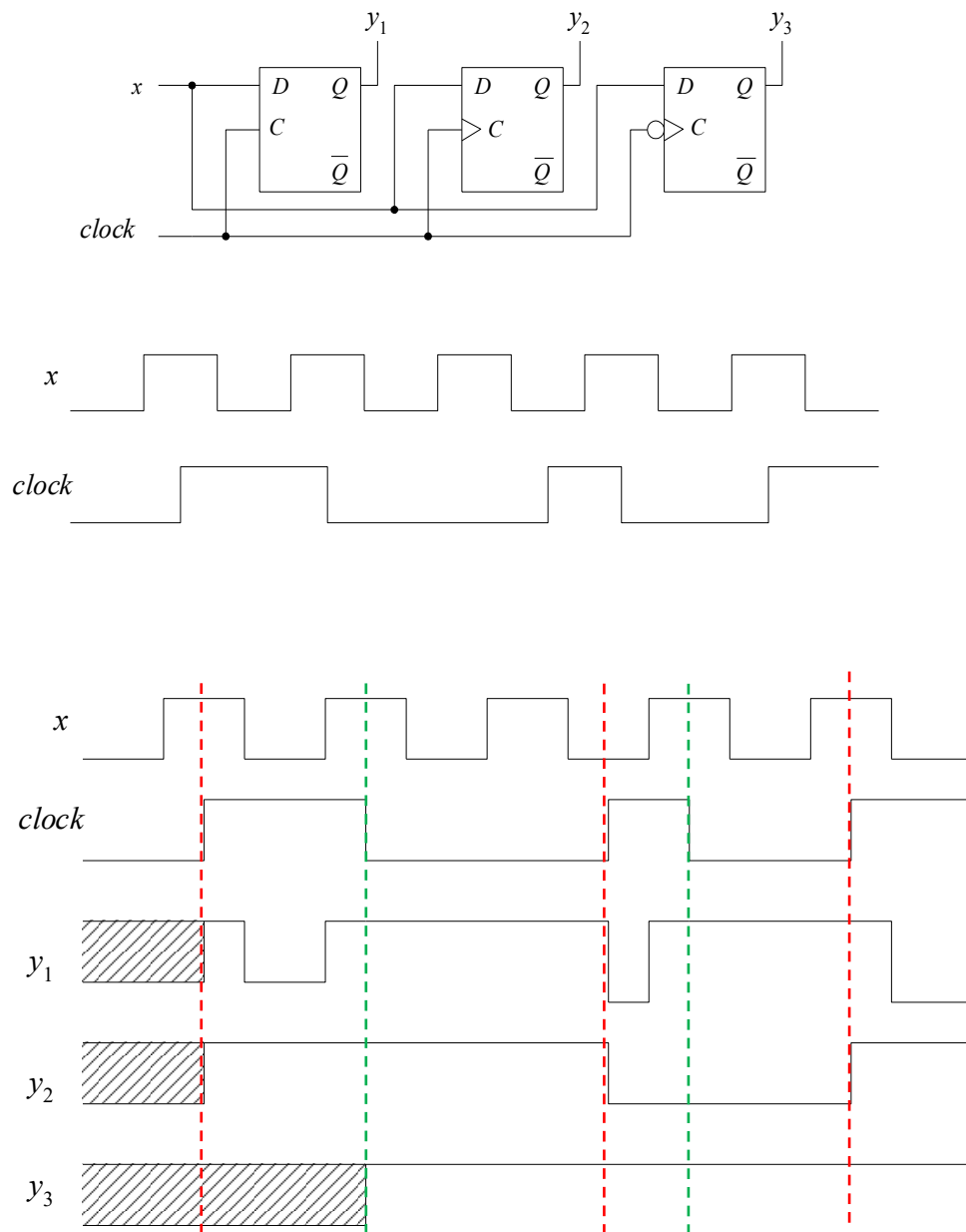
2. The circuit contains a D latch, a positive-edge-triggered D flip-flop, and a negative edge-triggered D flip-flop. Complete the timing diagram for the waveform of signals y_1 , y_2 and y_3 .



  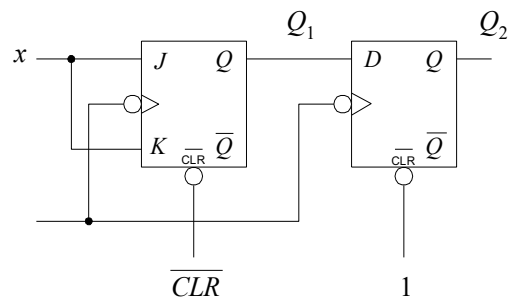3. The circuit contains a negative edge-triggered JK flip-flop and a D flip-flop. Complete the timing diagram by drawing the waveforms of signals Q_1 and Q_2 .



  4. Complete the timing diagram by drawing the waveforms of signals q_1 and q_2 .



$$D = x \quad K = \overline{q_1} \quad J = xq_1 \quad z = q_1q_2$$

