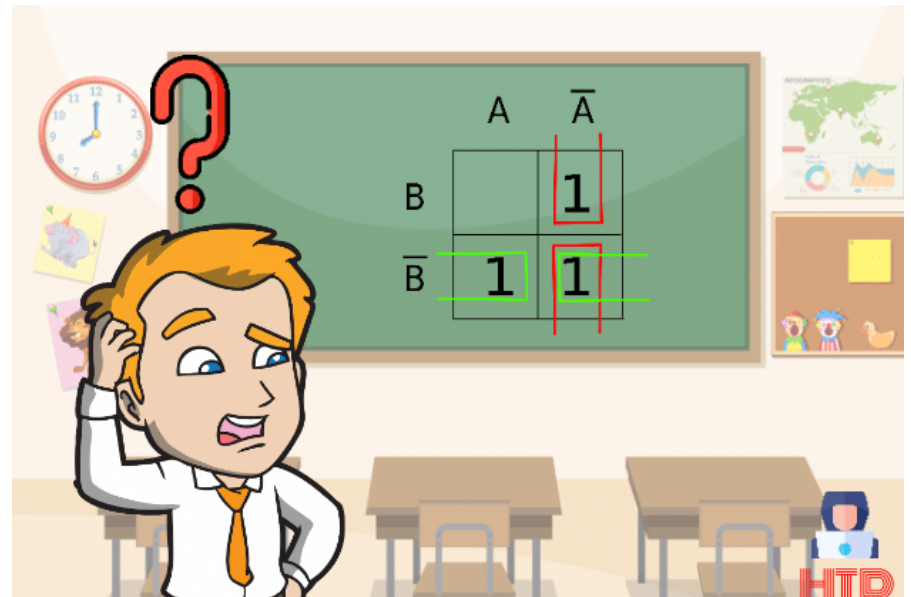


# EE2000 Logic Circuit Design

---

## Lecture 2 – Karnaugh Map and Quine-McCluskey (QM) Method



# What have we learnt so far?

1.1 Basic Logic Gates

1.2 Logic Circuit, Truth Table and Boolean Expression

1.3 Sum of Products vs Product of Sums and Canonical Form

1.4 Simplification using Boolean Algebra

- Based on experience

- Trial and error

Any systematic approach?

# What will you learn?

- 2.1 What is Karnaugh map
- 2.2 Simplify a Boolean Function using Karnaugh map
- 2.3 Simplify a Boolean function with Don't Care cases
- 2.4 Simplify a Boolean Function using Quine-McCluskey method
- 2.5 Simplify Boolean Functions (Multiple Outputs) by identifying common terms


# 2.1 Karnaugh Map

- In 1953, Maurice Karnaugh introduced a map method known as **Karnaugh map (K-map)**
- A straightforward procedure for minimizing Boolean functions in a tabular form
- **Graphical** representation of a truth table
- **Minterm** is used in the cell of the K-map
- $n$ -variable function has  $2^n$  cells:
  - Two-variable K-map has 4 cells
  - Three-variable K-map has 8 cells
  - Four-variable K-map has 16 cells

# Two-variable K-map

Variables are labeled on the upper left corner of the map

This column represents  $a = 1$

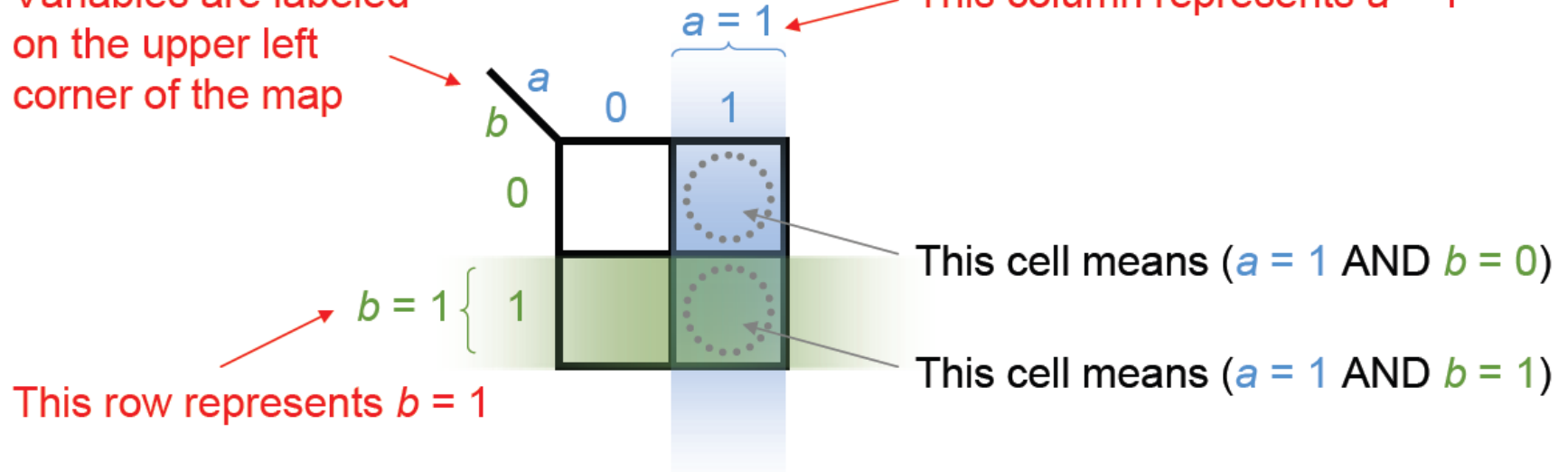

$b$	$a$	0	1
0		$a'b'$	$ab'$
1		$a'b$	$ab$

$b$	$a$	0	1
0		$m_0$	$m_2$
1		$m_1$	$m_3$

Minterm representations

# Plotting Functions in K-map

$f(a, b) = \sum m(0, 3)$  Canonical form (contains Minterm)

$b \backslash a$	0	1
	0	1
0	1	0
1	0	1

or

$b \backslash a$	0	1
	0	1
0	1	
1		1

Put a 0 or leave blank for those minterms not included in the function

Put a 1 in the corresponding cells

$f(a, b) = a'b' + ab'$  Function must be formed by Minterm

$b \backslash a$	0	1
	0	1
0	1	1
1	0	0

or

$b \backslash a$	0	1
	0	1
0	1	1
1		





Functions represented graphically with corresponding minterm cells labeled to value 1

# Example

Simplify  $f(a, b) = \Sigma m(0, 1, 3)$

Adjacency:  $a'b + ab = b$

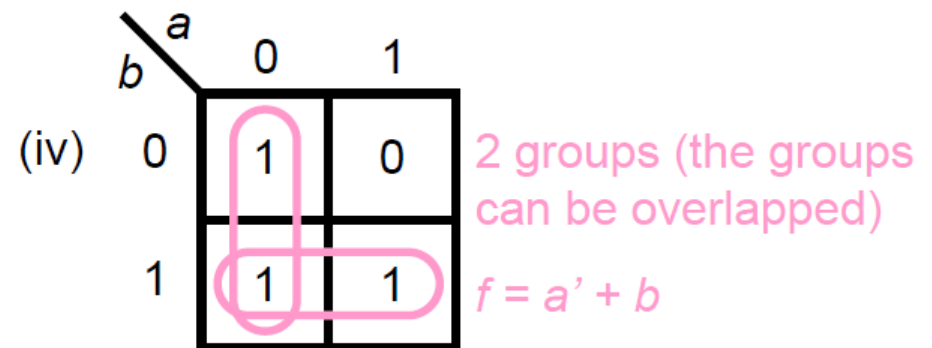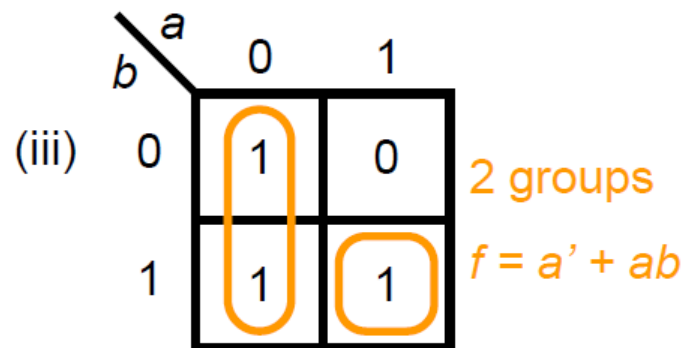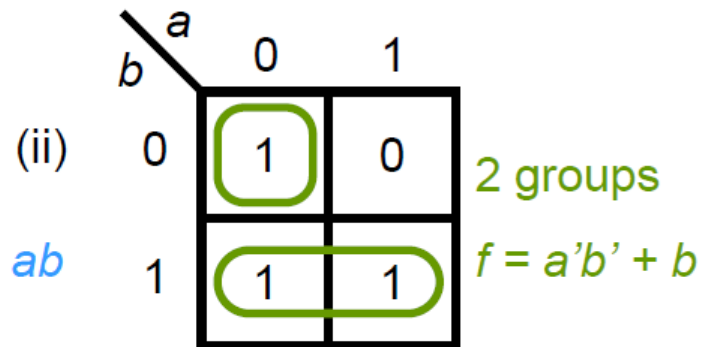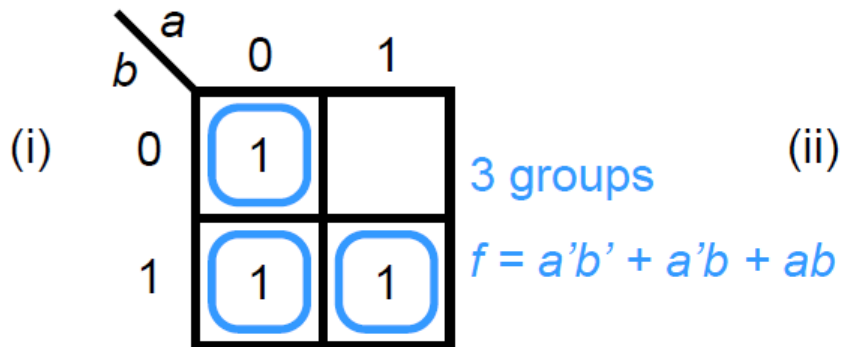*Many ways to group them. Which is the best solution?*



# Three-variable K-map

$a=0$   $b=1$

$c \backslash ab$	00	01	11	10
0	$a'b'c'$	$a'bc'$	$abc'$	$ab'c'$
1	$a'b'c$	$a'bc$	$abc$	$ab'c$

$c \backslash ab$	00	01	11	10
0	$m_0$	$m_2$	$m_6$	$m_4$
1	$m_1$	$m_3$	$m_7$	$m_5$

$c \backslash ab$	00	01	11	10
0				
1				

$b = 1$


$c = 1$

$a = 1$

- Cells are not organized in numerical order.
- Only 1-bit difference between two adjacent cells.
- Why?



# Gray code in K-map

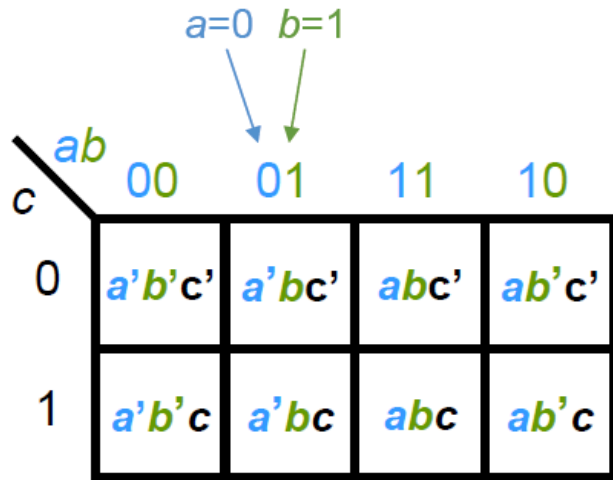

- Adjacent cells have 1-bit (1-variable) difference only

$$a'bc' \text{ and } abc'$$

- Forming a pair of adjacent binary combinations with neighboring cells.

$$a'bc' + abc' = bc'(a' + a) = bc'$$

**Rule of thumb:** Group adjacent 1's on the map to form the simplified product terms.

# Simplification of Product Terms

Example: Simplify  $f(a, b, c) = \sum m(6, 7)$

c \ ab	00	01	11	10
0			1	
1			1	

This group contains both 0 and 1 for  $c$  (i.e. no longer depends on  $c$ , depends on  $a$  and  $b$  only)

c \ ab	00	01	11	10
0	$m_0$	$m_2$	$m_6$	$m_4$
1	$m_1$	$m_3$	$m_7$	$m_5$

Using Boolean Algebra:

$$f(a, b, c) = abc' + abc$$

$$= ab \text{ (adjacency)}$$

Only one-variable difference

Whenever we group two adjacent cells on the map, they can form a product term with one less variables!

# More Examples

		<i>ab</i>			
		00	01	11	10
<i>c</i>	0			1	1
	1				

$$f(a, b, c) = abc' + ab'c'$$

$$= ac' \text{ (adjacency)}$$

We can even group adjacent 1's across the edges:


		<i>ab</i>			
		00	01	11	10
<i>c</i>	0	1			1
	1				

$$f(a, b, c) = a'b'c' + ab'c'$$

$$= b'c' \text{ (adjacency)}$$

Also one-variable difference!

# Wrap Around Adjacency

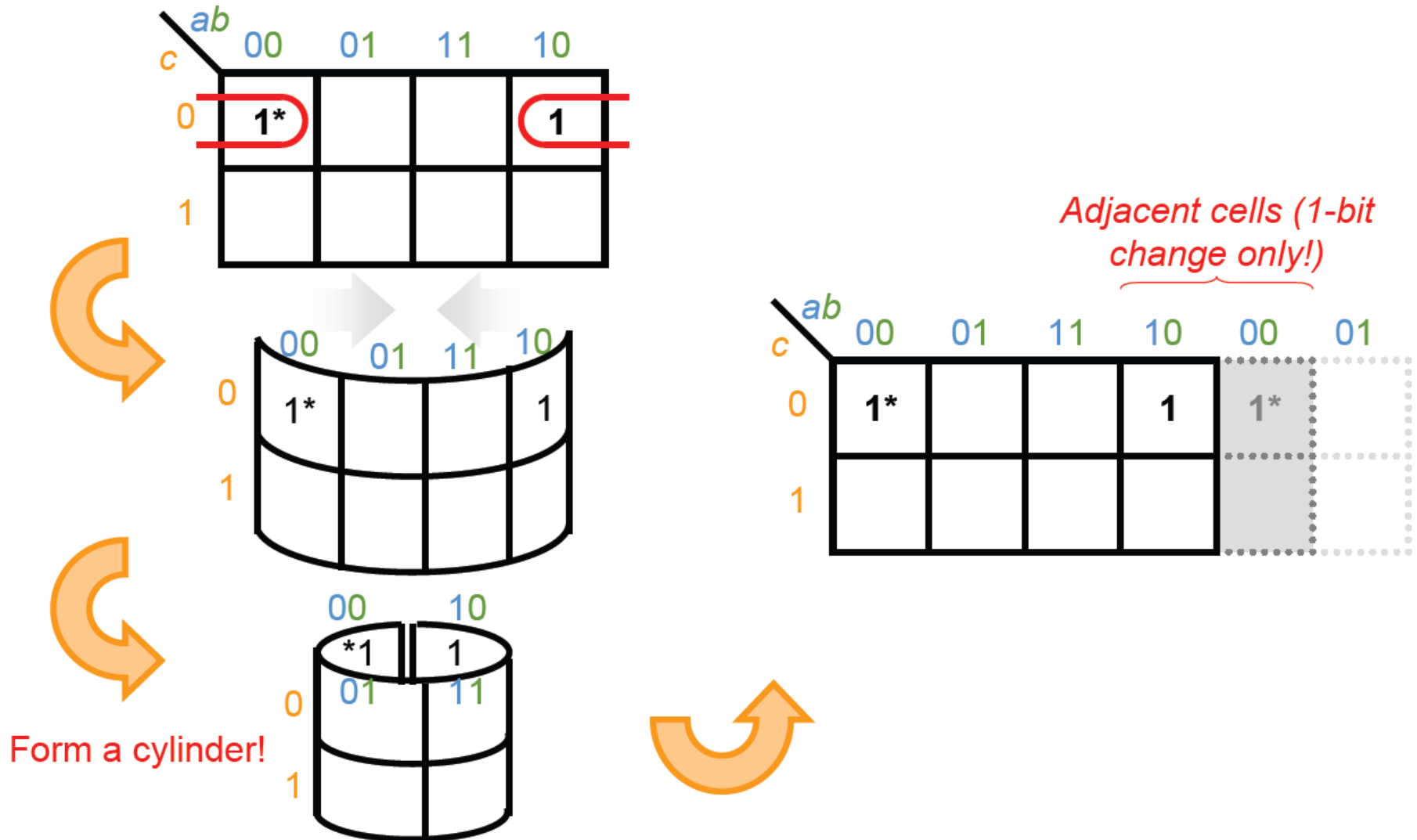

# What If We do not use Gray Code?

We can group these two adjacent 1's:

$c \backslash ab$		00	01	11	10
		0	1	1	0
0			1	1	
1					

$$f(a, b, c) = a'bc' + abc'$$

$$= bc'$$

But not these two: *Incorrect arrangement*

$c \backslash ab$		00	01	10	11
		0	1	1	0
0			1	1	
1					

$$f(a, b, c) = a'bc' + ab'c'$$

$$= c' (a'b + ab')$$

two-variable difference!

Cannot be simplified into a single term!

# Horizontal vs Vertical K-map

Label rows with first variable,  
columns with the others



$a \backslash bc$	00	01	11	10
0	$m_0$	$m_1$	$m_3$	$m_2$
1	$m_4$	$m_5$	$m_7$	$m_6$

Vertical orientation of  
three-variable K-map

$bc \backslash a$	0	1
00	$m_0$	$m_4$
01	$m_1$	$m_5$
11	$m_3$	$m_7$
10	$m_2$	$m_6$

Although there are different ways  
drawing the K-Maps, we use the same  
method to group the adjacent 1's!




# Four-variable K-map

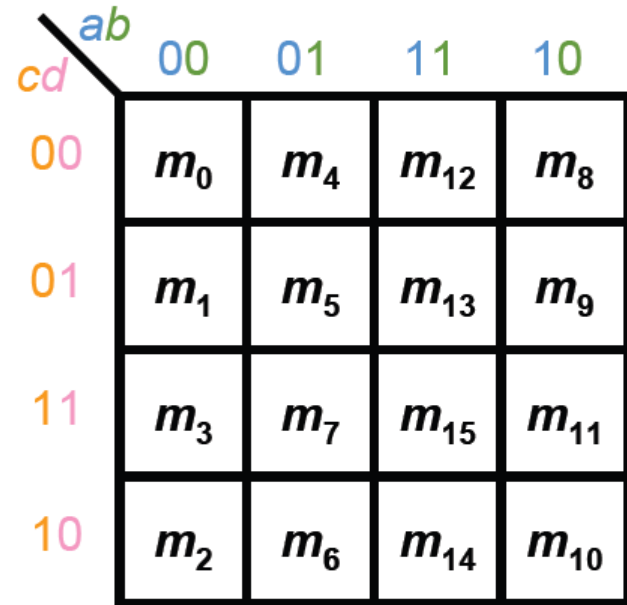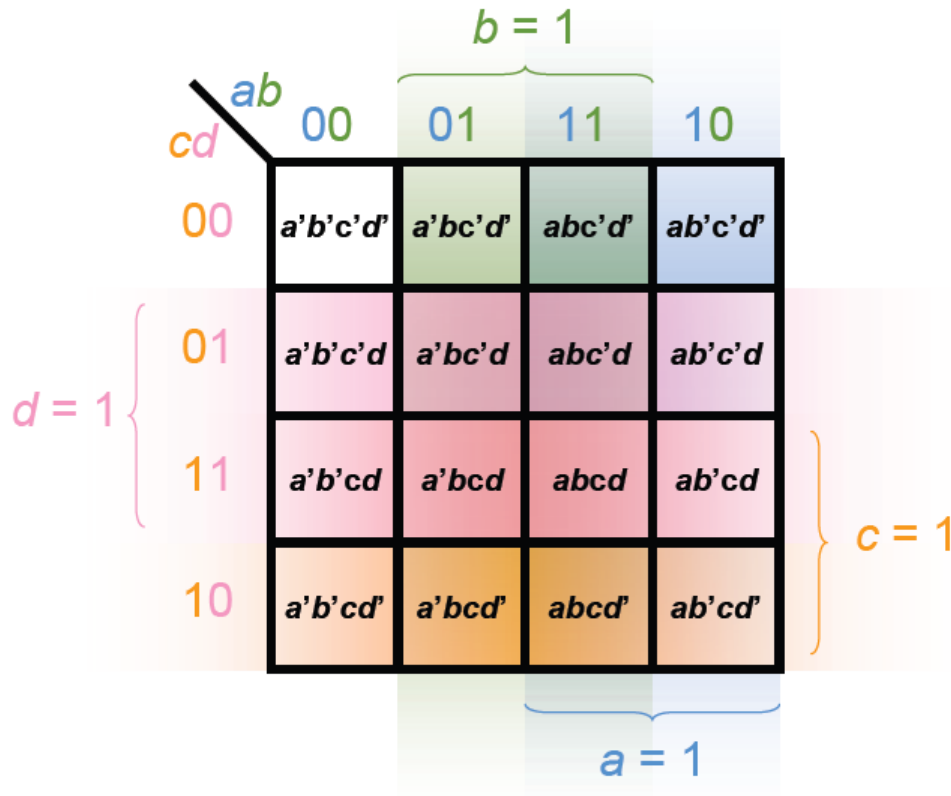

Note the Gray code order of the rows and columns


# Wrap-around Adjacency

$ab$		00	01	11	10
$cd$	00	$m_0$	$m_4$	$m_{12}$	$m_8$
	01	$m_1$	$m_5$	$m_{13}$	$m_9$
	11	$m_3$	$m_7$	$m_{15}$	$m_{11}$
	10	$m_2$	$m_6$	$m_{14}$	$m_{10}$

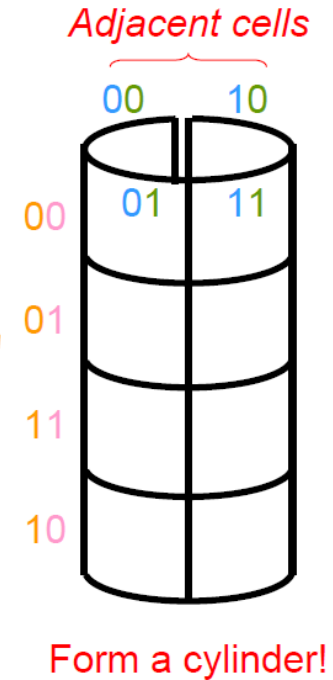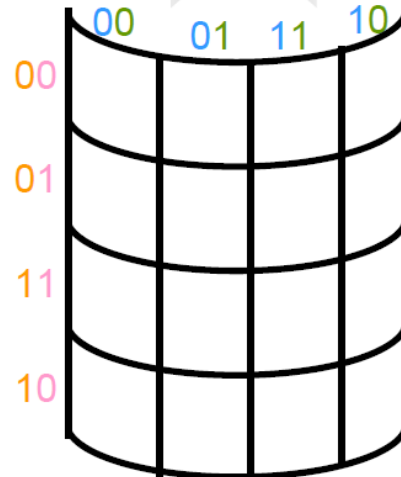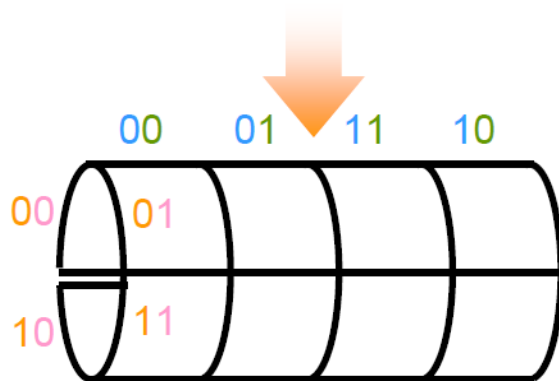




# Imagine the Map as...

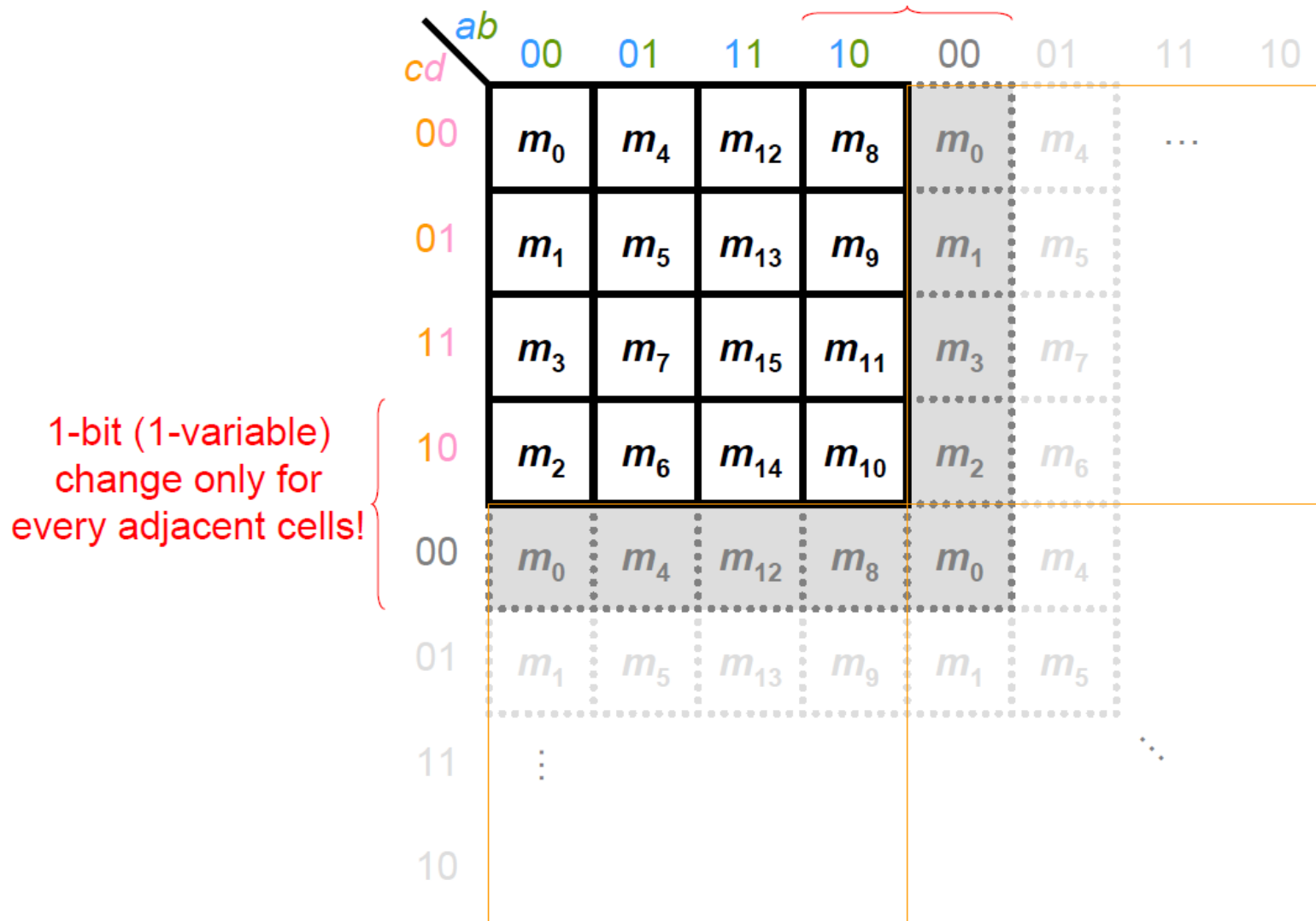


# Types of Group Size

Group of 2 adjacent cells

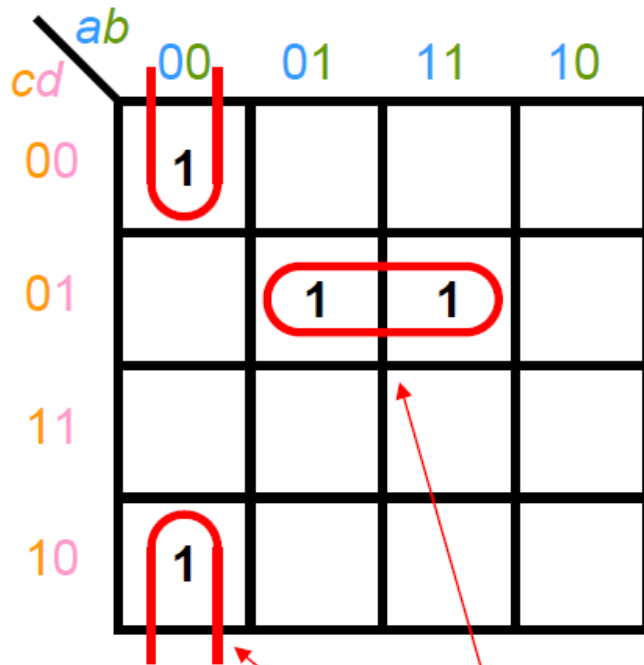

$$f(a, b, c, d) = a'b'd' + bc'd$$

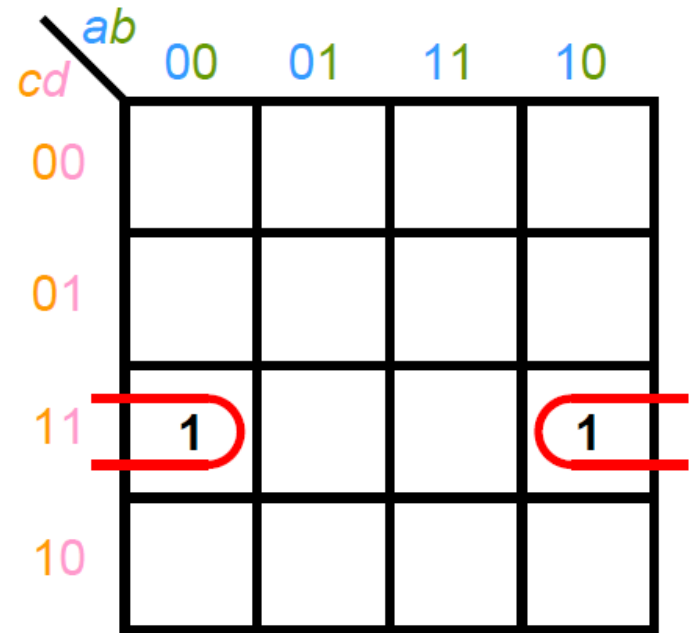


$$f(a, b, c, d) = b'cd$$

# Types of Group Size

Group of 4 adjacent cells

<i>ab</i>	00	01	11	10
<i>cd</i> 00				
01				
11	1	1	1	1
10				

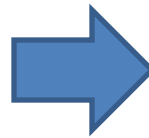
$$\begin{aligned}f(a, b, c, d) &= a'cd + acd \\ &= cd\end{aligned}$$




<i>ab</i>	00	01	11	10
<i>cd</i> 00				
01				
11	1	1	1	1
10				

$$f(a, b, c, d) = cd$$

# Types of Group Size

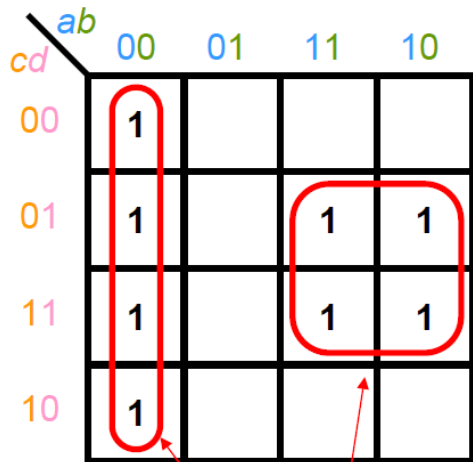


$$f(a, b, c, d) = a'b' + ad$$

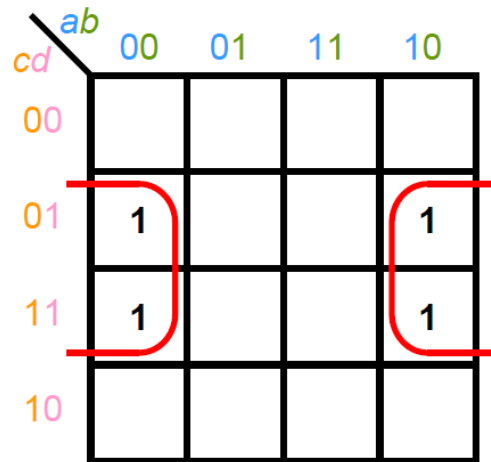


$$f(a, b, c, d) = b'd$$

Across 4 corners:

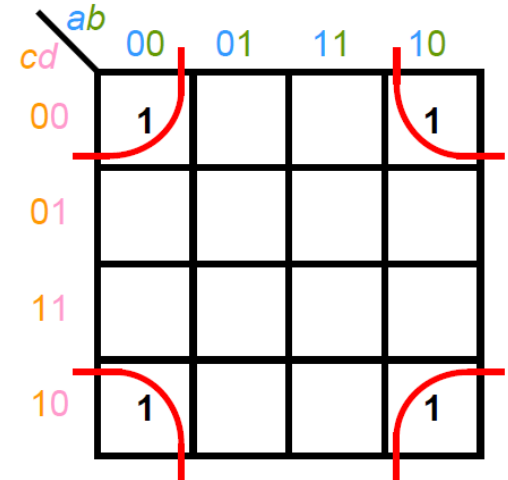


$$f(a, b, c, d) = b'd'$$

# Are These Adjacent Cells?

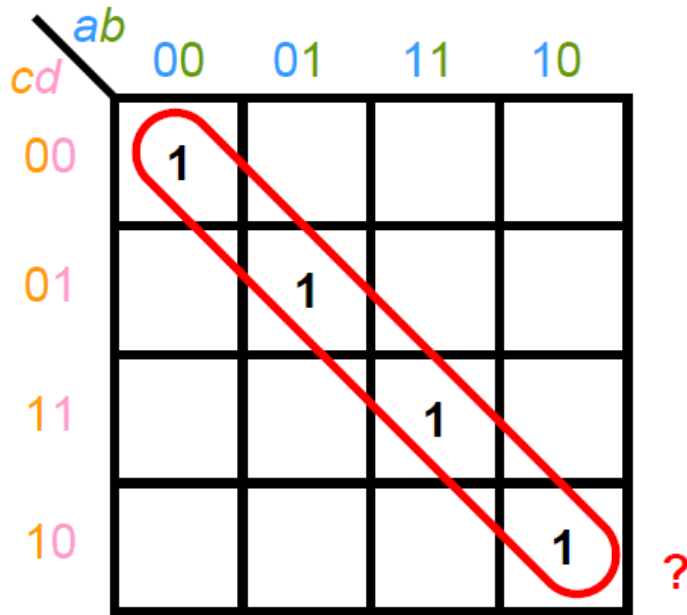

Diagonal?

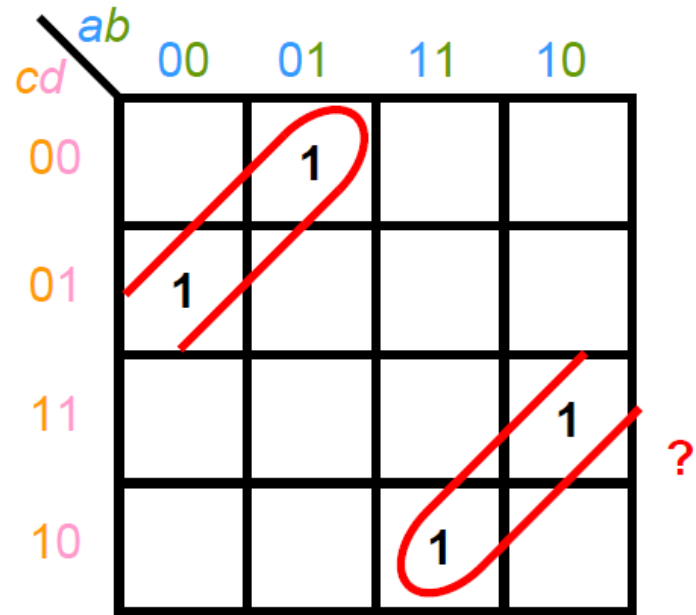

Magic square?

# Types of Group Size


Group of 8 adjacent cells

A 4x4 Karnaugh map for variables a, b, c, and d. The columns are labeled with ab (00, 01, 11, 10) and the rows with cd (00, 01, 11, 10). The map shows 1s in the first and last rows (cd=00 and cd=10) for all values of ab. Two red lines group these 1s into a single group of 8 cells, representing the simplified function d'.


<i>cd</i> \ <i>ab</i>	00	01	11	10
00	1	1	1	1
01				
11				
10	1	1	1	1

$$f(a, b, c, d) = d'$$

# Summary

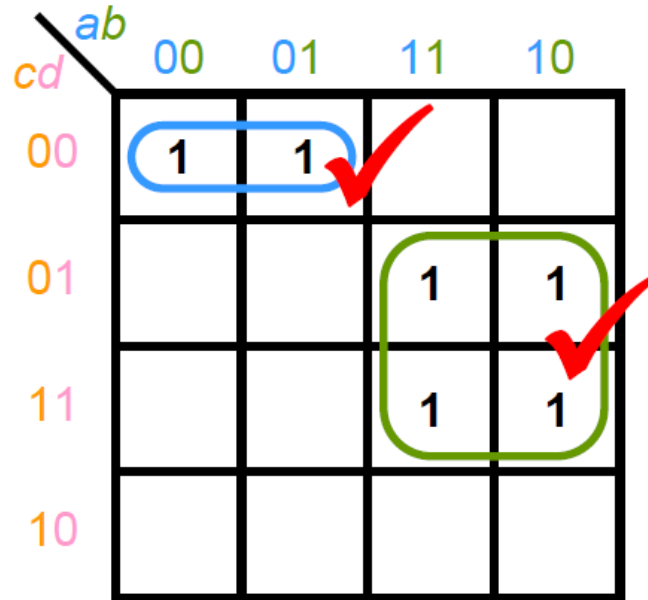

Group size is power of 2 (e.g. 2, 4, 8)

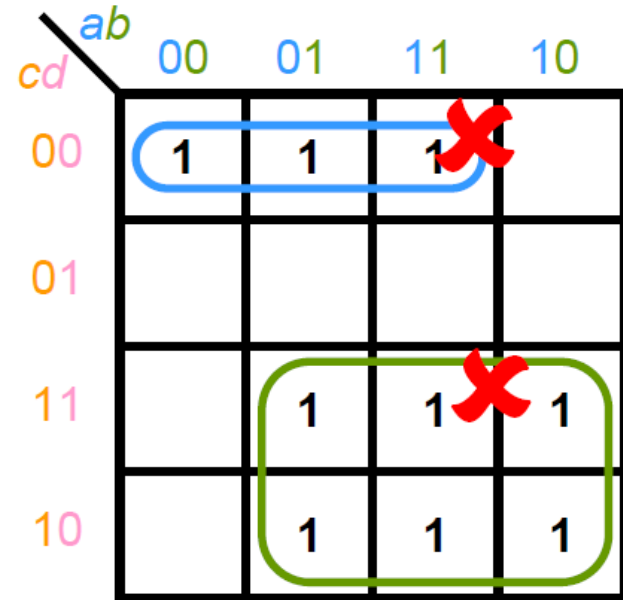

Other group size is illegal

- Booleans function to be minimized by K-map are always in Canonical SOP or POS (will discuss later) form
- Arrange cells in 1-bit difference
- Group adjacent cells in group size of  $2^n$ , e.g. 2, 4, 8
- Apply adjacency law

## 2.2 Minimization using Karnaugh Map


- Group adjacent cells in group size of  $2^n$ , e.g. 2, 4, 8
- Rules:
  1. Find the fewest groups that can cover all cells marked with 1s.
  2. The groups should be as large as possible.
- Goal:
  1. Reduce the number of product terms to minimum
  2. Save the cost



# Example

Simplify  $f(a, b, c) = \sum m(0, 1, 2, 3, 4, 5)$


*Which solution is better?*

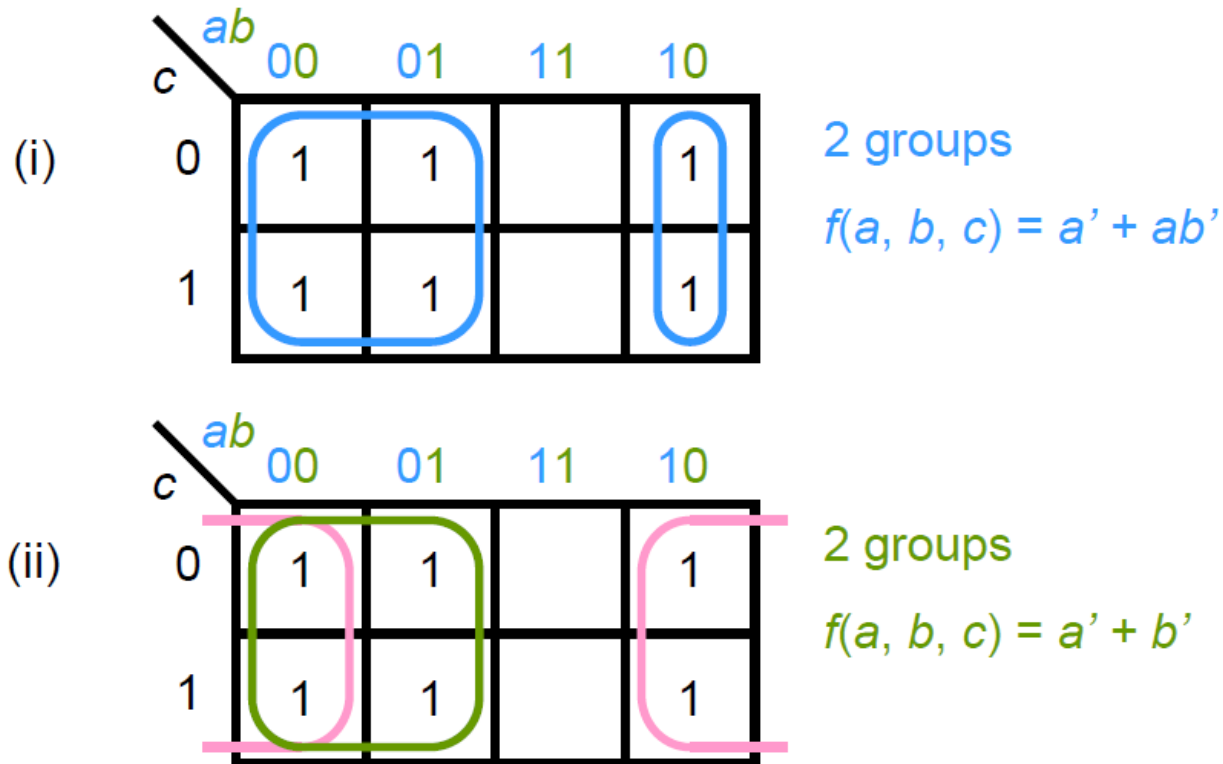


Groups should be as large as possible!
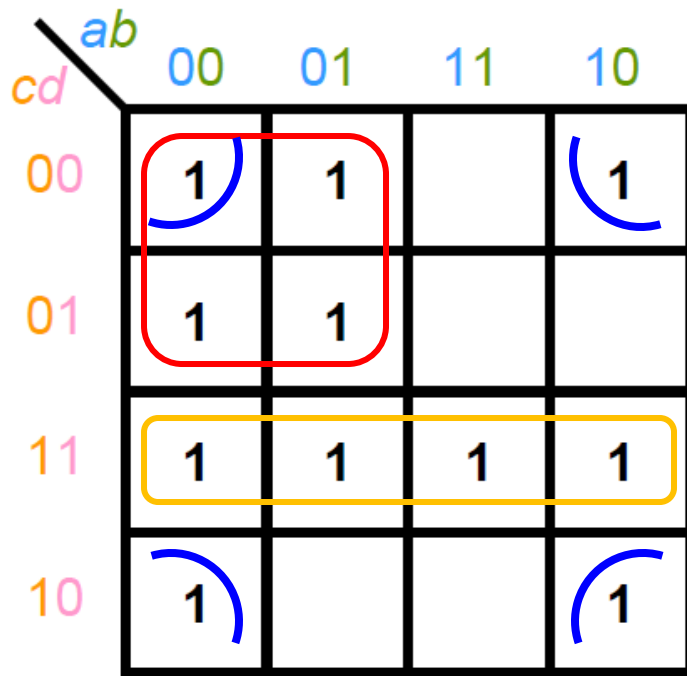
# Example


Simplify  $f(a, b, c, d) = \sum m(0, 1, 2, 3, 4, 5, 7, 8, 10, 11, 15)$



# Redundant Grouping

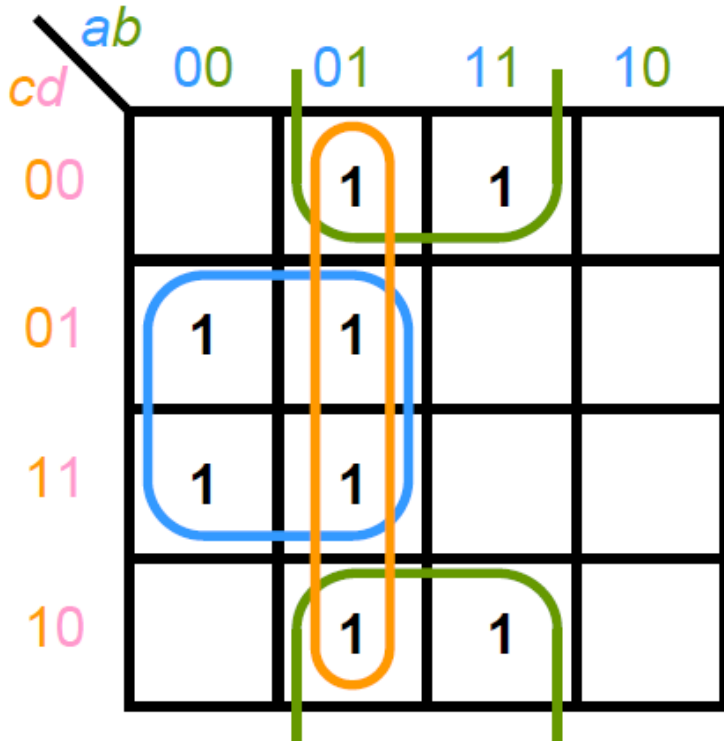

Three groups overlapped!

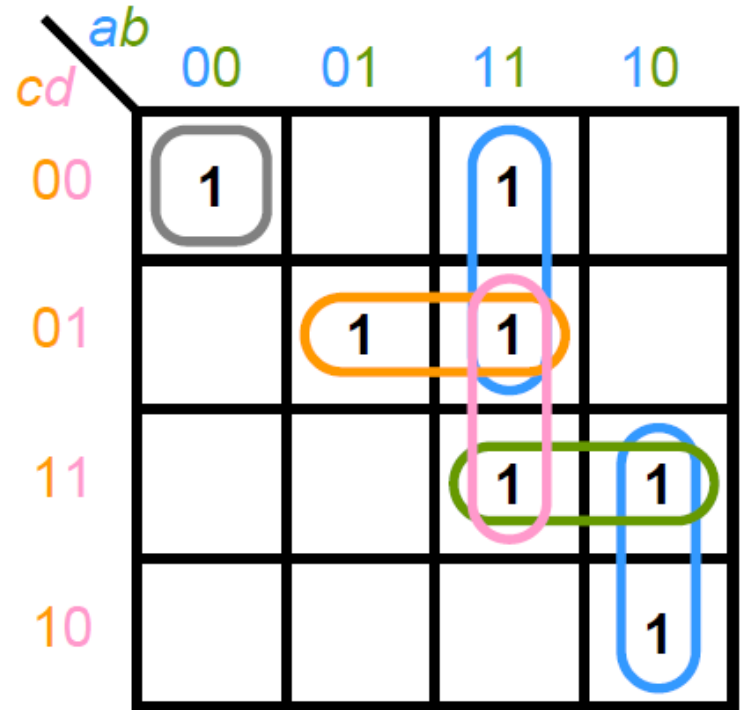


Too many overlaps!
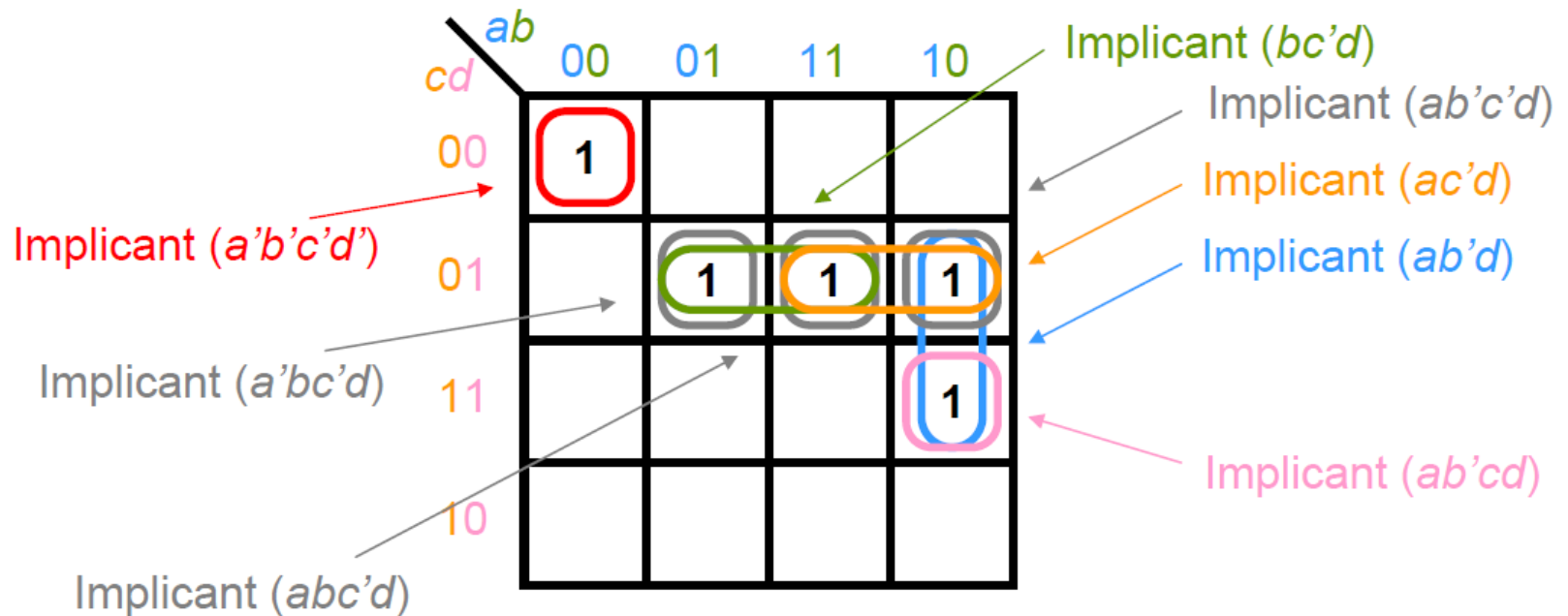
# Terminology


**Implicant:** A product term is an implicant such that the function is 1 whenever the product term is 1.

- In K-map, an implicant is a rectangle of 1, 2, 4, 8,... of 1's.



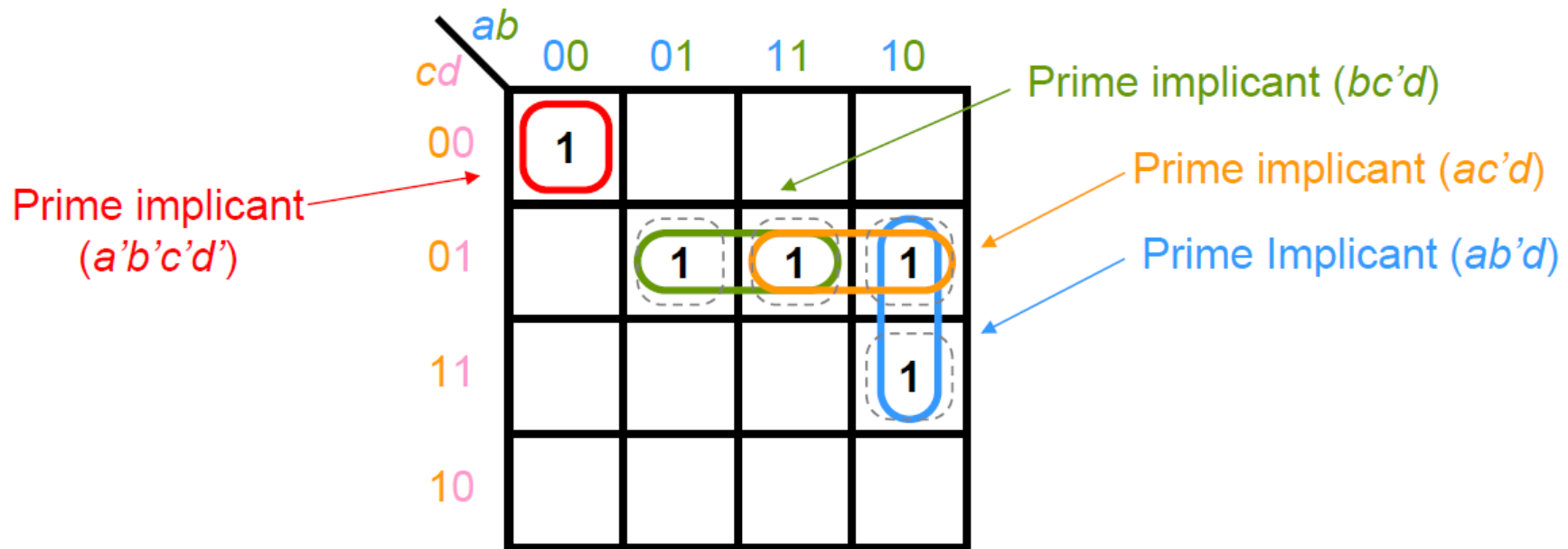
# Terminology

**Prime Implicant:** An implicant that is not fully contained in any one other implicant.


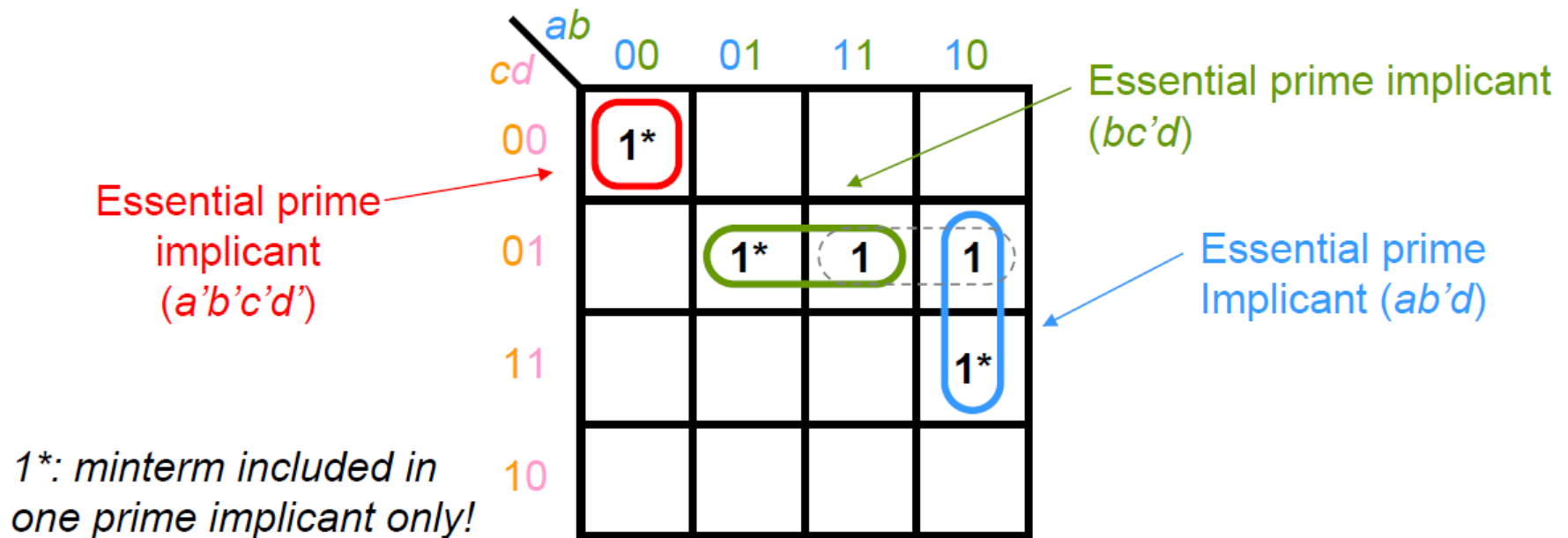
# Terminology

**Essential Prime Implicant:** If a minterm is included in only one prime implicant, that prime implicant is essential prime implicant.



# Systematic Approach


## ➤ Rules:

1. Find the fewest groups that can cover all cells marked with 1s.
2. The groups should be as large as possible.

## ➤ Approach:


1. Determine all PIs.
2. Select EPIs.
3. Add PI to include the remaining minterm.

# Previous Example

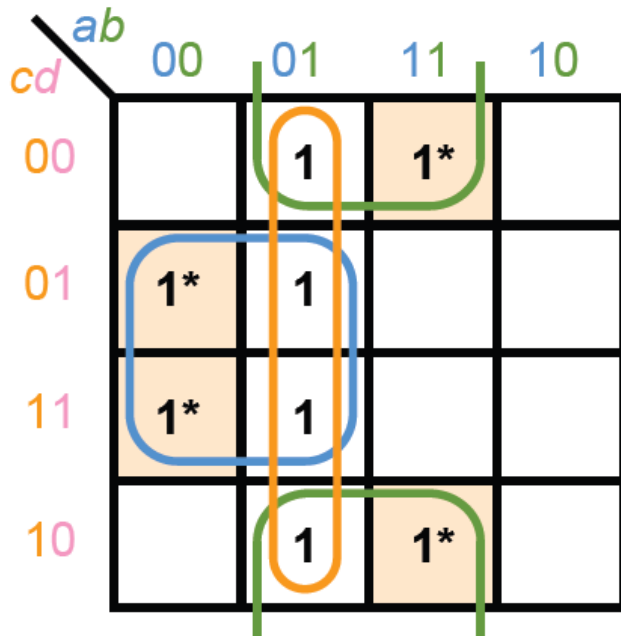

PIs:

EPI:


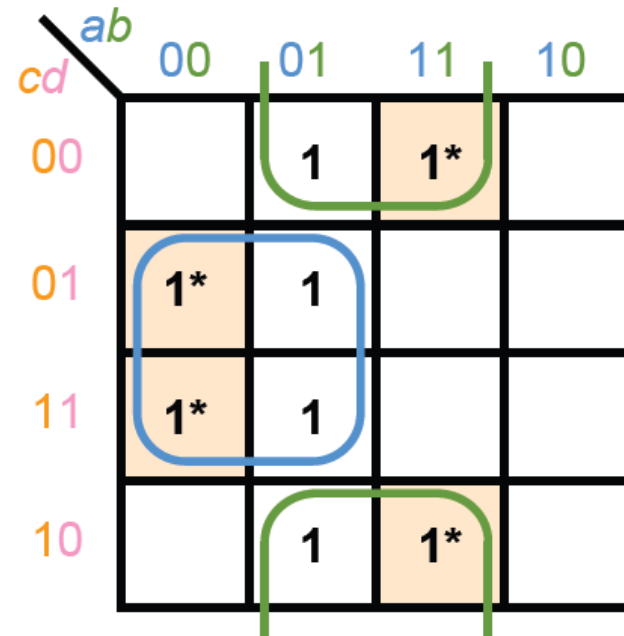


Select the essential prime implicants and no remaining minterms left!

$$f(a, b, c, d) = a'd + bd'$$




# Previous Example

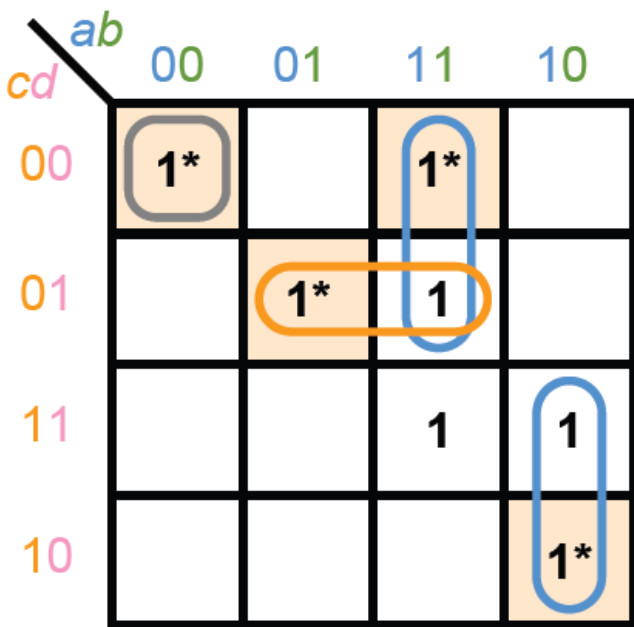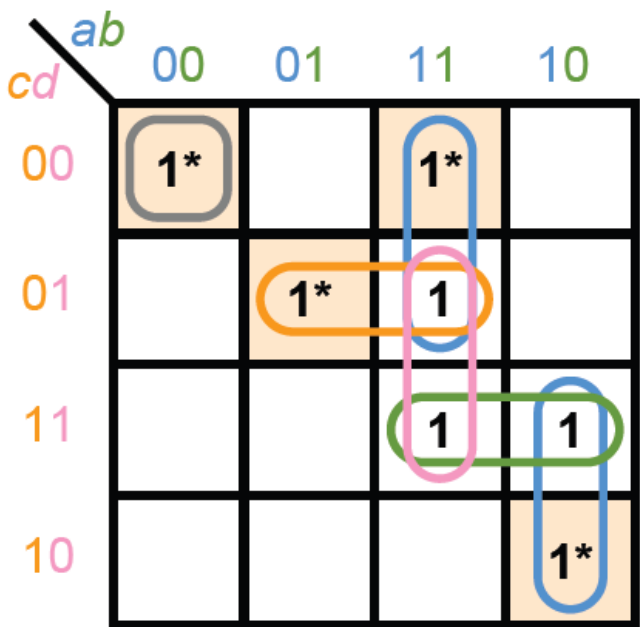

Select the essential prime implicants first


Still have a remaining minterm!

# Previous Example

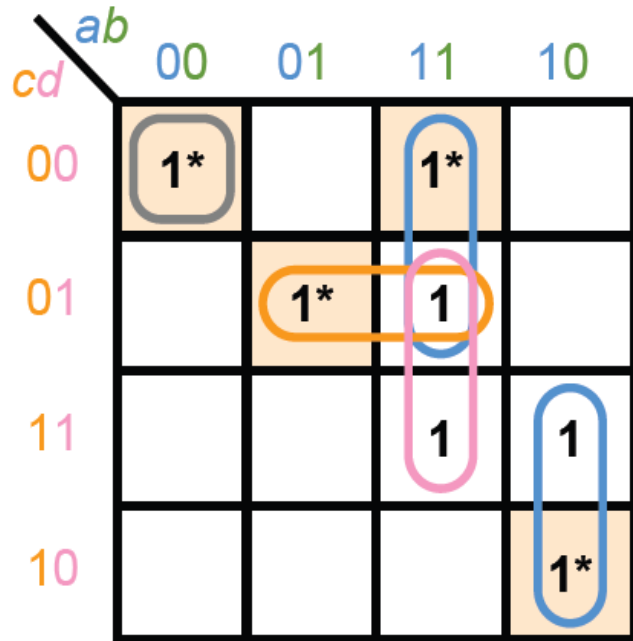

$$f(a, b, c, d) = a'b'c'd' + abc' + ab'c + bc'd + abd$$

or

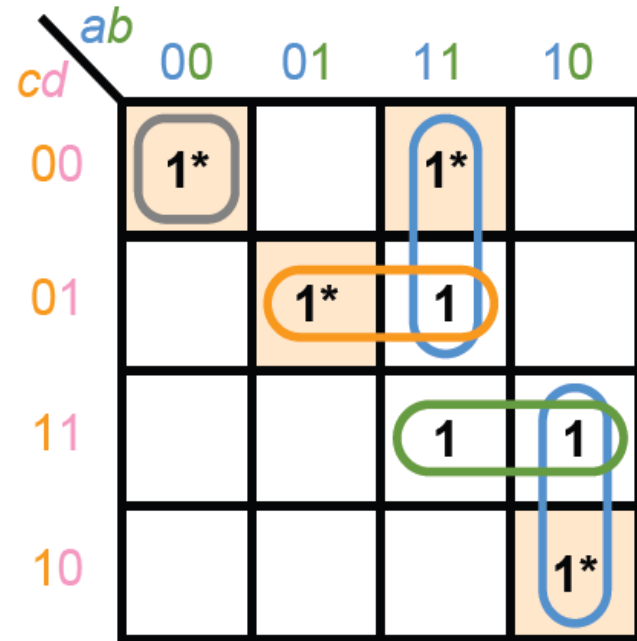

$$f(a, b, c, d) = a'b'c'd' + abc' + ab'c + bc'd + acd$$

We can choose either  or 

# Exercise

1. Identify all PIs.
2. Select all EPIs.
3. Add PIs of remaining minterms.

<i>cd</i> \ <i>ab</i>	00	01	11	10
	00	01	11	10
00	1	1	1	1
01				1
11		1		1
10	1	1	1	

# Exercise

1. Identify all PIs.
2. Select all EPIs.
3. Add PIs of remaining minterms.

$ab$		00	01	11	10
$cd$	00	1	1	1	1
	01				1
	11		1		1
	10	1	1	1	

$ab$		00	01	11	10
$cd$	00	1	1	1	1
	01				1
	11		1		1
	10	1	1	1	

# Exercise

Find all minimum sum of products expressions for the following K-map.

$ab$		00	01	11	10
$cd$	00	1	1		1
	01		1	1	1
	11		1	1	
	10	1	1		1

# Exercise

<i>cd</i>	<i>ab</i>			
	00	01	11	10
00	1	1		1
01				
11		1		1
10	1			

<i>cd</i>	<i>ab</i>			
	00	01	11	10
00	1	1		1
01		1	1	1
11		1	1	
10	1	1		1

# How about POS?

[Step 1] Group the 0s to obtain the complement of the  $f$  in **SOP** form

[Step2] Apply DeMorgan's Theorem to find  $f$  in **POS** form OR express them in Maxterm

# Example

Simplify  $f(a, b, c, d) = \Sigma m(0, 1, 2, 5, 8, 9, 10)$  in POS form

	$ab$	00	01	11	10
$cd$					
00		1	0	0	1
01		1	1	0	1
11		0	0	0	0
10		1	0	0	1

Fill the 1s and 0s into the map

	$ab$	00	01	11	10
$cd$					
00		1	0	0	1
01		1	1	0	1
11		0	0	0	0
10		1	0	0	1

Group the 0s using the same procedure as grouping the 1s

$$f'(a, b, c, d) = ab + cd + bd'$$

$$f(a, b, c, d) = (a'+b')(c'+d')(b'+d)$$



## 2.3 Boolean Functions with Don't Care Cases

The output of Boolean functions are **incompletely specified functions**,

- For some input conditions, the outputs are unspecified
- Input condition has no effects to the function
- Output values are defined as **don't Care**
- Don't Care term can be minterm / maxterms
- Don't Care term indicates by an  $\times$ ,  $d$ ,  $\phi$  or  $\varphi$

# Truth Table with Don't Care

$a$	$b$	$f$
0	0	0
0	1	1
1	0	1
1	1	X

*What the table says is:*

$f$  is 0 if  $(a = 0 \text{ AND } b = 0)$   
 $f$  is 1 if  $(a = 0 \text{ AND } b = 1), \text{ or } (a = 1 \text{ AND } b = 0)$   
 $f$  can be 0 or 1 if  $(a = 1 \text{ AND } b = 1)$

$$f(a, b) = \Sigma m(1, 2) + \Sigma d(3)$$

$a$	$b$	$f_1$	$f_2$
0	0	0	0
0	1	1	1
1	0	1	1
1	1	0	1

Both  $f_1$  or  $f_2$  of table on the left are acceptable

$$f(a, b) = \Pi M(0) \Pi d(3)$$

# Don't Care term in K-map

Which solution is better?

b \ a	0	1
	0	1
0	0	1
1	1	X

b \ a	0	1
	0	1
0	0	1
1	1	0

$f_1$  implementation

2 groups

$$f = a'b + ab'$$

b \ a	0	1
	0	1
0	0	1
1	1	1

$f_2$  implementation

2 groups

$$f = a + b$$

# Is it a Good Solution?

Simplify  $f(a, b, c, d) = \sum m(1, 3, 7, 11, 15) + \sum d(0, 2, 5)$

$cd \backslash ab$	00	01	11	10
00	X	0	0	0
01	1	X	0	0
11	1	1	1	1
10	X	0	0	0

$cd \backslash ab$	00	01	11	10
00	X	0	0	0
01	1	X	0	0
11	1	1	1	1
10	X	0	0	0

$$f(a, b, c, d) = a'b'd + cd$$

# Other Solutions

1. Identify PIs that must include all 1s but don't care term  $\times$  is optional.
2. Use  $\times$  when possible to create larger group size.
3. Select the EPIs first, then remaining PIs

	$ab$			
	00	01	11	10
$cd$ 00	X	0	0	0
01	1	X	0	0
11	1	1	1	1
10	X	0	0	0

$$f(a, b, c, d) = a'b' + cd$$

	$ab$			
	00	01	11	10
$cd$ 00	X	0	0	0
01	1	X	0	0
11	1	1	1	1
10	X	0	0	0

$$f(a, b, c, d) = a'd + cd$$

Choose to include those Xs that give largest PIs

# Exercise

Find all minimum sum of products and all minimum product of sums expressions for the following Boolean Function.

$$f(a, b, c, d) = \sum m(1, 3, 4, 6, 11) + \sum d(0, 8, 10, 12, 13)$$

		<i>ab</i>			
		00	01	11	10
<i>cd</i>	00	$m_0$	$m_4$	$m_{12}$	$m_8$
	01	$m_1$	$m_5$	$m_{13}$	$m_9$
	11	$m_3$	$m_7$	$m_{15}$	$m_{11}$
	10	$m_2$	$m_6$	$m_{14}$	$m_{10}$

# Exercise

$$f(a, b, c, d) = \sum m(1, 3, 4, 6, 11) + \sum d(0, 8, 10, 12, 13)$$

$cd \backslash ab$	00	01	11	10
00				
01	<input type="checkbox"/>	<input type="checkbox"/>		
11	<input type="checkbox"/>			
10				

$cd \backslash ab$	00	01	11	10
00				
01	<input type="checkbox"/>	<input type="checkbox"/>		
11	<input type="checkbox"/>			
10				

$cd \backslash ab$	00	01	11	10
00				
01	<input type="checkbox"/>	<input type="checkbox"/>		
11	<input type="checkbox"/>			
10				

# Exercise

$$f(a, b, c, d) = \sum m(1, 3, 4, 6, 11) + \sum d(0, 8, 10, 12, 13)$$

$cd \backslash ab$	00	01	11	10
00				
01	<input type="checkbox"/>	<input type="checkbox"/>		
11	<input type="checkbox"/>			
10				

$cd \backslash ab$	00	01	11	10
00				
01	<input type="checkbox"/>	<input type="checkbox"/>		
11	<input type="checkbox"/>			
10				



# 5-variable K-map

$V=0$

WX \ YZ				
	00	01	11	10
00	$m_0$	$m_1$	$m_3$	$m_2$
01	$m_4$	$m_5$	$m_7$	$m_6$
11	$m_{12}$	$m_{13}$	$m_{15}$	$m_{14}$
10	$m_8$	$m_9$	$m_{11}$	$m_{10}$

$V=1$

WX \ YZ				
	00	01	11	10
00	$m_{16}$	$m_{17}$	$m_{19}$	$m_{18}$
01	$m_{20}$	$m_{21}$	$m_{23}$	$m_{22}$
11	$m_{28}$	$m_{29}$	$m_{31}$	$m_{30}$
10	$m_{24}$	$m_{25}$	$m_{27}$	$m_{26}$

# 6-variable K-map

CD

EF

00011110

00	m0	m4	m12	m8
01	m1	m5	m13	m9
11	m3	m7	m15	m11
10	m2	m6	m14	m10

AB=00

CD

EF

00011110

00	m32	m36	m44	m40
01	m33	m37	m45	m41
11	m35	m39	m47	m43
10	m34	m38	m46	m42

AB=10

CD

EF

00011110

00	m16	m20	m28	m24
01	m17	m21	m29	m25
11	m19	m23	m31	m27
10	m18	m22	m30	m26

AB=01

CD

EF

00011110

00	m48	m52	m60	m56
01	m49	m53	m61	m57
11	m51	m55	m63	m59
10	m50	m54	m62	m58

AB=11

## 2.4 Quine-McCluskey (QM) Method

- Developed by W. V. Quine and E. J. McCluskey in 1956
- Functionally identical to Karnaugh map
- More efficient in computer algorithms
- Ease to handle large number of variables

For number of variables that is less than or equal to 4, we use K-map; otherwise, QM method will be more efficient.

# Procedure of QM-method (4-variable)

## Step 1: Partition (Group minterms by the number of 1's)

$w$	$x$	$y$	$z$	Minterms
0	0	0	0	$m_0$
0	0	0	1	$m_1$
0	0	1	0	$m_2$
0	0	1	1	$m_3$
0	1	0	0	$m_4$
0	1	0	1	$m_5$
0	1	1	0	$m_6$
0	1	1	1	$m_7$
1	0	0	0	$m_8$
1	0	0	1	$m_9$
1	0	1	0	$m_{10}$
1	0	1	1	$m_{11}$
1	1	0	0	$m_{12}$
1	1	0	1	$m_{13}$
1	1	1	0	$m_{14}$
1	1	1	1	$m_{15}$



Minterms	$wxyz$
$m_0$	0000
$m_1$	0001
$m_2$	0010
$m_4$	0100
$m_8$	1000
$m_3$	0011
$m_5$	0101
$m_6$	0110
$m_9$	1001
$m_{10}$	1010
$m_{12}$	1100
$m_7$	0111
$m_{11}$	1011
$m_{13}$	1101
$m_{14}$	1110
$m_{15}$	1111

Given in test  
and exam

# Procedure of QM-method (4-variable)

## Step 1: Partition (Group minterms by the number of 1's)

Simplify  $f(a, b, c, d) = \Sigma m(1, 4, 5, 6, 8, 9, 10, 12, 14)$

Minterms	$abcd$
$m_1$	0001
$m_4$	0100
$m_8$	1000
$m_5$	0101
$m_6$	0110
$m_9$	1001
$m_{10}$	1010
$m_{12}$	1100
$m_{14}$	1110

# Procedure of QM-method (4-variable)

Step 2: Combine (Apply adjacency property to each pair of terms in consecutive groups)

- Combine adjacent group implicants into  $(n-1)$  variable implicants
- Mark the changed bit with “-” and tick the combined implicants

Minterms	<i>abcd</i>
$m_1$	0001 ✓
$m_4$	0100
$m_8$	1000
$m_5$	0101 ✓
$m_6$	0110
$m_9$	1001 ✓
$m_{10}$	1010
$m_{12}$	1100
$m_{14}$	1110

Minterms	<i>abcd</i>
$m_1, m_5$	0-01
$m_1, m_9$	-001

# Procedure of QM-method (4-variable)

Step 2: Combine (Apply adjacency property to each pair of terms in consecutive groups)

- Combine adjacent group implicants into  $(n-1)$  variable implicants
- Mark the changed bit with “-” and tick the combined implicants

Minterms	<i>abcd</i>
$m_1$	0001 ✓
$m_4$	0100 ✓
$m_8$	1000
$m_5$	0101 ✓
$m_6$	0110 ✓
$m_9$	1001 ✓
$m_{10}$	1010
$m_{12}$	1100 ✓
$m_{14}$	1110

Minterms	<i>abcd</i>
$m_1, m_5$	0-01
$m_1, m_9$	-001
$m_4, m_5$	010-
$m_4, m_6$	01-0
$m_4, m_{12}$	-100

# Procedure of QM-method (4-variable)

Step 2: Combine (Apply adjacency property to each pair of terms in consecutive groups)

- Combine adjacent group implicants into  $(n-1)$  variable implicants
- Mark the changed bit with “-” and tick the combined implicants

Minterms	<i>abcd</i>
$m_1$	0001 ✓
$m_4$	0100 ✓
$m_8$	1000 ✓
$m_5$	0101 ✓
$m_6$	0110 ✓
$m_9$	1001 ✓
$m_{10}$	1010 ✓
$m_{12}$	1100 ✓
$m_{14}$	1110

Minterms	<i>abcd</i>
$m_1, m_5$	0-01
$m_1, m_9$	-001
$m_4, m_5$	010-
$m_4, m_6$	01-0
$m_4, m_{12}$	-100
$m_8, m_9$	100-
$m_8, m_{10}$	10-0
$m_8, m_{12}$	1-00



# Procedure of QM-method (4-variable)

Step 2: Combine (Apply adjacency property to each pair of terms in consecutive groups)

- Combine adjacent group implicants into  $(n-1)$  variable implicants
- Mark the changed bit with “-” and tick the combined implicants

Minterms	<i>abcd</i>
$m_1$	0001 ✓
$m_4$	0100 ✓
$m_8$	1000 ✓
$m_5$	0101 ✓
$m_6$	0110 ✓
$m_9$	1001 ✓
$m_{10}$	1010 ✓
$m_{12}$	1100 ✓
$m_{14}$	1110 ✓

Minterms	<i>abcd</i>
$m_1, m_5$	0-01
$m_1, m_9$	-001
$m_4, m_5$	010-
$m_4, m_6$	01-0
$m_4, m_{12}$	-100
$m_8, m_9$	100-
$m_8, m_{10}$	10-0
$m_8, m_{12}$	1-00
$m_6, m_{14}$	-110
$m_{10}, m_{14}$	1-10
$m_{12}, m_{14}$	11-0

# Procedure of QM-method (4-variable)

Step 2: Combine (Apply adjacency property to each pair of terms in consecutive groups)

- Combine adjacent group implicants into  $(n-1)$  variable implicants
- Mark the changed bit with “-” and tick the combined implicants

Minterms	<i>abcd</i>
$m_1$	0001 ✓
$m_4$	0100 ✓
$m_8$	1000 ✓
$m_5$	0101 ✓
$m_6$	0110 ✓
$m_9$	1001 ✓
$m_{10}$	1010 ✓
$m_{12}$	1100 ✓
$m_{14}$	1110 ✓

Minterms	<i>abcd</i>
$m_1, m_5$	0-01
$m_1, m_9$	-001
$m_4, m_5$	010-
$m_4, m_6$	01-0 ✓
$m_4, m_{12}$	-100 ✓
$m_8, m_9$	100-
$m_8, m_{10}$	10-0
$m_8, m_{12}$	1-00
$m_6, m_{14}$	-110 ✓
$m_{10}, m_{14}$	1-10
$m_{12}, m_{14}$	11-0 ✓

Minterms	<i>abcd</i>
$m_4, m_6, m_{12}, m_{14}$	-1-0

# Procedure of QM-method (4-variable)

Step 2: Combine (Apply adjacency property to each pair of terms in consecutive groups)

- Combine adjacent group implicants into  $(n-1)$  variable implicants
- Mark the changed bit with “-” and tick the combined implicants

Minterms	<i>abcd</i>
$m_1$	0001 ✓
$m_4$	0100 ✓
$m_8$	1000 ✓
$m_5$	0101 ✓
$m_6$	0110 ✓
$m_9$	1001 ✓
$m_{10}$	1010 ✓
$m_{12}$	1100 ✓
$m_{14}$	1110 ✓

Minterms	<i>abcd</i>
$m_1, m_5$	0-01
$m_1, m_9$	-001
$m_4, m_5$	010-
$m_4, m_6$	01-0 ✓
$m_4, m_{12}$	-100 ✓
$m_8, m_9$	100-
$m_8, m_{10}$	10-0 ✓
$m_8, m_{12}$	1-00 ✓
$m_6, m_{14}$	-110 ✓
$m_{10}, m_{14}$	1-10 ✓
$m_{12}, m_{14}$	11-0 ✓

Minterms	<i>abcd</i>
$m_4, m_6, m_{12}, m_{14}$	-1-0
$m_8, m_{10}, m_{12}, m_{14}$	1--0

# Procedure of QM-method (4-variable)

## Step 3: Identify Prime Implicants (PIs)

-All unmarked terms

Minterms	<i>abcd</i>
$m_1$	0001 ✓
$m_4$	0100 ✓
$m_8$	1000 ✓
$m_5$	0101 ✓
$m_6$	0110 ✓
$m_9$	1001 ✓
$m_{10}$	1010 ✓
$m_{12}$	1100 ✓
$m_{14}$	1110 ✓

Minterms	<i>abcd</i>
$m_1, m_5$	0-01 $PI_3$
$m_1, m_9$	-001 $PI_4$
$m_4, m_5$	010- $PI_5$
$m_4, m_6$	01-0 ✓
$m_4, m_{12}$	-100 ✓
$m_8, m_9$	100- $PI_6$
$m_8, m_{10}$	10-0 ✓
$m_8, m_{12}$	1-00 ✓
$m_6, m_{14}$	-110 ✓
$m_{10}, m_{14}$	1-10 ✓
$m_{12}, m_{14}$	11-0 ✓

Minterms	<i>abcd</i>
$m_4, m_6, m_{12}, m_{14}$	-1-0 $PI_1$
$m_8, m_{10}, m_{12}, m_{14}$	1--0 $PI_2$

# Procedure of QM-method (4-variable)

## Step 4: Generate PI chart

- Identify minterms that are covered by only 1 PI
- Identify essential PIs

$$f(a, b, c, d) = \sum m(1, 4, 5, 6, 8, 9, 10, 12, 14)$$

PI	Minterms	<i>abcd</i>	1	4	5	6	8	9	10	12	14
PI <sub>1</sub>	$m_4, m_6, m_{12}, m_{14}$	-1-0									
PI <sub>2</sub>	$m_8, m_{10}, m_{12}, m_{14}$	1--0									
PI <sub>3</sub>	$m_1, m_5$	0-01									
PI <sub>4</sub>	$m_1, m_9$	-001									
PI <sub>5</sub>	$m_4, m_5$	010-									
PI <sub>6</sub>	$m_8, m_9$	100-									

# Procedure of QM-method (4-variable)

## Step 4: Generate PI chart

- Identify minterms that are covered by only 1 PI
- Identify essential PIs

$$f(a, b, c, d) = \sum m(1, 4, 5, 6, 8, 9, 10, 12, 14)$$

PI	Minterms	$abcd$	1	4	5	6	8	9	10	12	14
PI <sub>1</sub>	$m_4, m_6, m_{12}, m_{14}$	-1-0		x		x				x	x
PI <sub>2</sub>	$m_8, m_{10}, m_{12}, m_{14}$	1--0					x		x	x	x
PI <sub>3</sub>	$m_1, m_5$	0-01	x		x						
PI <sub>4</sub>	$m_1, m_9$	-001	x					x			
PI <sub>5</sub>	$m_4, m_5$	010-		x	x						
PI <sub>6</sub>	$m_8, m_9$	100-					x	x			

# Procedure of QM-method (4-variable)

## Step 4: Generate PI chart

- Identify minterms that are covered by only 1 PI
- Identify essential PIs

PI	Minterms	$abcd$	1	4	5	6	8	9	10	12	14
$PI_1$	$m_4, m_6, m_{12}, m_{14}$	-1-0		x		x				x	x
$PI_2$	$m_8, m_{10}, m_{12}, m_{14}$	1--0					x		x	x	x
$PI_3$	$m_1, m_5$	0-01	x		x						
$PI_4$	$m_1, m_9$	-001	x					x			
$PI_5$	$m_4, m_5$	010-		x	x						
$PI_6$	$m_8, m_9$	100-					x	x			

$\therefore PI_1$  and  $PI_2$  are essential PIs.

# Procedure of QM-method (4-variable)

## Step 5: Reduce PI chart

- Remove the rows of EPIs and the columns that covered by them

PI	Minterms	$abcd$	1	4	5	6	8	9	10	12	14
$PI_1$	$m_4, m_6, m_{12}, m_{14}$	-1-0		x		x				x	x
$PI_2$	$m_8, m_{10}, m_{12}, m_{14}$	1--0					x		x	x	x
$PI_3$	$m_1, m_5$	0-01	x		x						
$PI_4$	$m_1, m_9$	-001	x					x			
$PI_5$	$m_4, m_5$	010-		x	x						
$PI_6$	$m_8, m_9$	100-					x	x			



# Procedure of QM-method (4-variable)

## Step 5: Reduce PI chart

- Remove the rows of EPIs and the columns that covered by them

PI	Minterms	<i>abcd</i>	1	5	9
PI <sub>3</sub>	$m_1, m_5$	0-01	x	x	
PI <sub>4</sub>	$m_1, m_9$	-001	x		x
PI <sub>5</sub>	$m_4, m_5$	010-		x	
PI <sub>6</sub>	$m_8, m_9$	100-			x

### Solution 1

PI	Minterms	<i>abcd</i>	1	5	9
PI <sub>3</sub>	$m_1, m_5$	0-01	x	x	
PI <sub>4</sub>	$m_1, m_9$	-001	x		x

### Solution 2

PI	Minterms	<i>abcd</i>	1	5	9
PI <sub>3</sub>	$m_1, m_5$	0-01	x	x	
PI <sub>6</sub>	$m_8, m_9$	100-			x

### Solution 3

PI	Minterms	<i>abcd</i>	1	5	9
PI <sub>4</sub>	$m_1, m_9$	-001	x		x
PI <sub>5</sub>	$m_4, m_5$	010-		x	

# Procedure of QM-method (4-variable)

## Step 6: Express the Boolean Function

PI	Minterms	<i>abcd</i>
PI <sub>1</sub>	$m_4, m_6, m_{12}, m_{14}$	-1-0
PI <sub>2</sub>	$m_8, m_{10}, m_{12}, m_{14}$	1--0
PI <sub>3</sub>	$m_1, m_5$	0-01
PI <sub>4</sub>	$m_1, m_9$	-001

$$f(a, b, c, d) = \text{PI}_1 + \text{PI}_2 + \text{PI}_3 + \text{PI}_4$$

$$= bd' + ad' + a'c'd + b'c'd$$

PI	Minterms	<i>abcd</i>
PI <sub>1</sub>	$m_4, m_6, m_{12}, m_{14}$	-1-0
PI <sub>2</sub>	$m_8, m_{10}, m_{12}, m_{14}$	1--0
PI <sub>3</sub>	$m_1, m_5$	0-01
PI <sub>6</sub>	$m_8, m_9$	100-

$$f(a, b, c, d) = \text{PI}_1 + \text{PI}_2 + \text{PI}_3 + \text{PI}_6$$

$$= bd' + ad' + a'c'd + ab'c'$$


PI	Minterms	<i>abcd</i>
PI <sub>1</sub>	$m_4, m_6, m_{12}, m_{14}$	-1-0
PI <sub>2</sub>	$m_8, m_{10}, m_{12}, m_{14}$	1--0
PI <sub>4</sub>	$m_1, m_9$	-001
PI <sub>5</sub>	$m_4, m_5$	010-

$$f(a, b, c, d) = \text{PI}_1 + \text{PI}_2 + \text{PI}_4 + \text{PI}_5$$


$$= bd' + ad' + b'c'd + a'bc'$$
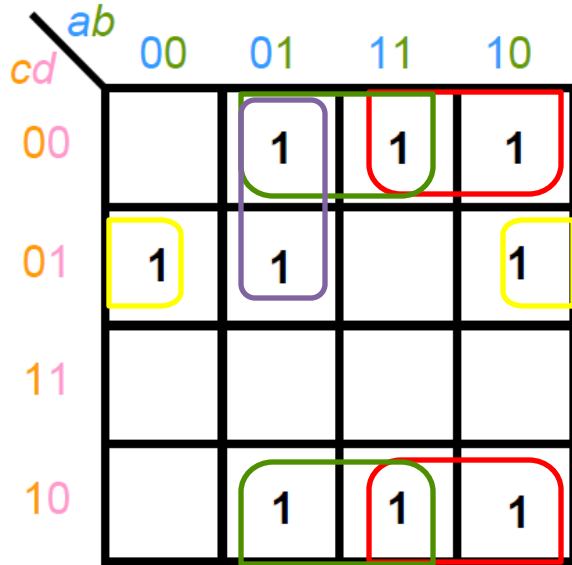
# Verification by K-map


Simplify  $f(a, b, c, d) = \sum m(1, 4, 5, 6, 8, 9, 10, 12, 14)$


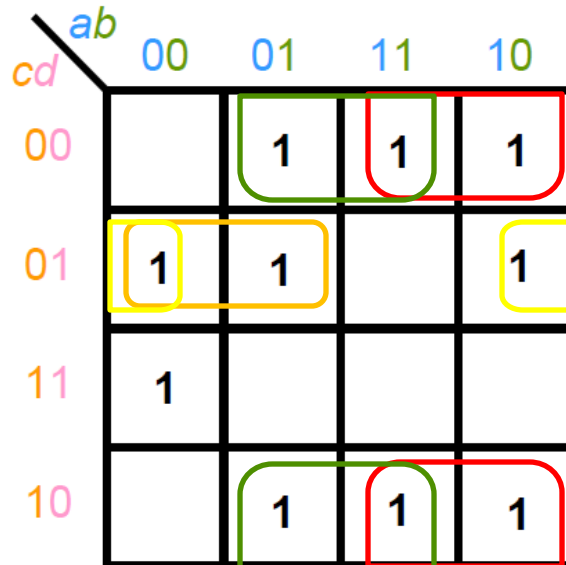
$$f(a, b, c, d) = bd' + ad' \\ + a'bc' + b'c'd$$


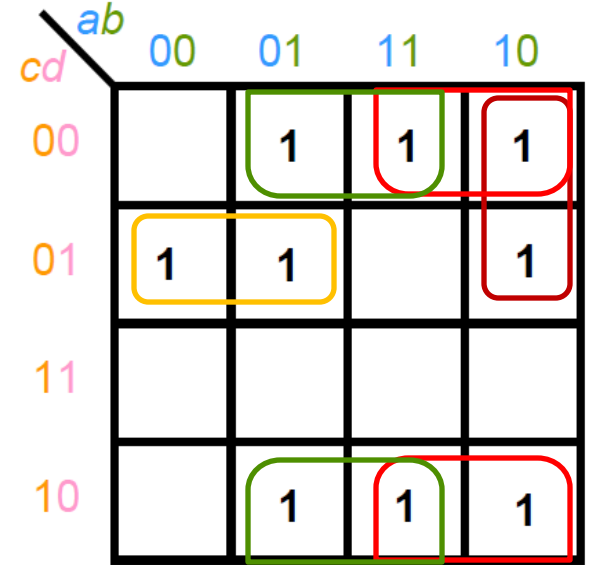
$$f(a, b, c, d) = bd' + ad' \\ + a'c'd + b'c'd$$



$$f(a, b, c, d) = bd' + ad' \\ + a'c'd + ab'c'$$

# Don't Care Case

## Step 1-3 (Partition, Combine, List Pls): Include Don't Care minterms

Simplify  $f(a, b, c, d) = \Sigma m(4, 8, 9, 10, 12, 15) + \Sigma d(2, 6, 13)$

Minterms	<i>abcd</i>
$m_2$	0010 ✓
$m_4$	0100 ✓
$m_8$	1000 ✓
$m_6$	0110 ✓
$m_9$	1001 ✓
$m_{10}$	1010 ✓
$m_{12}$	1100 ✓
$m_{13}$	1101 ✓
$m_{15}$	1111 ✓

Minterms	<i>abcd</i>
$m_2, m_6$	0-10 $PI_2$
$m_2, m_{10}$	-010 $PI_3$
$m_4, m_6$	01-0 $PI_4$
$m_4, m_{12}$	-100 $PI_5$
$m_8, m_9$	100- ✓
$m_8, m_{10}$	10-0 $PI_6$
$m_8, m_{12}$	1-00 ✓
$m_9, m_{13}$	1-01 ✓
$m_{12}, m_{13}$	110- ✓
$m_{13}, m_{15}$	11-1 $PI_7$

Minterms	<i>abcd</i>
$m_8, m_9, m_{12}, m_{13}$	1-0- $PI_1$

# Don't Care Case

## Step 4: Generate PI chart

### - Exclude Don't Care Minterms

Simplify  $f(a, b, c, d) = \sum m(4, 8, 9, 10, 12, 15) + \sum d(2, 6, 13)$

PI	Minterms	$abcd$	4	8	9	10	12	15
PI <sub>1</sub>	$m_8, m_9, m_{12}, m_{13}$	1-0-						
PI <sub>2</sub>	$m_2, m_6$	0-10						
PI <sub>3</sub>	$m_2, m_{10}$	-010						
PI <sub>4</sub>	$m_4, m_6$	01-0						
PI <sub>5</sub>	$m_4, m_{12}$	-100						
PI <sub>6</sub>	$m_8, m_{10}$	10-0						
PI <sub>7</sub>	$m_{13}, m_{15}$	11-1						

## Step 5-6: Reduce PI chart & express the Boolean Function

# Exercise (Don't Care Case)


## Step 5-6: Reduce PI chart & express the Boolean Function

PI	Minterms	$abcd$	4	8	9	10	12	15
PI <sub>1</sub>	$m_8, m_9, m_{12}, m_{13}$	1-0-		x	x		x	
PI <sub>2</sub>	$m_2, m_6$	0-10						
PI <sub>3</sub>	$m_2, m_{10}$	-010				x		
PI <sub>4</sub>	$m_4, m_6$	01-0	x					
PI <sub>5</sub>	$m_4, m_{12}$	-100	x				x	
PI <sub>6</sub>	$m_8, m_{10}$	10-0		x		x		
PI <sub>7</sub>	$m_{13}, m_{15}$	11-1						x

PI	Minterms	$abcd$		

$f(a, b, c, d)$

# Summary

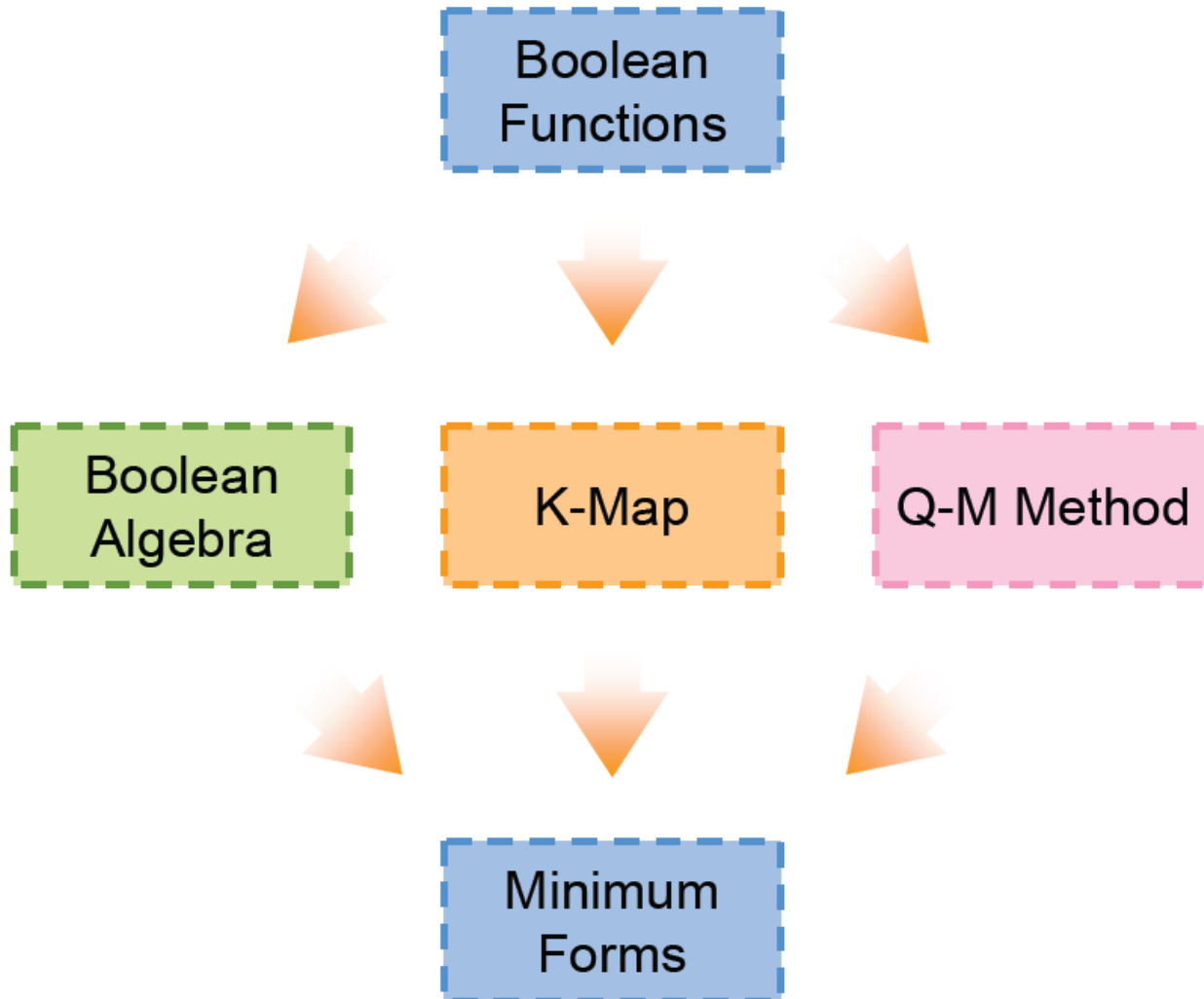

# Multiple Output Problems

c \ ab	00	01	11	10
	$m_0$	$m_2$	$m_6$	$m_4$
0				
1				

$$f(a, b, c) = \sum m(2, 3, 7)$$

c \ ab	00	01	11	10
0		1		
1		1	1	

$$g(a, b, c) = \sum m(4, 5, 7)$$

c \ ab	00	01	11	10
0				1
1			1	1



# Multiple Output Problems

$$f(a, b, c) = \sum m(2, 3, 7)$$

c \ ab	00	01	11	10
0		1		
1		1	1	

$$f(a, b, c) = a'b + bc$$


$$g(a, b, c) = \sum m(4, 5, 7)$$

c \ ab	00	01	11	10
0				1
1			1	1


$$g(a, b, c) = ab' + ac$$

# Multiple Output Problems

$$f(a, b, c) = a'b + bc$$

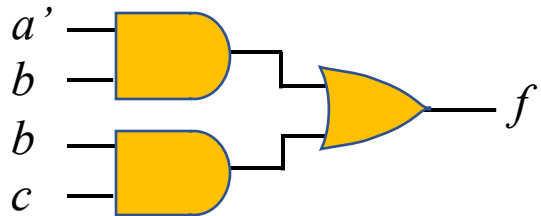

$$g(a, b, c) = ab' + ac$$

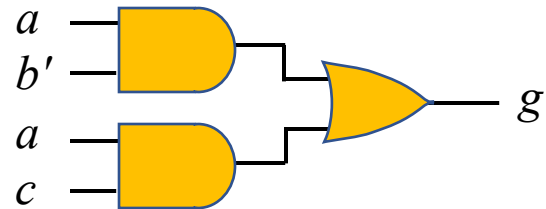

12 gate inputs and 6 gates (how to reduce the cost?)

# Multiple Output Problems

c \ ab	00	01	11	10
	$m_0$	$m_2$	$m_6$	$m_4$
0				
1				

$$f(a, b, c) = \sum m(2, 3, 7)$$

c \ ab	00	01	11	10
0		1		
1		1	1	

$$f(a, b, c) = a'b + bc$$

$$g(a, b, c) = \sum m(4, 5, 7)$$

c \ ab	00	01	11	10
0				1
1			1	1

$$g(a, b, c) = ab' + ac$$

# Multiple Output Problems

c \ ab	00	01	11	10
	$m_0$	$m_2$	$m_6$	$m_4$
0				
1				

$$f(a, b, c) = \sum m(2, 3, 7)$$

c \ ab	00	01	11	10
0		1		
1		1	1	

$$f(a, b, c) = a'b + abc$$

$$g(a, b, c) = \sum m(4, 5, 7)$$


c \ ab	00	01	11	10
0				1
1			1	1

$$g(a, b, c) = ab' + abc$$

# Multiple Output Problems

$$f(a, b, c) = a'b + abc$$

$$g(a, b, c) = ab' + abc$$

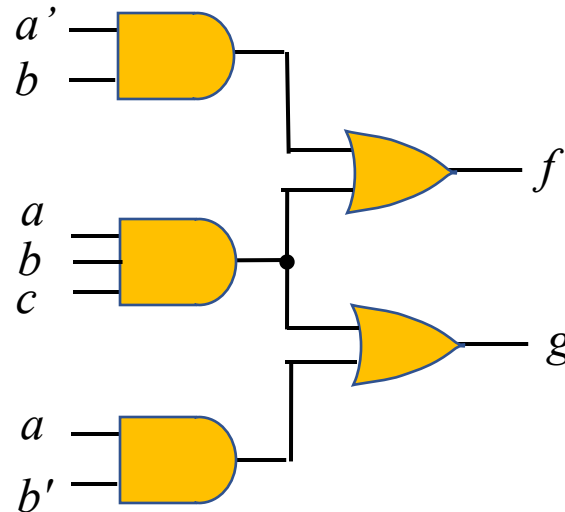

11 gate inputs and 5 gates!!!

# Exercise

Reduce the following functions that will use the least number of gates and gate inputs.

$f(a, b, c, d)$

$cd \backslash ab$	00	01	11	10
00	1	1		1
01	1	1		1
11				
10	1	1		

$g(a, b, c, d)$

$cd \backslash ab$	00	01	11	10
00				1
01				1
11			1	1
10	1	1	1	1

# Exercise

Reduce the following functions that will use the least number of gates and gate inputs.

$f(a, b, c, d)$

$cd \backslash ab$	00	01	11	10
00	1	1		1
01	1	1		1
11				
10	1	1		

$g(a, b, c, d)$

$cd \backslash ab$	00	01	11	10
00				1
01				1
11			1	1
10	1	1	1	1