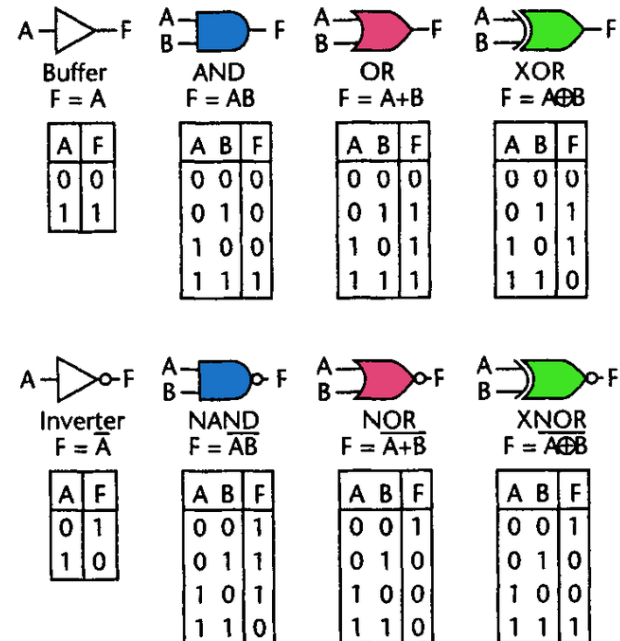


EE2000 Logic Circuit Design

Lecture 11 – Revision



Exercise

$$\{(b' + c')'(c + bc')(ab'c' + b' + c') + [(a + c')(b + c)]'\}'$$

$$= \{(b' + c')'(c + bc')(b' + c') + [(a + c')(b + c)]'\}'$$

Absorption

$$= [(a + c')(b + c)]'' \quad \text{Complement}$$

$$= (a + c')(b + c) \quad \text{Involution}$$




$$= ab + ac + bc'$$

$$= ac + bc' \quad \text{Consensus}$$

Common mistake: Copy wrongly and DeMorgan Theorem


Exercise

Which function(s) might have a timing hazard problem?
How to eliminate the hazard?

   


Test 2 - Question 4

(a) Design a functional block (FCB) to generate an odd parity (P) bit from 4-bit data (A_3, A_2, A_1, A_0) using only two 1-bit full adders (FAs).

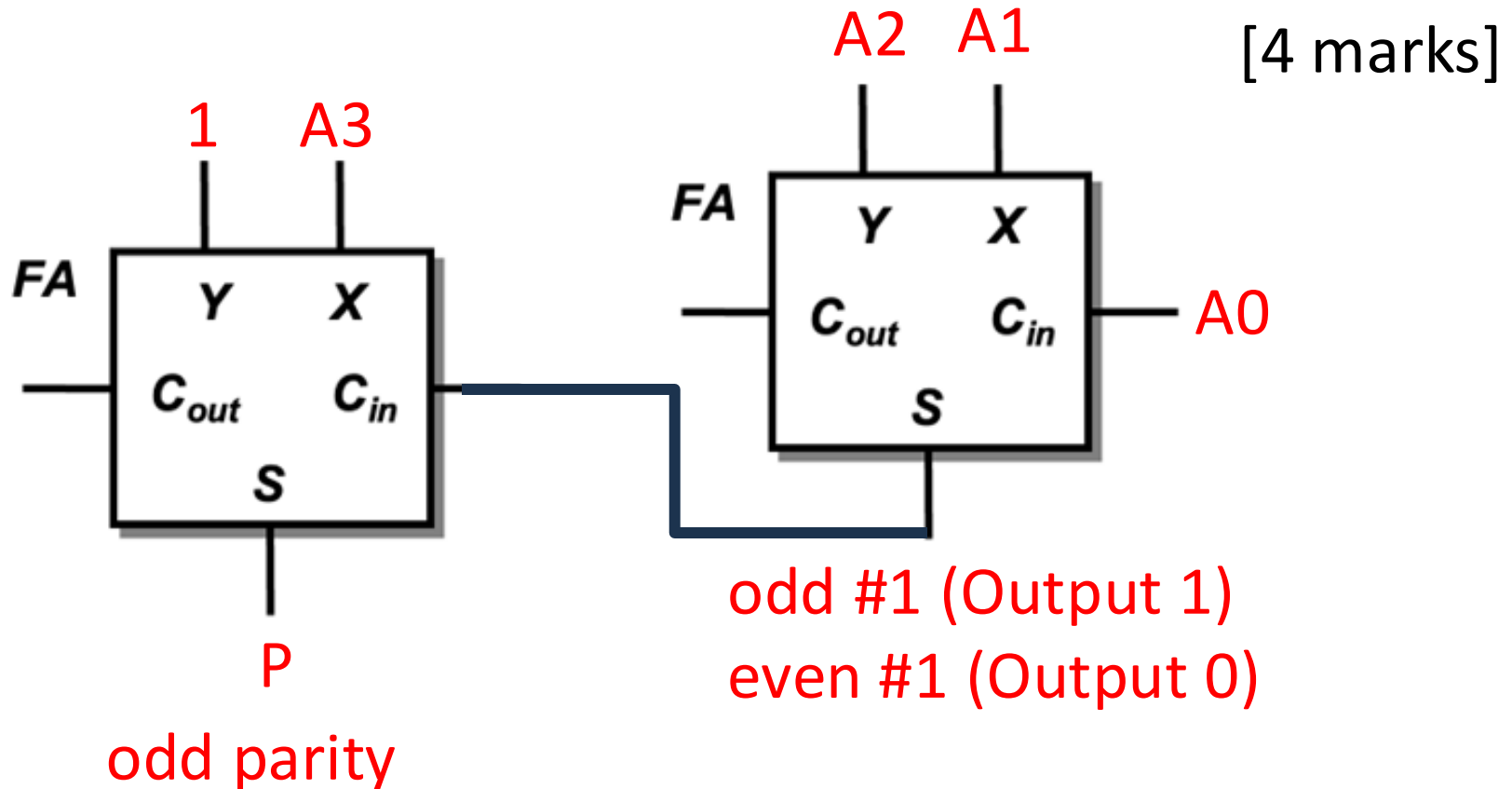


Test 2 - Question 4

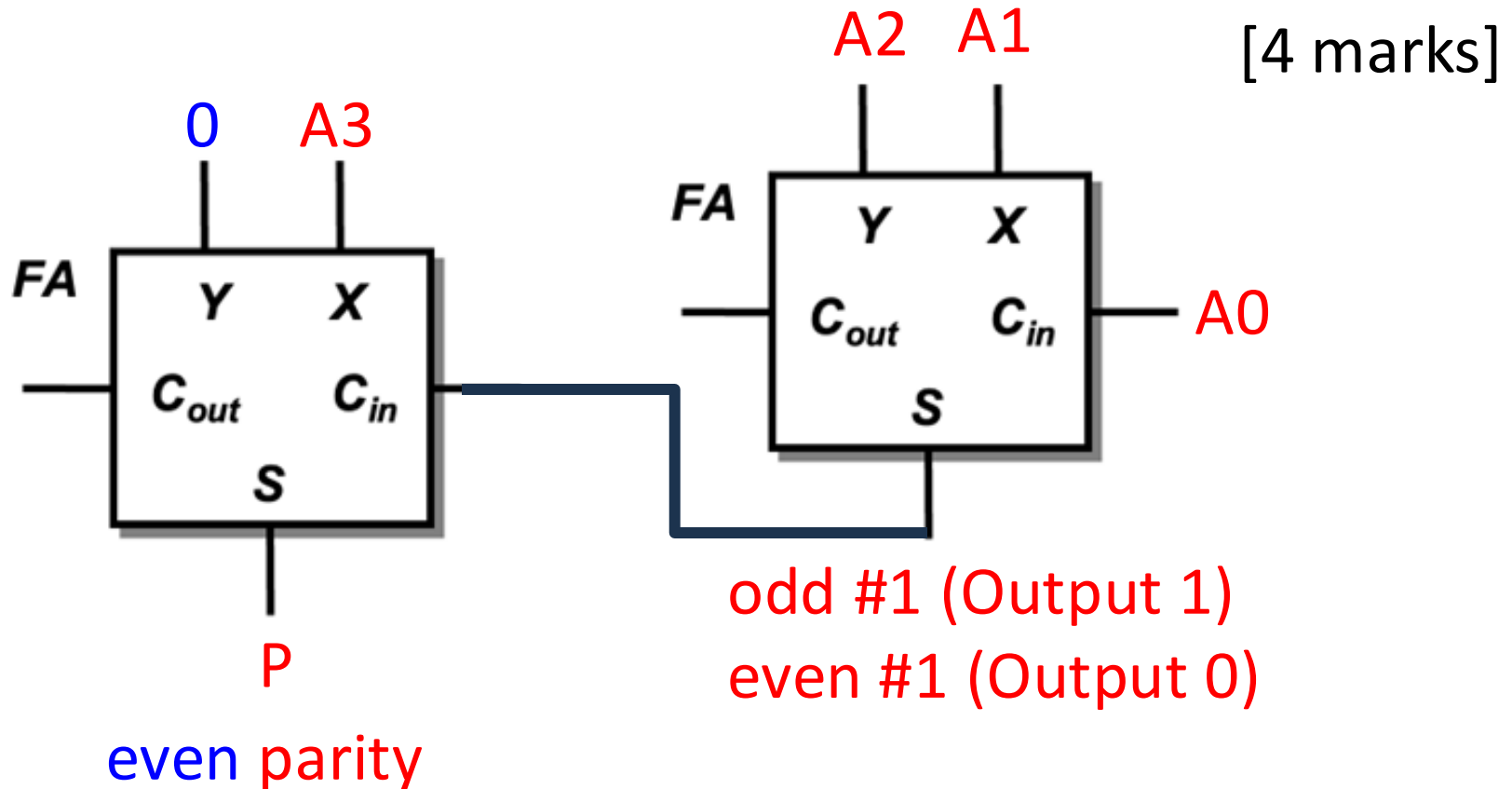(a) Design a functional block (FCB) to generate an **even** parity (P) bit from 4-bit data (A3, A2, A1, A0) using only two 1-bit full adders (FAs).









 Exercise

Design a circuit to generate an odd parity (p) for a 4-bit data (w, x, y, z) using one 8-to-1-line MUX and one NOT gate only.



w	x	y	z	p
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	0
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	1
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

      


Test 2 – Question 3


$$x(a, b, c, d) = \Sigma m(3, 4, 6, 13) + \Sigma d(2, 5, 7, 10, 11, 12, 14)$$

$$y(a, b, c, d) = \Sigma m(0, 1, 3, 5, 10, 15) + \Sigma d(4, 7, 18, 11)$$

 
$$z(a, b, c, d) = \Pi M(2, 3, 4, 5, 7, 11, 12, 15) \Pi d(8, 10)$$



$$x' = b'c' + ac$$

 

$$y' = ac' + bcd' + a'cd'$$

 


$$z = b'c' + bcd' + ac'd$$


$$x' = b'c' + ac$$

$$y' = ac' + bcd' + a'cd'$$

$$z = b'c' + bcd' + ac'd$$

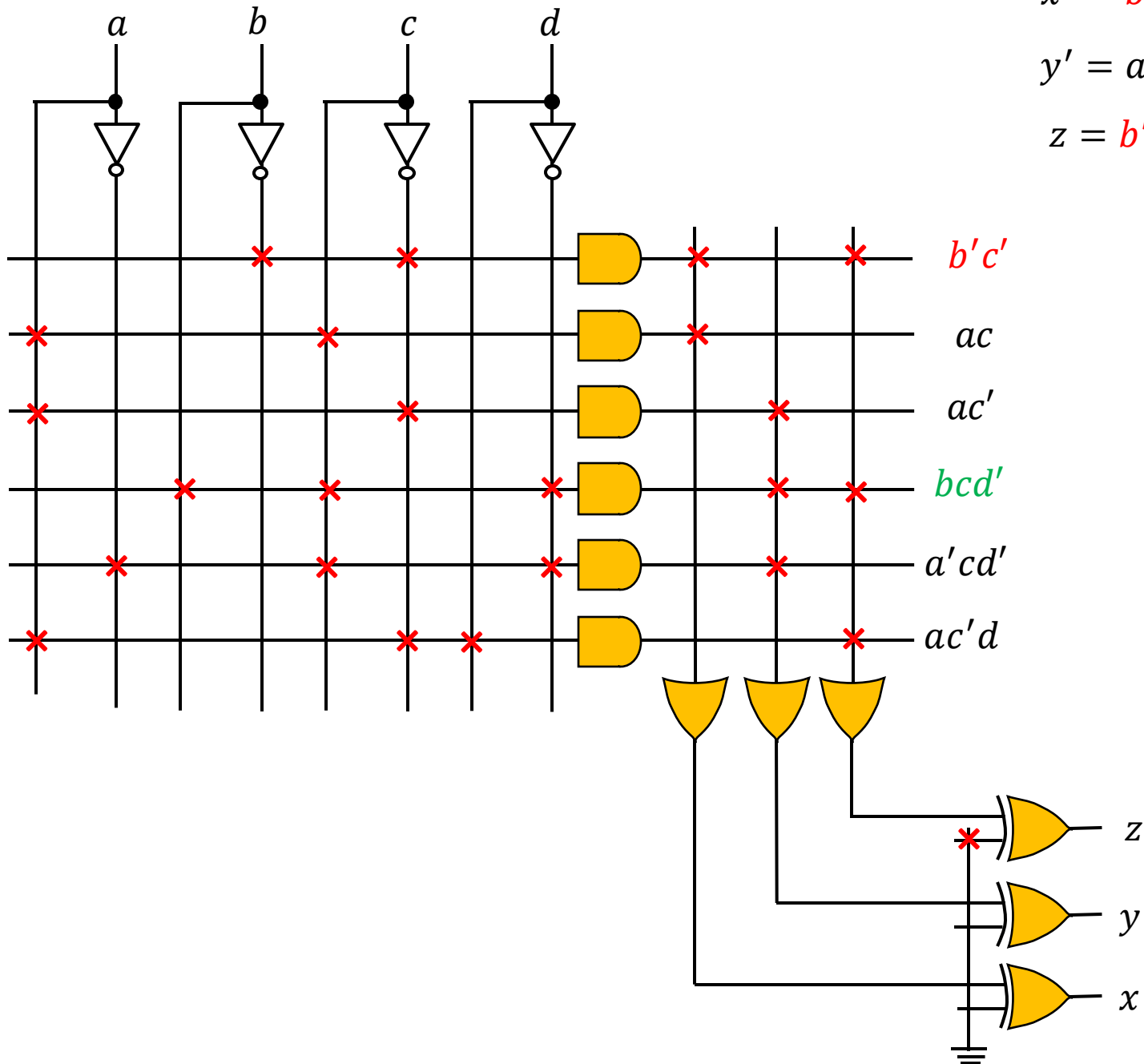

Test 2 – Question 1 (Past Year Exam Q)

 


$$D = x$$

$$T = x'$$

$$J = K = q_2'$$

$$z = q_1 q_2' q_3$$

 

Test 2 – Question 3

Given the following VHDL code. Work out the truth table and specify the function of the circuits.

```
architecture Behavior of function1 is
  signal s1: std_logic;
begin
  process (a, b)
  begin
    if a = '1' then
      s1 <= '1';
    elsif rising_edge(b) then
      s1 <= s1;
    elsif falling_edge(b) then
      if x = '0' then
        s1 <= s1;
      else
        s1 <= not s1;
      end if;
    end if;
  end process;
  z <= s1;
end Behavior;
```

Inputs: a, b, x

Output: z

a	b	x	s1	z
1	x	x	1	1
0	↑, 0, 1	x	s1	z
0	↓	0	s1	z
0	↓	1	s1'	z'

Asynchronous active high
preset input

Negative edge-triggered T-FF

Exercise (Past Year Question)

Design a Moore machine using D-FFs with 1 input x and 1 output z such that $z = 1$ if x has been '1' or '0' consecutively for two or more clock times. Provide the state diagram and the Boolean functions of the flip-flops' inputs and the circuit output. Draw the circuit diagram clearly.


[10 marks]

A: First '0'


B: Second "00", output 1

C: First '1'

D: Second "11", output 1

 


Exercise

 


Present State (Q1 Q2)	Input x	Present Output z	Next State Q1* Q2*
A (0 0)	0	0	0 1
A (0 0)	1	0	1 0
B (0 1)	0	1	0 1
B (0 1)	1	1	1 0
C (1 0)	0	0	0 0
C (1 0)	1	0	1 1
D (1 1)	0	1	0 0
D (1 1)	1	1	1 1


Exercise

 


$$D_1 = Q_1^* = x$$

 

$$z = Q_2$$

 

$$D_2 = Q_2^* = xQ_1 + x'Q_1'$$

 


Exercise

Design the same sequence detector using a Mealy machine with T-FFs. Provide the state diagram and the Boolean functions of the flip-flops' inputs and the circuit output. A circuit diagram is not needed. [7 marks]

A: Reset to 1st zero *if next input is 0, remains at A output 1 else B

 B: one '1' is detected *if next input is 1, remains at B output 1 else A



Present State (Q)	Input X	Next state Q^*	Output Z
A (0)	0	0	1
A (0)	1	1	0
B (1)	0	0	0
B (1)	1	1	1

$$T = xQ' + Qx'$$

$$Z = Q'x' + Qx$$


```

if (Bin = "01") then
    s1 <= s1(1 downto 0) & Cin;
elsif (Bin = "10") then
    s1 <= Din & s1(2 downto 1);
elsif (Bin = "11") then
    s1 <= Ain;
end if;
end if;
Eout <= s1;
end process;

```

Asynchronous active-high reset input

Negative edge-triggered

3-bit bidirectional register

Bin "01" shift left

Bin "10" shift right

Bin "11" parallel load

Bin "00" HOLD

Inputs						Signal	Output
Ain (3-bits)	Bin (2-bit)	Cin	Din	clk	rst	s1 (3-bit)	Eout (3-bit)
xxx	xx	x	x	x	1	000	000
xxx	xx	x	x	↑, 0, 1	0	s1	Eout
xxx	01	Cin	Din	↓	0	s1(1)s1(0)Cin	E(1)E(0)Cin
xxx	10	Cin	Din	↓	0	Dins1(2)s1(1)	DinE(2)E(1)
A(2)A(1)A(0)	11	Cin	Din	↓	0	A(2)A(1)A(0)	A(2)A(1)A(0)
xxx	00	x	x	↓	0	s1	Eout

Exercise (Past Year Question)

count from 12 to 68 (*e.g.*, 23 in decimals equivalent to 0010 0011 in BCD 8421). Note that the clear (CLR) and load (LOAD) are synchronous inputs.

