

EE2000 Logic Circuit Design

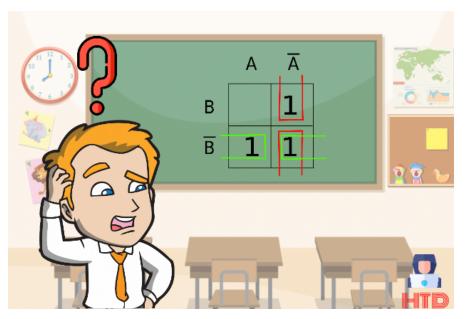Lecture 2 – Karnaugh Map and Quine-McCluskey (QM) Method




hackthedeveloper.com

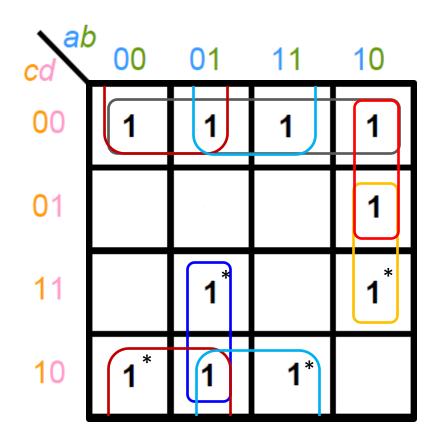
- 1. Identify all PIs.
- 2. Select all EPIs.
- 3. Add PIs of remaining minterms.




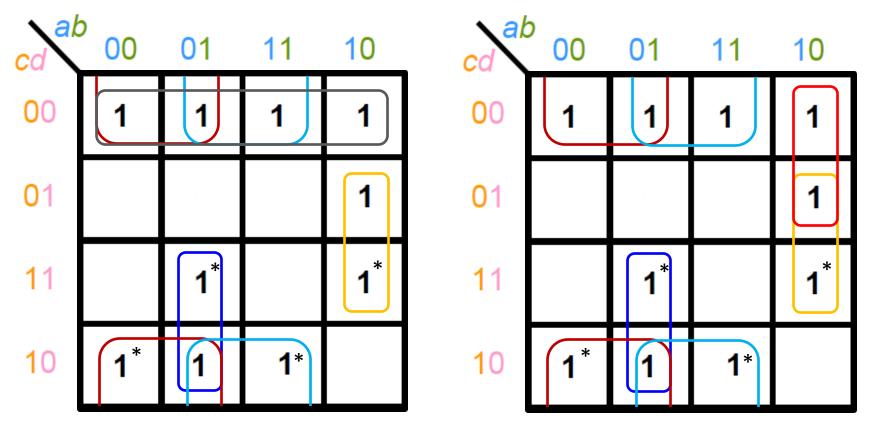
- 1. Identify all PIs.
- 2. Select all EPIs.
- 3. Add PIs of remaining minterms.



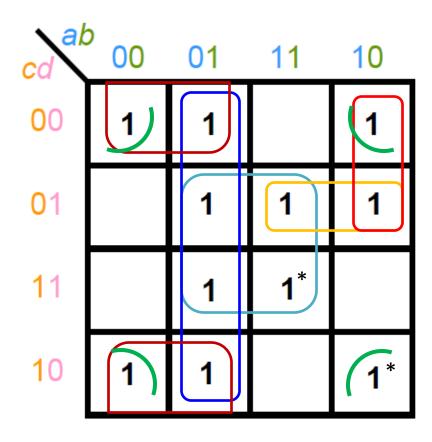Find all minimum sum of products expressions for the following K-map.



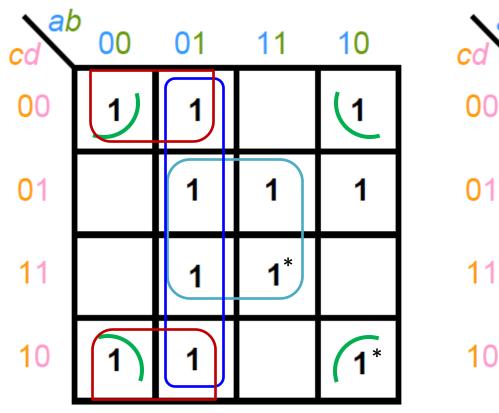

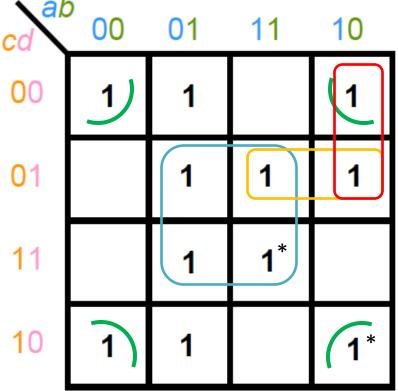

$$f = bd + b'd' + a'd' + ac'd$$


$$f = bd + b'd' + a'b + ac'd$$


$$f = bd + b'd' + a'd' + ab'c'$$

$$f = bd + b'd' + a'b + ab'c'$$

Find all minimum sum of products and all minimum product of sums expressions for the following Boolean Function.
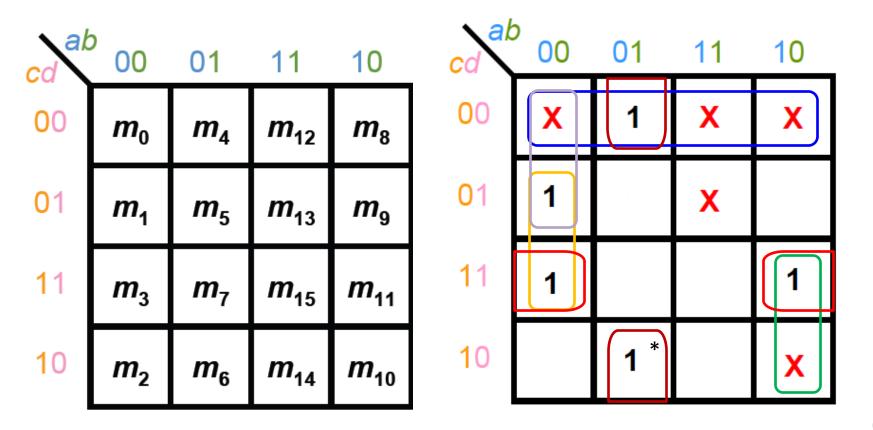
$$f(a,b,c,d) = \sum m(1,3,4,6,11) + \sum d(0,8,10,12,13)$$



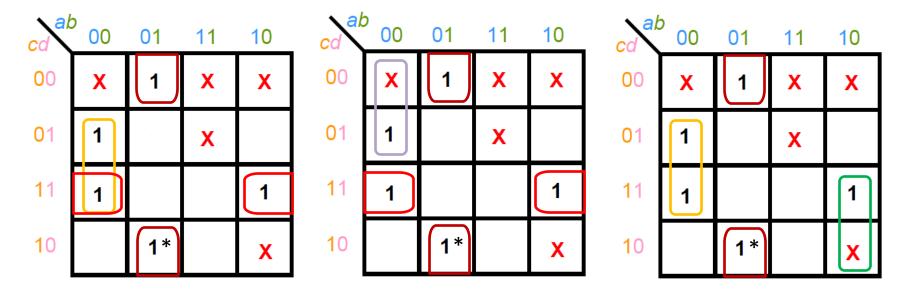



$$f = a'bd' + a'b'd + b'cd$$

$$f = a'bd' + a'b'c' + b'cd$$

$$f = a'bd' + a'b'd + ab'c$$

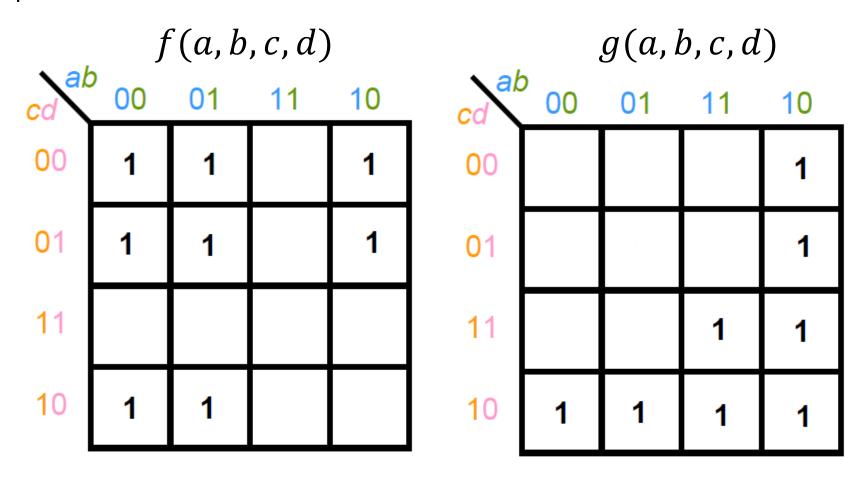
Reduce the following functions that will use the least number of gates and gate inputs.



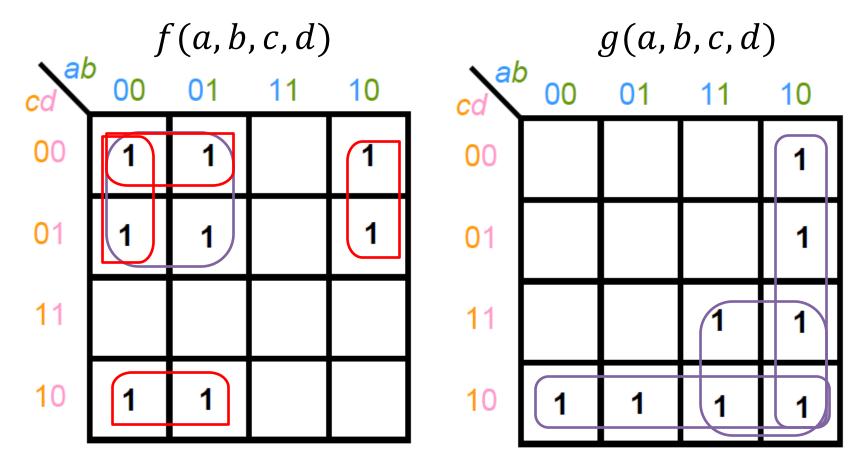

$$f(a,b,c,d) = a'c' + b'c' + a'd'$$
$$g(a,b,c,d) = ab' + ac + cd'$$

18 gate inputs and 8 gates!!!

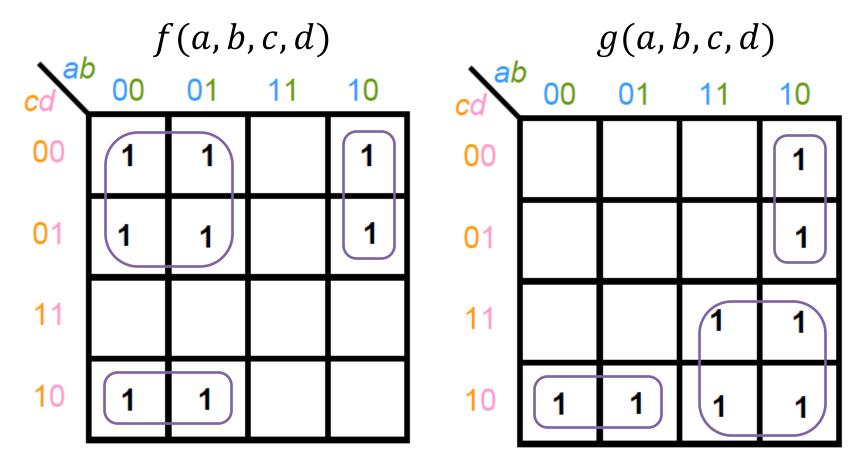

$$f(a,b,c,d) = a'c' + ab'c' + a'cd'$$
$$g(a,b,c,d) = ac + ab'c' + a'cd'$$

16 gate inputs and 6 gates!!!