

# EE2000 Logic Circuit Design

---

## Lecture 6 – Programmable Logic Devices



[mouser.com](https://www.mouser.com)

# What will you learn?



- 6.1 What are Programmable Logic Devices
- 6.2 Implement a Boolean function using a Programmable Read-only Memory (PROM)
- 6.3 Implement a Boolean function using a Programming Array Logic (PAL)
- 6.4 Implement a Boolean function using a Programming Logic Array (PLA)
- 6.5 What are the basic components of a Field Programmable Gate Array Logic (FPGA) and their functions

# 6.1 Programmable Logic Devices

- Logic circuits constructed using discrete logic gates for a fixed function are not reconfigurable/programmable
- Programmable Logic Devices (PLDs) are integrated circuit chips that have undefined function at the time of manufacture
- It has to be programmed by user to implement the desired function
- For design and prototyping

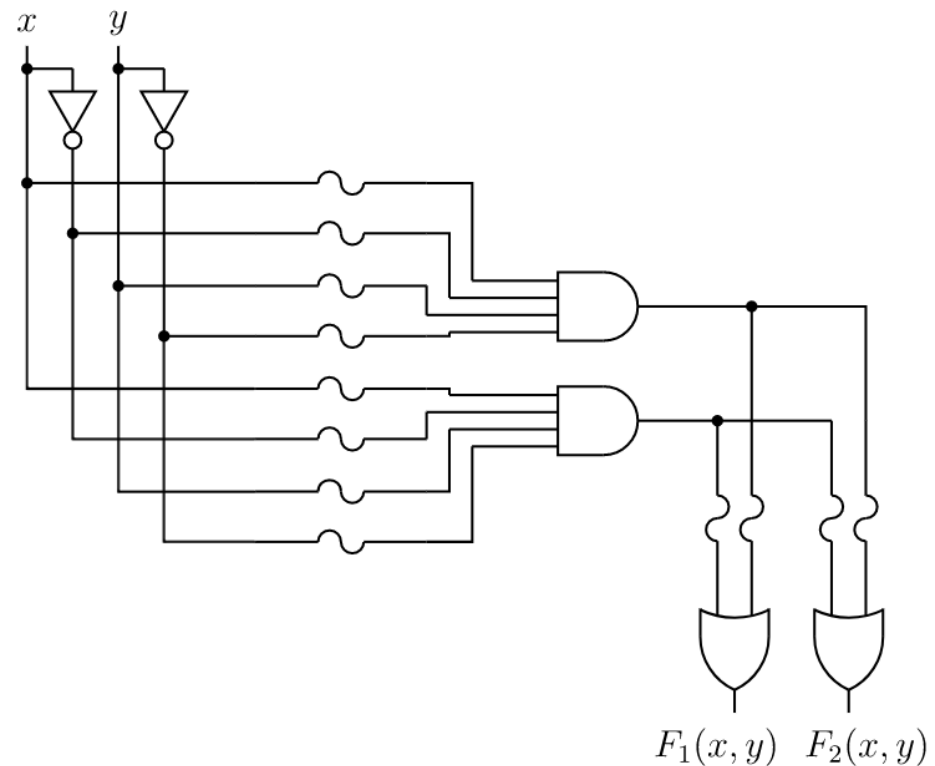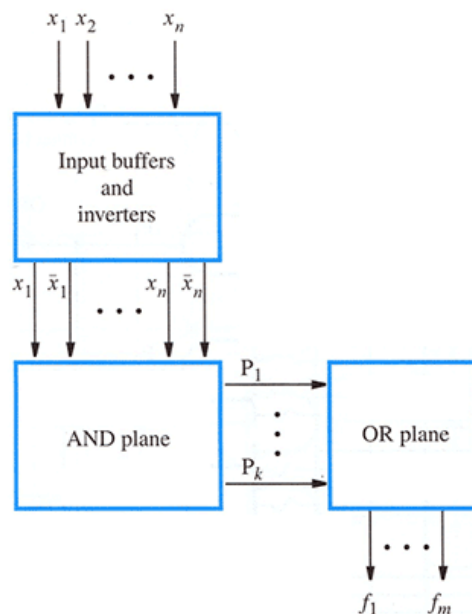
# General Structure of PLD

To implement two-level combinational logic in Sum-of-Products Form




# PLD Notation


## Fusible link

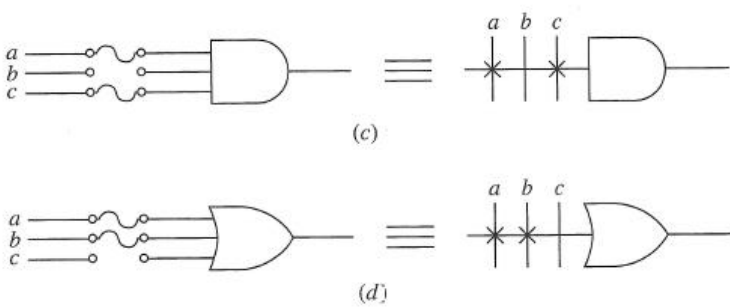


## Hard-wired connection

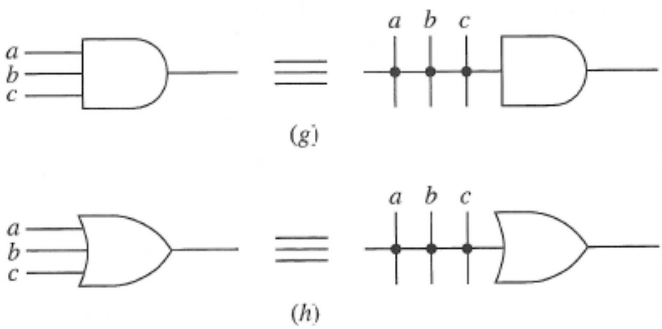


## All fuses are intact

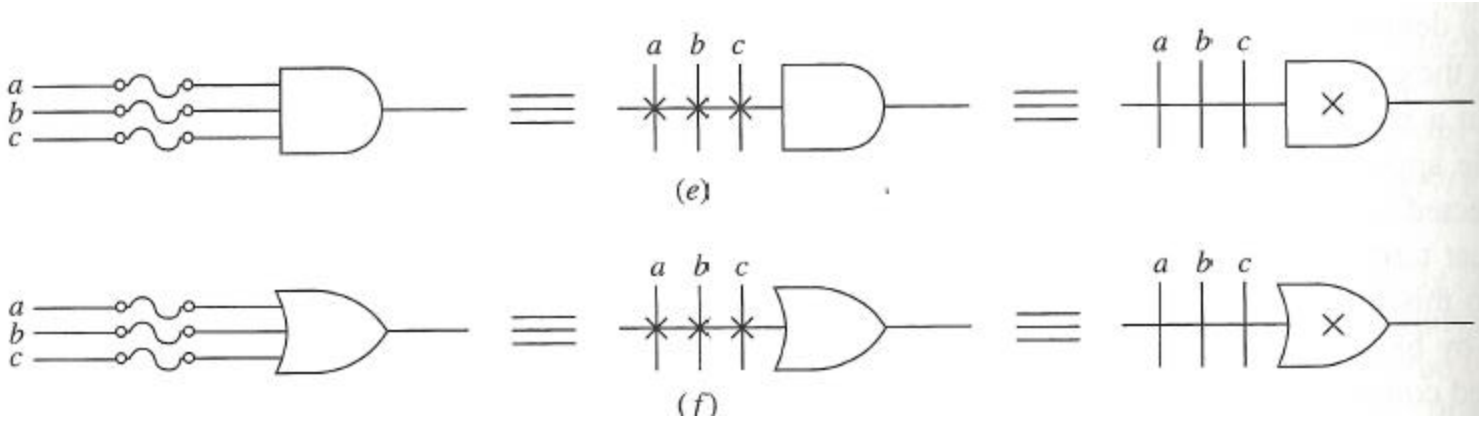


# PLD Notation

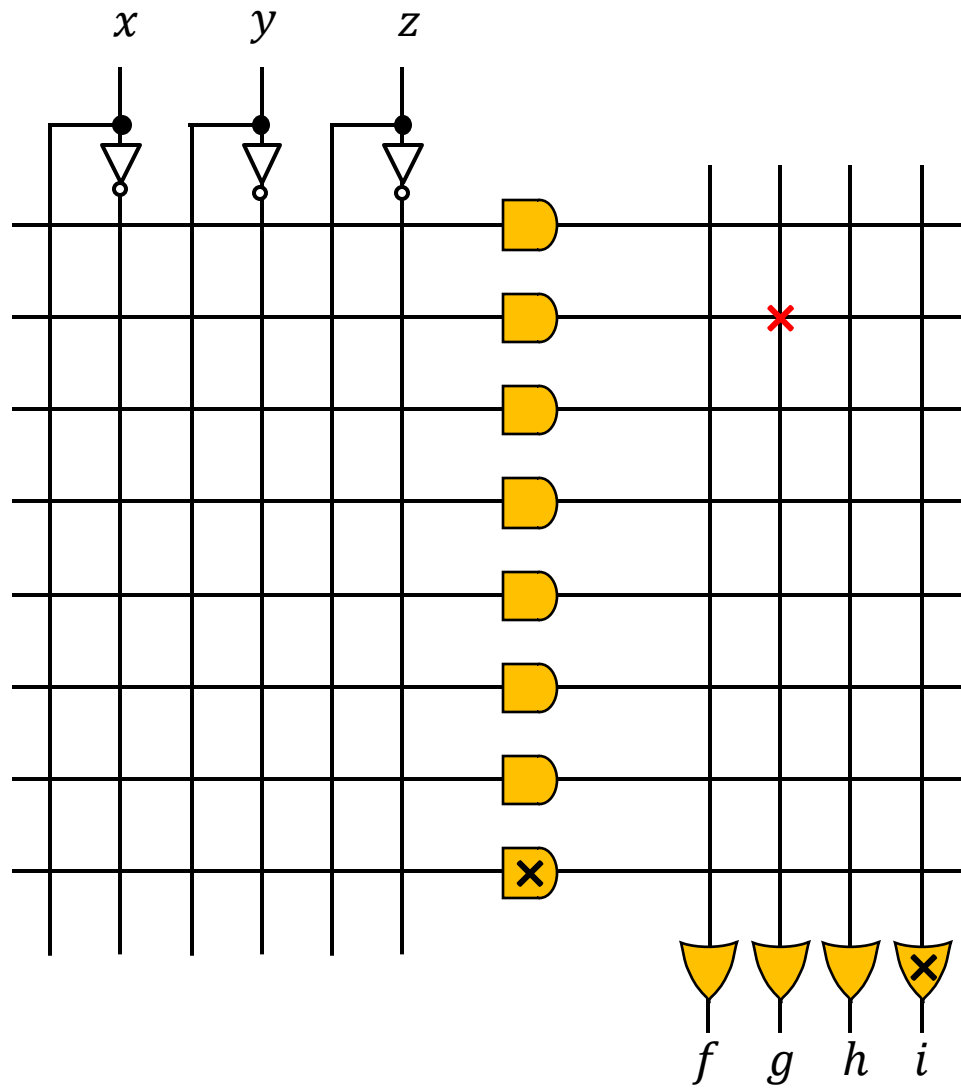

Closed connection

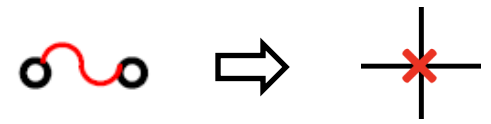

Open connection

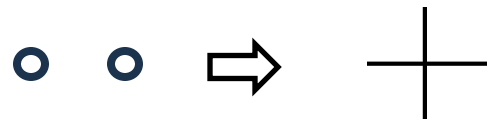

Fixed connection at factory





All connected


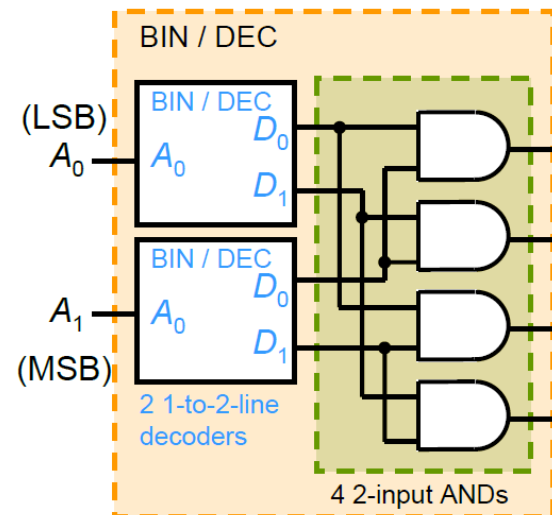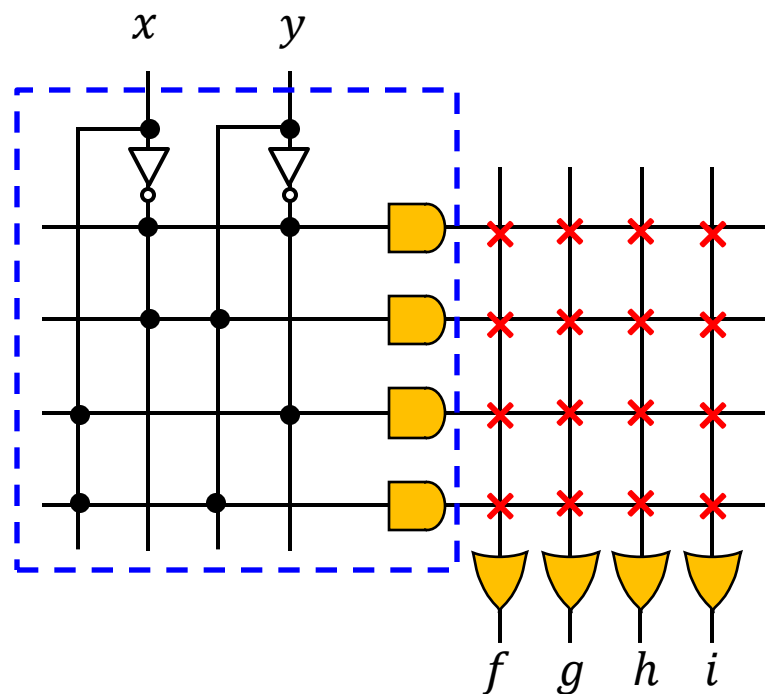
# 6.2 Programmable Read-Only Memory

- Has fixed AND array and programmable OR array
- $n$  inputs require  $2^n$  AND gates and can be implemented using  $n \times 2^n$  decoder




# Example (8 × 4 PROM)

Realize the following functions with an 8 × 4 PROM


$$f_3(a, b, c) = \sum m(2, 3, 5) \quad f_1(a, b, c) = \sum m(1, 2, 4, 5, 6)$$
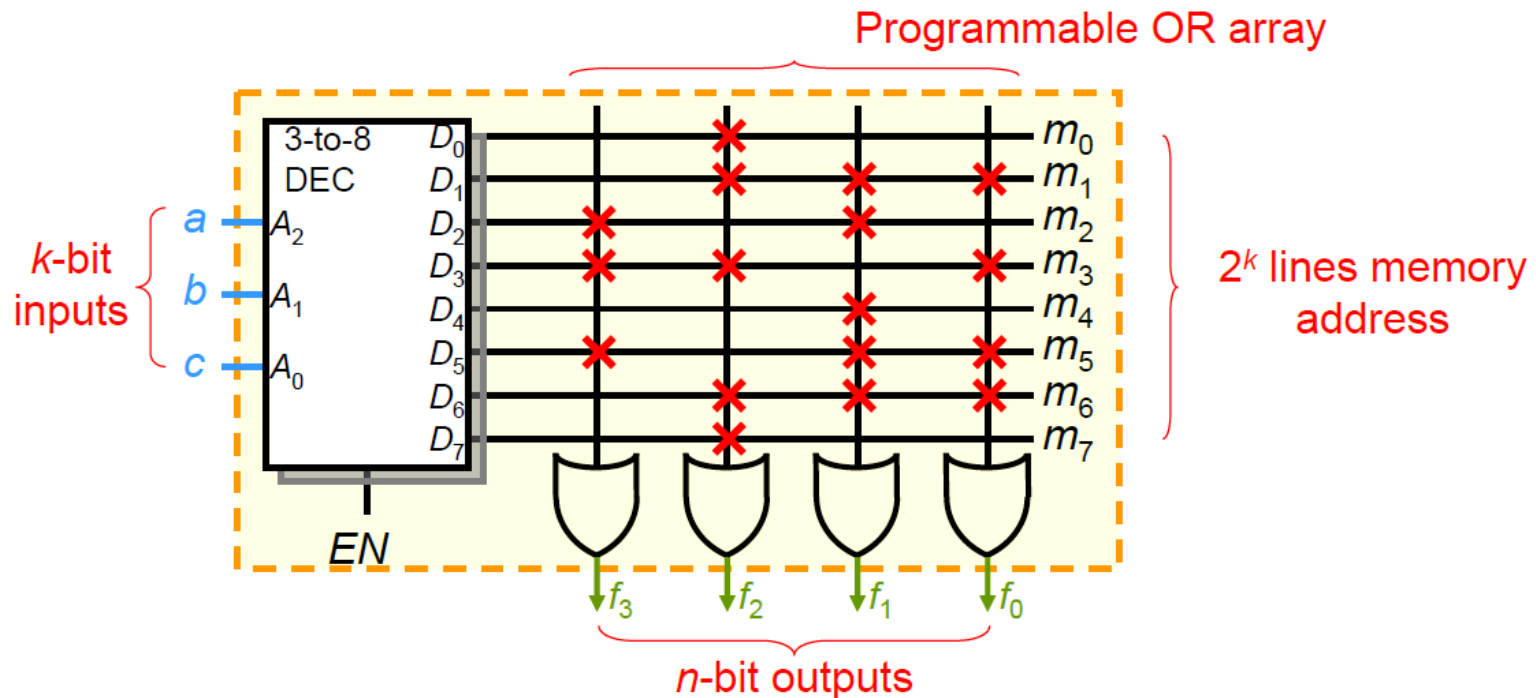
$$f_2(a, b, c) = \sum m(0, 1, 3, 6, 7) \quad f_0(a, b, c) = \sum m(1, 3, 5, 6)$$





# Why is it called as memory?

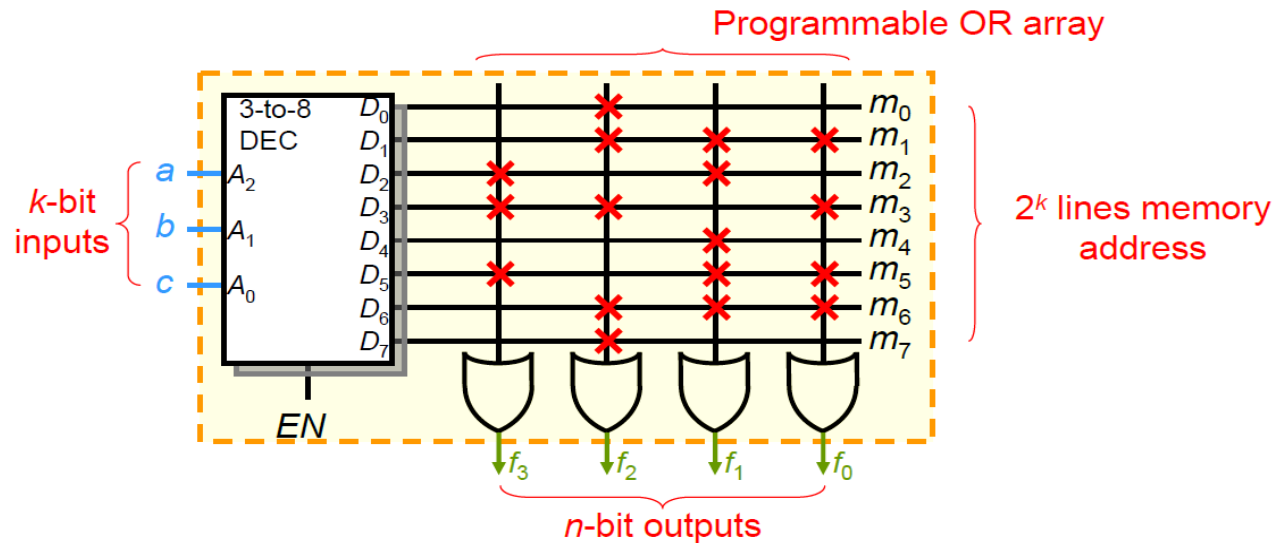

- An essential memory device in which **permanent** binary information is stored (even when the power is turned off, the information is still there).
- $k$ -bit address inputs and  $n$ -bit data outputs
- Inputs: address for the memory
- Outputs: the word ( $n$  data bits) stored in ROM selected by the  $k$ -bit input address


# Types of ROM

- PROM: Programmed by the user only once; non-reprogrammable
- EPROM (Erasable & Programmable Read-Only Memory): Possible to erase it by exposure to UV light; Charge is stored during programming and can dissipate upon UV exposure
- EEPROM (Electrically Erasable PROM): Reprogrammable using voltage (10K times)

## 6.3 Programmable Array Logic (PAL)


- PAL: The OR array is fixed
- PLA is a general design for implementing sum-of-product terms, whereas the PAL has fixed sum-of-product terms
- Design for **PAL** device is easier, but not as flexible as that for PLA

# PAL Diagram I

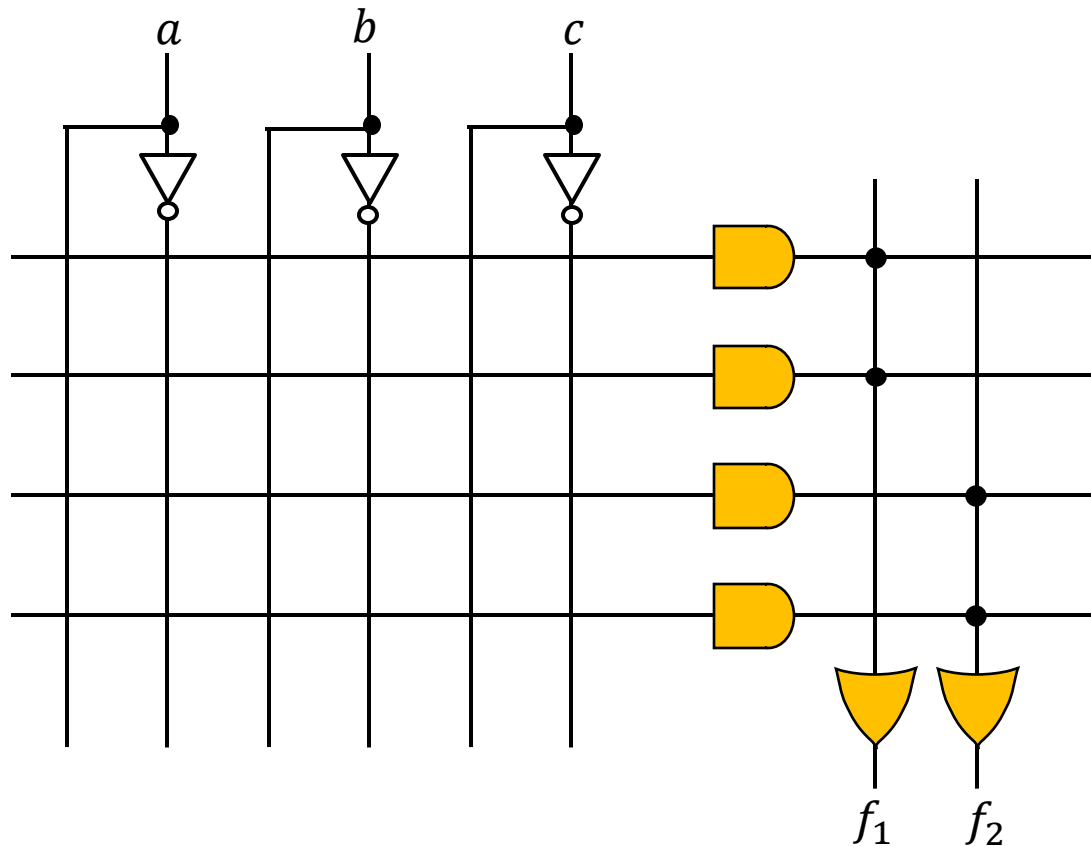

- 3 inputs
- 2 outputs
- Each output can have the most 2 product terms

# PAL Diagram II

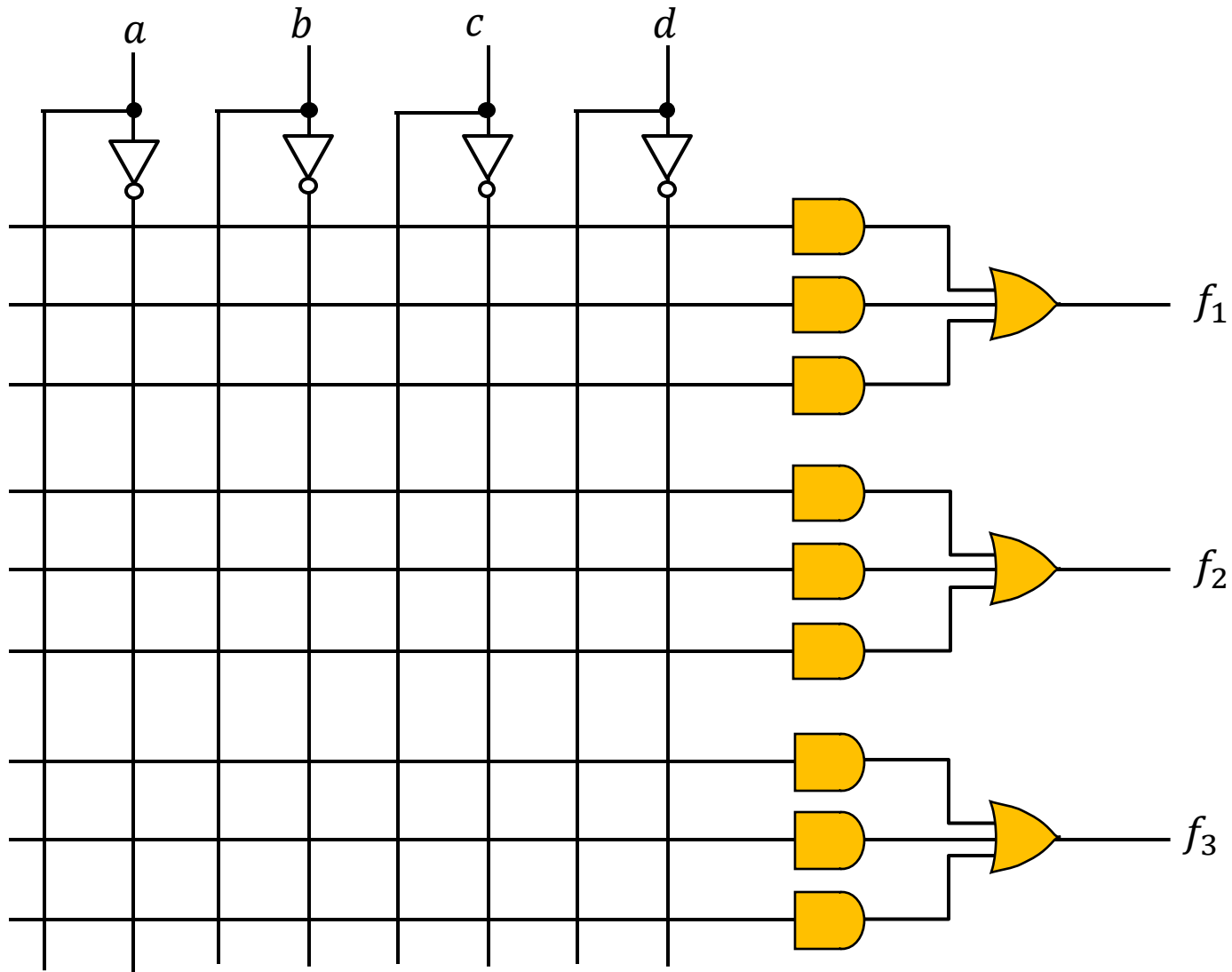


# Example

$$f_1(a, b, c, d) = abc' + a'b'cd'$$


$$f_2(a, b, c, d) = a + bcd$$

$$f_3(a, b, c, d) = a'b + cd + b'd'$$

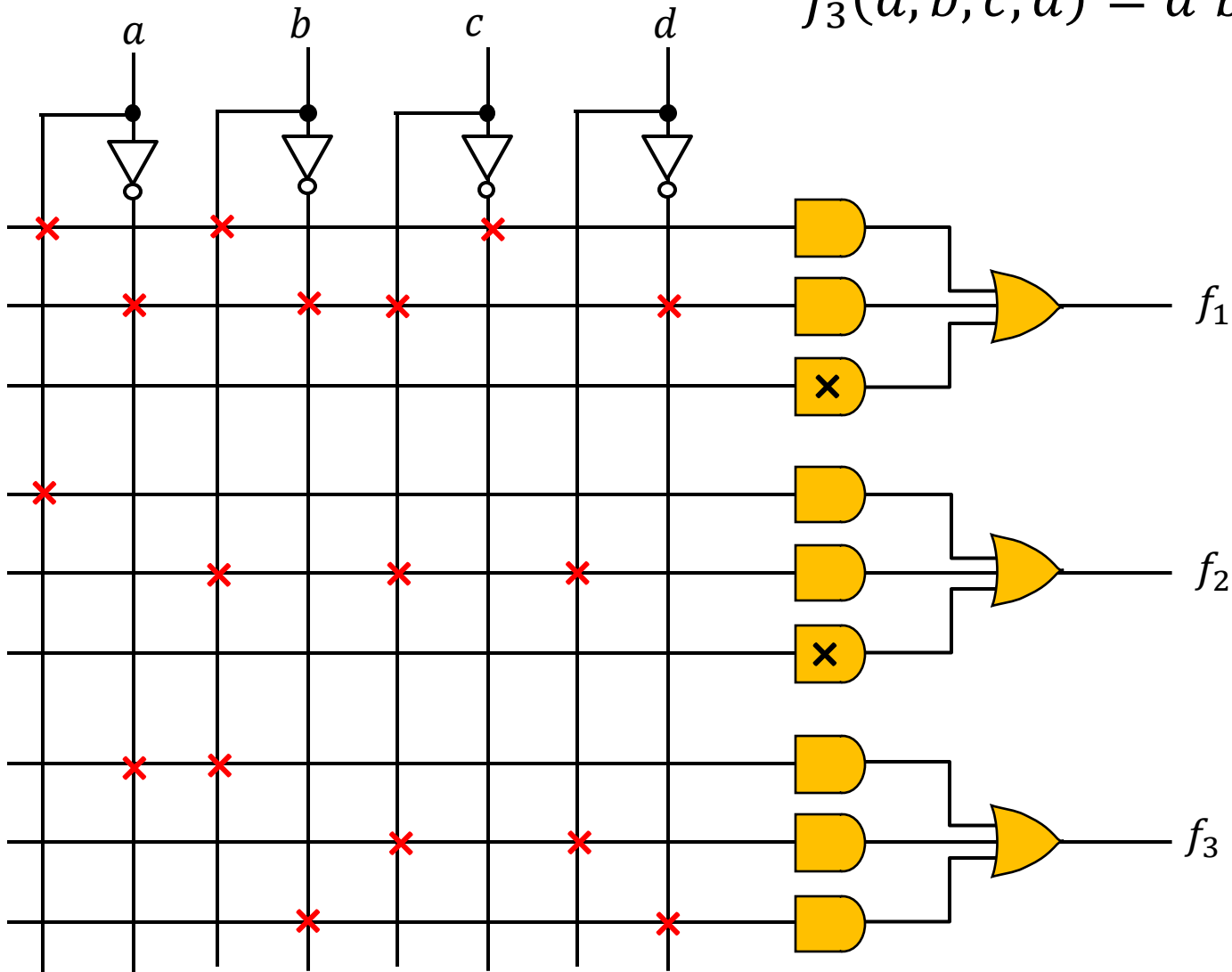
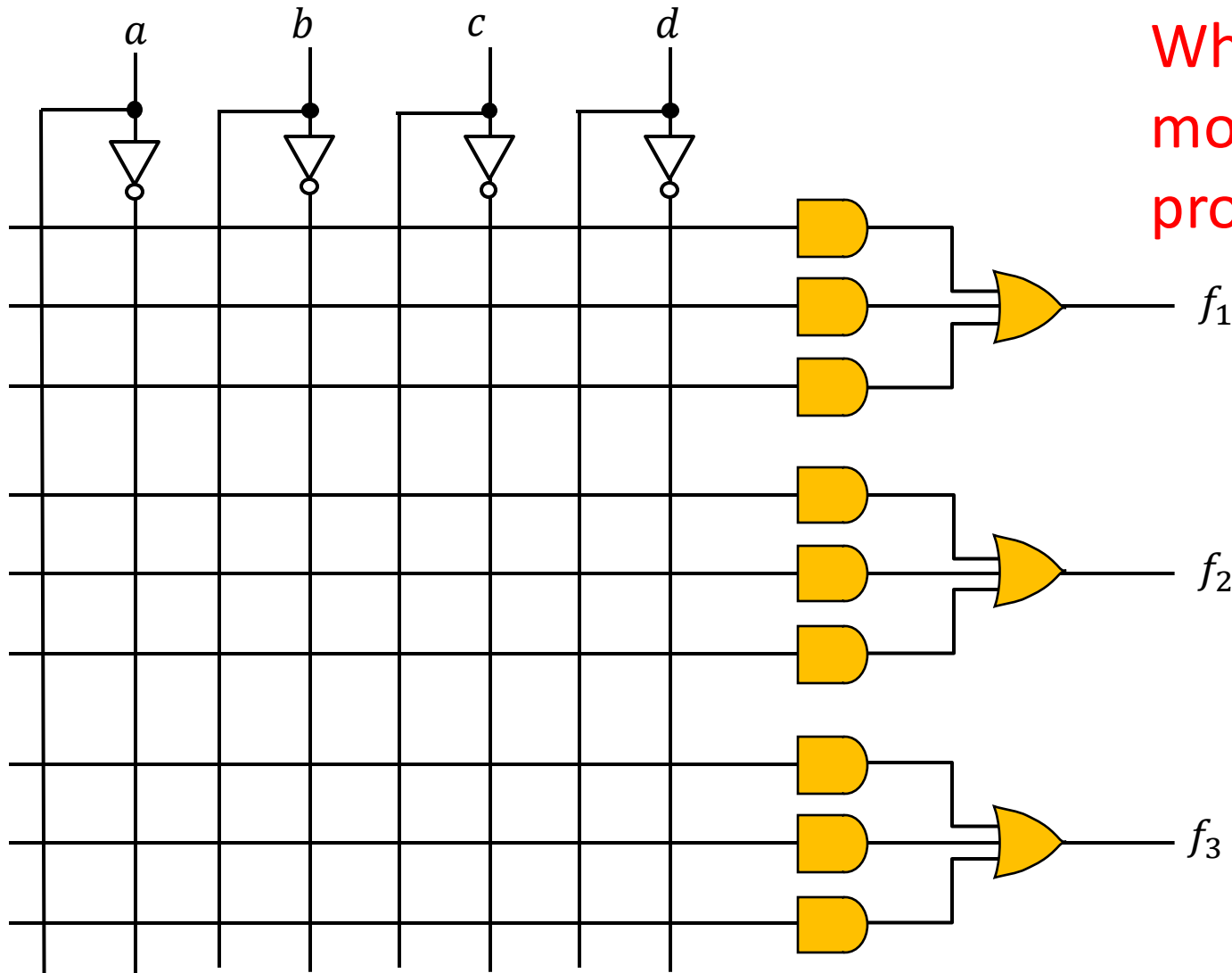
# Limitation

$$f_1(a, b, c, d) = abc' + a'b'cd' + ad + ab'$$
$$f_2(a, b, c, d) = a + bcd$$




What if we need  
more than 3  
product terms?

# Solution: Feedback

$$f_1(a, b, c, d) = abc' + a'b'cd' + ad + ab'$$

$$f_2(a, b, c, d) = a + bcd$$

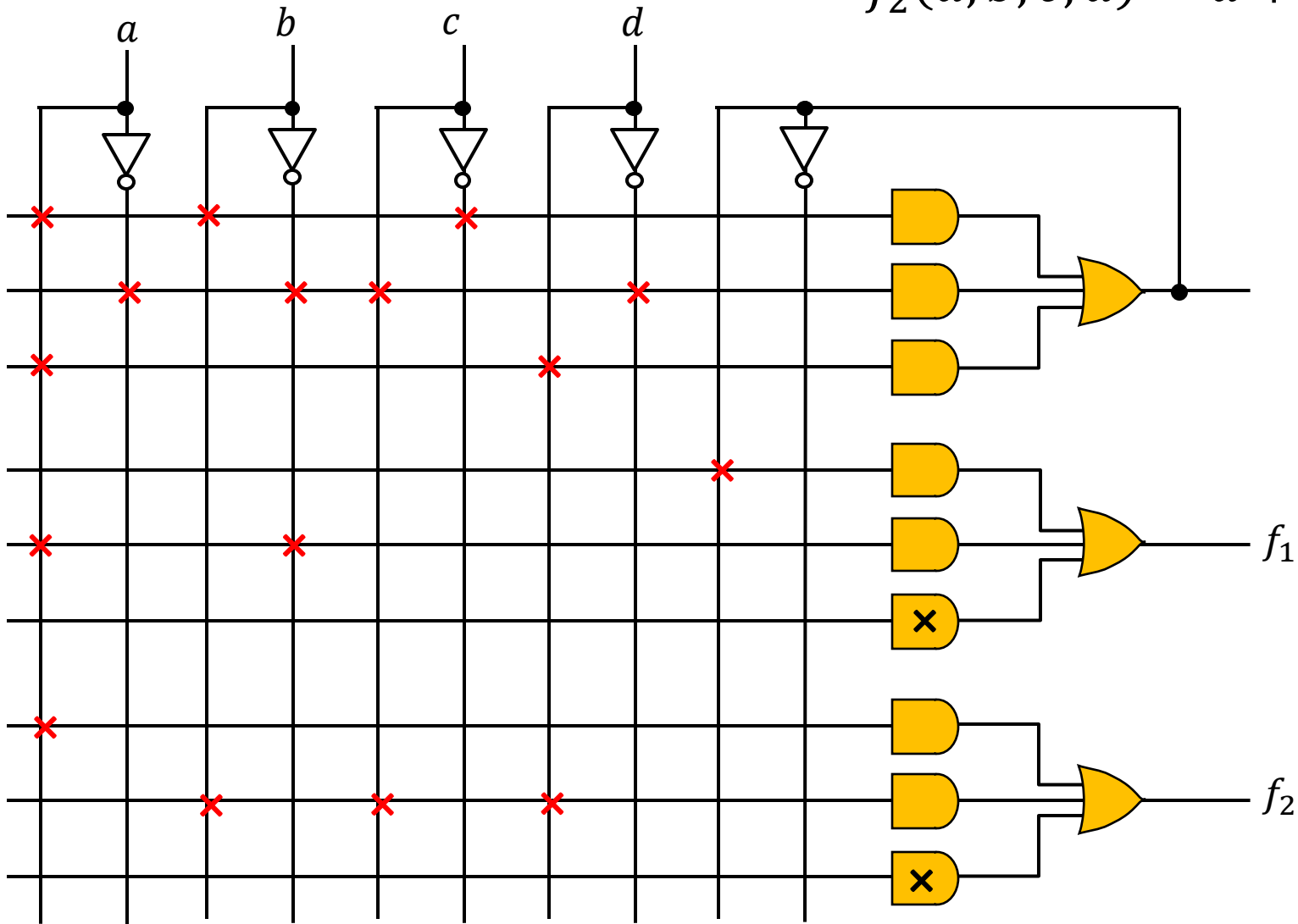



# Exercise

Implement the following functions with the PAL shown in next slide.

$$x(a, b, c, d) = \sum m(2, 12, 13)$$

$$y(a, b, c, d) = \sum m(7, 8, 9, 10, 11, 12, 13, 14, 15)$$

$$z(a, b, c, d) = \sum m(1, 2, 8, 12, 13)$$

cd \ ab	00	01	11	10
	$m_0$	$m_4$	$m_{12}$	$m_8$
00				
01				
11				
10				

$x$

cd \ ab	00	01	11	10
00				
01				
11				
10				


$y$

cd \ ab	00	01	11	10
00				
01				
11				
10				

$z$

cd \ ab	00	01	11	10
00				
01				
11				
10				

# Exercise

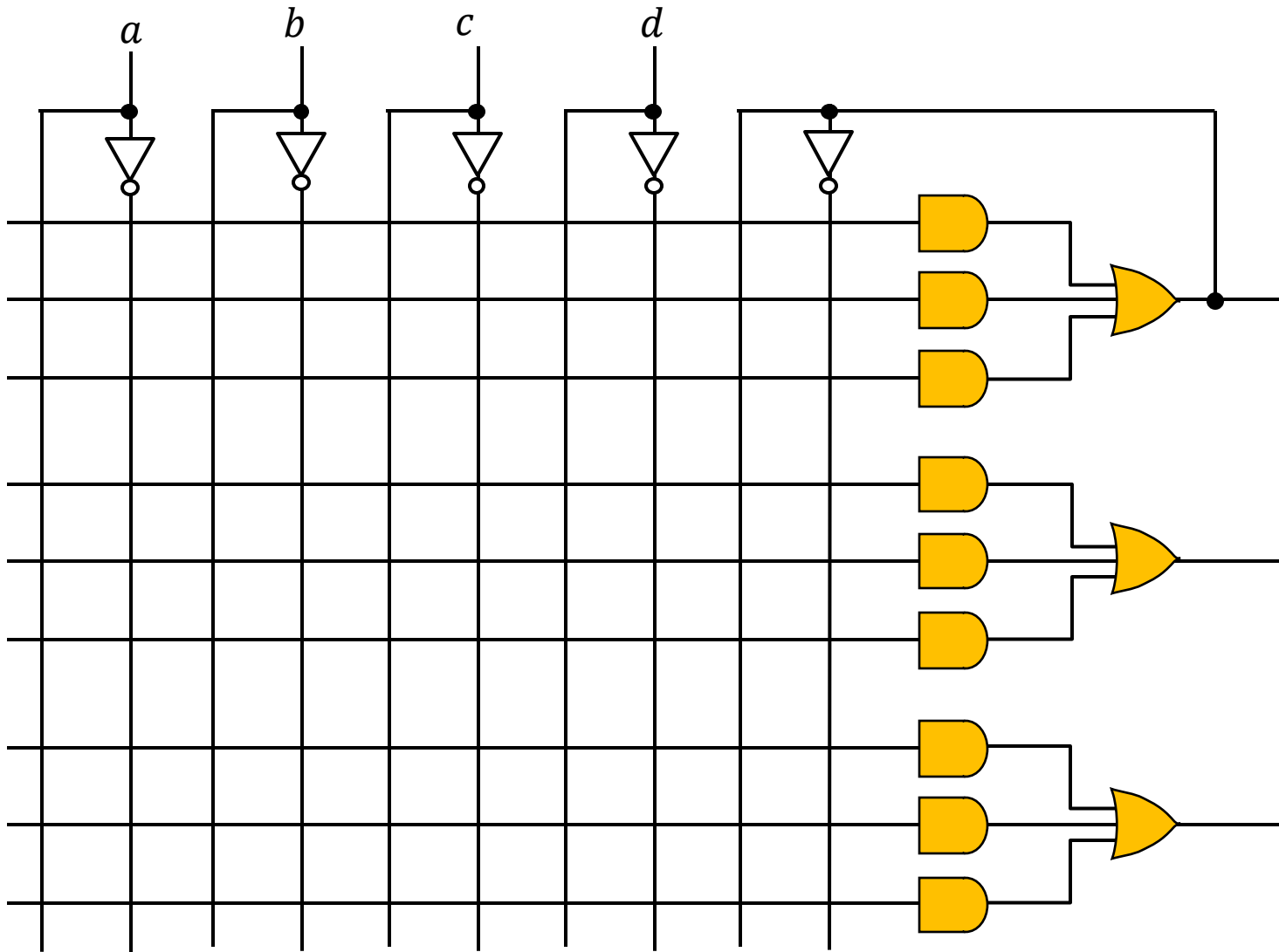

# Exercise

Implement the following functions with the PAL shown in next slide.

$$x(a, b, c, d) = \sum m(2, 12, 13)$$

$$y(a, b, c, d) = \sum m(2, 5, 8, 9, 10, 11, 12, 13)$$

$$z(a, b, c, d) = \sum m(1, 2, 8, 12, 13)$$

cd \ ab	00	01	11	10
	$m_0$	$m_4$	$m_{12}$	$m_8$
00				
01				
11				
10				

$x$

cd \ ab	00	01	11	10
00				
01				
11				
10				


$y$

cd \ ab	00	01	11	10
00				
01				
11				
10				


$z$

cd \ ab	00	01	11	10
00				
01				
11				
10				


# Exercise

 

# PAL16R6

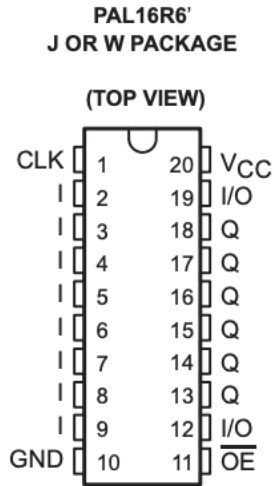


27 mm × 7.6 mm

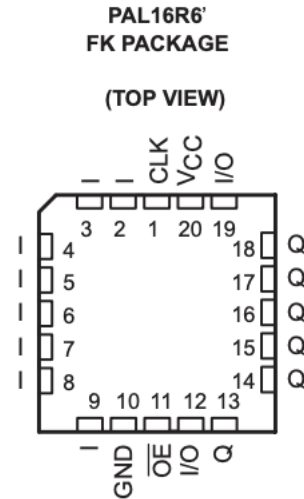

9 mm × 9 mm

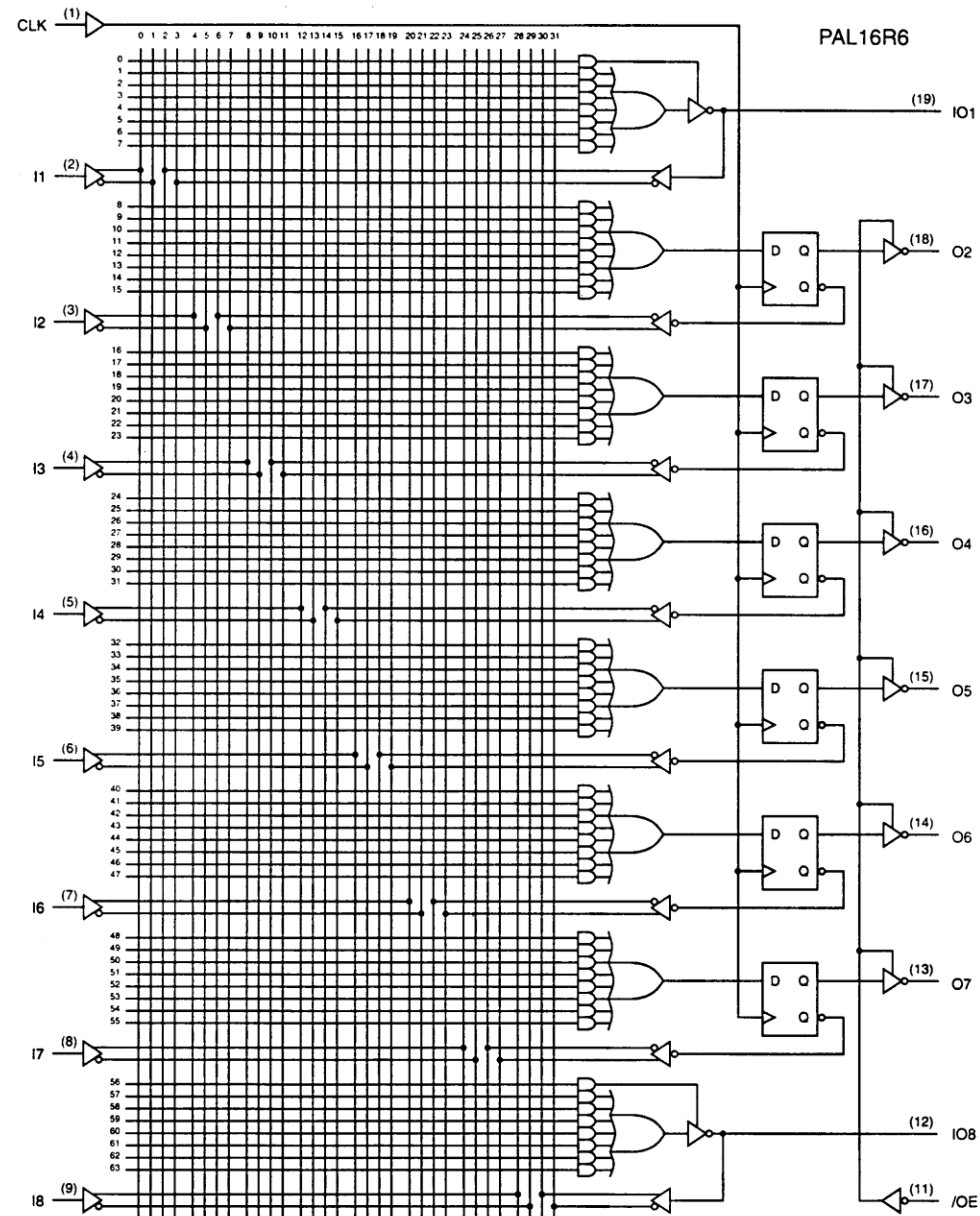- A PAL device with **16** inputs, **6** outputs with **D-latch** (1-bit memory device), and 2 un-buffered outputs
- **8** inputs are feedback from outputs
- This device can be used for designing a sequential circuit (Lecture 7)



## 6.4 Programmable Logic Array (PLA)

- PLA: Both AND and OR array are programmable
- For PROM, realize a Boolean Function based on minterm canonical expression. No minimization!
- For PLA, AND gates are programmable
  - Based on sum-of-product but may not be canonical
  - Logic designer is bounded by the number of product terms available in the AND-array
  - Simplification is necessary!

# Example

$$f_1(a, b, c) = \sum m(0, 1, 2, 6)$$

$$f_2(a, b, c) = \sum m(1, 2, 3, 4, 6)$$

		<i>ab</i>			
		00	01	11	10
<i>c</i>	0	$m_0$	$m_2$	$m_6$	$m_4$
	1	$m_1$	$m_3$	$m_7$	$m_5$

$f_1$

		<i>ab</i>			
		00	01	11	10
<i>c</i>	0	1	1	1	
	1	1			

$f_2$

		<i>ab</i>			
		00	01	11	10
<i>c</i>	0		1	1	1
	1	1	1		

$$f_1(a, b, c) = a'b' + bc'$$


$$f_2(a, b, c) = a'c + bc' + ac'$$

Four distinct  
product term

# Example

$$f_1(a, b, c) = a'b' + bc'$$

$$f_2(a, b, c) = a'c + bc' + ac'$$

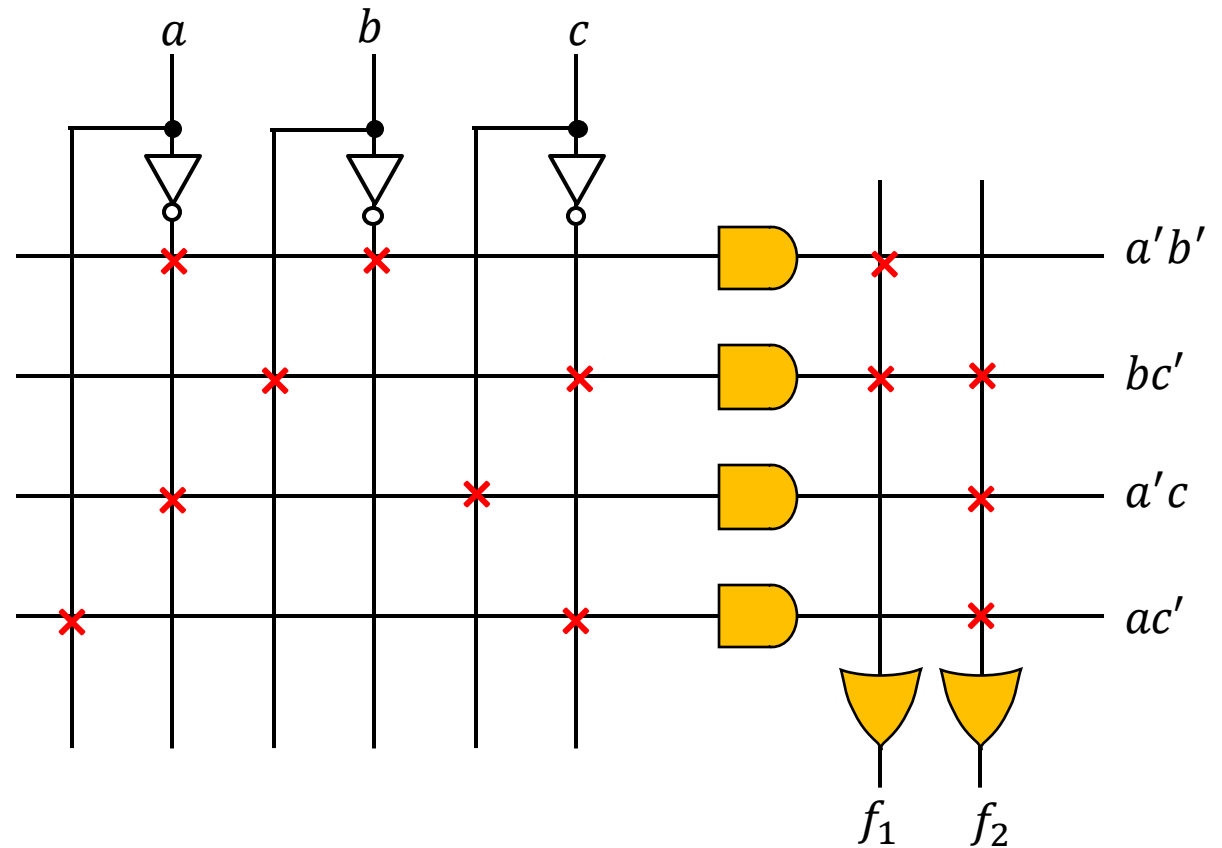




# Exercise


$$f_1(a, b, c) = \sum m(0, 2, 3, 6)$$

$$f_2(a, b, c) = \sum m(3, 6, 7)$$

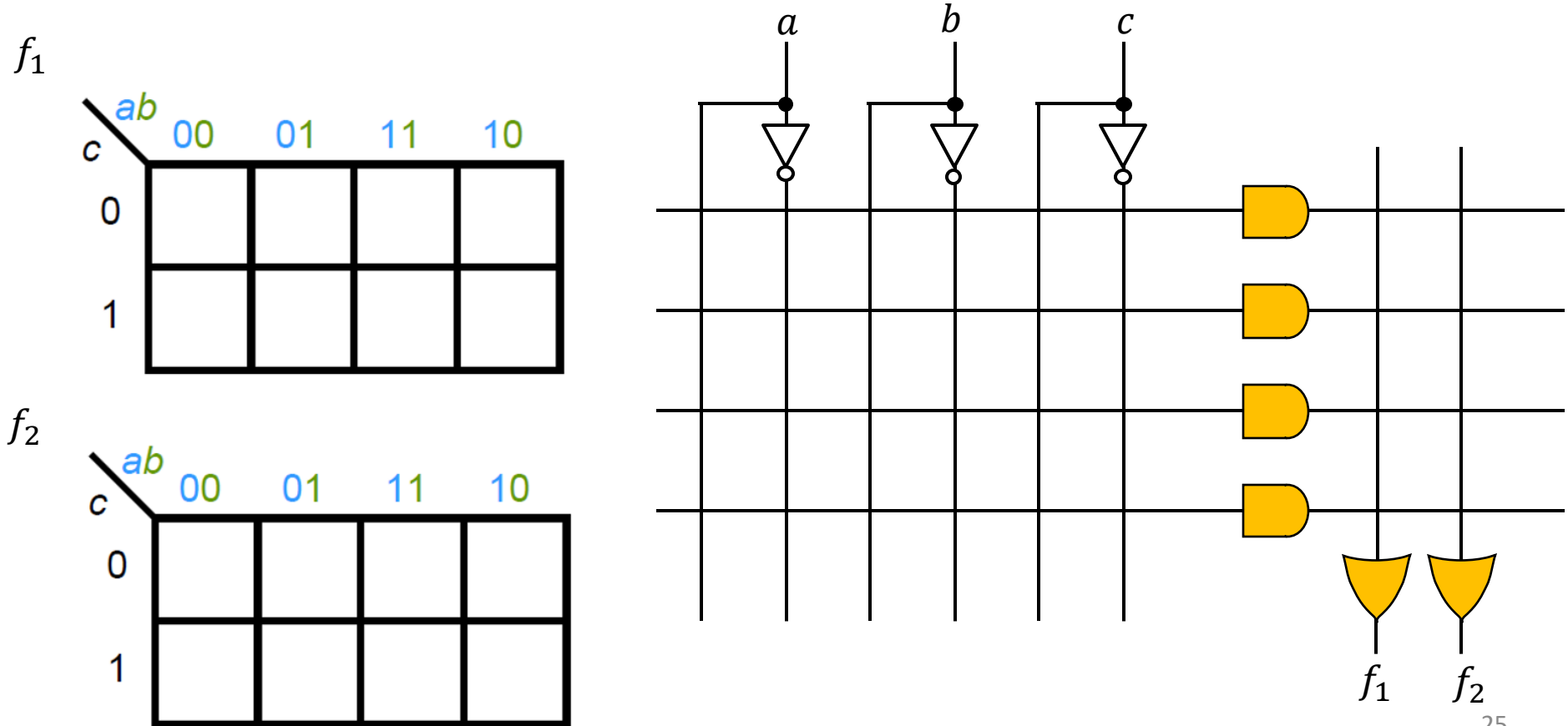
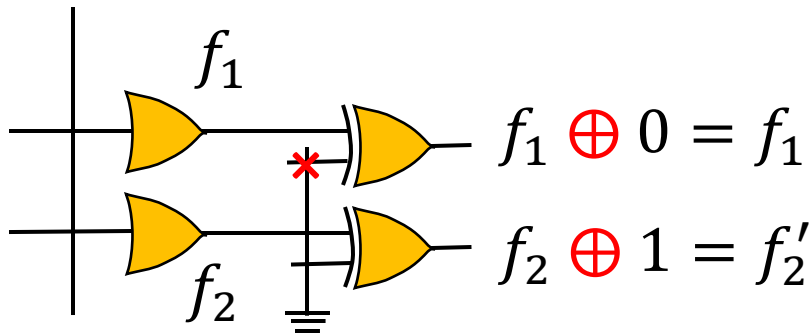
# Additional Features

- Addition of XOR gate after OR gate
- To provide flexibility for either a true output or a complemented output
- One of the inputs is connected to the ground when the fuse is intact
- If blown, the input is 1



# Example

Implement the following functions with a PLA

$$f_1(a, b, c) = ab' + ac + a'bc' \quad f_2'(a, b, c) = ac + bc$$

**PLA Programming Table**


Product terms	Input			Output	
	$a$	$b$	$c$	$f_1$	$f_2$
$ab'$	1	0	-	1	-
$ac$	1	-	1	1	1
$a'bc'$	0	1	0	1	-
$bc$	-	1	1	-	1
T/C				T	C

T: Uncomplemented output

C: Complemented output

# Example

Product terms	Input			Output	
	$a$	$b$	$c$	$f_1$	$f_2$
$ab'$	1	0	-	1	-
$ac$	1	-	1	1	1
$a'bc'$	0	1	0	1	-
$bc$	-	1	1	-	1
	T/C			T	C

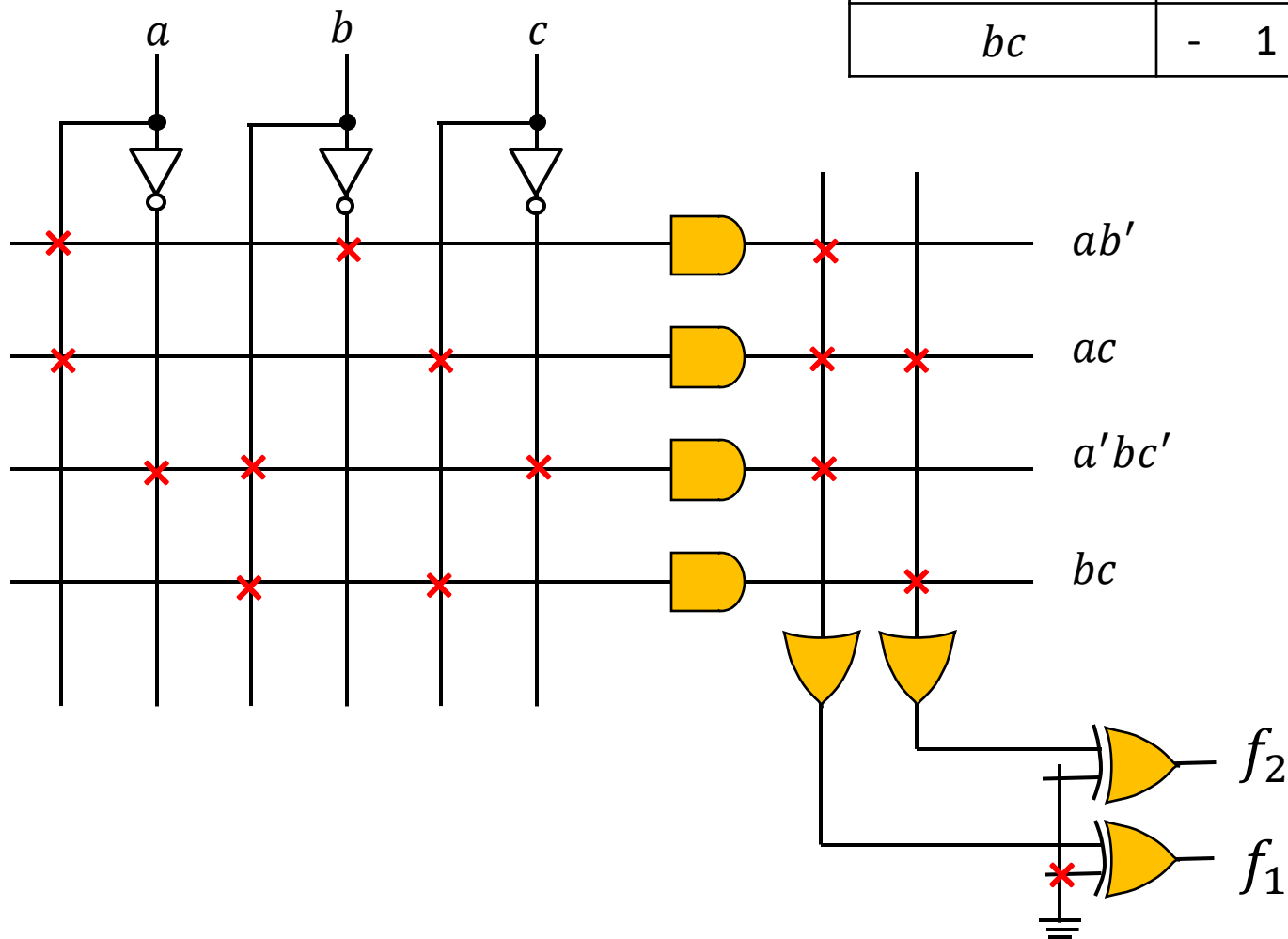

# Exercise

Implement the following functions using the PLA in next slide.

$$f_1(a, b, c, d) = \sum m(0, 2, 3, 5, 7, 8, 10, 12, 13, 15)$$

$$f_2(a, b, c, d) = \sum m(0, 4, 6, 7, 8, 10, 14, 15)$$

$f_1$

$cd \backslash ab$	00	01	11	10
00				
01				
11				
10				

$f_2$

$cd \backslash ab$	00	01	11	10
00				
01				
11				
10				

# Exercise

Implement the following functions using the PLA in next slide.

$$f_1(a, b, c, d) = \sum m(0, 2, 3, 5, 7, 8, 10, 12, 13, 15)$$

$$f_2(a, b, c, d) = \sum m(0, 4, 6, 7, 8, 10, 14, 15)$$


$f_1$

$cd \backslash ab$	00	01	11	10
00				
01				
11				
10				


$f_2$

$cd \backslash ab$	00	01	11	10
00				
01				
11				
10				


# Exercise

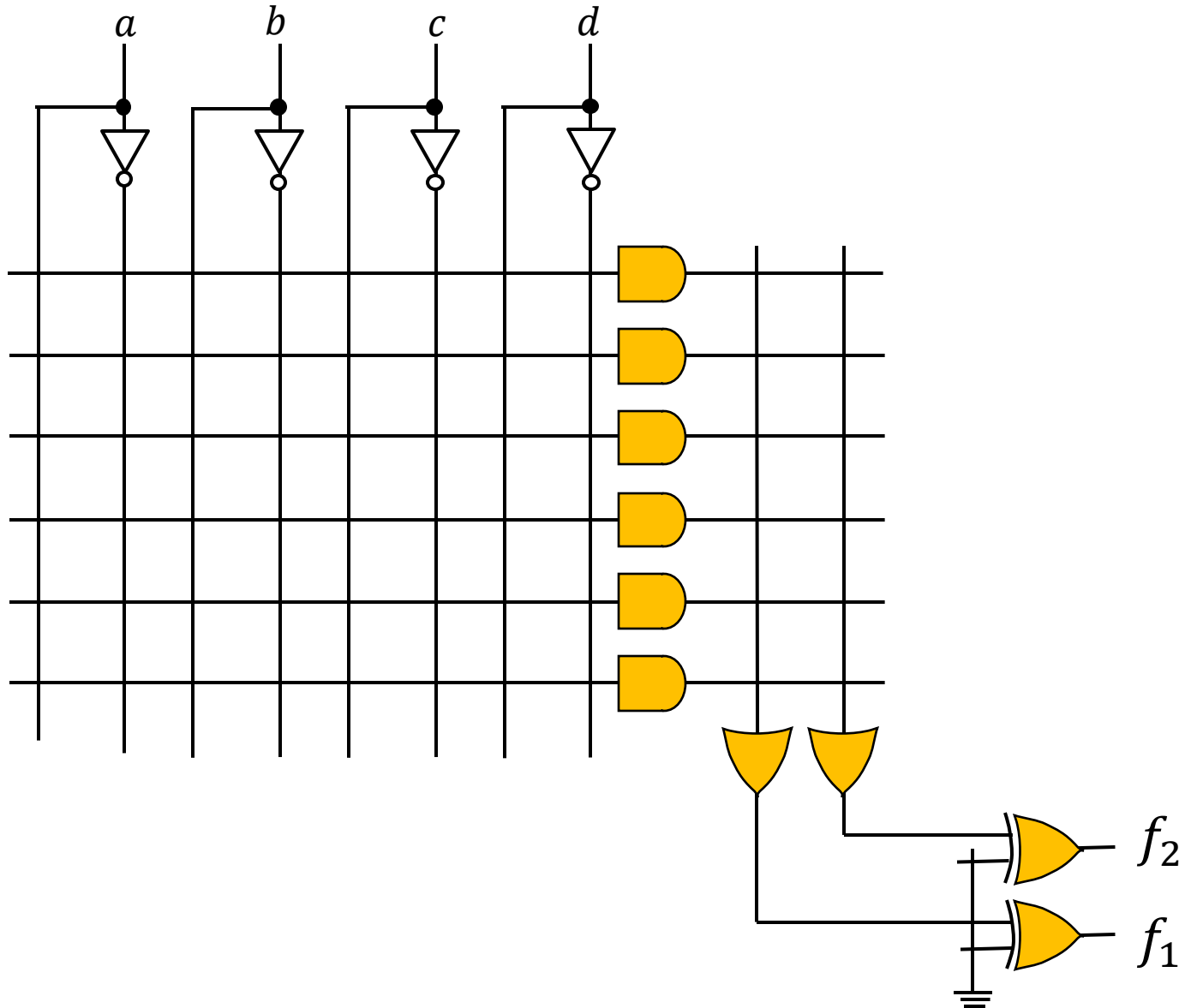


# Summary

 

(a) Programmable read-only memory (PROM)

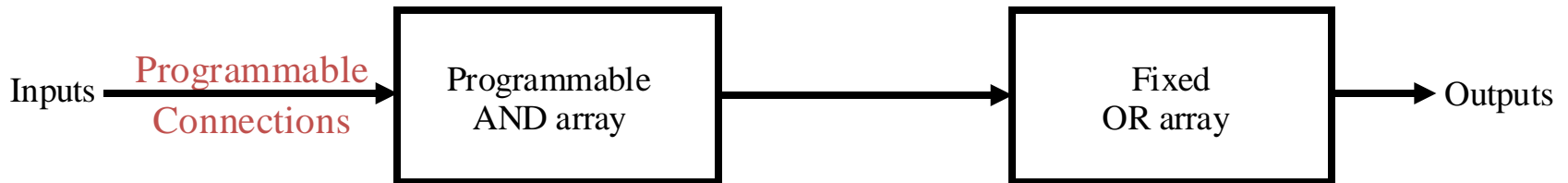

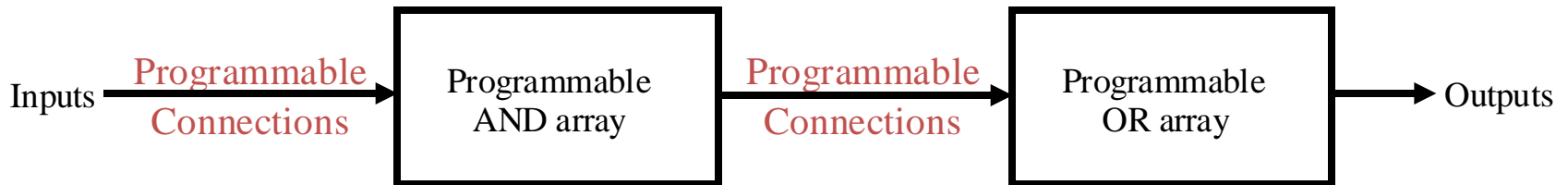(b) Programmable array logic (PAL) device





(c) Programmable logic array (PLA) device




# Given in Test and Exam

## Programmable Logic Devices

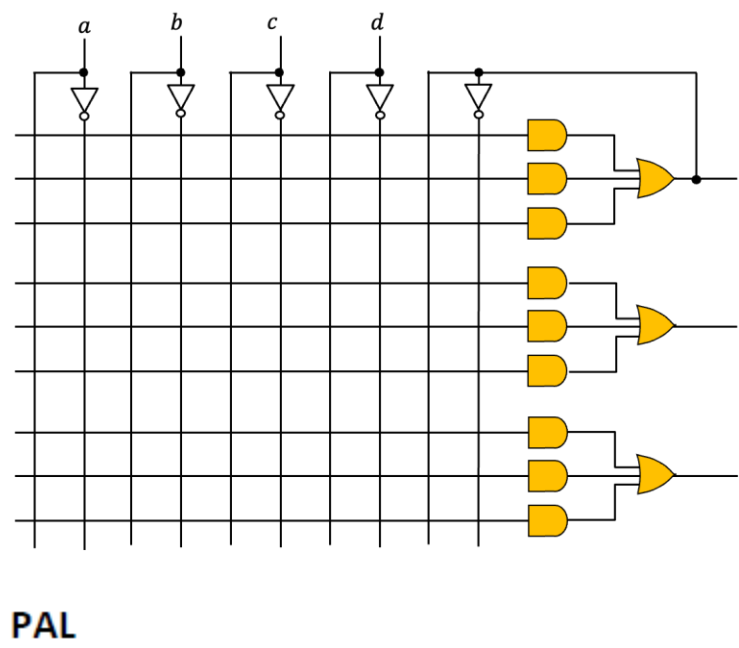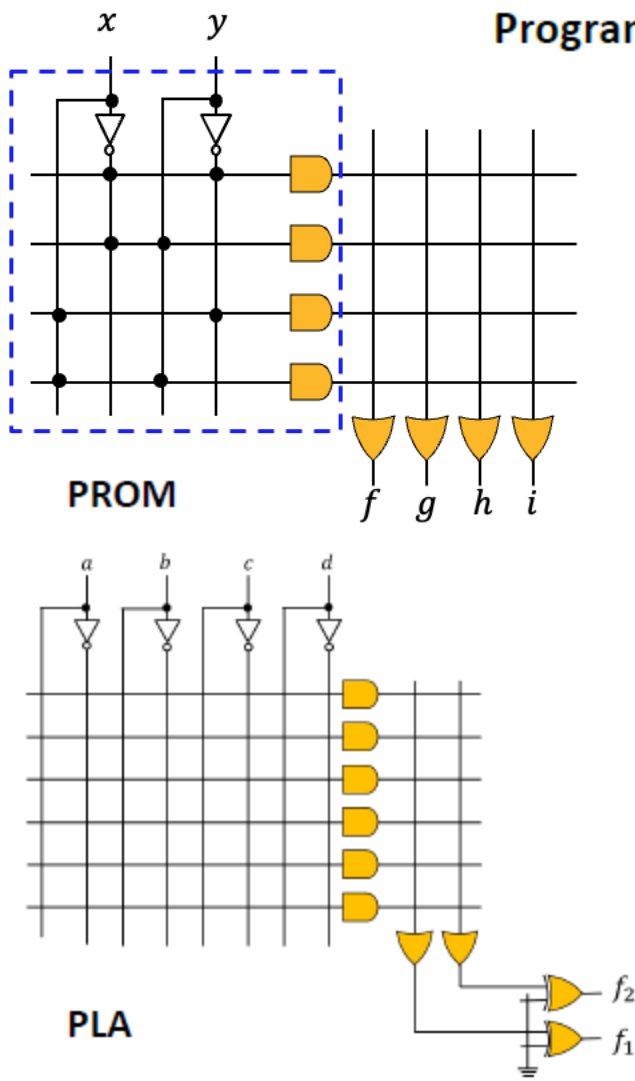
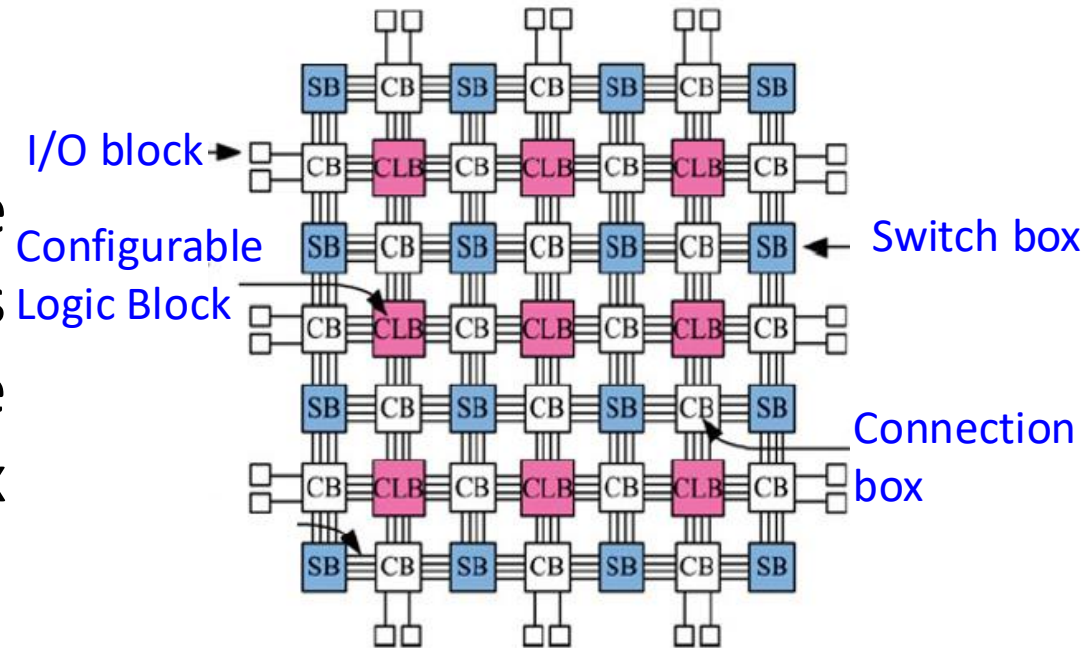
# 6.5 Field Programmable Gate Array Logic


- FPGAs consist of a large number of logic blocks with programmable interconnects in matrix form.




- Three basic components
  - **Configurable Logic Block:** To create logic circuit
  - **I/O Block:** To connect the external inputs/outputs
  - **Switch/Connection Box:** For interconnection between CLB and I/Os.
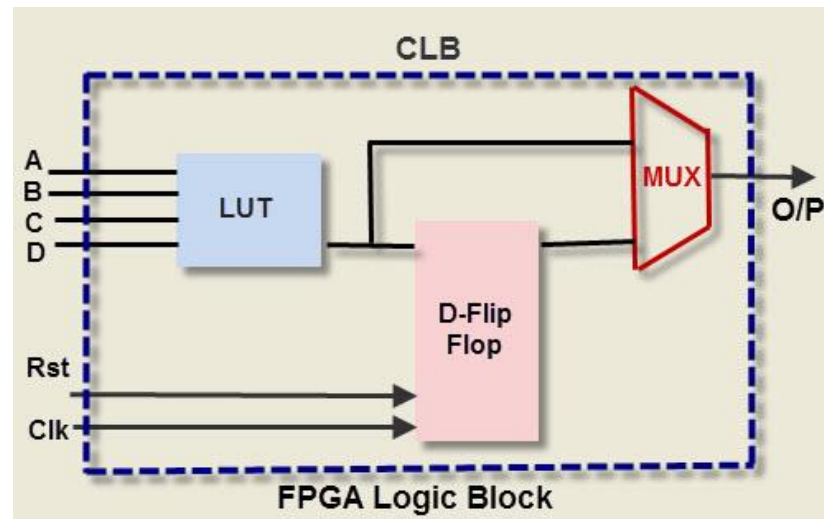
# Configurable Logic Block

- A configurable logic block (CLB) consists of a **look-up-table (LUT)**
- The LUT is for implementing the **truth table** of a logic function (*e.g.*, 4-input Boolean function)
- Additional elements are for control or other functions: D-FF (store output), MUX (select output)



# Look-up Tables (LUTs)

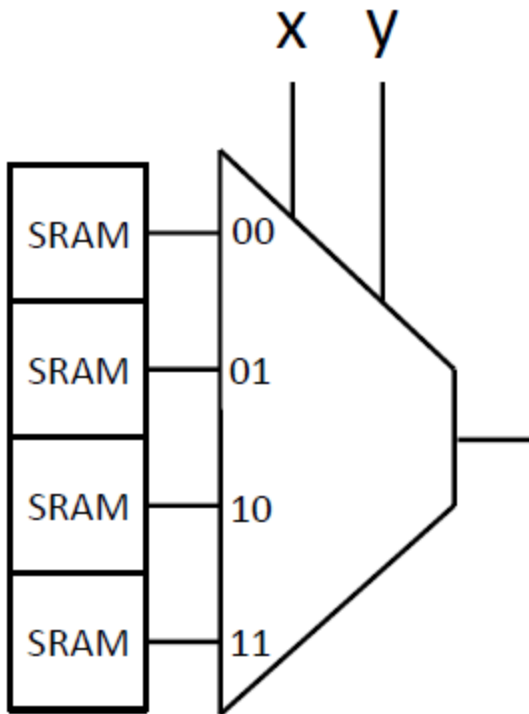

## Commercial FPGAs



- Xilinx: 6-LUT
- Altera: 6-LUT
- Microsemi: 4-LUT

For x-input LUT, the number of memory locations is  $2^x$

- 2-LUT:  $2^2 = 4$
- 4-LUT:  $2^4 = 16$



# Look-up Tables (LUTs)

x	y	z
0	0	A
0	1	B
1	0	C
1	1	D

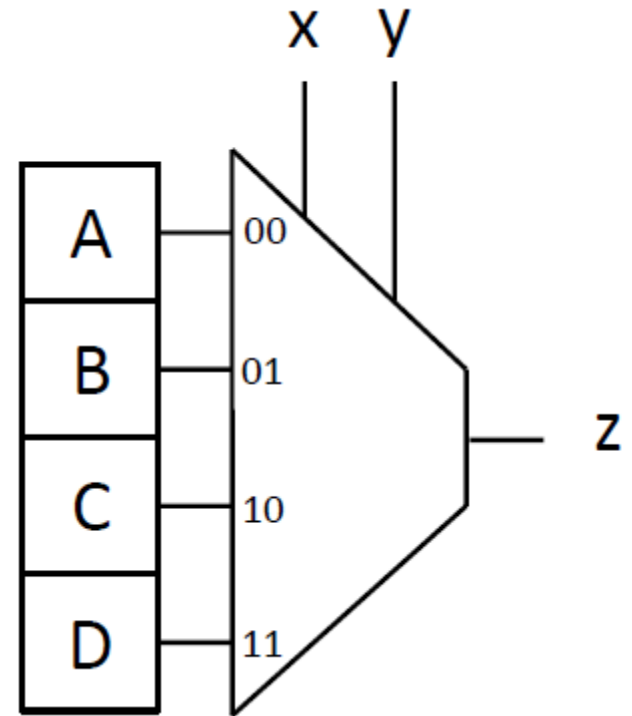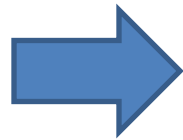



# Example (AND gate)

x	y	z
0	0	0
0	1	0
1	0	0
1	1	1

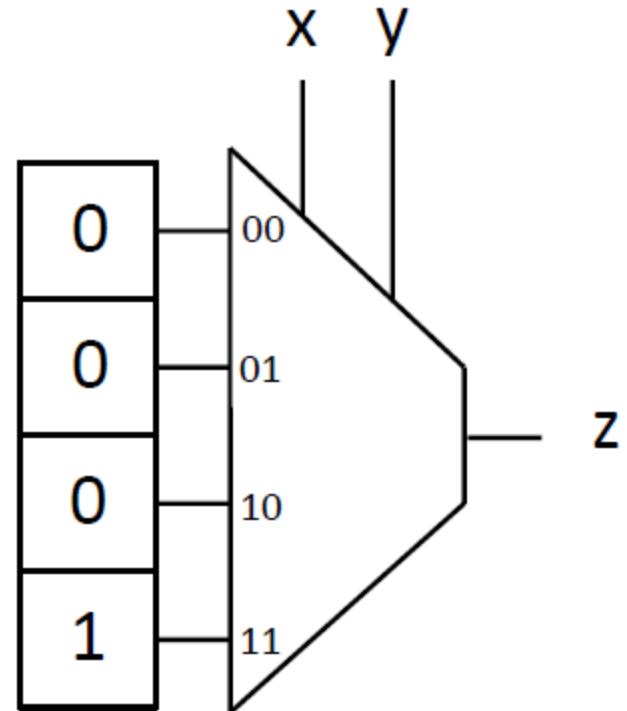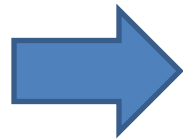



# Example (OR gate)

x	y	z
0	0	0
0	1	1
1	0	1
1	1	1

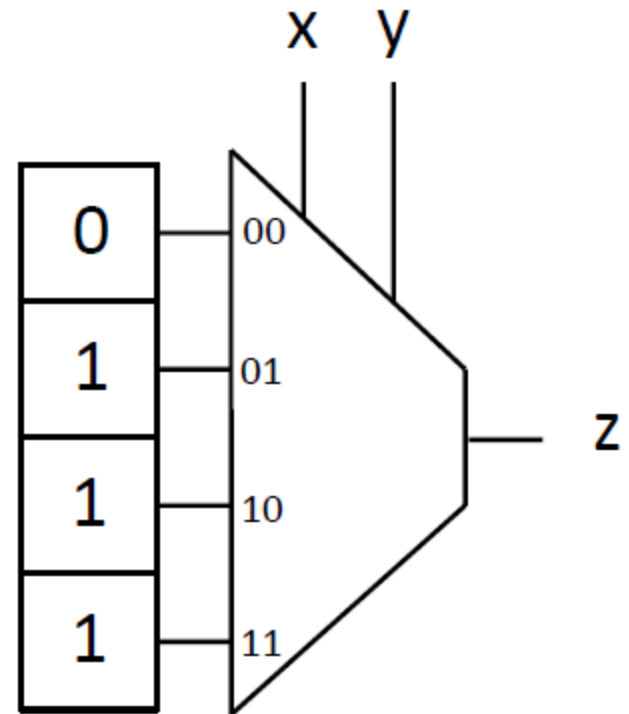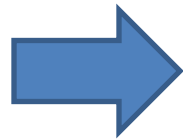

# Exercise (XOR)

x	y	z
0	0	
0	1	
1	0	
1	1	

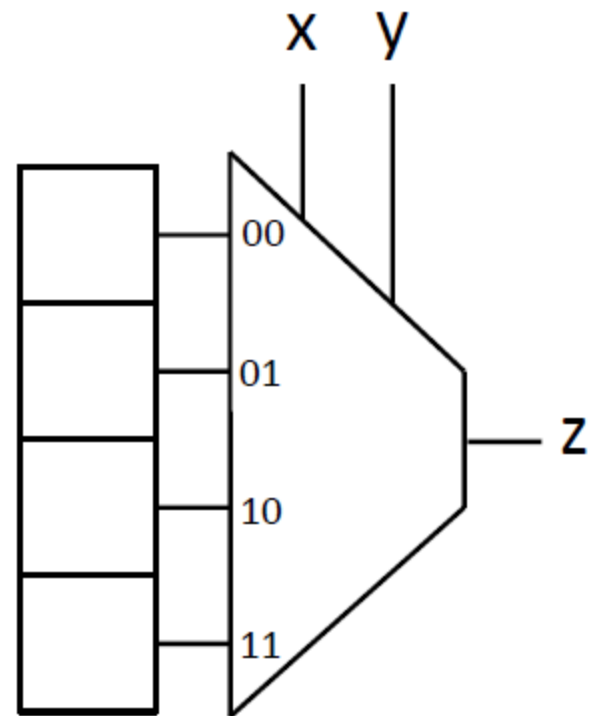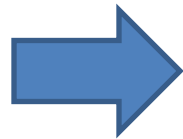



# Features of LUTs

- An  $n$ -LUT can implement any  $n$ -input logic functions
- Logic minimization: Reduce the number of inputs


Why not a large LUT?

- LUTs grow exponentially based on the number of inputs
  - 64 inputs and 1 output  $\rightarrow 2^{64}$  memory bits
- Large LUT  $\rightarrow$  long delay, less flexible
- Small LUTs: Design components that can be reused (transforming a complex circuit into simpler circuits)


# Solution for Large Inputs

## Map circuits onto multiple LUTs

- Example: Use 2-input LUTs

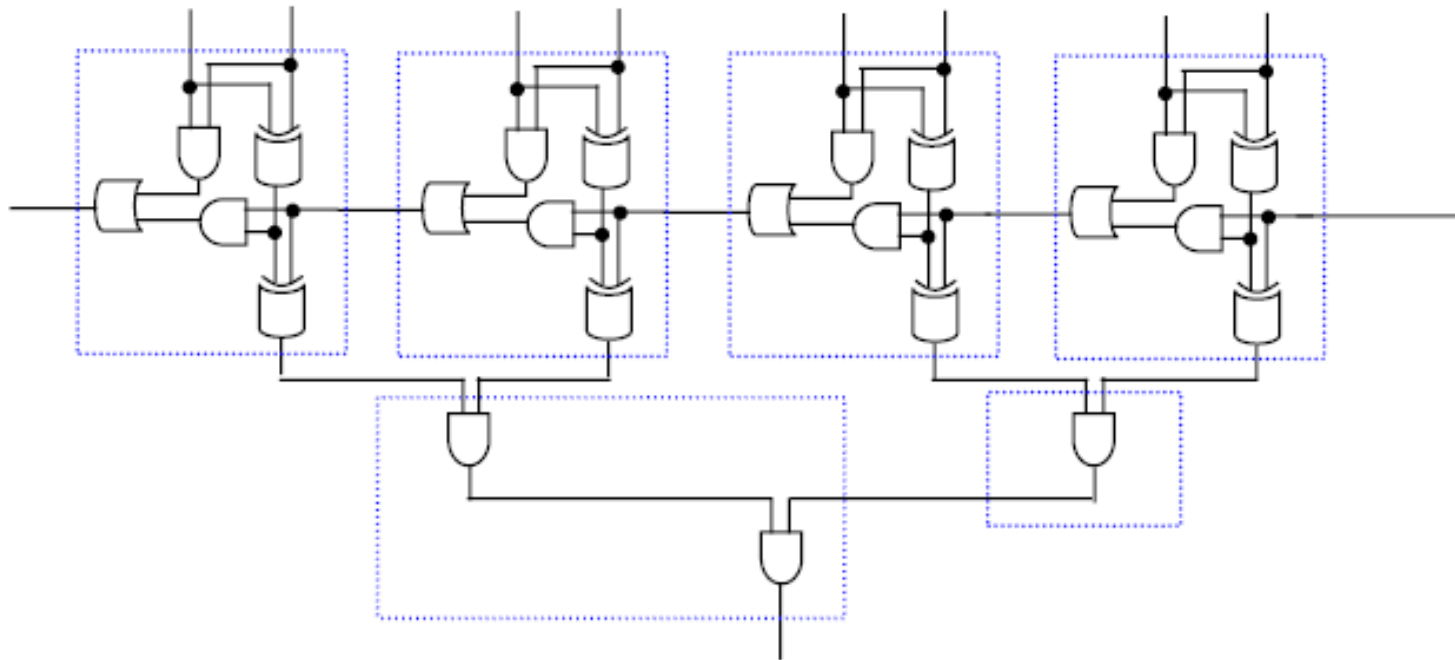


# Example (4-input LUT)

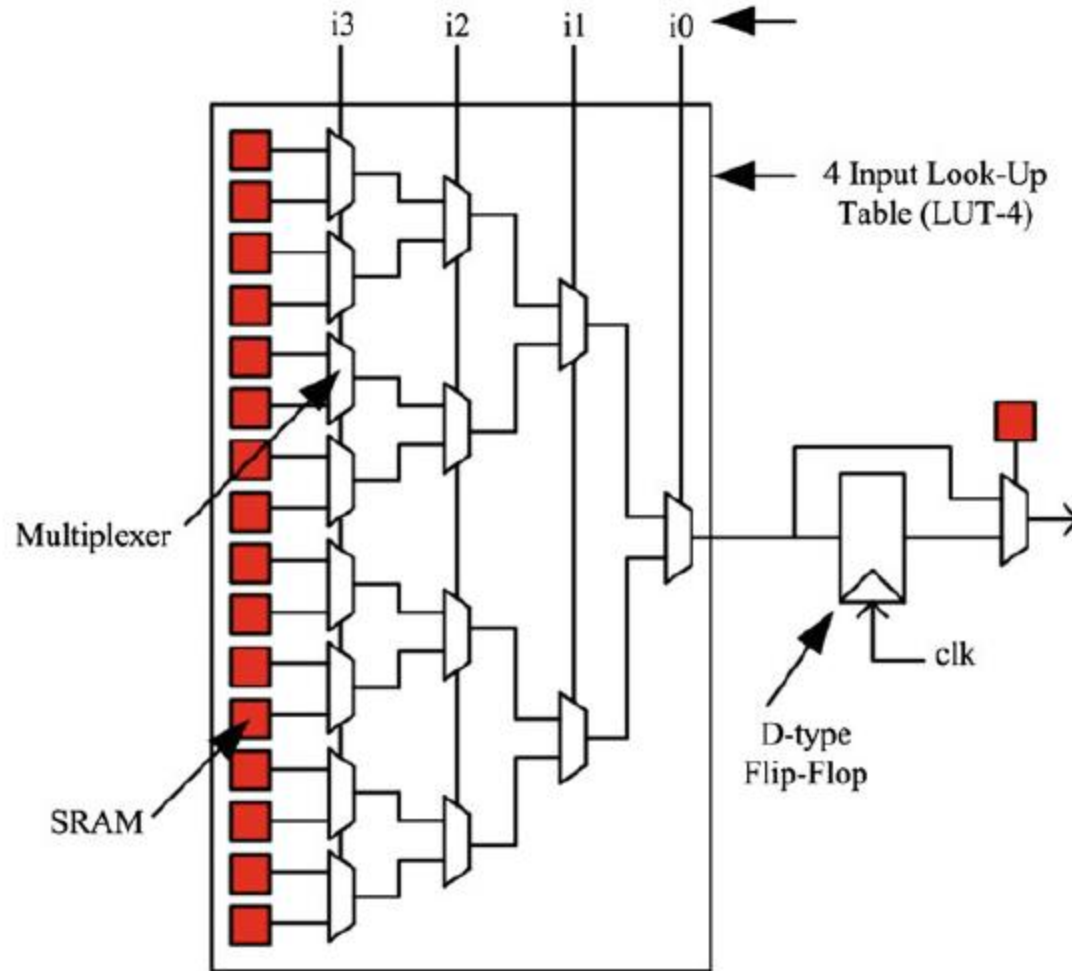
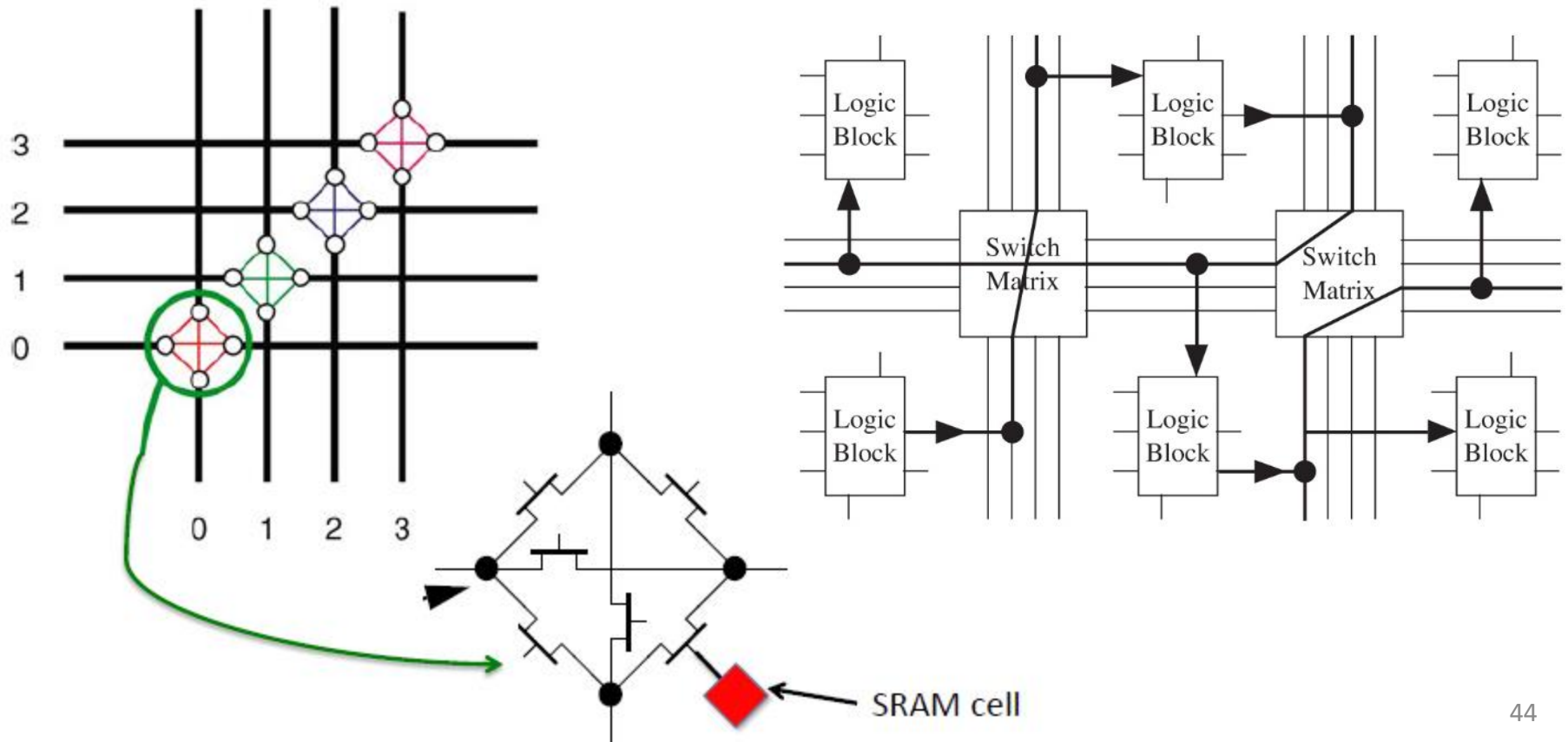
# Interconnects


- FPGAs use **switch matrices** to provide interconnects for logic blocks and I/Os
- Each switch is controlled by the SRAM cell



# I/O Standards


- FPGA output may be connected to device with different electrical requirements
- The FPGA pin I/O standard must be specified
- I/O Standards:
  - LVTTTL: low-voltage transistor-transistor logic; 3.3-V standard that can tolerate 5-V signals.
  - LVCMOS: low-voltage complementary metal-oxide semiconductor; LVCMOS2, a 2.5-V standard that can tolerate 5-V signals.
  - ...

# FPGA Design Flow

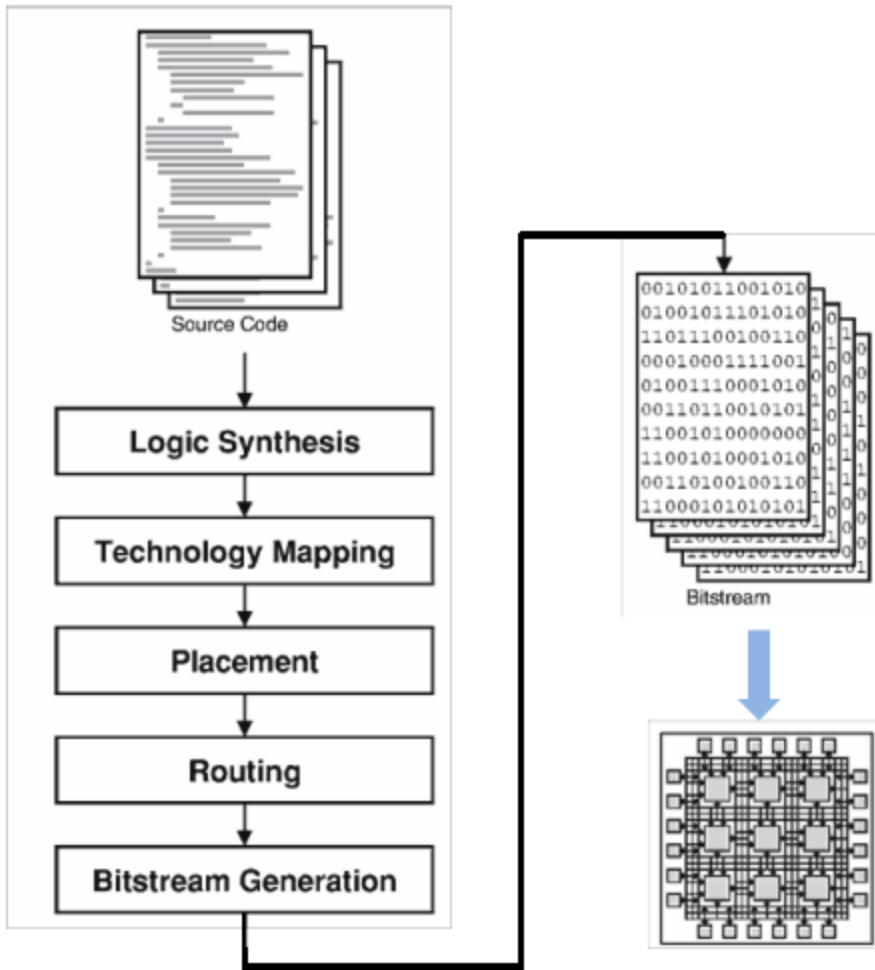

1. **Source Code:** Create a model of the design in a hardware description language such as VHDL or Verilog
2. **Simulation:** Simulate and debug the design
3. **Synthesis:** Analyze the VHDL code and implement the described logic
4. **Technology Mapping:** Transform the logic network to the LUT network

# FPGA Design Flow

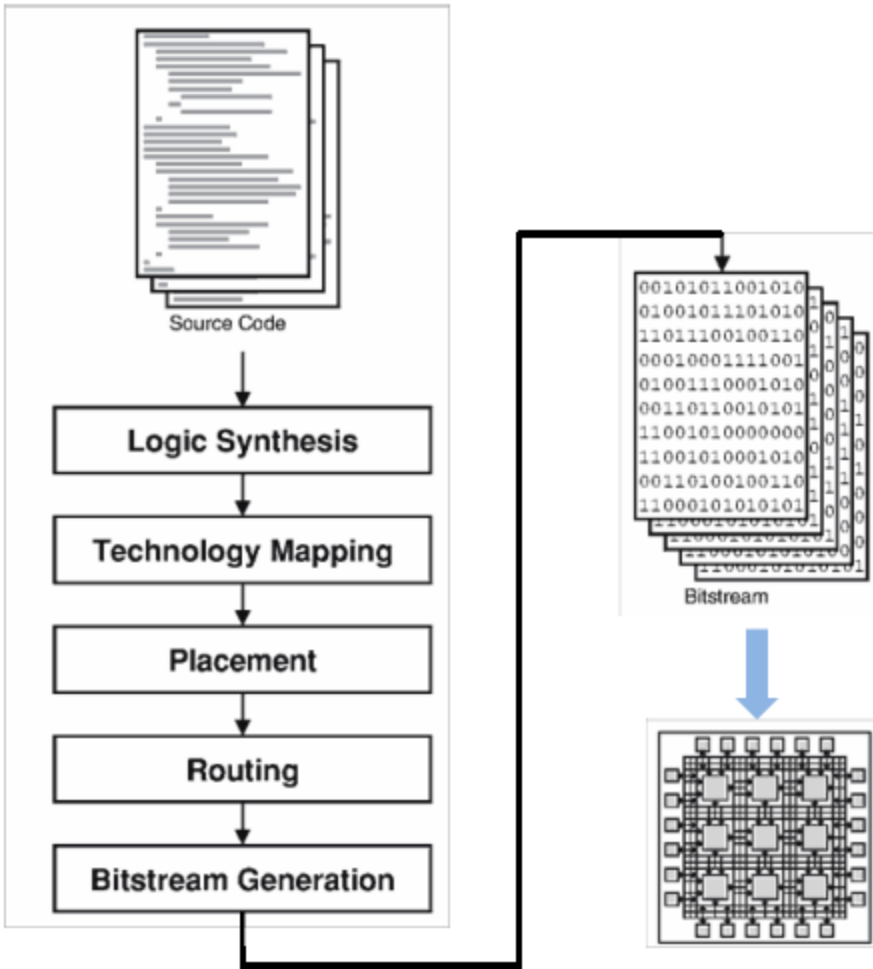

**5. Placement/Routing:** Place and interconnect all LUTs, I/Os, etc.

**6. Bitstream Generation:** Create a configuration file for all SRAM cells (logic and interconnect)

**7. Program** the FPGA based on the bitstream configuration file

**Input:** VHDL Source Codes

**Output:** Configuration bitstream