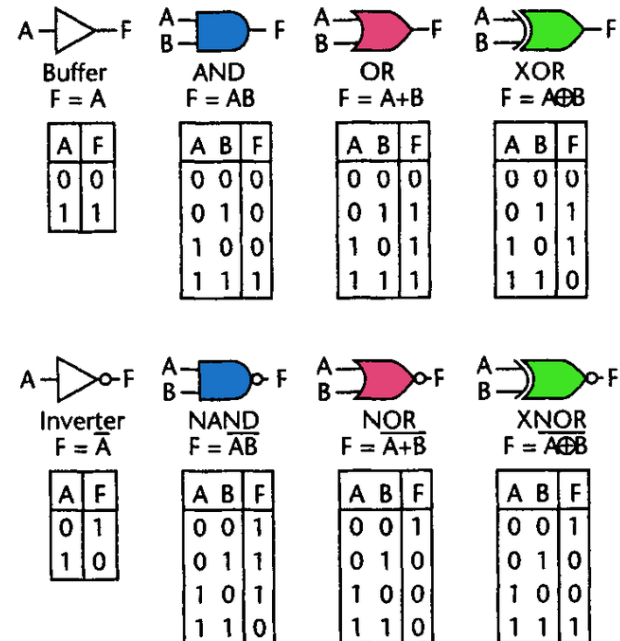



# EE2000 Logic Circuit Design

---

## Lecture 1 – Logic Function and Boolean Algebra





# Exercises

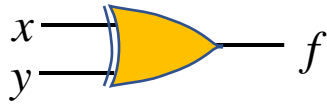


$x$	$y$	$f$
0	0	0
0	1	1
1	0	1
1	1	0

$$f = x'y + xy'$$

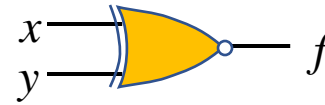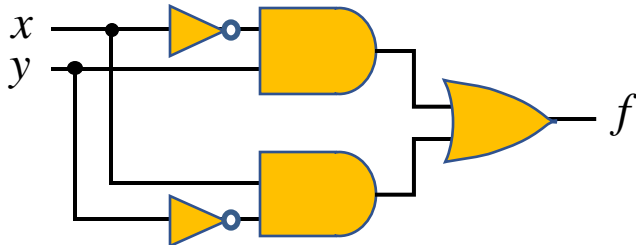

$x$	$y$	$f$
0	0	1
0	1	0
1	0	0
1	1	1


$$f = x'y' + xy$$

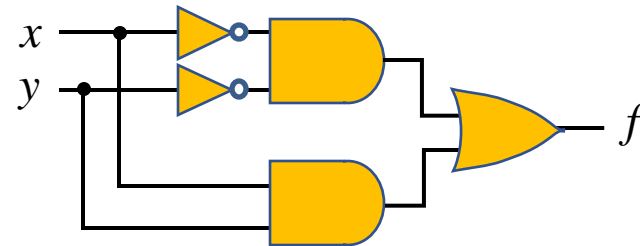

# Exercises

Given the Boolean function  $f(x, y, z) = xy' + x'z'$ , draw the Logic Circuit and work out the truth table.

<i>Inputs</i>			$xy'$	$x'z'$	<i>Output</i>
$x$	$y$	$z$			$f(x, y, z)$
0	0	0	0	1	1
0	0	1	0	0	0
0	1	0	0	1	1
0	1	1	0	0	0
1	0	0	1	0	1
1	0	1	1	0	1
1	1	0	0	0	0
1	1	1	0	0	0

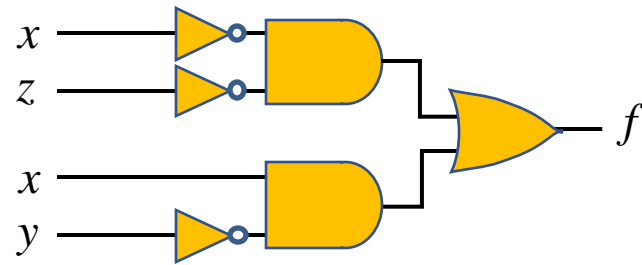

# Question

- Which of the following has the same function as  $x + x'y$ ?

a)  $x + xy'$

b)  $x + y$

c)  $x' + y$

d)  $y$

$$\begin{aligned}x + x'y &= (x + x')(x + y) && \text{distributive} \\ &= 1 \cdot (x + y) && \text{complement} \\ &= x + y && \text{identity}\end{aligned}$$

# Exercise

- Simplify the following expression.

$$xyz' + xyz + xy'z + x'yz + x'y'z + x'y'z'$$

$$= xy + xy'z + x'yz + x'y' \quad \text{adjacency}$$

$$= x(y + y'z) + x'(y' + yz) \quad \text{simplification}$$

$$= x(y + z) + x'(y' + z)$$

$$= xy + x'y' + z(x + x') \quad \text{complement}$$

$$= xy + x'y' + z$$

5 literals; 3 terms

# Exercise

- Simplify the following expression.

$$(x + y + z)(x + y + z')(x + y' + z)(x + y' + z') \quad \text{adjacency}$$

$$= (x + y)(x + y')$$

$$= x$$

1 literal; 1 term

# Question

Which of the following can be simplified using consensus theorem?

a)  $xy'z + wx' + wy'z' + wy$

b)  $wxy' + xyz' + w'xz' + yz$

c)  $wx' + xy'z + w'yz' + x'yz'$