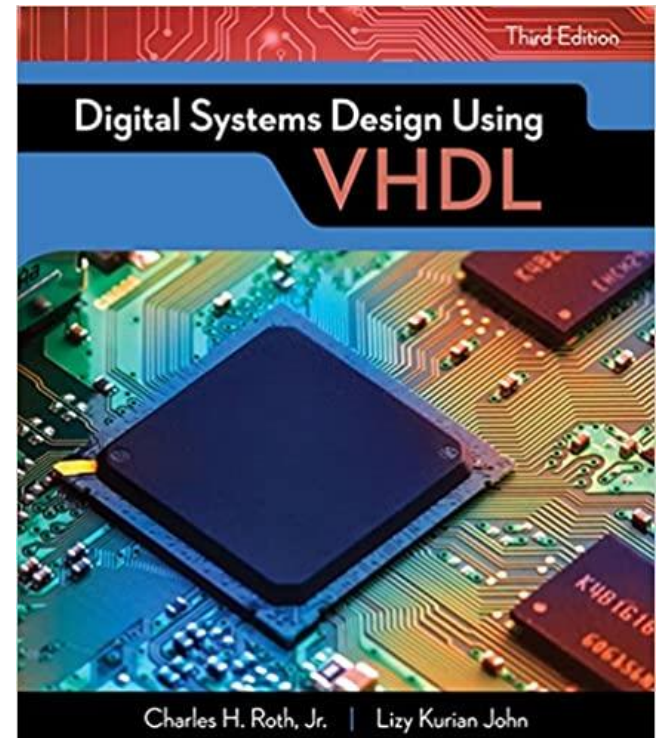


EE2000 Logic Circuit Design

Lecture 4- VHDL



Question

Which of the following identifier is illegal to be used as an entity name in VHDL?

- TwO_gaTE Legal
- 2_gate Illegal – cannot start with a number
- T2-gate Illegal – cannot have other symbol
- _2gate Illegal – cannot start with underscore
- AND Illegal – Reserved word

Exercise

```
signal C: bit_vector (0 to 3);  
signal D: bit_vector (3 downto 0);  
signal A: bit_vector (7 downto 0);
```

```
C <= "1101";  
D <= C;  
A(6 downto 3) <= D;
```

Determine the stored value in the following bit object

```
C(0) = 1  C(1) = 1  C(2) = 0  C(3) = 1  
D(3) = 1  D(2) = 1  D(1) = 0  D(0) = 1  
A(6) = 1  A(5) = 1  A(4) = 0  A(3) = 1
```

Exercise

Transform the following logic expression to VHDL code

1) $f = ab' + a'b$

```
f <= a AND NOT b OR NOT a AND b;  
f <= (a AND NOT b) OR (NOT a AND b);
```

2) $f = a(b' + a')b$

```
f <= a AND (NOT b OR NOT a) AND b;
```


Exercise

Transform the following logic expression to VHDL code

Boolean	VHDL Boolean
$Y = \overline{AB}$	<pre>Y <= NOT (A AND B) ; or Y <= A NAND B ;</pre>
$Y = \overline{A + B}$	<pre>Y <= NOT (A OR B) ; or Y <= A NOR B ;</pre>
$Y = A + BC$	<pre>Y <= A OR (B AND C) ;</pre>
$Y = C\overline{X + D}$	<pre>Y <= C AND NOT (X OR D) ;</pre>
$Y = A\overline{B}C + \overline{A}\overline{B}C + \overline{A}BC$	<pre>Y <= (A AND NOT B AND C) OR (NOT A AND NOT B AND C) OR (NOT (A AND B) AND C) ;</pre>

 Exercise

Write your own VHDL statement to describe the logic circuit



```
S1 <= x1 OR x2;  
S2 <= x3 AND x4;  
F <= S1 XOR S2;
```


OR

```
F <= (x1 OR x2) XOR (x3  
AND x4);
```

- The Left-hand style is more readable and traceable but needs to declare two more signals
- In contrast, the Right-hand style uses fewer lines of code but is a bit difficult for debugging
- They both have the same result after being synthesized

 Exercise

Write your own VHDL statement to describe the logic circuit



```
Sig1 <= x XOR y;  
Sig2 <= x AND y;  
Sig3 <= Sig1 AND Cin;  
s <= Cin XOR Sig1;  
Cout <= Sig3 OR Sig2;
```