

# EE2000 Logic Circuit Design



---

## Lecture 5 – Combinational Functional Blocks



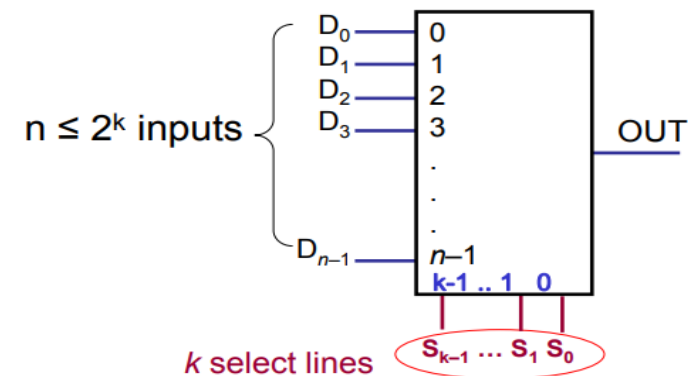 
# Multiplexer (MUX)

- Basically a digital switch
- Pass one of the inputs to the output
- Selected by the control input.




- $k$  control inputs
- $n$  data inputs,  $n \leq 2^k$
- 1 output

# 2-to-1 Multiplexer (MUX)

 

Input			Output
$S$	$D_1$	$D_0$	
0	x	x	$D_0$
1	x	x	$D_1$

$$\text{OUT} = S'D_0 + SD_1$$

 

# 4-to-1 Multiplexer (MUX)

## ■ Specification:

■  $m = 4$


■  $n = \log_2 m = 2$

## ■ Formulation:

Inputs						Output
$I_0$	$I_1$	$I_2$	$I_3$	$S_1$	$S_0$	$Y$
x	x	x	x	0	0	$I_0$
x	x	x	x	0	1	$I_1$
x	x	x	x	1	0	$I_2$
x	x	x	x	1	1	$I_3$
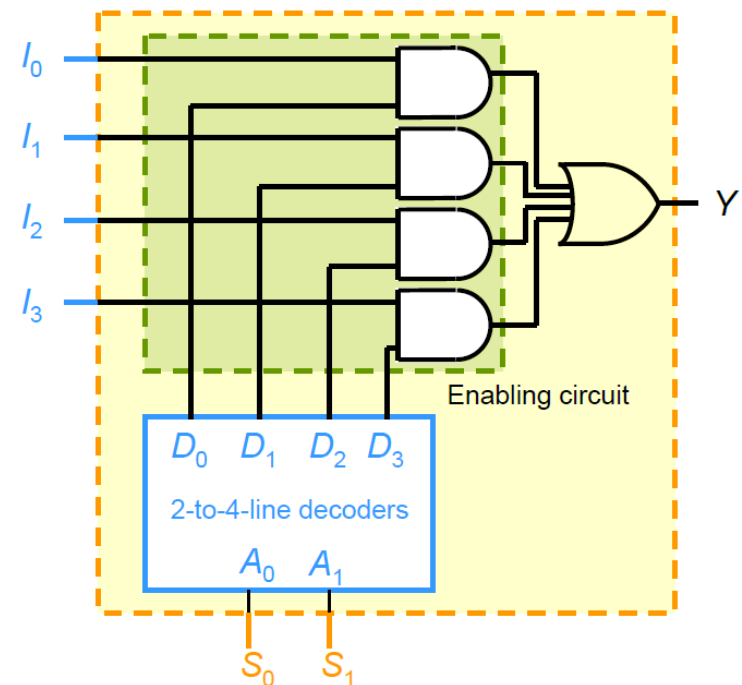
## ■ Optimization:

■  $Y(I_0, I_1, I_2, I_3, S_1, S_0) =$   
 $S_1' S_0' I_0 + S_1' S_0 I_1 +$   
 $S_1 S_0' I_2 + S_1 S_0 I_3$



# Example

Realize the function  $f(w, x, y, z) = \sum m(1, 2, 5, 7, 9, 11, 13)$  using a 4-to-1 MUX

STEP 1: Plot the K-map

$wx \backslash yz$		00	01	11	10
00		1			1
01		1	1		
11		1			
10		1	1		

# Example

STEP 2: Since 4-to-1 MUX has 2 control inputs, choose two variables for these inputs

$$w = S_1 \quad x = S_0$$

$wx$	$yz$			
	00	01	11	10
00		1		1
01		1	1	
11		1		
10		1	1	

STEP 3:

$$f(w = 0, x = 0) = y'z + yz'$$

$$f(w = 0, x = 1) = z$$

$$f(w = 1, x = 1) = y'z$$

$$f(w = 1, x = 0) = z$$

# Example


$$w = S_1 \quad x = S_0$$

$$f(w = 0, x = 0) = y'z + yz'$$

$$f(w = 0, x = 1) = z$$

$$f(w = 1, x = 1) = y'z$$

$$f(w = 1, x = 0) = z$$

 

**Question:** How can we realize the function using 2-to-1 muxs?

# Exercise

Realize the function  $f(w, x, y, z) = \sum m(1, 2, 5, 7, 9, 11, 13)$  using a 2-to-1 MUX

$wx$ \ $yz$		00	01	11	10
00			1		1
01			1	1	
11			1		
10			1	1	



# Exercise

Realize the function  $f(w, x, y, z) = \sum m(1, 2, 5, 7, 9, 11, 13)$  using an 8-to-1 MUX


$wxyz$	$F$
0000	0
0001	1
0010	1
0011	0
0100	0
0101	1
0110	0
0111	1

$wxyz$	$F$
1000	0
1001	1
1010	0
1011	1
1100	0
1101	1
1110	0
1111	0



# Summary

With		2-to-1 Mux	4-to-1 Mux	8-to-1 Mux
wxyz	F	$S_0=w$	$S_1=w, S_0=x$	$S_2=w, S_1=x, S_0=y$
0000	0	$I_0 = xz + y'z + x'yz'$	$I_0 = y \oplus z$	$I_0 = z$
0001	1			$I_1 = z'$
0010	1			
0011	0			
0100	0		$I_1 = z$	$I_2 = z$
0101	1			
0110	0			$I_3 = z$
0111	1			
1000	0	$I_1 = x'z + y'z$	$I_2 = z$	$I_4 = z$
1001	1			
1010	0			$I_5 = z$
1011	1			
1100	0		$I_3 = y'z$	$I_6 = z$
1101	1			
1110	0			$I_7 = 0$
1111	0			

# Cascading Multiplexers

 


Inputs						Output
$I_0$	$I_1$	$I_2$	$I_3$	$S_1$	$S_0$	$Y$
x	x	x	x	0	0	$I_0$
x	x	x	x	0	1	$I_1$
x	x	x	x	1	0	$I_2$
x	x	x	x	1	1	$I_3$

  

 
# Demultiplexer (DMUX)

- Reverse the function of MUX
- Route a single input to one of the many outputs
- Selected by the control input.


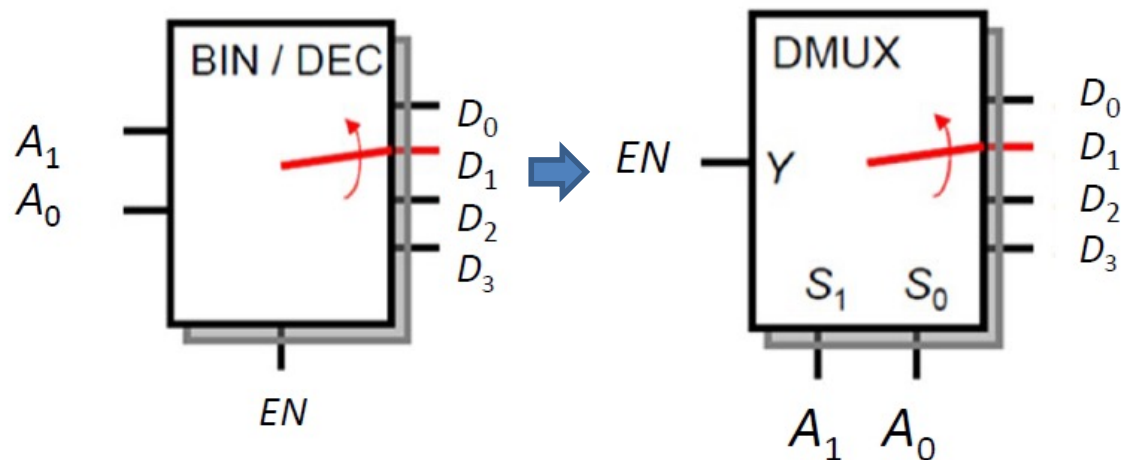
# Demultiplexer (DMUX)


- Remember the decoder with Enable?
- The decoder can perform demultiplexer if we take EN as the input line,  $A_i$  (input lines of decoder) as the selection inputs



Input	Select lines		Output			
$EN$	$A_1$	$A_0$	$D_3$	$D_2$	$D_1$	$D_0$
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	1	0	0	1	0	0
1	1	1	1	0	0	0
0	X	X	0	0	0	0

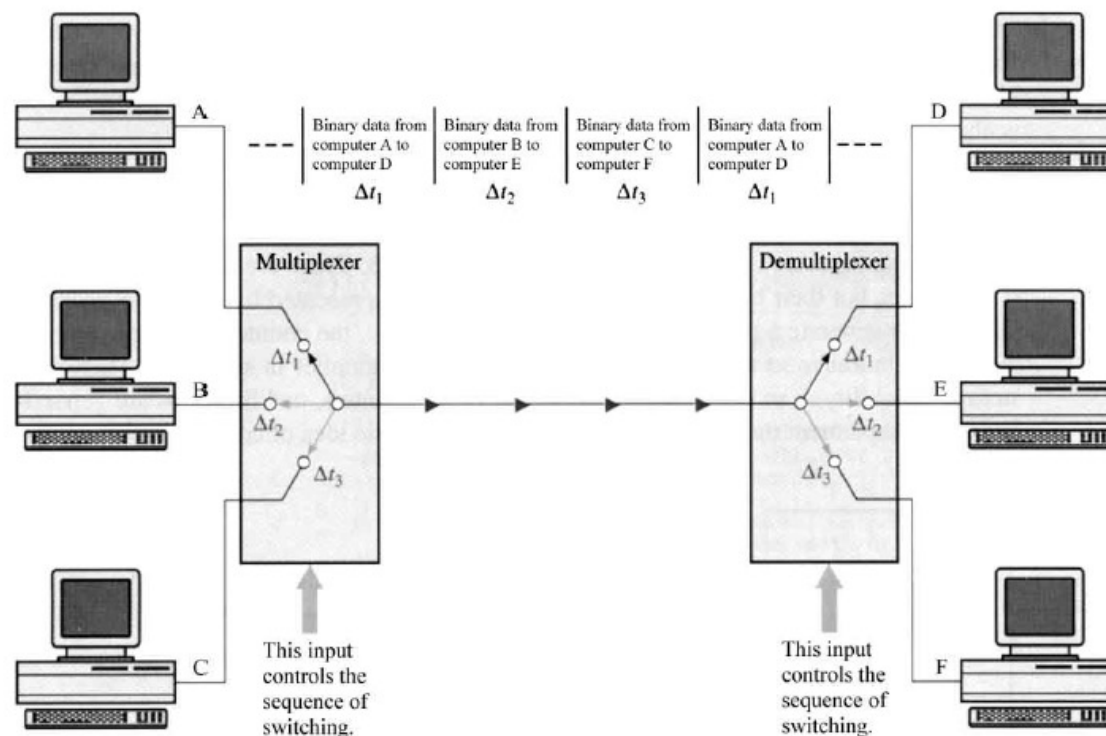
# Example of MUX & DMUX Application

- A MUX allows digital information from several sources to be routed onto a single line for transmission over that line to a common destination
- A DMUX basically reverses the multiplexing function




# Summary

Only 1 output is '1'

 


Binary Decoder

 


MUX

Only 1 input is '1'

 

Binary Encoder

1 input

 

DMUX

# Lab Session 2

## Objectives

- Learn the modular design flow
- Implement a **1-bit Full-Adder** using VHDL
- Implement a **4-bit Full-Adder** using VHDL


### 1-bit Full-Adder

Input			Output	
i_Cin	i_A	i_B	o_S	o_Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


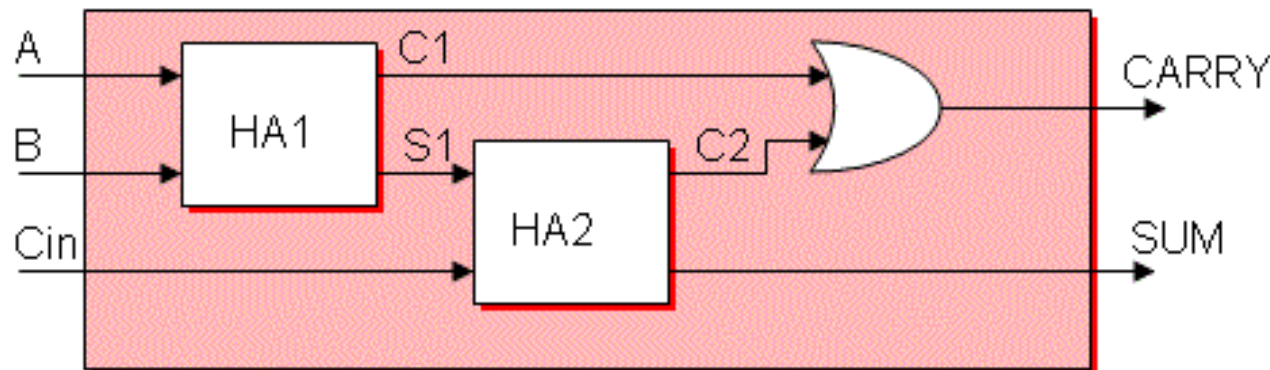
# Components and Instantiation

- **Structural modeling**: Modular design of a complex project
- When designing a complex project, we can split it into two or more simple designs (sub-modules/sub-circuits/**components**)
- Example: A full adder (FA) contains of 2 half adders (HAs); Half adder can be modeled by a **component**



# Structural Modeling

- **Structural modeling** or modular design allows us to pack low-level functionalities into modules
- Allows a designed module to be **reused** without the need to reinvent and re-test the same functions/modules every time
- To include a **component** into a **module**, we need to
  - (1) declare** the component
  - (2) instantiate** the componentin **architecture**

# Component Declaration

- An architecture may contain multiple components and they must be declared first

```
architecture [name] ...  
[signal]
```

```
component XX          -- Component declaration  
...  
end component;
```

```
component YY          -- Component declaration  
...  
end component;
```

```
begin  
...          -- Component instantiation  
end [name];
```

# Half Adder

Create the sub-module of half adder first

$$\text{sum} = a \oplus b \quad \text{carry} = a \cdot b = ab$$

Inputs		Outputs	
<i>a</i>	<i>b</i>	<i>c</i>	<i>s</i>
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

```
--sub module(half adder) entity declaration
entity halfadder is
port (a : in   STD_LOGIC;
       b : in   STD_LOGIC;
       sum : out STD_LOGIC;
       carry : out STD_LOGIC
       );
end halfadder;

architecture Behavioral of halfadder is
begin
  sum <= a xor b;
  carry <= a and b;
end Behavioral;
```

# Full Adder

```
--top module(full adder) entity declaration
```

```
entity fulladder is
```

```
    port (a : in std_logic;  
          b : in std_logic;  
          cin : in std_logic;  
          sum : out std_logic;  
          carry : out std_logic  
          );
```

```
end fulladder;
```

```
--top module architecture declaration
```


```
architecture behavior of fulladder is
```

```
    component halfadder
```

```
    port (
```

```
        a : in std_logic;  
        b : in std_logic;  
        sum : out std_logic;  
        carry : out std_logic  
    );
```

```
    end component;
```

 


```
--sub-module(half adder) is  
declared as a component  
before the keyword "begin"
```

# Component Instantiation

Differences between a **component** and an **entity** declaration:

- **Entity** declaration declares a circuit model containing one or multiple architectures
- **Component** declaration declares a **virtual circuit** template, which must be **instantiated** to take effect during the design
- **Instantiation** – To map the signals in the entity with the input/output of the component
- **Port map** is required for component **instantiation**

# Full Adder

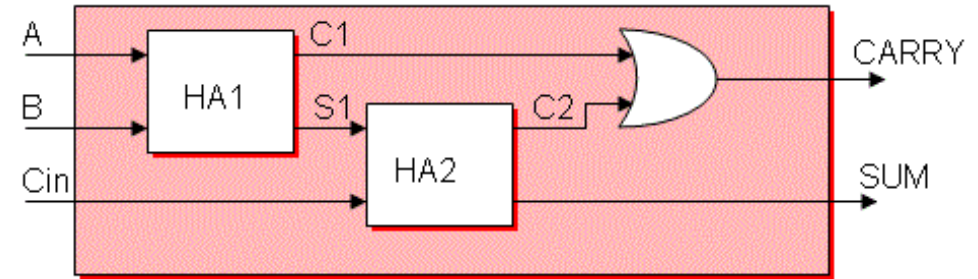

- Two HAs are needed
- Internal signals **s1,c1,c2** are used to connect the two HAs
- In HA, we define **port (a:in STD\_LOGIC; b:in STD\_LOGIC; sum:out STD\_LOGIC; carry:out STD\_LOGIC);**

```
signal s1,c1,c2 : std_logic:='0';  --declare internal signal


begin

--Provide a different name for each half adder.
--instantiate and do port map for the half adders.


HA1 : halfadder port map (a,b,s1,c1);
HA2 : halfadder port map (s1,cin,sum,c2);
carry <= c1 or c2;  --final carry calculation

end;
```

# Half-Adder 1

 

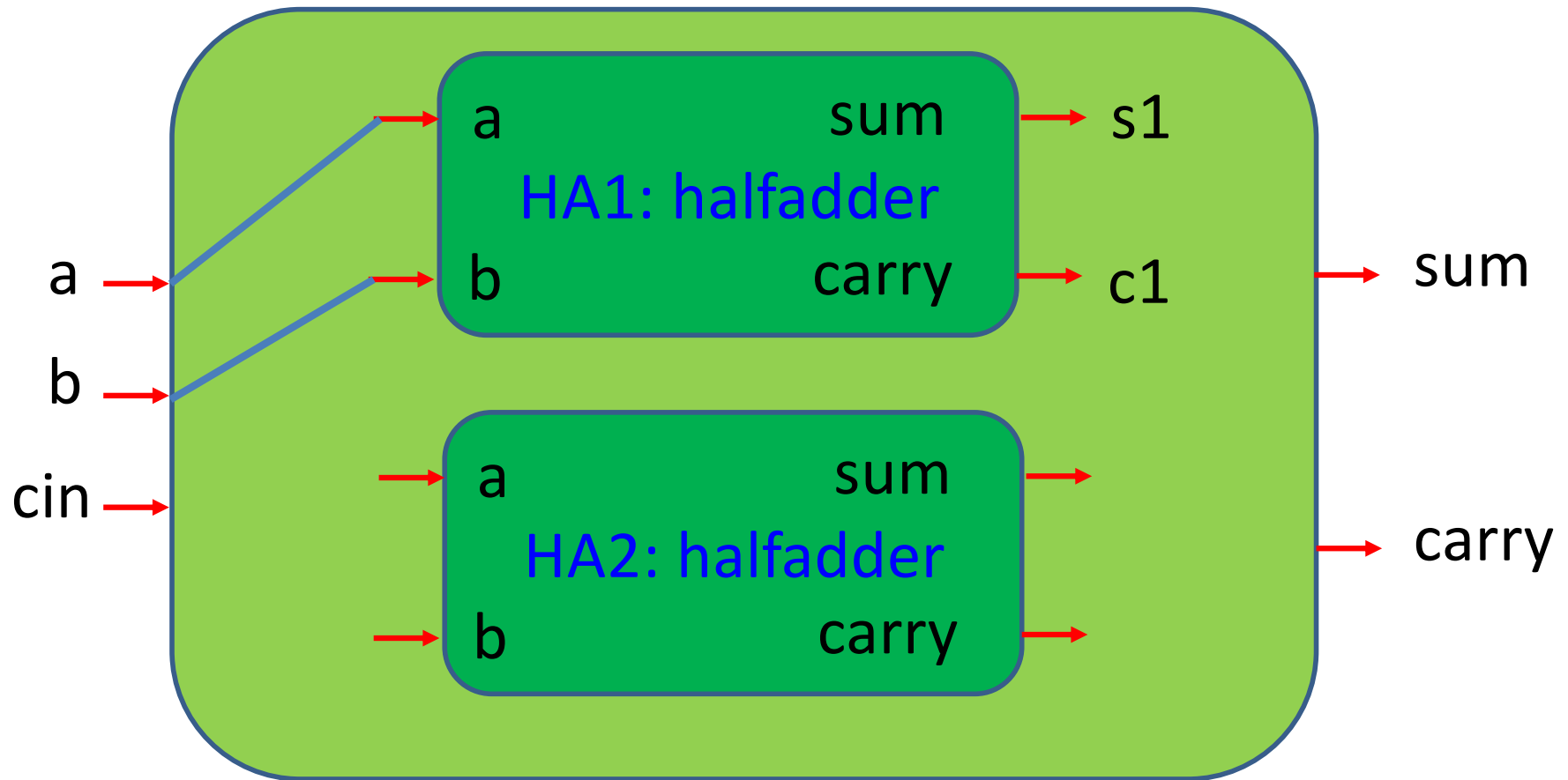
```
HA1 : halfadder port map (a,b,s1,c1);
```






# Half-Adder 2

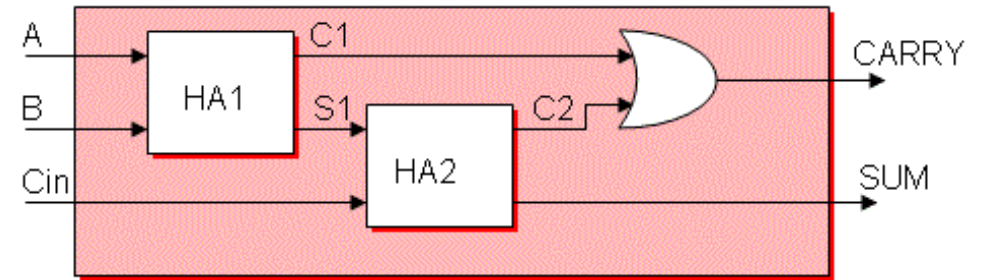
 
```
HA2 : halfadder port map (s1,cin,sum,c2);
```



```
carry <= c1 or c2;
```

# 1-bit Full-Adder

Input			Output	
i_Cin	i_A	i_B	o_S	o_Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

```
Library IEEE;
```

```
Use IEEE.STD_LOGIC_1164.ALL;
```

```
Entity full_adder_1bit is
```

```
Port (
```

```
    i_A: in STD_LOGIC;
```

```
    i_B: in STD_LOGIC;
```

```
    i_Cin: in STD_LOGIC;
```

```
    o_S: out STD_LOGIC;
```

```
    o_Cout: out STD_LOGIC);
```

```
End full_adder_1bit;
```


```
Architecture Behavioral of full_adder_1bit is
```

```
Begin
```

```
    --Add Your own code here
```

```
End Behavioral;
```

# 4-bit Full-Adder

 

```
Library IEEE;
```

```
Use IEEE.STD_LOGIC_1164.ALL;
```

```
Entity full_adder_4bits is
```

```
Port (
```

```
    i_A: in STD_LOGIC_VECTOR (3 DOWNT0 0);
```

```
    i_B: in STD_LOGIC_VECTOR (3 DOWNT0 0);
```

```
    i_Ci: in STD_LOGIC;
```

```
    o_S: out STD_LOGIC_VECTOR (3 DOWNT0 0);
```

```
    o_Cout: out STD_LOGIC
```

```
);
```

```
end full_adder_4bits;
```

# 4-bit Full-Adder

Architecture Behavioral of full\_adder\_4bits is

```
SIGNAL ci: STD_LOGIC_VECTOR (3 DOWNTO 0);
```

```
COMPONENT full_adder_1bit is
```

```
Port (
```

```
  i_A: in STD_LOGIC;
```

```
  i_B: in STD_LOGIC;
```

```
  i_Cin: in STD_LOGIC;
```

```
  o_S: out STD_LOGIC;
```

```
  o_Cout: out STD_LOGIC
```

```
);
```

```
END COMPONENT;
```

```
begin
```


```
ci(0) <= i_Ci;
```

```
uut0: full_adder_1bit PORT MAP(i_A(0), i_B(0), ci(0), o_S(0), ci(1));
```

```
  --Write your own code here to instantiate other three units.
```

```
  -- ...
```


```
end Behavioral;
```

 

# Hardware

**Table 12 - Push Button Connections**

Signal Name	Subsection	Zynq pin
BTNU	PL	T18
BTNR	PL	R18
BTND	PL	R16
BTNC	PL	P16
BTNL	PL	N15
PB1	PS	D13 (MIO 50)
PB2	PS	C10 (MIO 51)

 

**Table 13 - DIP Switch Connections**

Signal Name	Zynq pin
SW0	F22
SW1	G22
SW2	H22
SW3	F21
SW4	H19
SW5	H18
SW6	H17
SW7	M15

**Table 14 - LED Connections**

Signal Name	Subsection	Zynq pin
LD0	PL	T22
LD1	PL	T21
LD2	PL	U22
LD3	PL	U21
LD4	PL	V22
LD5	PL	W22
LD6	PL	U19
LD7	PL	U14
LD9	PS	D5 (MIO7)

- SW0-SW3 as input i\_A, SW4-SW7 as input i\_B, push button BTNL as input i\_Ci
- LD0-LD3 as o\_S, LD4 as o\_Cout

# Results

*Run synthesis, implementation  
and Generate bitstream file*

- Program Device
- Observe and verify the result