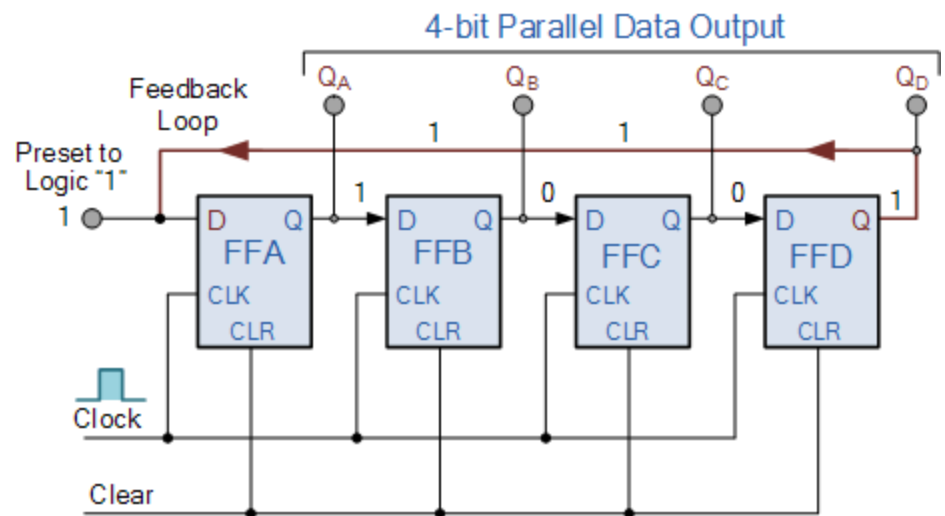


# EE2000 Logic Circuit Design

---

## Lecture 10 – Sequential Functional Blocks: Registers and Counters



# Exercise


Use T FFs and logic gates to design a synchronous counter with counting sequence 0, 4, 2, 1, 6...

## Step 1:

- States: 5 states  $\rightarrow$  3 flip-flops
- Largest number 6  $\rightarrow (110)_2 \rightarrow$  3 outputs
- Behavior: 000  $\rightarrow$  100  $\rightarrow$  010  $\rightarrow$  001  $\rightarrow$  110...

# Exercise
 
## STEP 2: Work out the State Diagram and Table



Present State			Next State		
$Q_A$	$Q_B$	$Q_C$	$Q_A$	$Q_B$	$Q_C$
0	0	0	1	0	0
0	0	1	1	1	0
0	1	0	0	0	1
0	1	1	x	x	x
1	0	0	0	1	0
1	0	1	x	x	x
1	1	0	0	0	0
1	1	1	x	x	x

# Exercise

**STEP 3:** Work out  $T_A, T_B, T_C$

Present State			Next State			Flip-Flop		
$Q_A$	$Q_B$	$Q_C$	$Q_A$	$Q_B$	$Q_C$	$T_A$	$T_B$	$T_C$
0	0	0	1	0	0	1	0	0
0	0	1	1	1	0	1	1	1
0	1	0	0	0	1	0	1	1
0	1	1	x	x	x	x	x	x
1	0	0	0	1	0	1	1	0
1	0	1	x	x	x	x	x	x
1	1	0	0	0	0	1	1	0
1	1	1	x	x	x	x	x	x

$T_A = Q'_B + Q_A$

$Q_A Q_B$		00	01	11	10
$Q_C$	0	1	0	1	1
	1	1	x	x	x

$T_B = Q_A + Q_B + Q_C$

$Q_A Q_B$		00	01	11	10
$Q_C$	0	0	1	1	1
	1	1	x	x	x

$T_C = Q'_A Q_B + Q_C$


$Q_A Q_B$		00	01	11	10
$Q_C$	0	0	1	0	0
	1	1	x	x	x

# Exercise

$$T_A = Q'_B + Q_A$$

$$T_B = Q_A + Q_B + Q_C$$

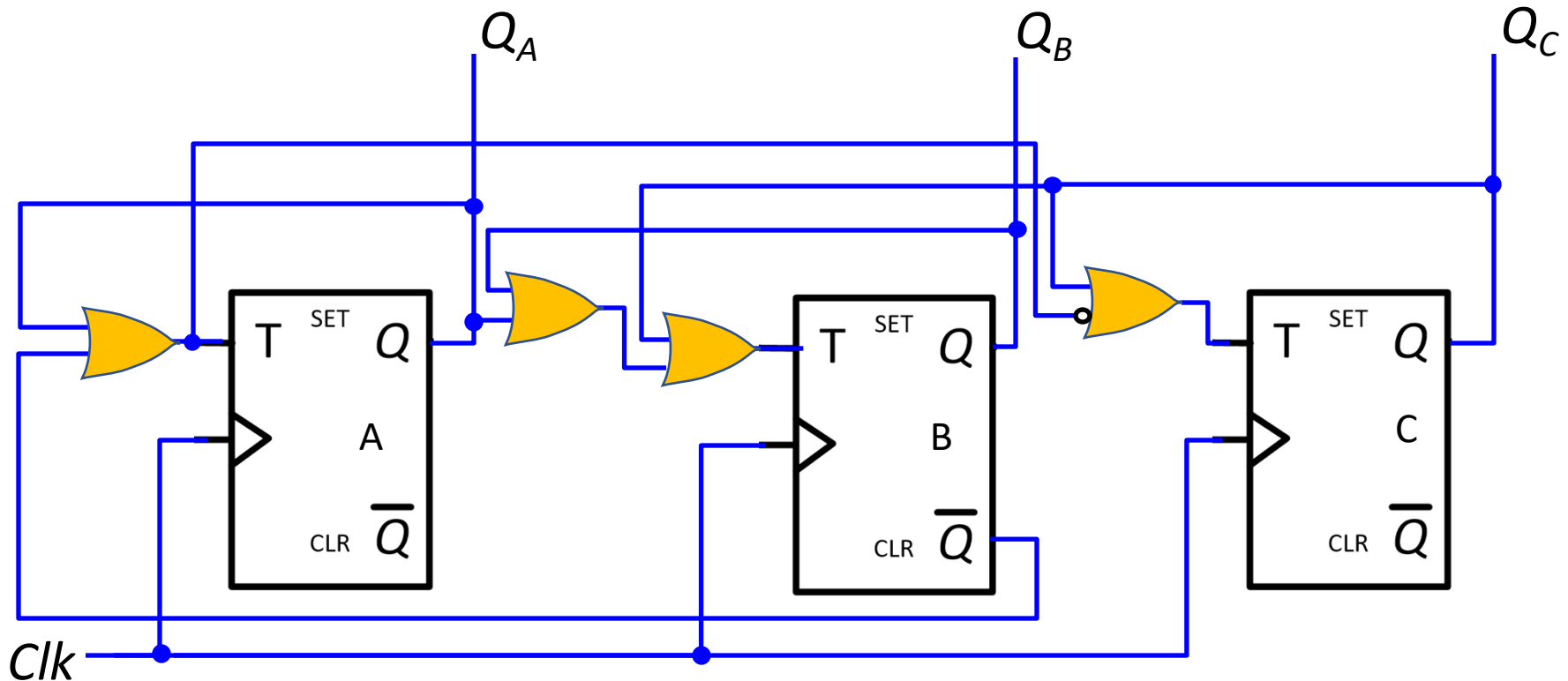**STEP 4:** Draw the Circuit  $T_C = Q'_A Q_B + Q_C = (Q_A + Q'_B)' + Q_C$



# Exercise


Determine the state transition of remaining states

Present State			Next State			Flip-Flop		
$Q_A$	$Q_B$	$Q_C$	$Q_A$	$Q_B$	$Q_C$	$T_A$	$T_B$	$T_C$
0	0	0	1	0	0	1	0	0
0	0	1	1	1	0	1	1	1
0	1	0	0	0	1	0	1	1
0	1	1						
1	0	0	0	1	0	1	1	0
1	0	1						
1	1	0	0	0	0	1	1	0
1	1	1						

$$T_A = Q'_B + Q_A$$

$$T_B = Q_A + Q_B + Q_C$$

$$T_C = Q'_A Q_B + Q_C$$

 

# Exercise


Determine the state transition of remaining states

Present State			Next State			Flip-Flop		
$Q_A$	$Q_B$	$Q_C$	$Q_A$	$Q_B$	$Q_C$	$T_A$	$T_B$	$T_C$
0	0	0	1	0	0	1	0	0
0	0	1	1	1	0	1	1	1
0	1	0	0	0	1	0	1	1
0	1	1	0	0	0	0	1	1
1	0	0	0	1	0	1	1	0
1	0	1	0	1	0	1	1	1
1	1	0	0	0	0	1	1	0
1	1	1	0	0	0	1	1	1

$$T_A = Q'_B + Q_A$$

$$T_B = Q_A + Q_B + Q_C$$


$$T_C = Q'_A Q_B + Q_C$$

 
 
# Exercise


Given an 8-bit serial-in parallel-out shift register as shown below, design a system with one output  $z$ , which is 1 only if the input  $x$  has been alternating for seven clock times (including the present one).

$$z = x\bar{A}\bar{B}\bar{C}\bar{D}\bar{E}\bar{F} + \bar{x}A\bar{B}C\bar{D}E\bar{F}$$






# Exercise

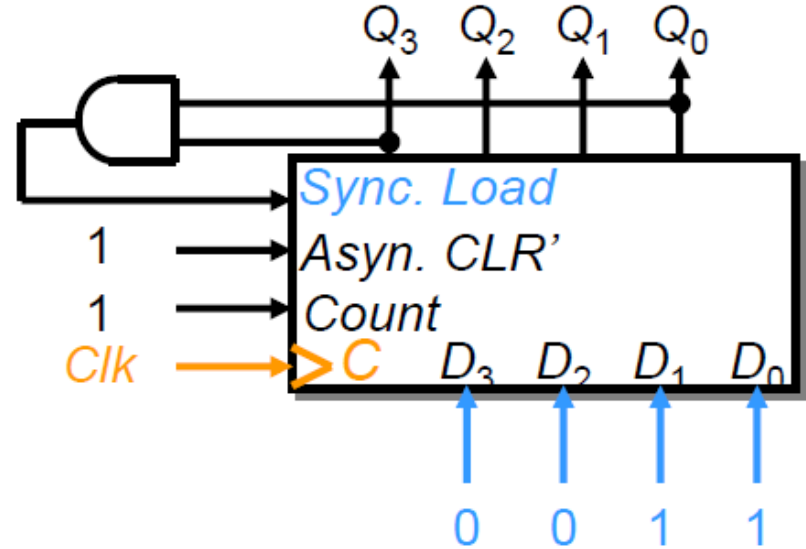

- Initial input: 0011
- Synchronous Load Bit:  $Q_3Q_0$   
→ Reset to 0011 after 1xx1
- Counter: 0011 → 0100 → 0101 → 0110 → 0111 → 1000 → 1001 → 0011
- Mod-7 counter

# Exercises

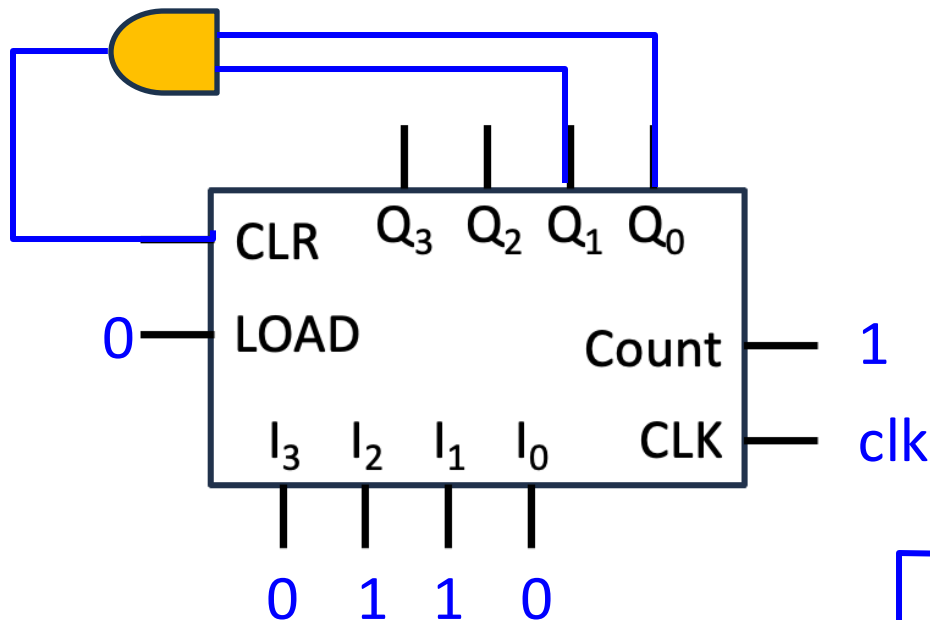

Counter: 0000 → 0001 →  
0010 → 0011 → 0000

Counter: 1000

→ 1001 → 1010 → 0000  
→ 0001 → 0010 → 0011  
→ 0100 → 0101 → 1000

