 


EE2000 Logic Circuit Design

Lecture 8– VHDL 2



Encoder (Decimal-to-BCD Encoder)

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

```
entity ENC3 is
```

```
    Port ( Q : in std_logic;
```

```
          R : in std_logic;
```

```
          S : in std_logic;
```

```
          T : in std_logic;
```

```
          U : in std_logic;
```

```
          V : in std_logic;
```

```
          W : in std_logic;
```

```
          X : in std_logic;
```

```
          Y : in std_logic;
```

```
          Z : in std_logic;
```

```
    OUT0 : out std_logic;
```

```
    OUT1 : out std_logic;
```

```
    OUT2 : out std_logic;
```

```
    OUT3 : out std_logic);
```

```
end ENC3;
```

```
architecture Behavioral of ENC3 is
```


```
begin
```

```
    process (Q,R,S,T,U,V,W,X,Y,Z)
```

```
    begin
```

```
    end process;
```

```
end Behavioral;
```

 

```
OUT0 <= R OR T OR V OR X OR Z;
```

```
OUT1 <= S OR T OR W OR X;
```

```
OUT2 <= U OR V OR W OR X;
```

```
OUT3 <= Y OR Z;
```

Enter your codes here

T-Flip Flop with RESET

Rising edge FF

Asyn Active High Reset

C	T	Q_{t+1}	$\overline{Q_{t+1}}$	State
0	x	Q_t	$\overline{Q_t}$	Hold
1	0	Q_t	$\overline{Q_t}$	Hold
1	1	$\overline{Q_t}$	Q_t	Toggle

```
library ieee;
use ieee.std_logic_1164.all;

entity TFF is
port(  T: in std_logic;
      clk: in std_logic;
      areset: in std_logic;
      Q: out std_logic;
end TFF;
```

```
architecture behavioral of TFF is
signal tmp : std_logic;
begin
process(clk, areset)
begin
    if areset = '1' then
        TMP <= '0';
    elsif rising_edge(clk) then
        if (T = '1') then
            TMP <= not TMP;
        end if;
    end if;
    Q <= TMP;
end process;
end behavioral;
```