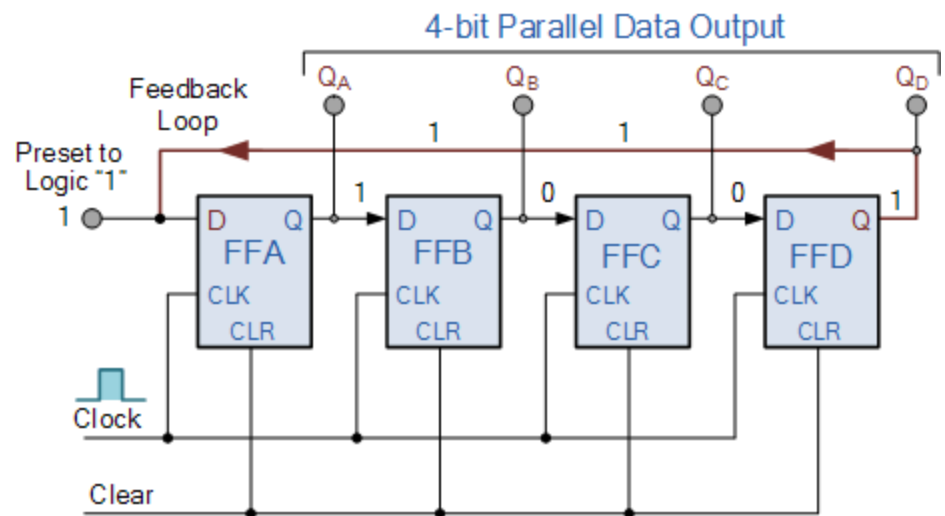


EE2000 Logic Circuit Design

Lecture 10 – Sequential Functional Blocks: Registers and Counters



Example (Counter)


Design a free-running synchronous counter with the counting sequence of 2, 4, 5, 3, 7, 2, 4, 5, ... (repetitive) using D flip-flops

Step 1:

- Input: Free-running \rightarrow no input
- States: 5 states \rightarrow 3 flip-flops
- Largest number 7 $\rightarrow (111)_2 \rightarrow$ 3 outputs
- Behavior: 010 \rightarrow 100 \rightarrow 101 \rightarrow 011 \rightarrow 111...

 Example (Counter)

STEP 2: Work out the State Diagram and Table



PS	NS	Output $Z_0 Z_1 Z_2$
S_A	S_B	0 1 0
S_B	S_C	1 0 0
S_C	S_D	1 0 1
S_D	S_E	0 1 1
S_E	S_A	1 1 1

■ $S_A = 010, S_B = 100, S_C = 101, S_D = 011, S_E = 111$

Example (Counter)

STEP 3: Assign FFs

5 states \rightarrow 3 FFs

PS	NS	Output $Z_0 Z_1 Z_2$
S_A	S_B	0 1 0
S_B	S_C	1 0 0
S_C	S_D	1 0 1
S_D	S_E	0 1 1
S_E	S_A	1 1 1




PS			NS			Output
Q_A	Q_B	Q_C	Q_A	Q_B	Q_C	$Z_0 Z_1 Z_2$
0	0	0	x	x	x	x x x
0	0	1	x	x	x	x x x
0	1	0	1	0	0	0 1 0
0	1	1	1	1	1	0 1 1
1	0	0	1	0	1	1 0 0
1	0	1	0	1	1	1 0 1
1	1	0	x	x	x	x x x
1	1	1	0	1	0	1 1 1

■ $S_A = 010, S_B = 100, S_C = 101, S_D = 011, S_E = 111$


Example (Counter)

STEP 4: Work out D_A , D_B , D_C


PS			NS			Output
Q_A	Q_B	Q_C	Q_A	Q_B	Q_C	$Z_0 Z_1 Z_2$
0	0	0	x	x	x	x x x
0	0	1	x	x	x	x x x
0	1	0	1	0	0	0 1 0
0	1	1	1	1	1	0 1 1
1	0	0	1	0	1	1 0 0
1	0	1	0	1	1	1 0 1
1	1	0	x	x	x	x x x
1	1	1	0	1	0	1 1 1

 

$$D_A = Q_A' + Q_C'$$

 

$$D_B = Q_C$$

 

$$D_C = Q_B' + Q_A' Q_C$$

Example (Counter)

STEP 5: Work out z

PS			NS			Output
Q_A	Q_B	Q_C	Q_A	Q_B	Q_C	$Z_0 Z_1 Z_2$
0	0	0	x	x	x	x x x
0	0	1	x	x	x	x x x
0	1	0	1	0	0	0 1 0
0	1	1	1	1	1	0 1 1
1	0	0	1	0	1	1 0 0
1	0	1	0	1	1	1 0 1
1	1	0	x	x	x	x x x
1	1	1	0	1	0	1 1 1

$$Z_0 = Q_A$$

$$Z_1 = Q_B$$


$$Z_2 = Q_C$$

Example (Counter)

$$D_A(Q_A, Q_B, Q_C) = Q_A' + Q_C'$$


$$D_B(Q_A, Q_B, Q_C) = Q_C$$

$$D_C(Q_A, Q_B, Q_C) = Q_B' + Q_A' Q_C$$

 

Is It Self Starting?

 Self starting: The counter will enter the main loop regardless on the initial state



$$D_A = Q_A' + Q_C'$$

$$D_B = Q_C$$

$$D_C = Q_B' + Q_A'Q_C$$

Present State	Next State
000	101
001	111
110	100

Exercise


Use T FFs and logic gates to design a synchronous counter with counting sequence 0, 4, 2, 1, 6...

Step 1:

- States
- Largest number
- Behavior

 Exercise

STEP 2: Work out the State Diagram and Table



Present State			Next State		
Q_A	Q_B	Q_C	Q_A	Q_B	Q_C
0	0	0			
0	0	1			
0	1	0			
0	1	1			
1	0	0			
1	0	1			
1	1	0			
1	1	1			

Exercise

STEP 3: Work out T_A, T_B, T_C

Present State			Next State			Flip-Flop		
Q_A	Q_B	Q_C	Q_A	Q_B	Q_C	T_A	T_B	T_C
0	0	0	1	0	0			
0	0	1	1	1	0			
0	1	0	0	0	1			
0	1	1	x	x	x			
1	0	0	0	1	0			
1	0	1	x	x	x			
1	1	0	0	0	0			
1	1	1	x	x	x			

$T_A =$

Q_C	$Q_A Q_B$			
	00	01	11	10
0				
1				

$T_B =$

Q_C	$Q_A Q_B$			
	00	01	11	10
0				
1				

$T_C =$

Q_C	$Q_A Q_B$			
	00	01	11	10
0				
1				




Exercise

$$T_A = Q'_B + Q_A$$

$$T_B = Q_A + Q_B + Q_C$$

STEP 4: Draw the Circuit
   
$$T_C = Q'_A Q_B + Q_C = (Q_A + Q'_B)' + Q_C$$



Exercise


Determine the state transition of remaining states

Present State			Next State			Flip-Flop		
Q_A	Q_B	Q_C	Q_A	Q_B	Q_C	T_A	T_B	T_C
0	0	0	1	0	0	1	0	0
0	0	1	1	1	0	1	1	1
0	1	0	0	0	1	0	1	1
0	1	1						
1	0	0	0	1	0	1	1	0
1	0	1						
1	1	0	0	0	0	1	1	0
1	1	1						

$$T_A = Q'_B + Q_A$$

$$T_B = Q_A + Q_B + Q_C$$

$$T_C = Q'_A Q_B + Q_C$$

 

What will you learn?

10.1 Learn various Registers

- Parallel load
- Bidirectional shift
- Example: Serial adder


10.2 Learn various Counters

- Asynchronous: Ripple
- Synchronous: Up-down, Modulo, Ring


10.1 Registers

- Memory used to store binary data
- A collection of flip-flops: To store ***n***-bit data, a register requires ***n*** flip-flops
- ***n***-bit register
 - ***n*** edge-triggered flip-flops
 - Clock pulse as the enable signal
- Parallel or serial design


Parallel-in Parallel-out Register

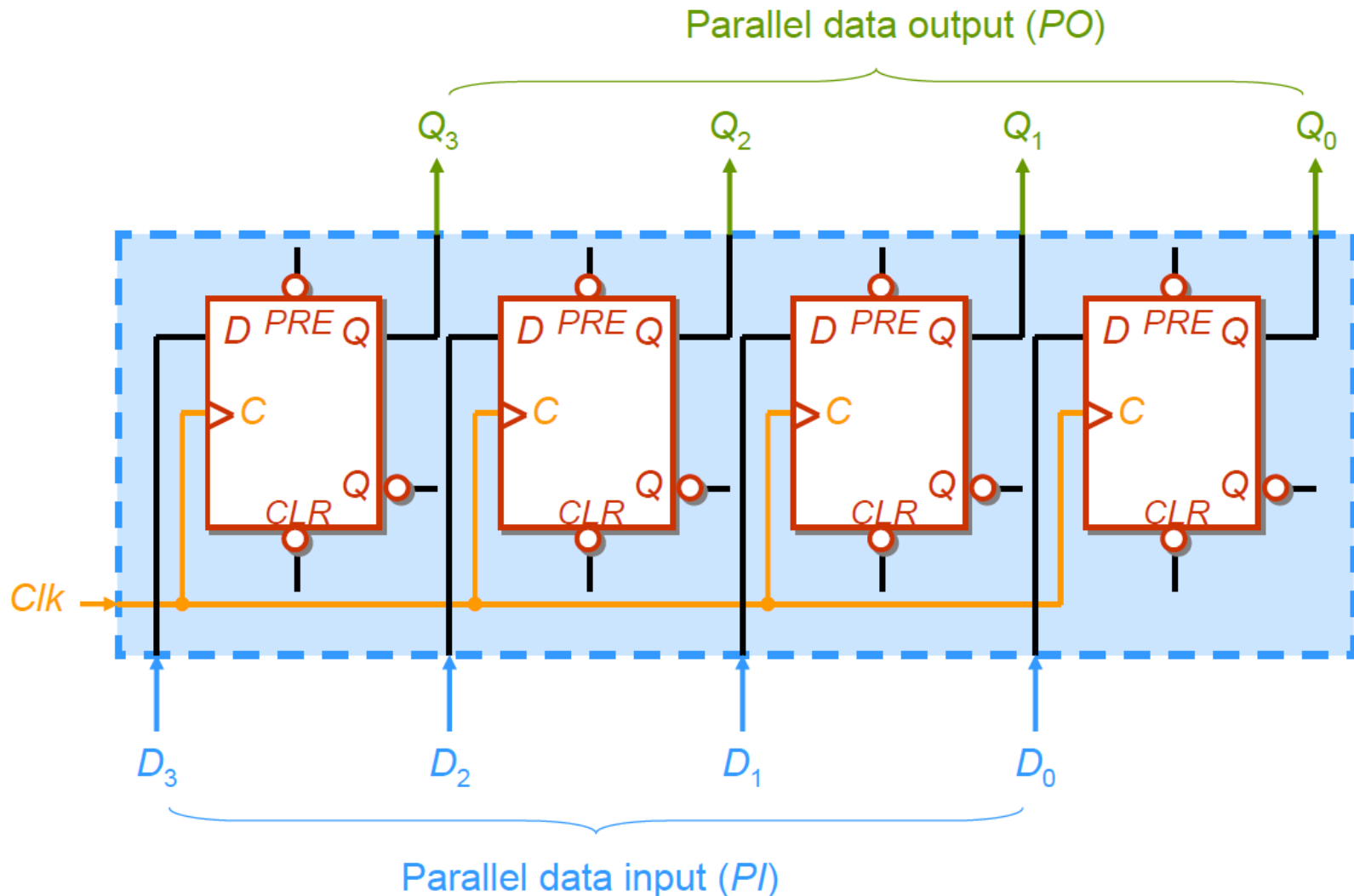

Example

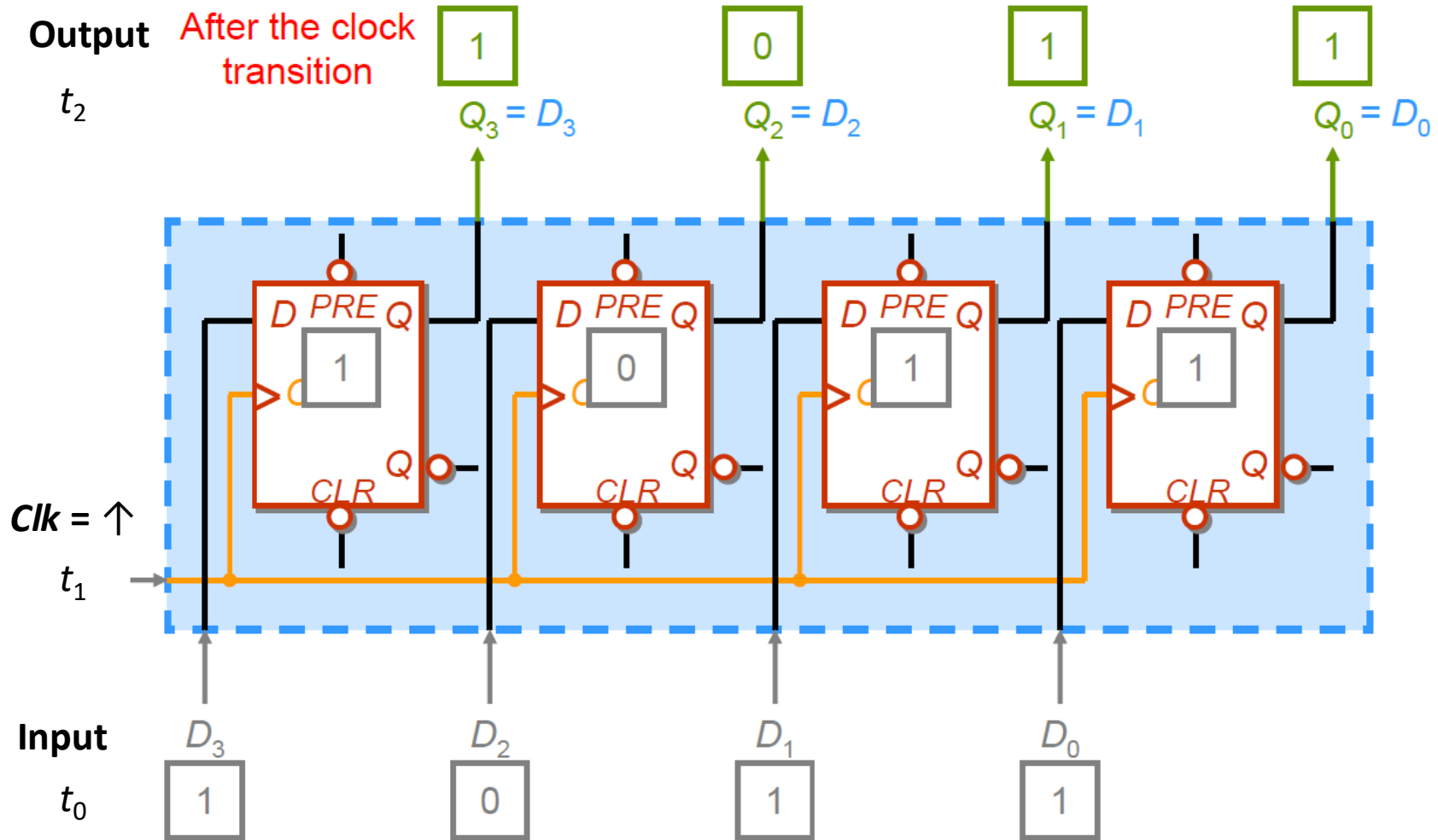


Register with Parallel Load

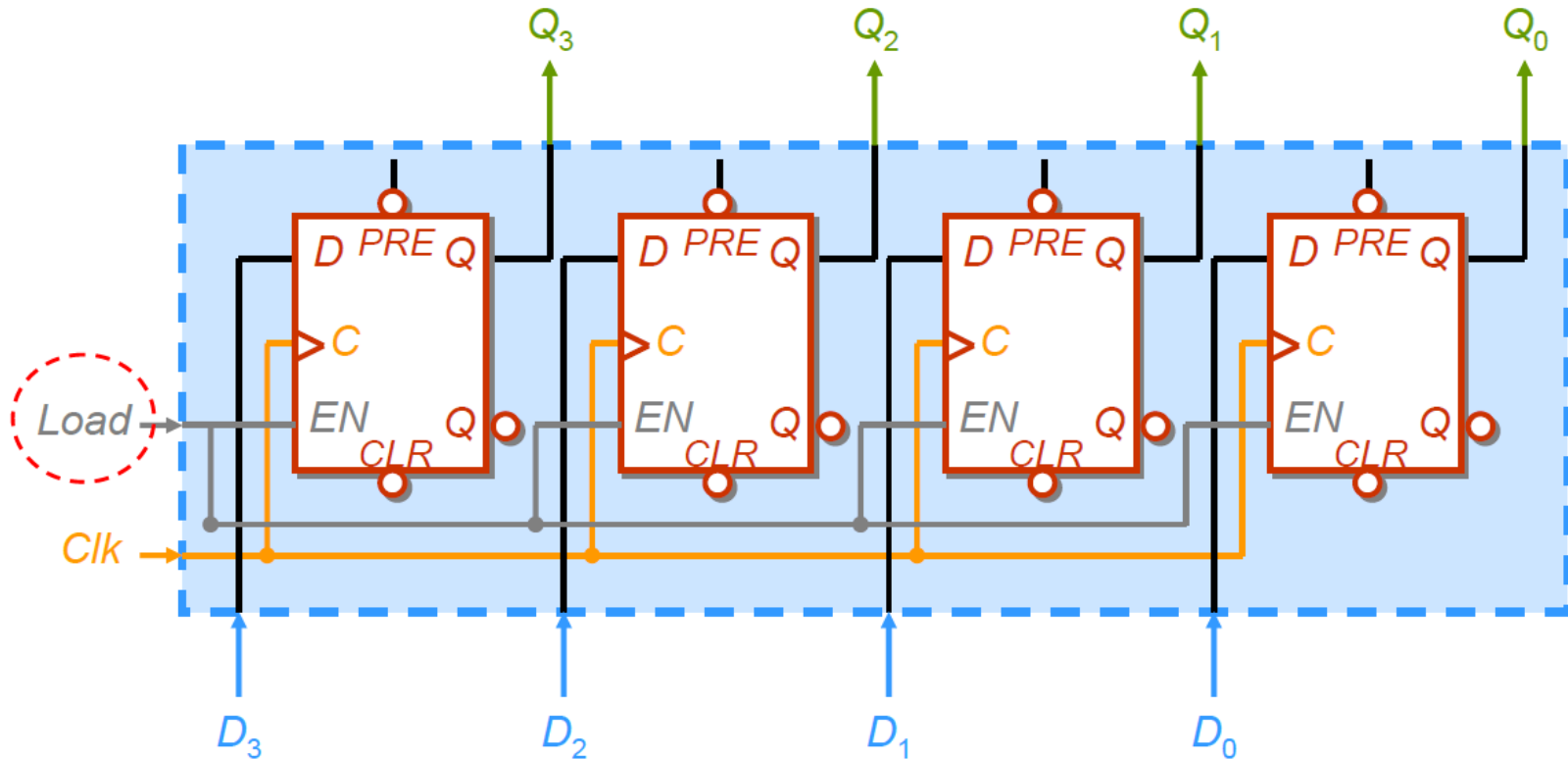


The register will load the inputs into the flip-flops only when *Clk* is at the rising edge AND *Load* = 1

Timing Diagram

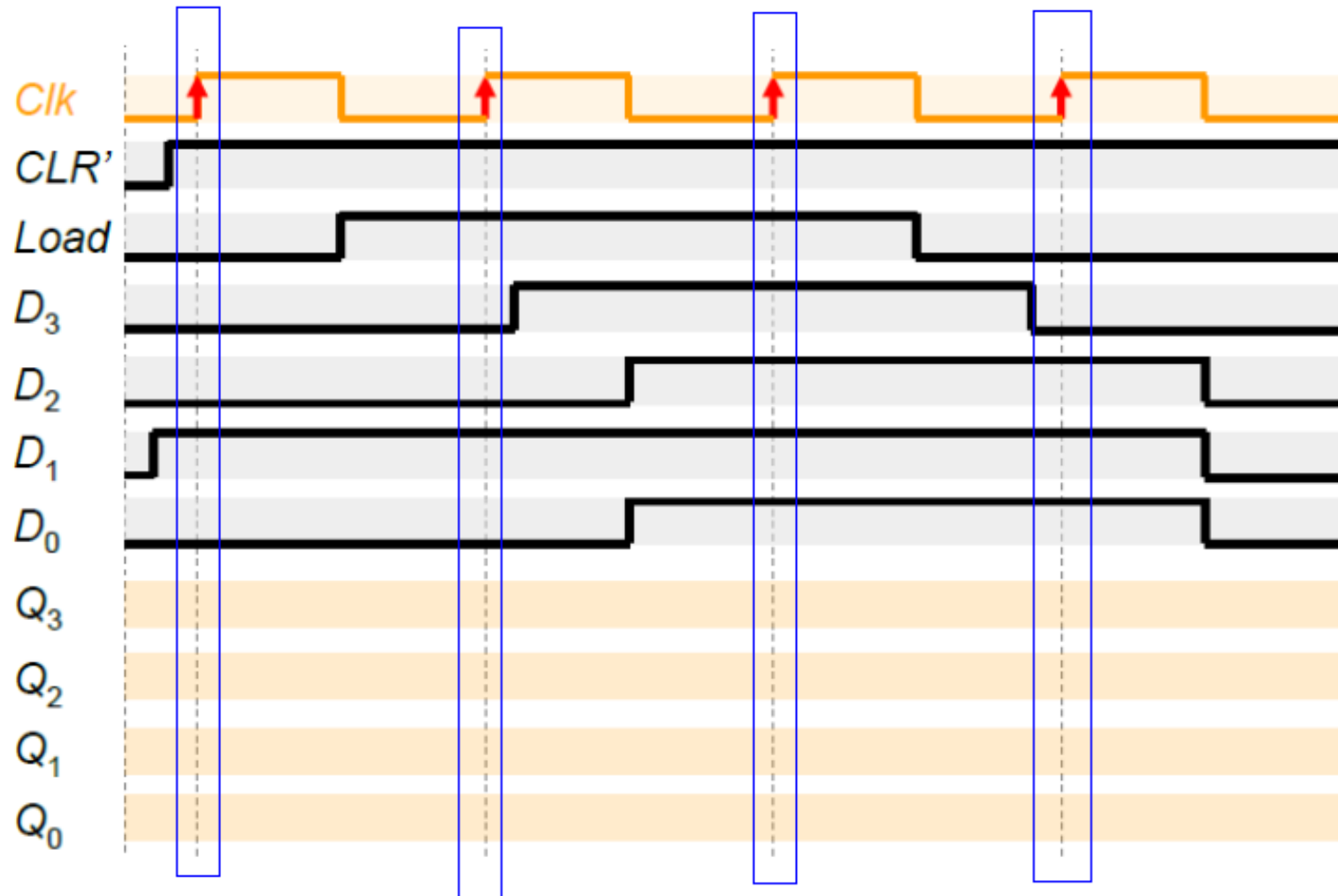


Timing Diagram


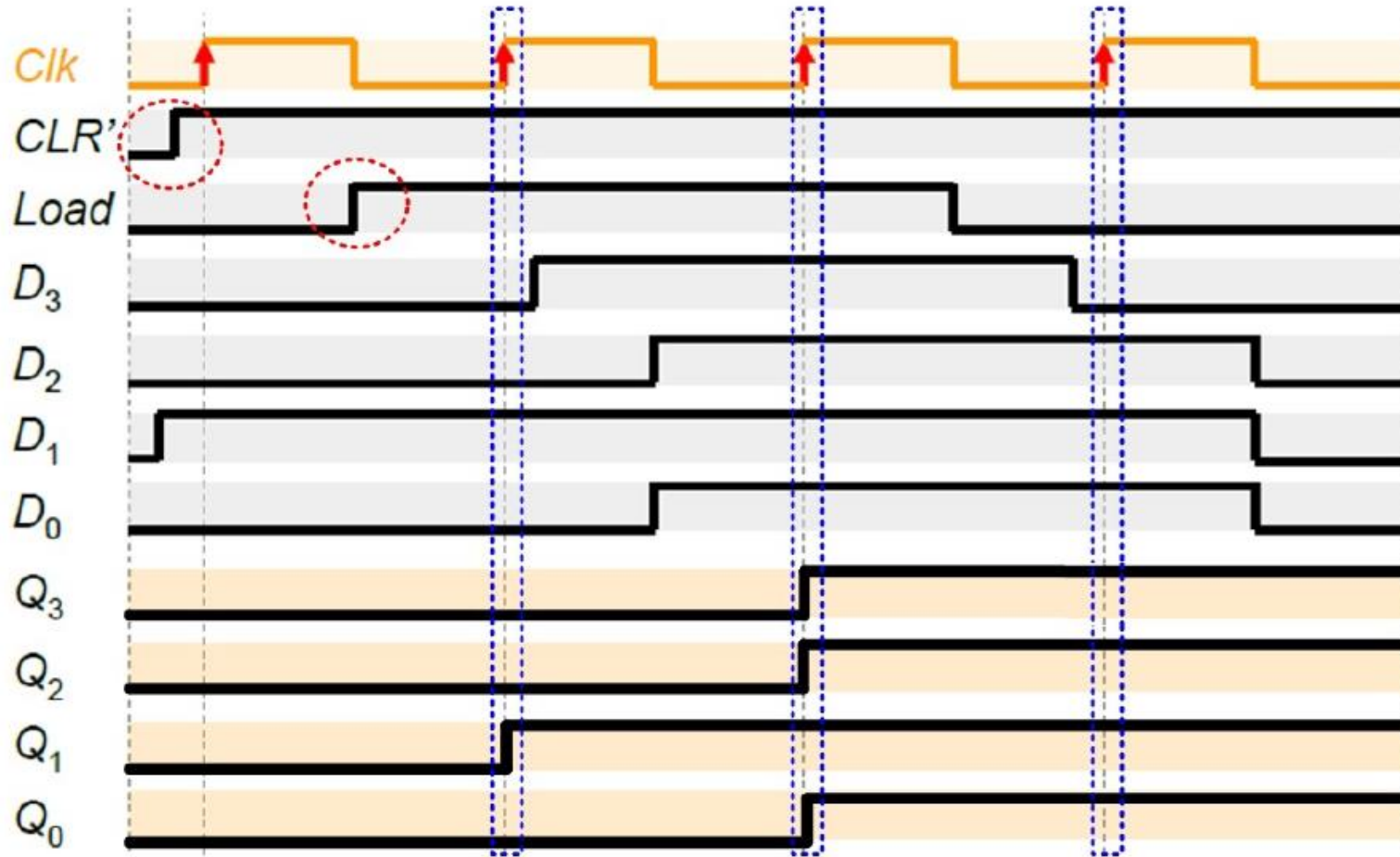


Shift Register

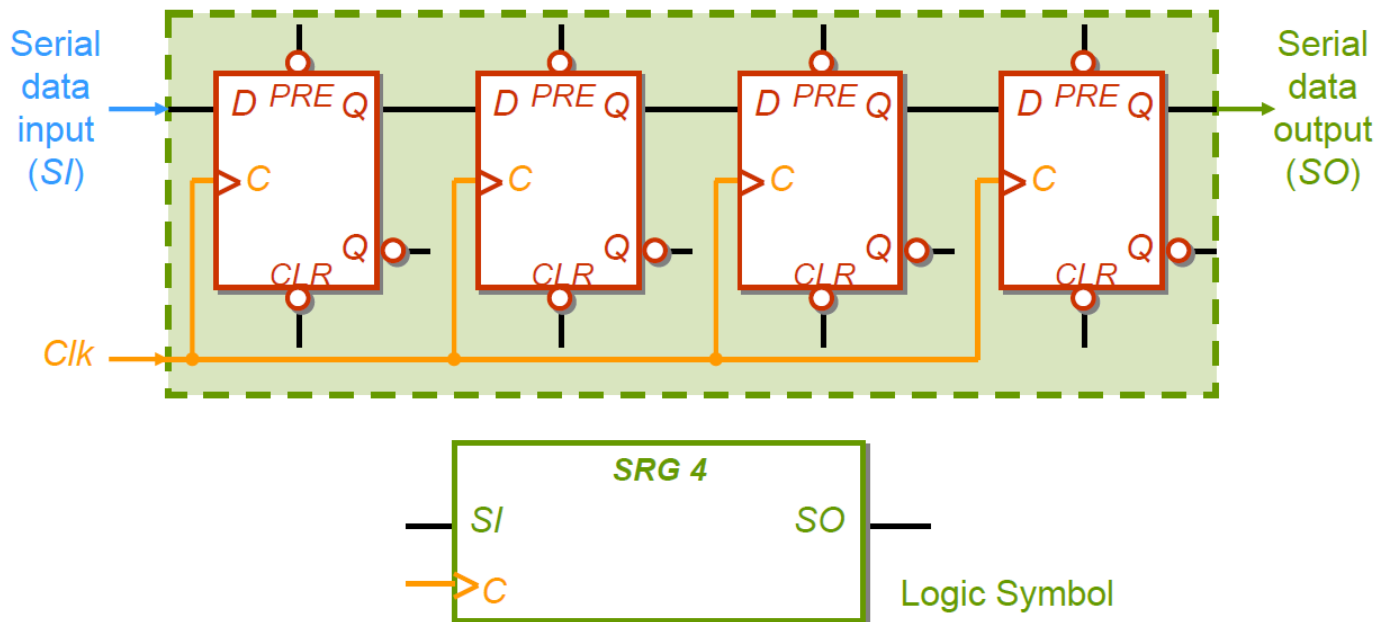
- Serial-in serial-out
- Data move (shift) to the next flip-flop on each clock



How Does It Work?

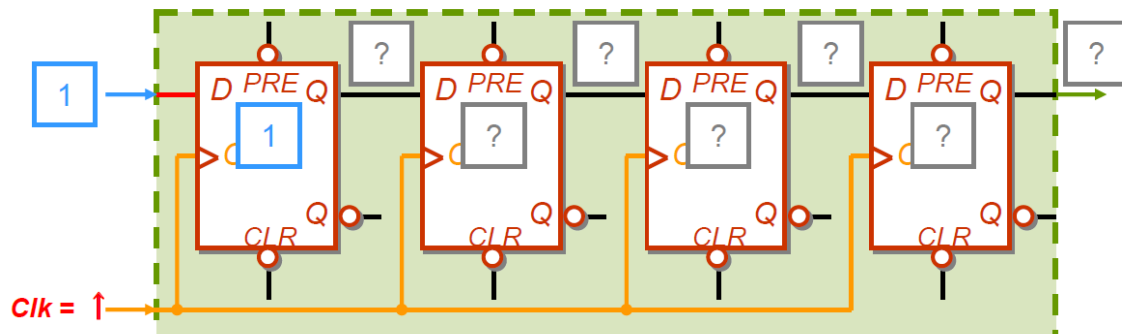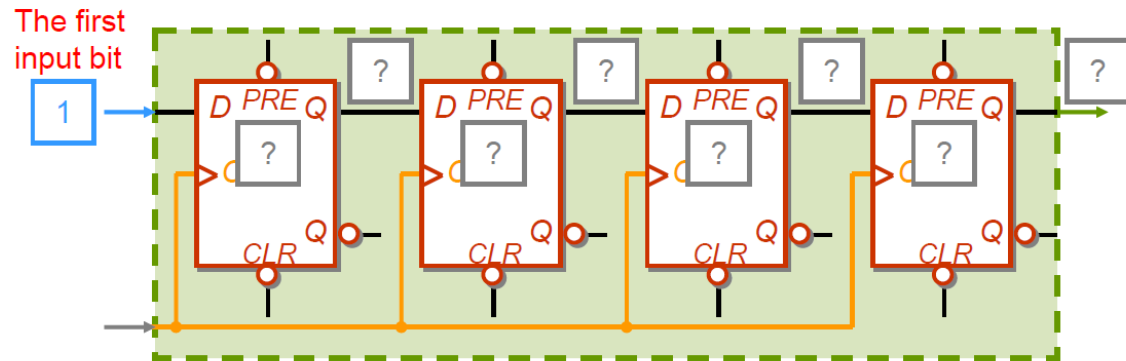


After the clock transition

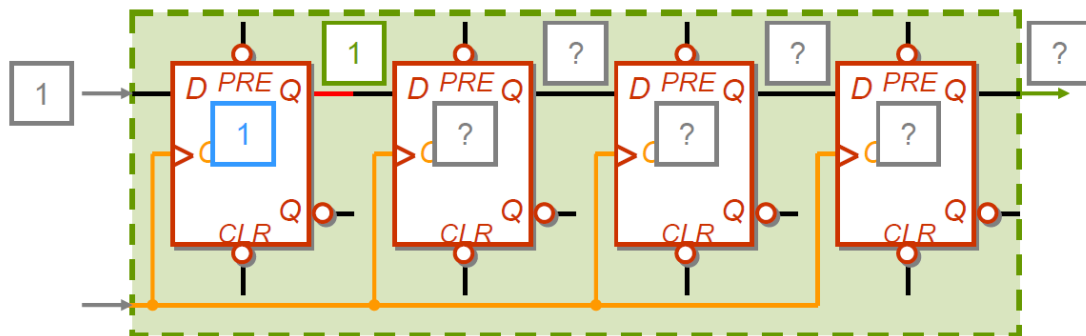


The next input bit

0

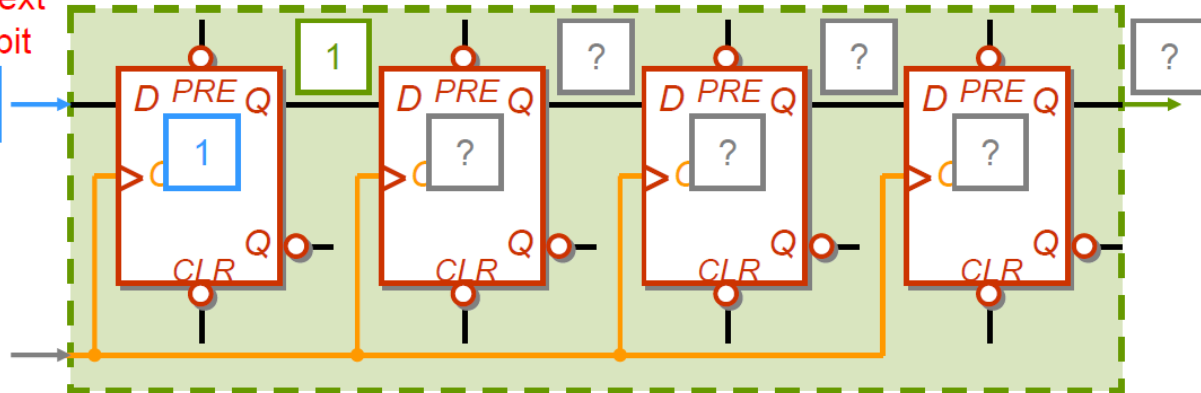


0

Clk = ↑

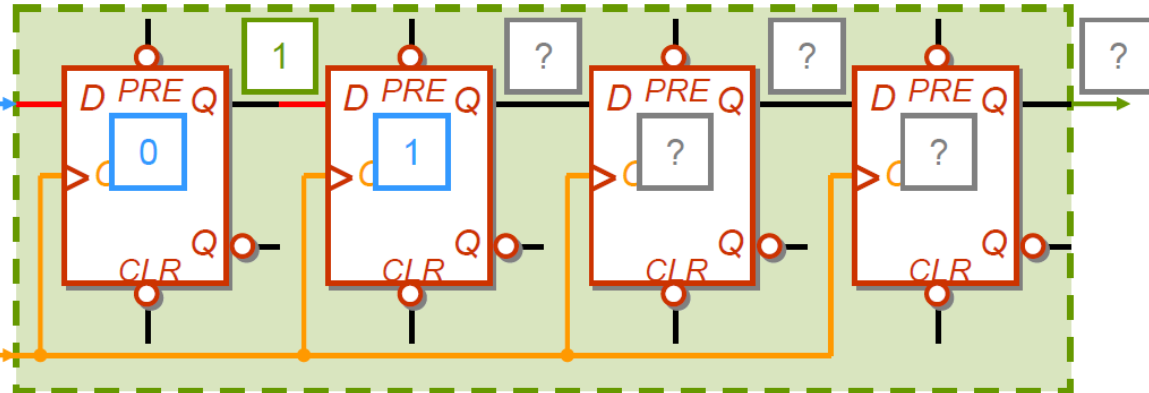


After the clock transition

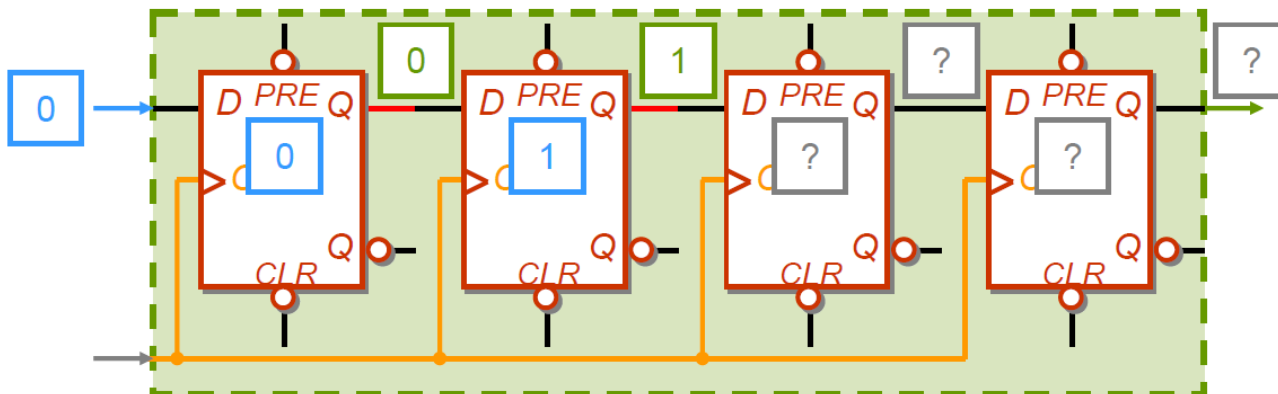

Exercise

Given an 8-bit serial-in parallel-out shift register as shown below, design a system with one output z , which is 1 only if the input x has been alternating for seven clock times (including the present one).



$z?$

 


Characteristics

- Shift register has a chain of flip-flops
- When the FFs are triggered, the stored bits will be shifted to the next FFs
- First-in-First-out structure
- Shift register with two shifting directions?
→ **Bidirectional shift register!**

Bidirectional Shift Register

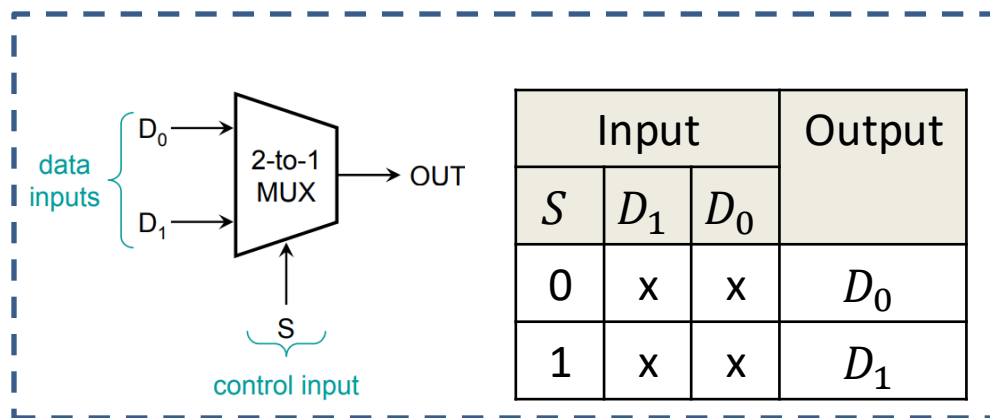 


How Does It Work?

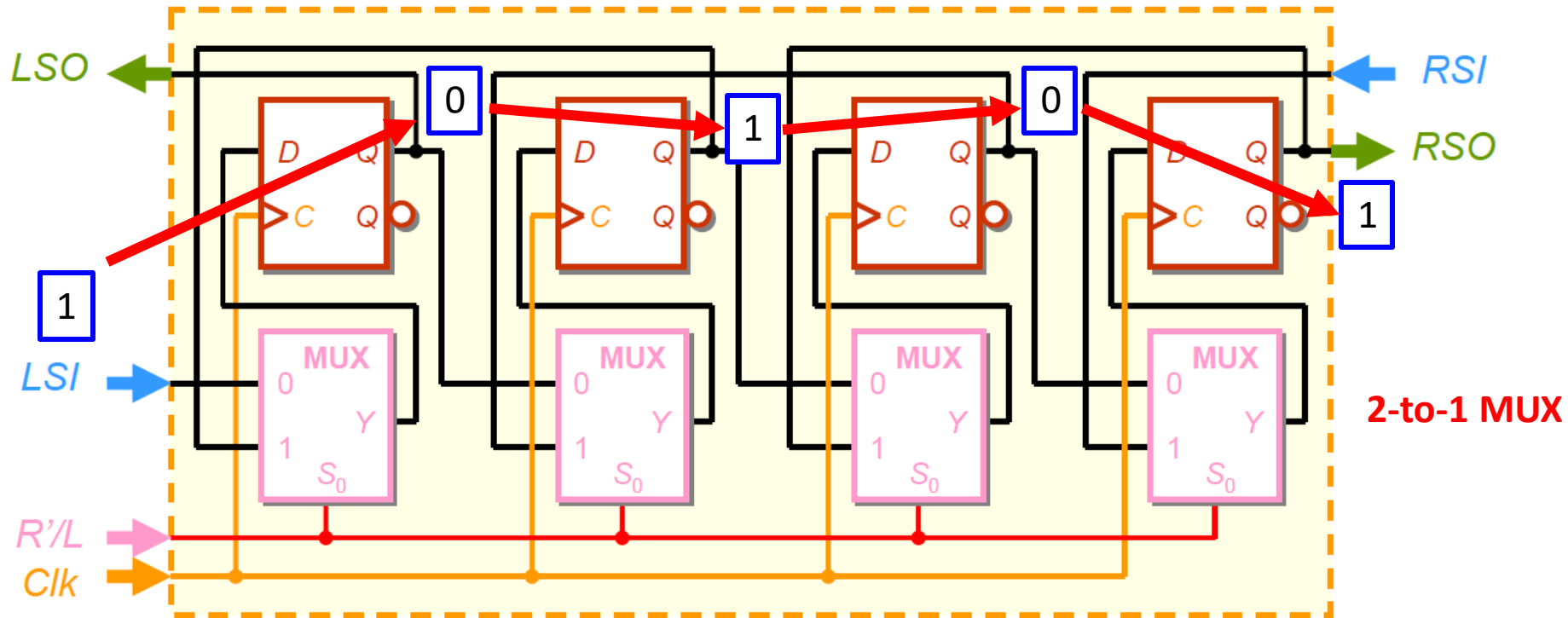


- Assume these are the initial states
- When $R' = 0$ ($L = 0$) and upon $\text{Clk} \uparrow$, stored bits shift to right!

How Does It Work?

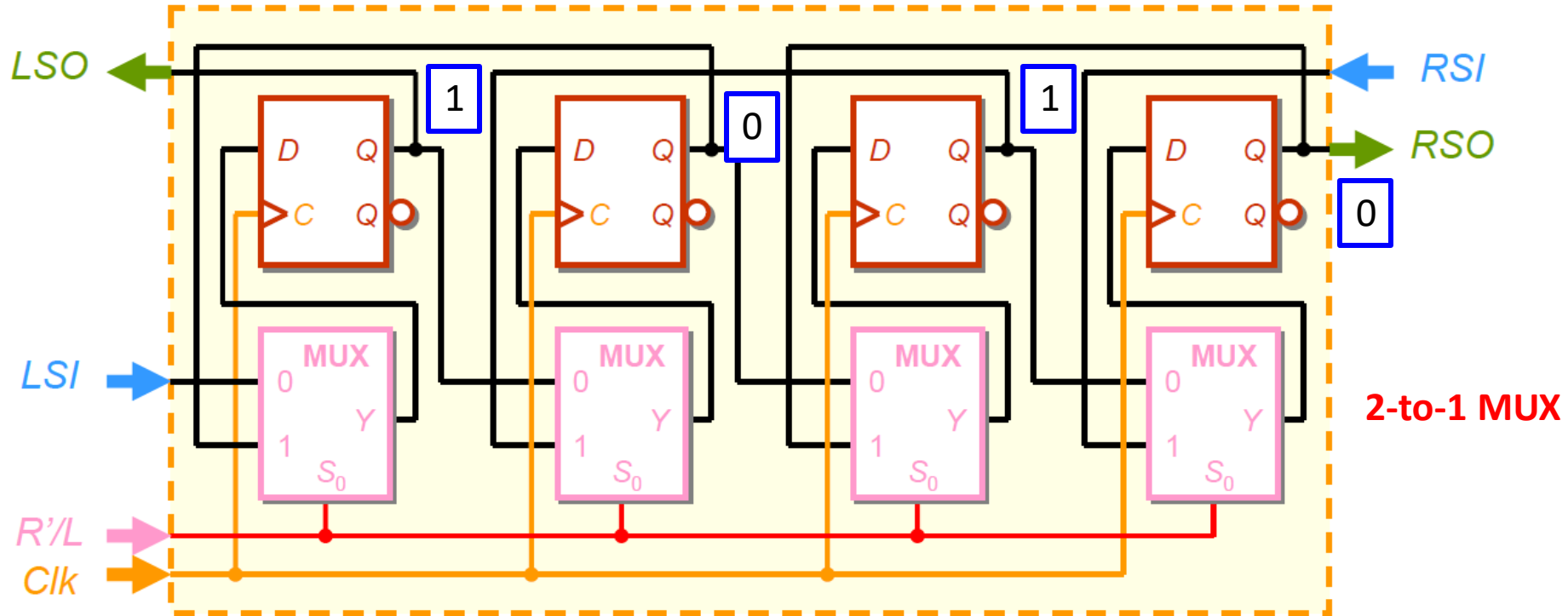


$Q_1Q_2Q_3Q_4 \Rightarrow$ "0101" becomes "1010"

How Does It Work?

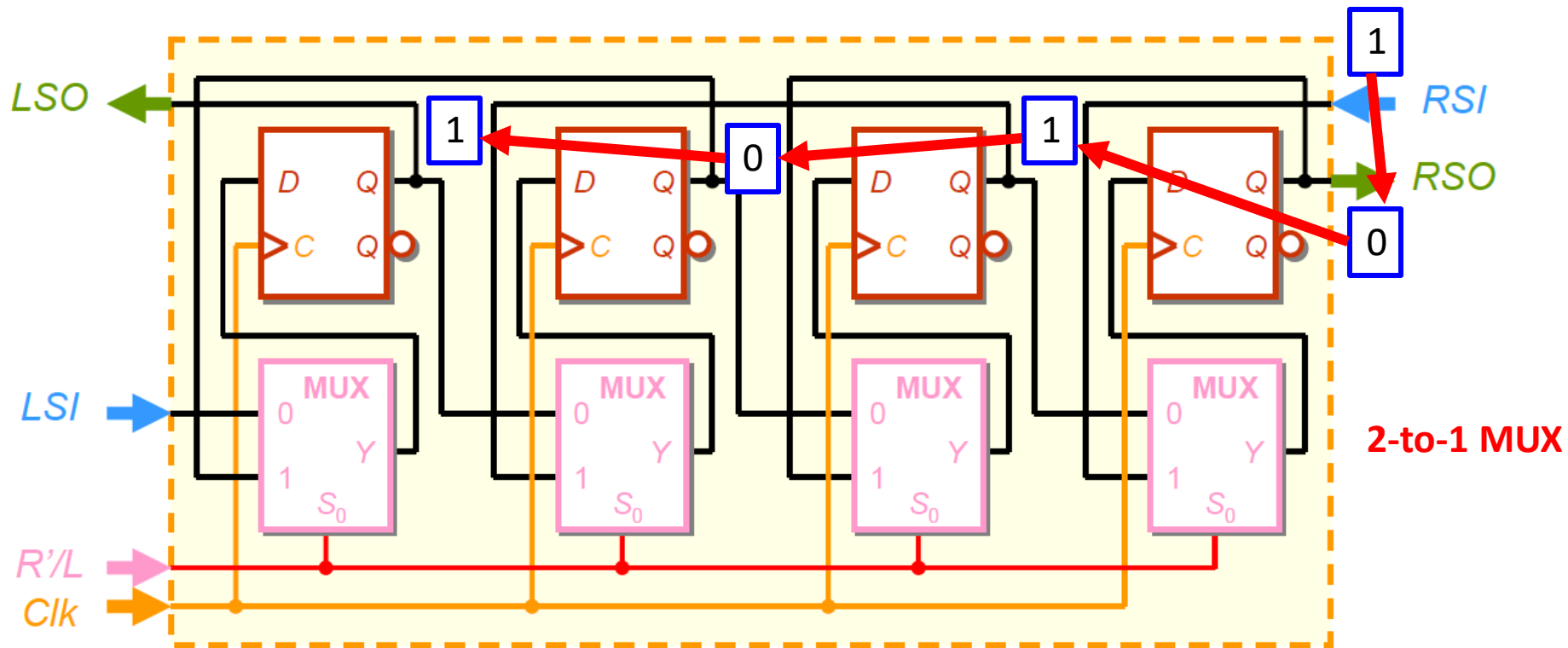


- Assume these are the initial states
- When $R' = 1$ ($L = 1$) and upon $\text{Clk} \uparrow$, stored bits shift to left!

How Does It Work?

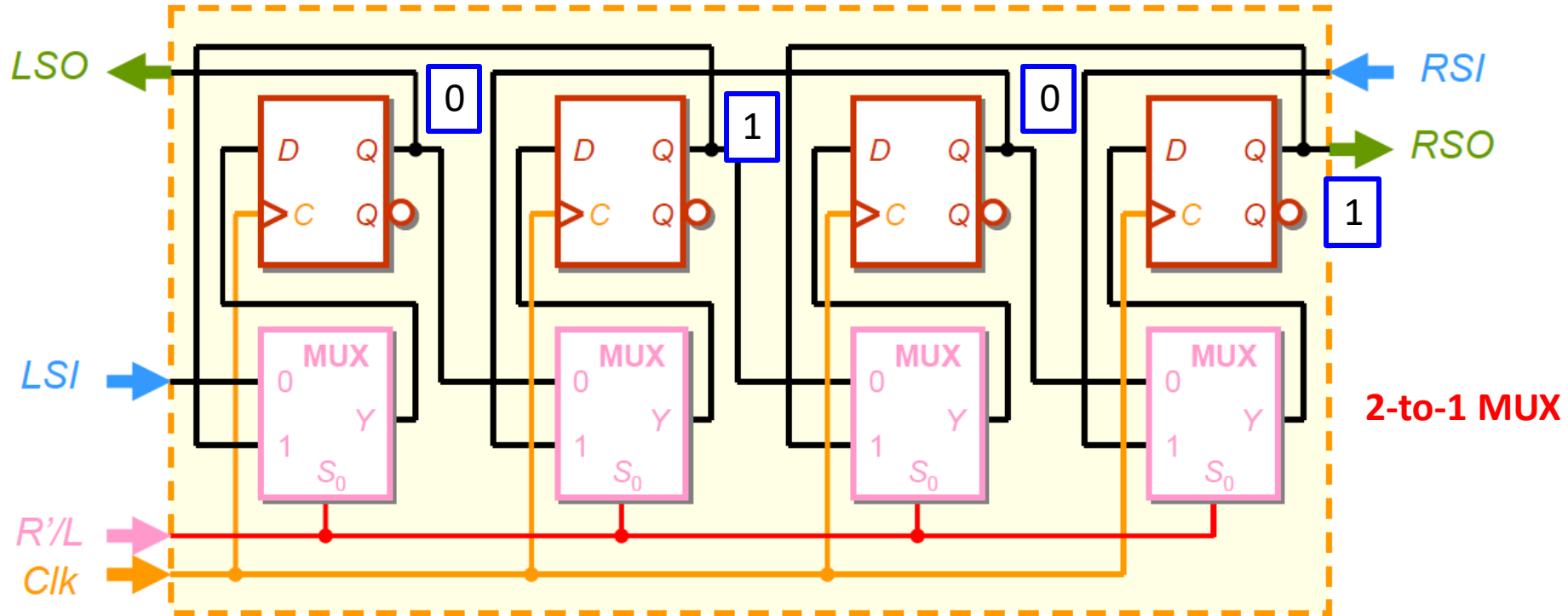


$Q_1Q_2Q_3Q_4 \Rightarrow$ "1010" becomes "0101"

 Bidirectional Shift Register + Parallel Load



How Does It Work?

 


S_1	S_0	Operation
0	0	HOLD
0	1	Shift right
1	0	Shift left
1	1	Parallel load

Timing Diagram


Shift right: $RQ_3Q_2Q_1$
Shift left: $Q_2Q_1Q_0L$

S_1	S_0	Operation
0	0	HOLD
0	1	Shift right
1	0	Shift left
1	1	Parallel load

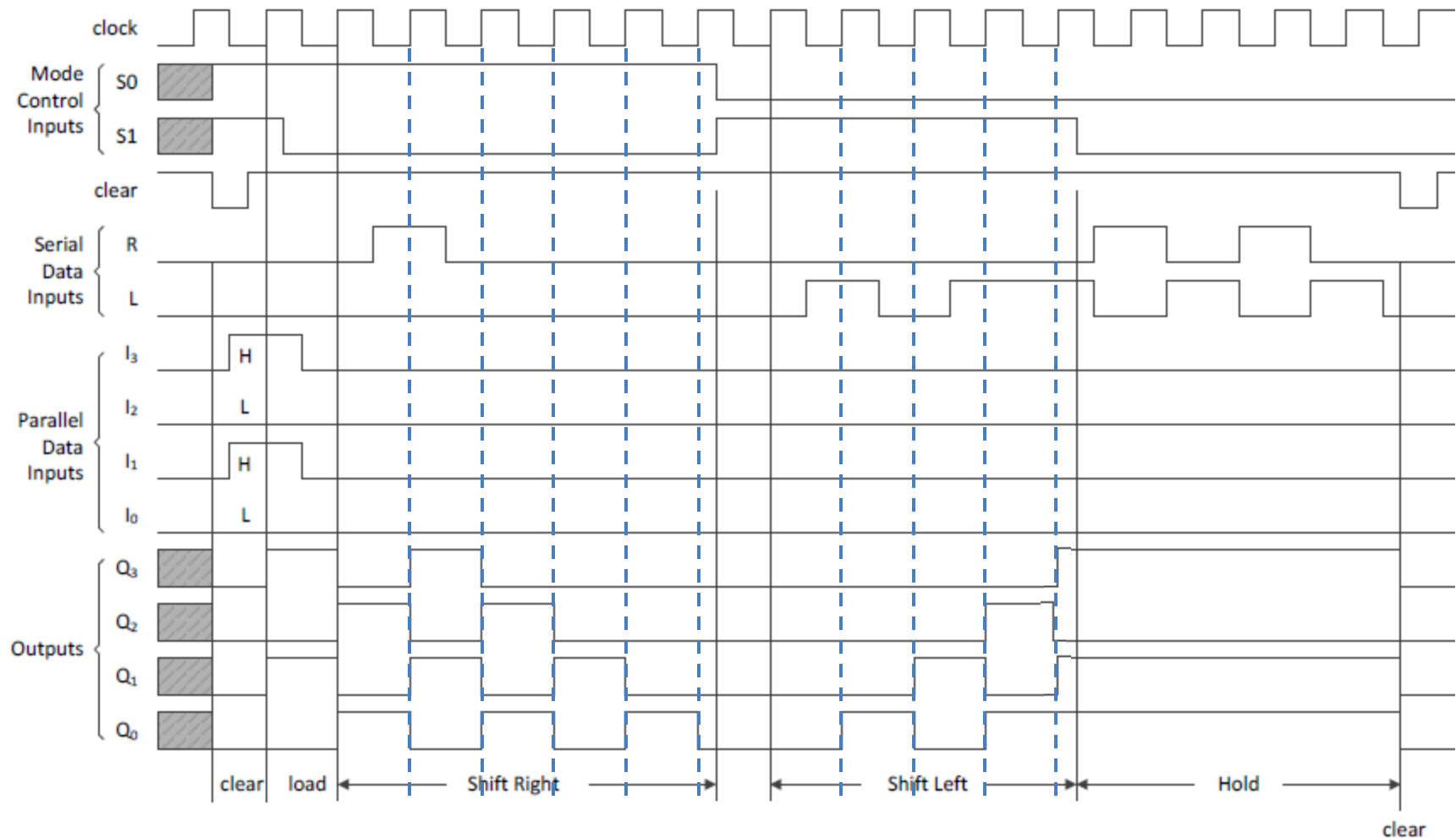

Serial Binary Adder


 
- A system that performs the addition of two binary numbers in serial form (bit by bit).



- What do we need?
 - 2 inputs: 2 shift registers
 - Perform addition: a Full Adder
 - Store Carry-out bit: a flip-flop
 - Store output: a shift register



How Does It Work?

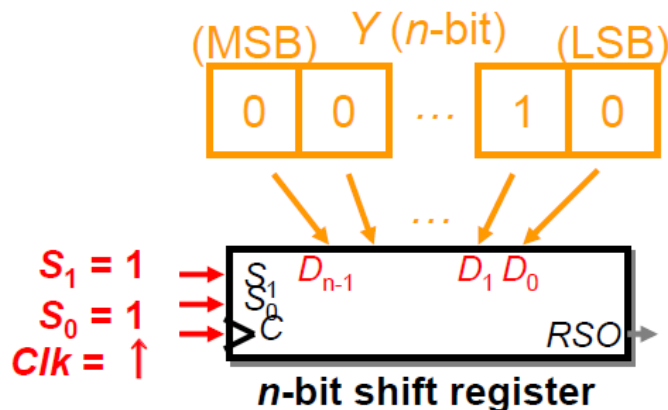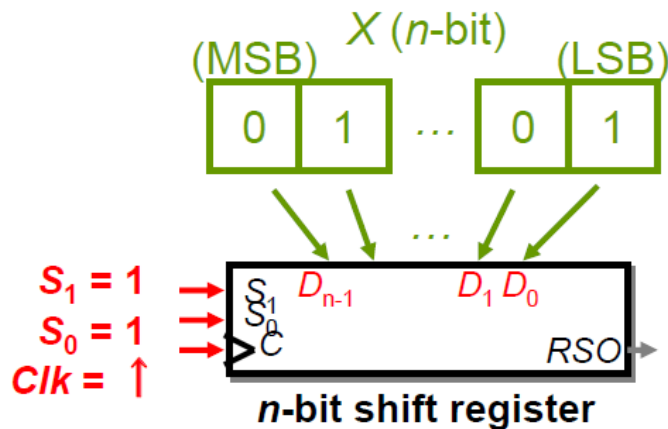STEP 1: Parallel loading of the two binary number X and Y (n -bit numbers into n -bit shift register)




How Does It Work?

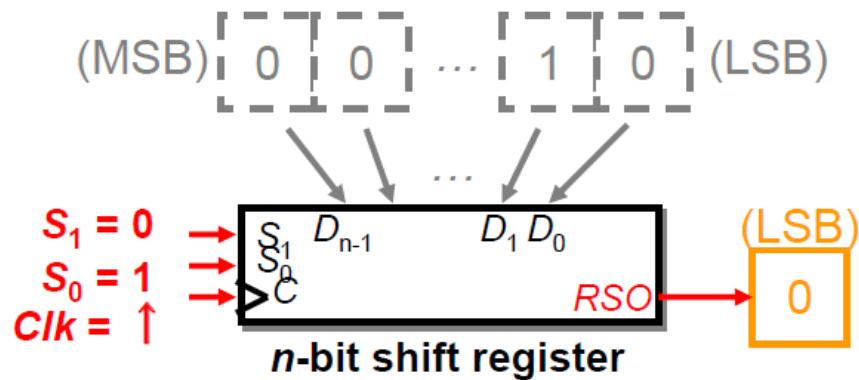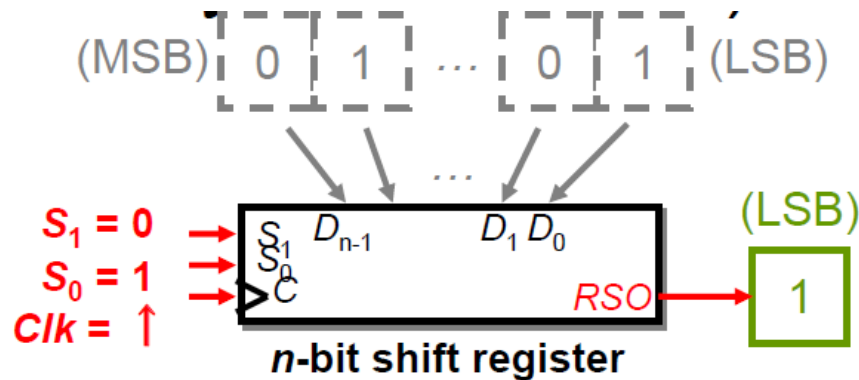STEP 2: Shift out the binary number bit-by-bit, starting from LSB first




How Does It Work?

STEP 3: Forward the bits to full adder

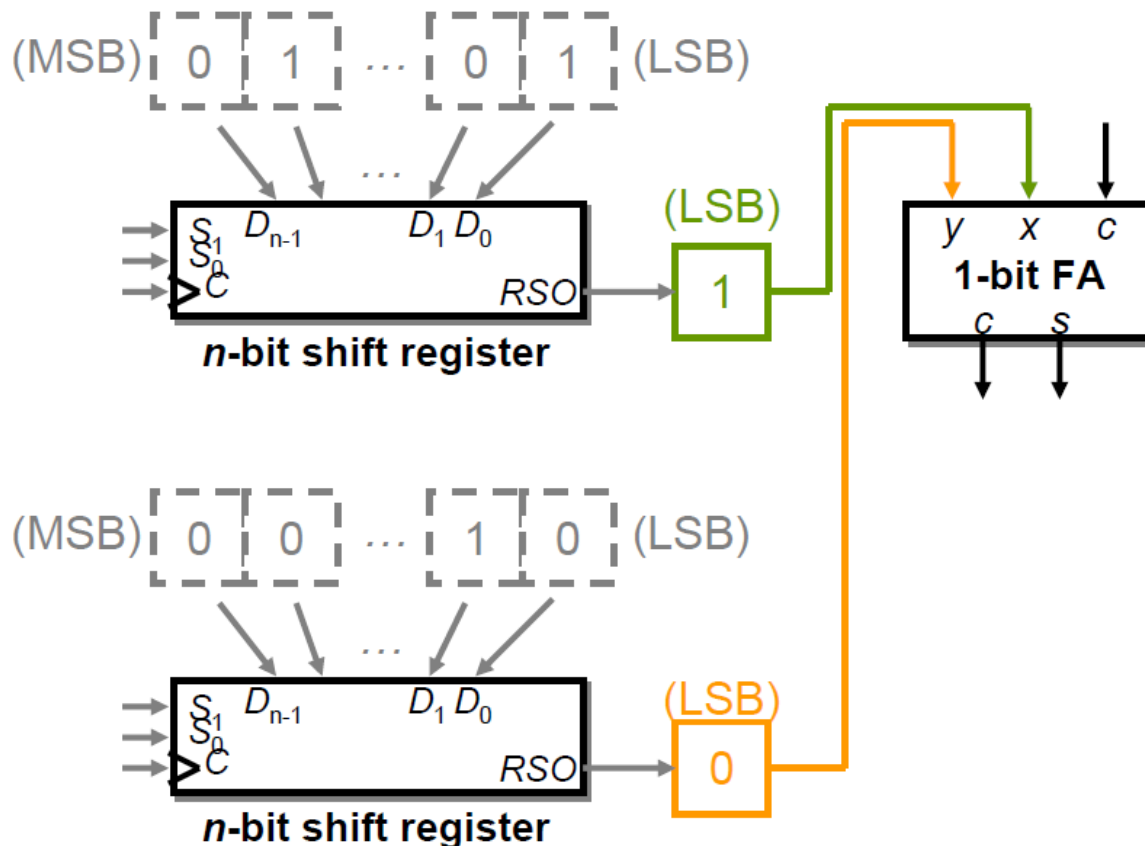


How Does It Work?

STEP 3: Perform one bit addition

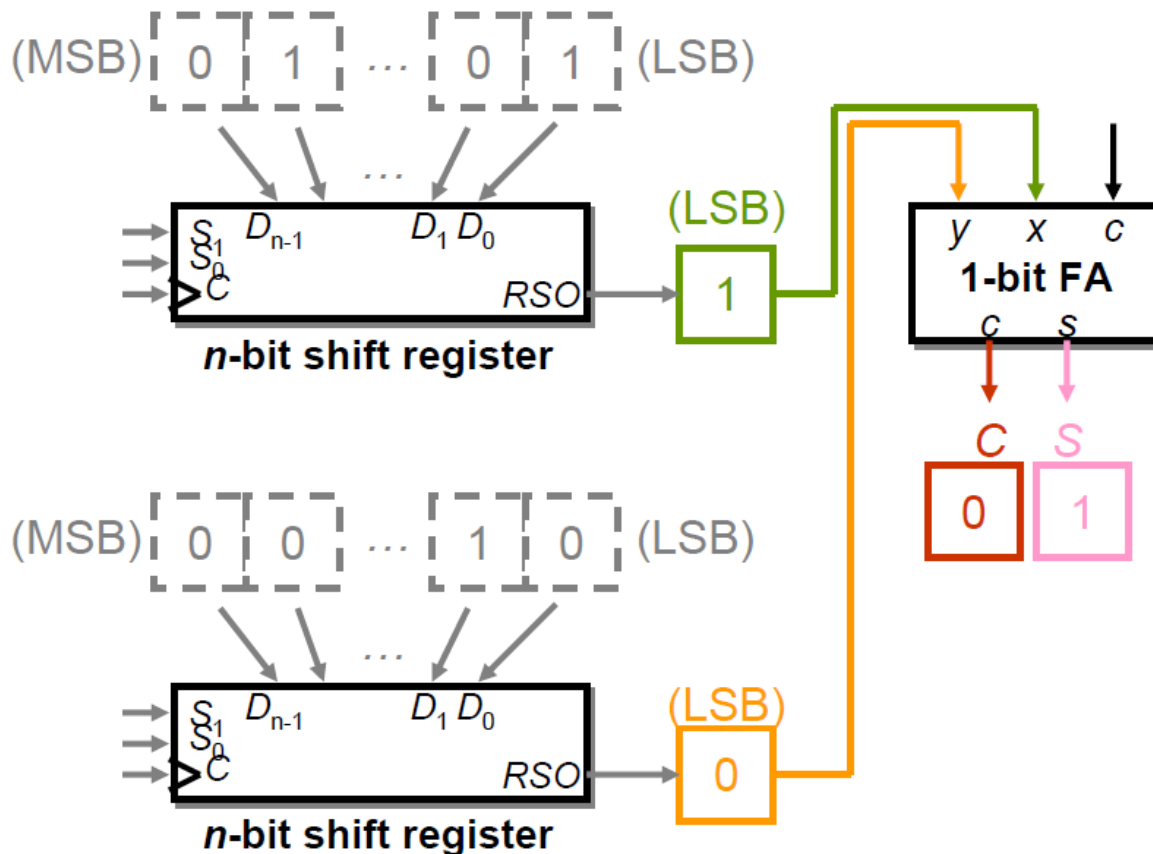


How Does It Work?

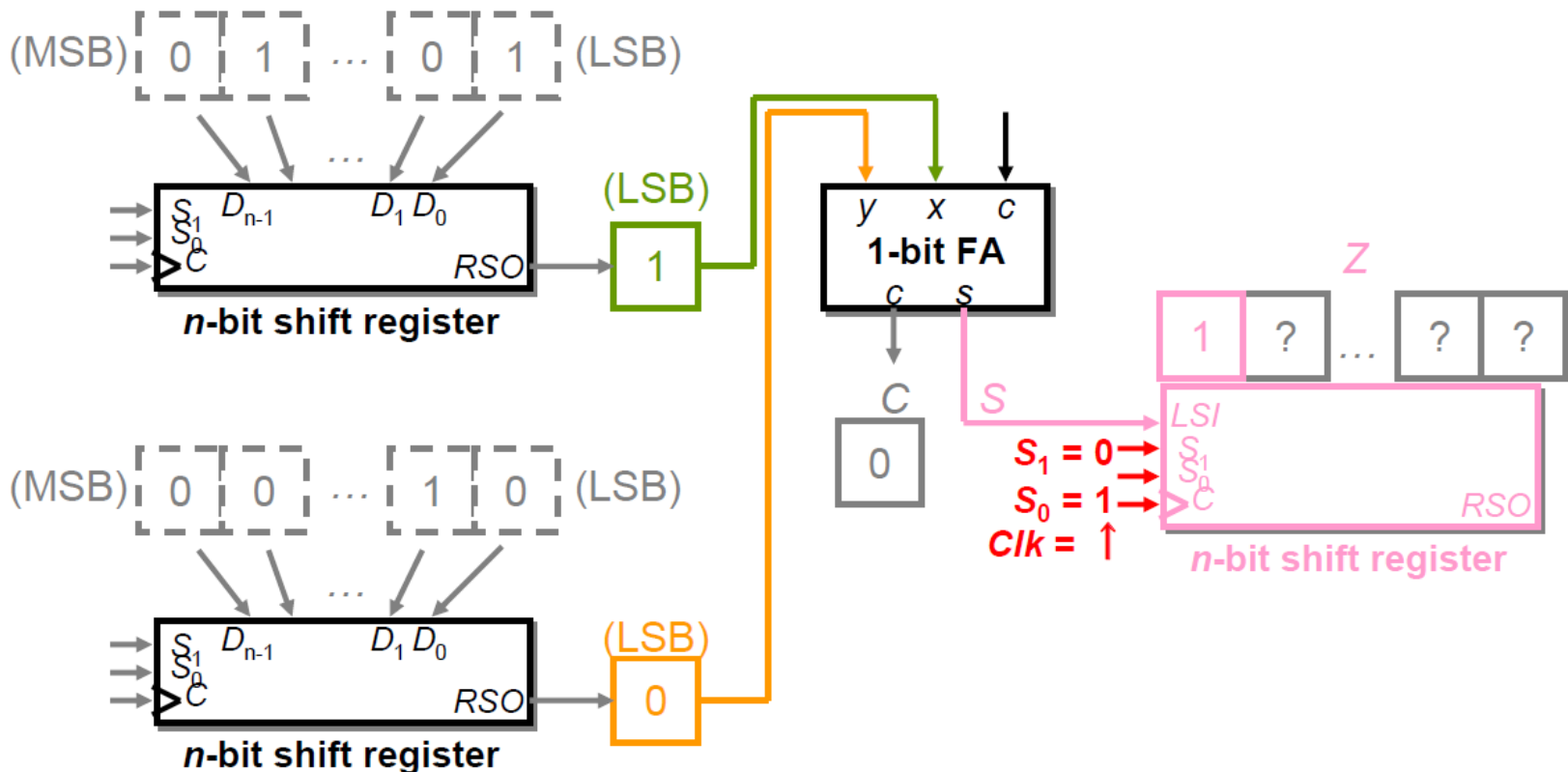STEP 4: Feed the 1-bit output sum (S) to the output shift register (Z)




How Does It Work?

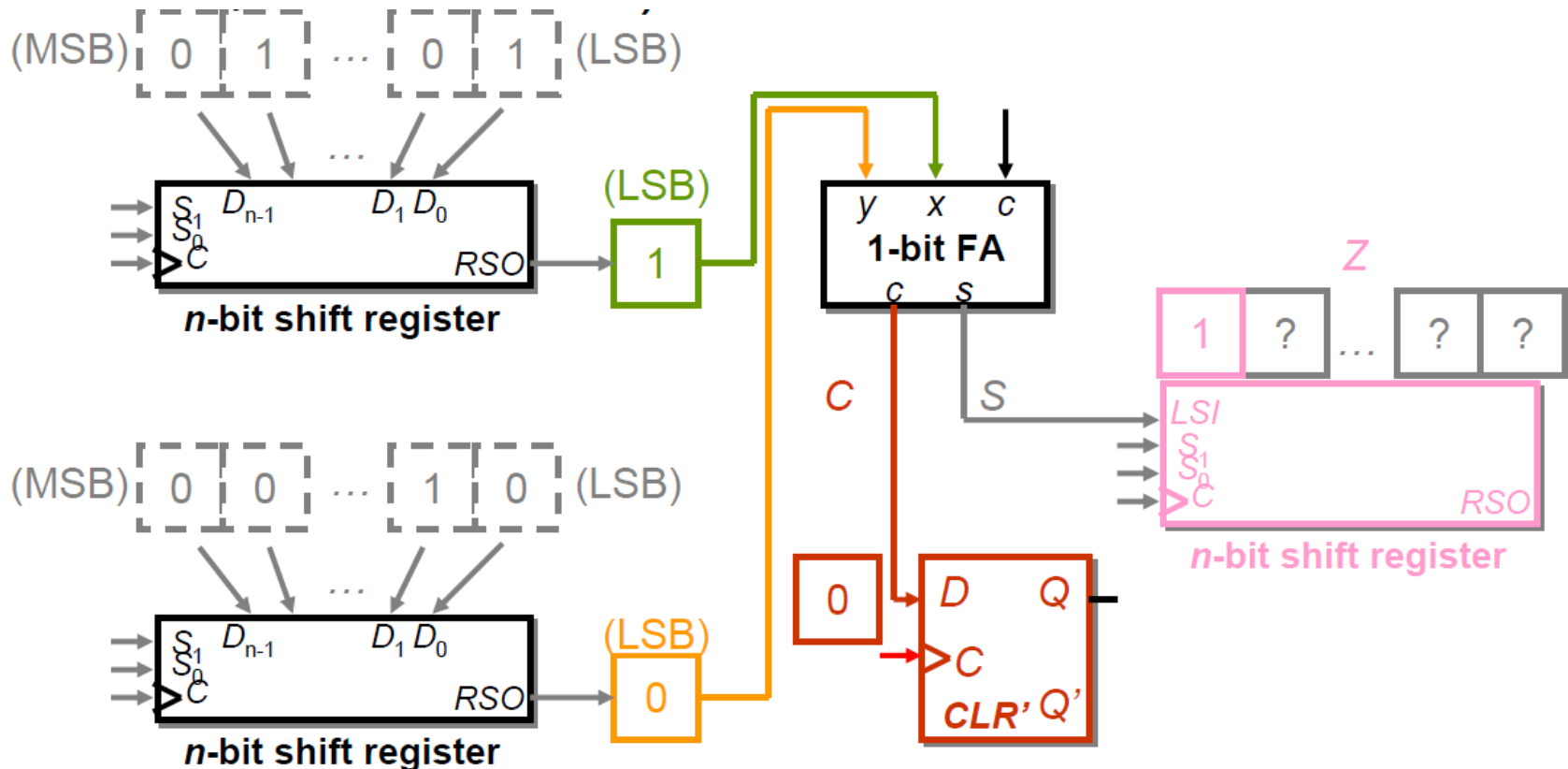STEP 5: Store the 1-bit Carry-out (C) to a flip-flop for later use




How Does It Work?

STEP 6: Calculate the next bit

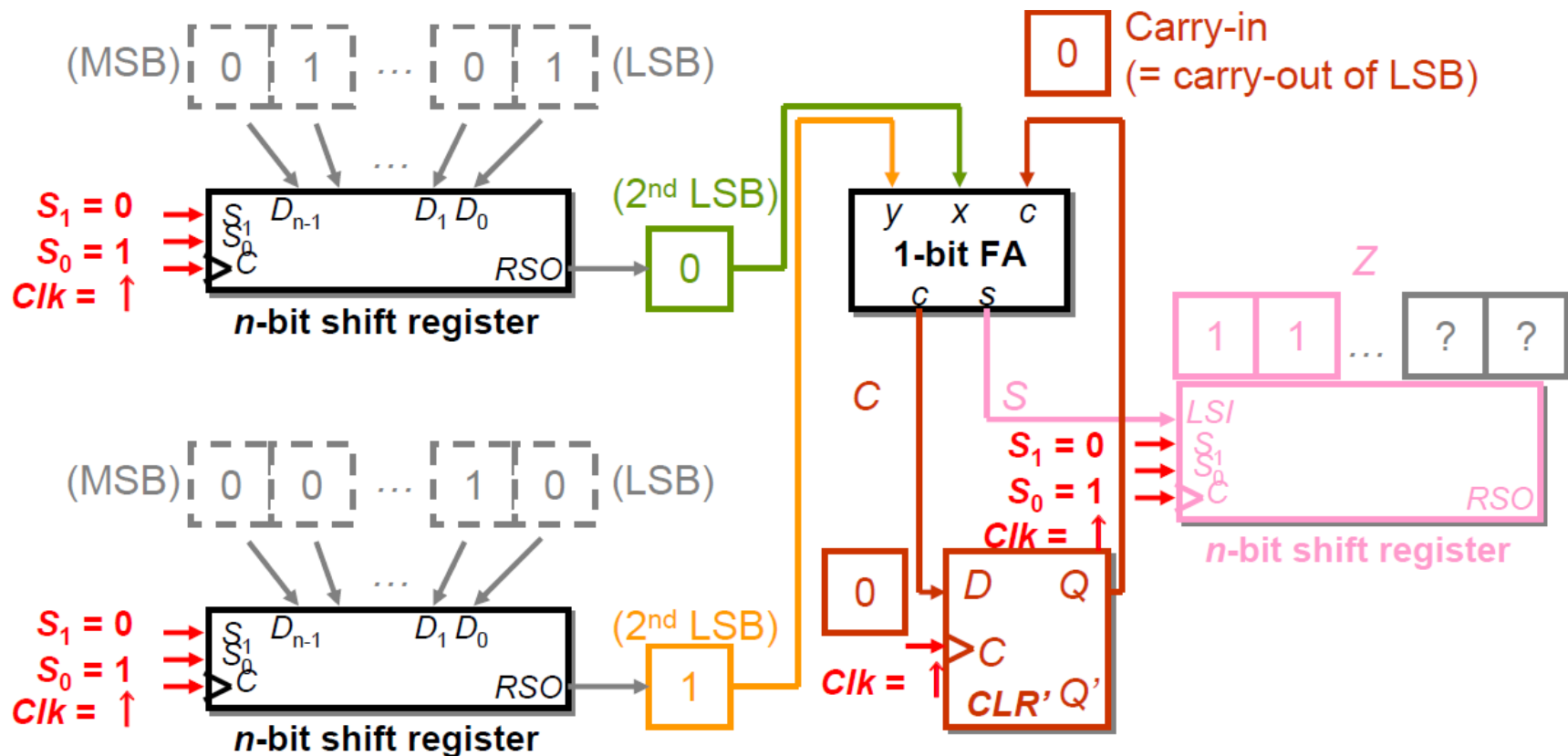


How Does It Work?

Last STEP: Calculate the MSB

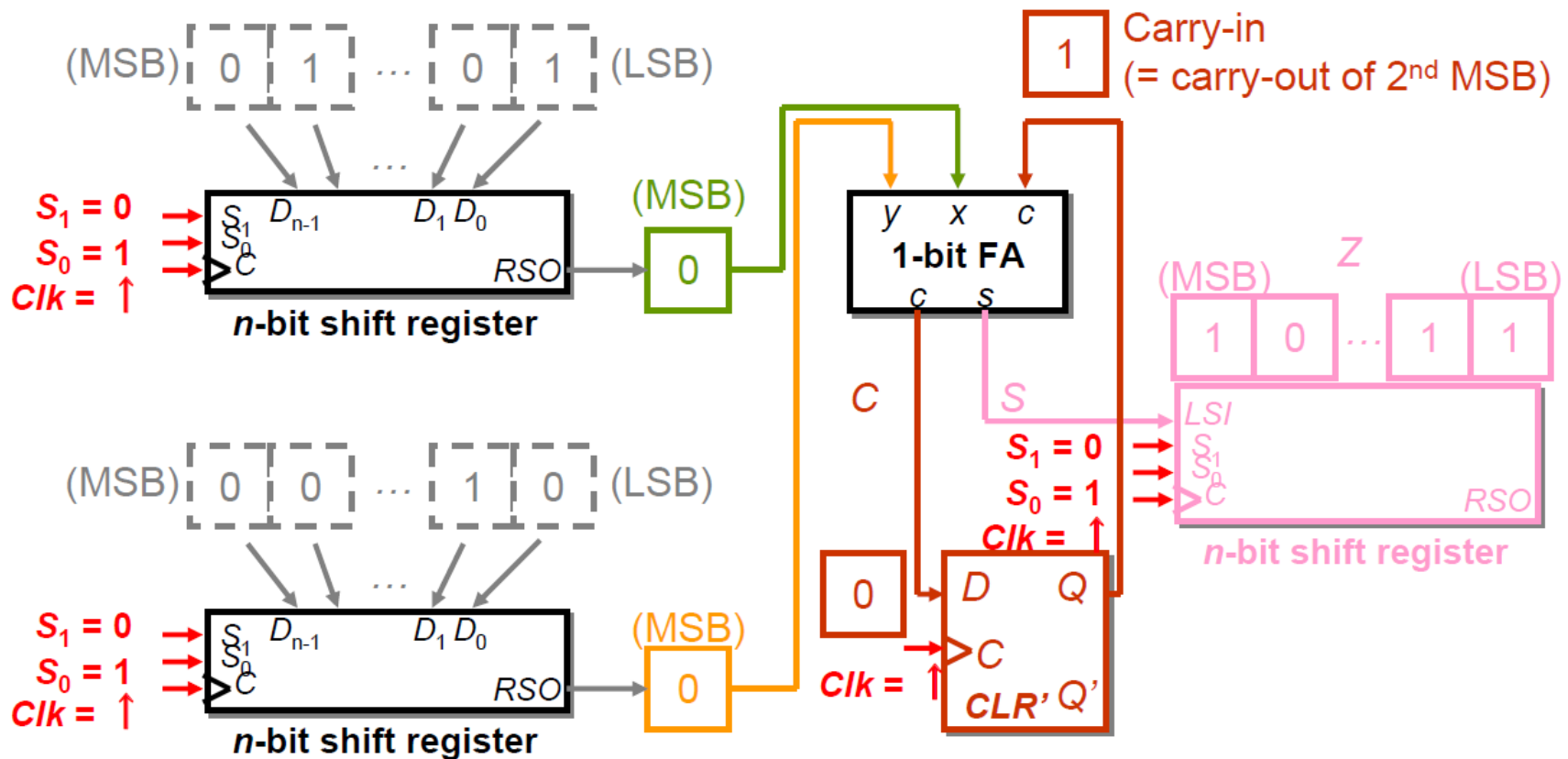

Serial Adder (Full Circuit)

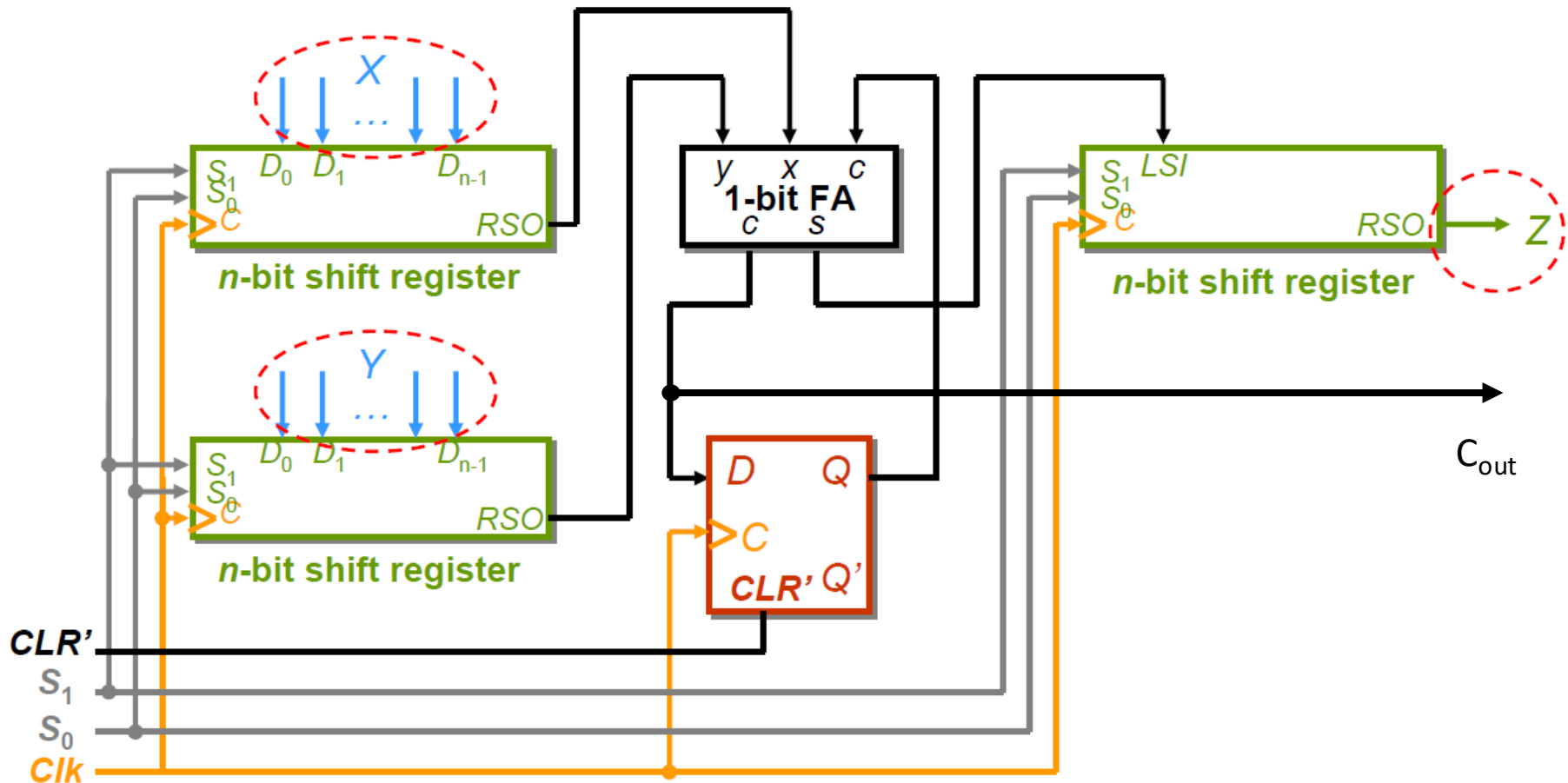

Input: X, Y (n -bit parallel load)

Adder: add the LSB first


Output: Z (n -bit serial out, LSB first)

$Z = X + Y$

10.2 Counters


- A special register that goes through a predefined sequence of states
- Used to control operations in a circuit
- Asynchronous counter such as ripple counter (FFs are triggered by the transition of other FFs)
- Synchronous counter: FFs are triggered by a common clock pulse signal

Ripple Counter (Asynchronous)

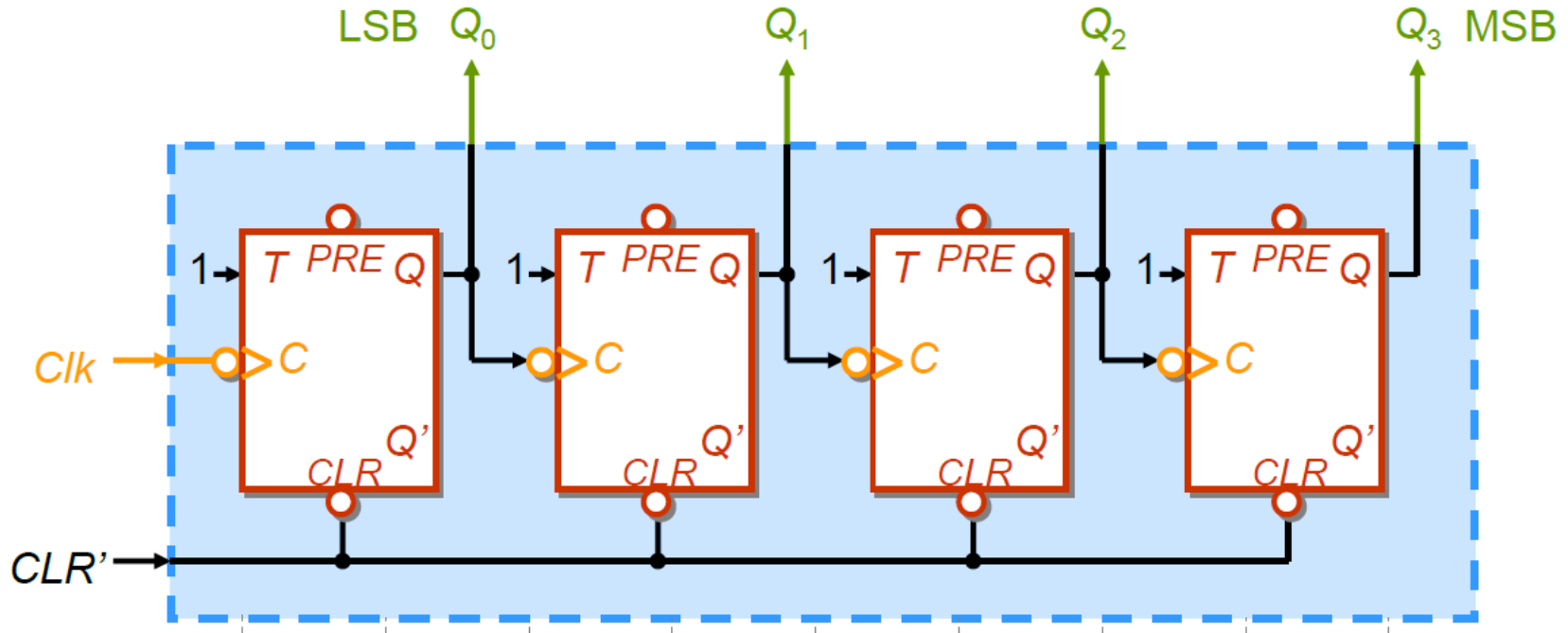

- Input signals all HIGH '1': Toggle mode
- First FF is triggered with Clk signal
- Subsequent FFs are triggered by the output transition of previous FFs.

How Does It Work?

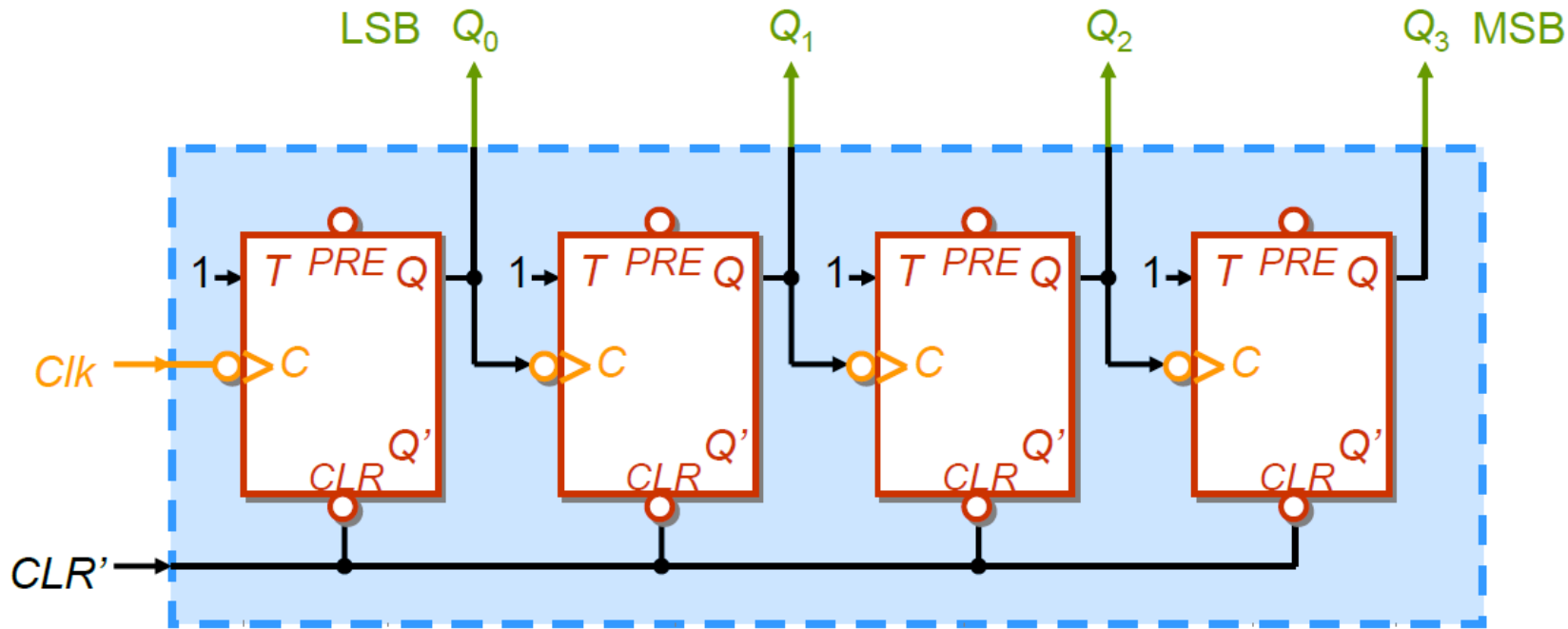


$Clk \downarrow$	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16
Q_0	0	1 → 0	1 → 0	1 → 0	1 → 0	1 → 0	1 → 0	1 → 0	1 → 0	1 → 0	1 → 0	1 → 0	1 → 0	1 → 0	1	1
Q_1	0	0	1	1 → 0	0	0	1	1 → 0	0	1	1 → 0	0	1	0	1	1
Q_2	0	0	0	0	1	1	1	1 → 0	0	0	0	1	1	1	1	1
Q_3	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1

Characteristics

Clk ↓	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16
Q_0	0	1 → 0	1 → 0	1 → 0	1 → 0	1 → 0	1 → 0	1 → 0	1 → 0	1 → 0	1 → 0	1 → 0	1 → 0	1 → 0	1	1
Q_1	0	0	1	1 → 0	0	1	1 → 0	0	1	1 → 0	0	1	1 → 0	0	1	1
Q_2	0	0	0	0	1	1	1	1 → 0	0	0	0	0	1	1	1	1
Q_3	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1


- Up Counter: from 0000 to 1111
- Asynchronous: Triggered by other FFs
- Problem?

Propagation Delay

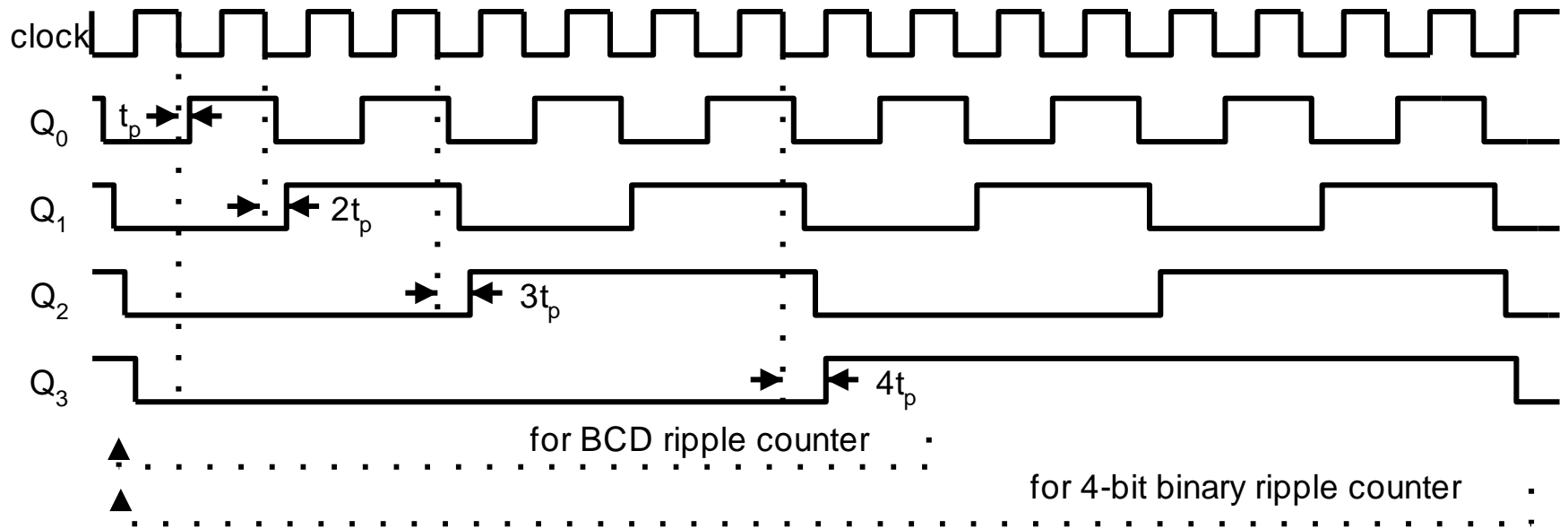


- Propagation delay will ripple through the “clock input” of FFs
- Last flip-flop has the largest delay $4t_p$ for 4-bit ripple counter

Synchronous Counter

 


All FFs are driven by a common clock, thus all the **change of states will occur at the same time** without further delay

Synchronous Counter

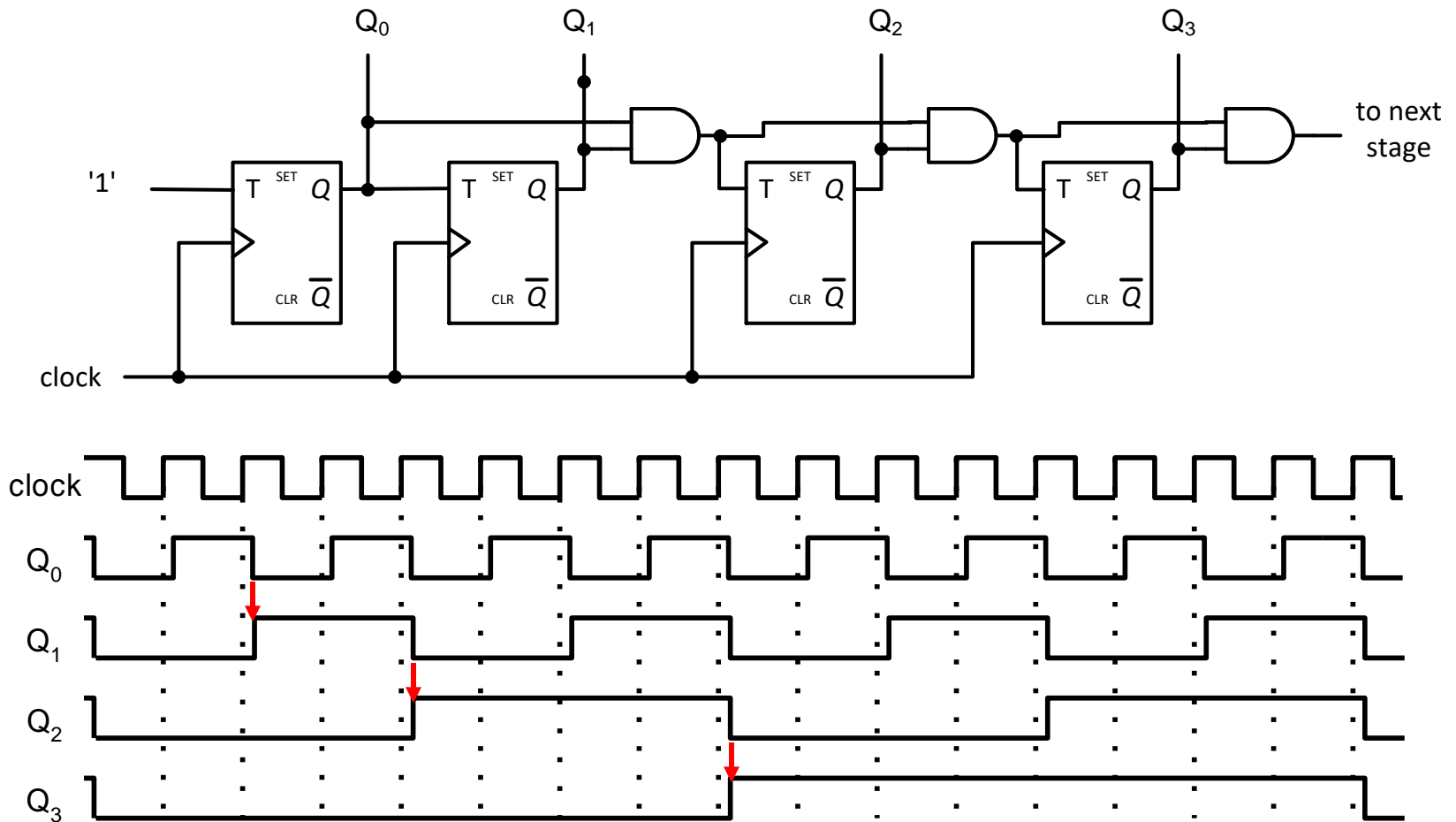



Delays of all FFs are their own propagation delays! No ripple!

Bidirectional (Up-Down) Counter

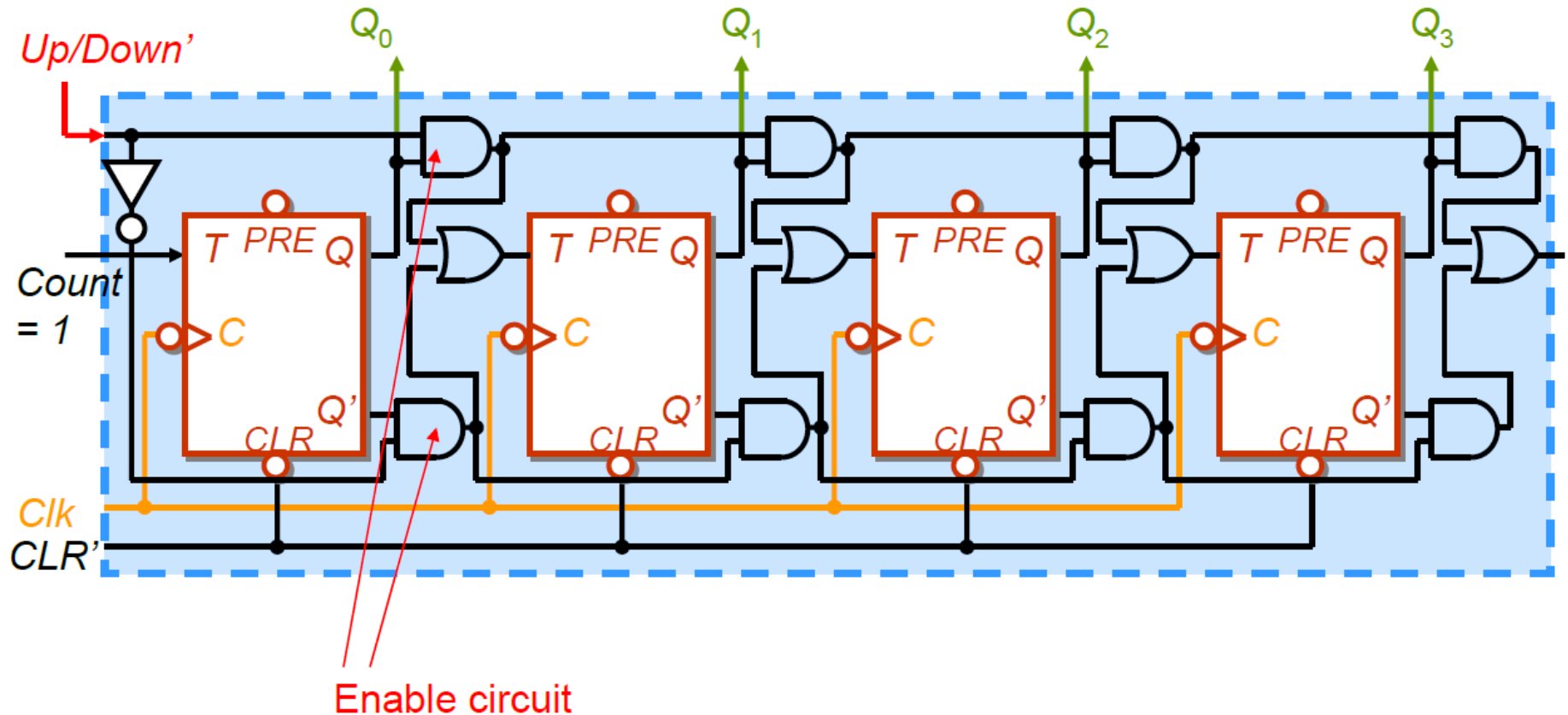


Additional input ***Up/Down'*** to control the counting direction by selecting feeding either ***Q*** or ***Q'*** to next ***T***


How Does It Work?

 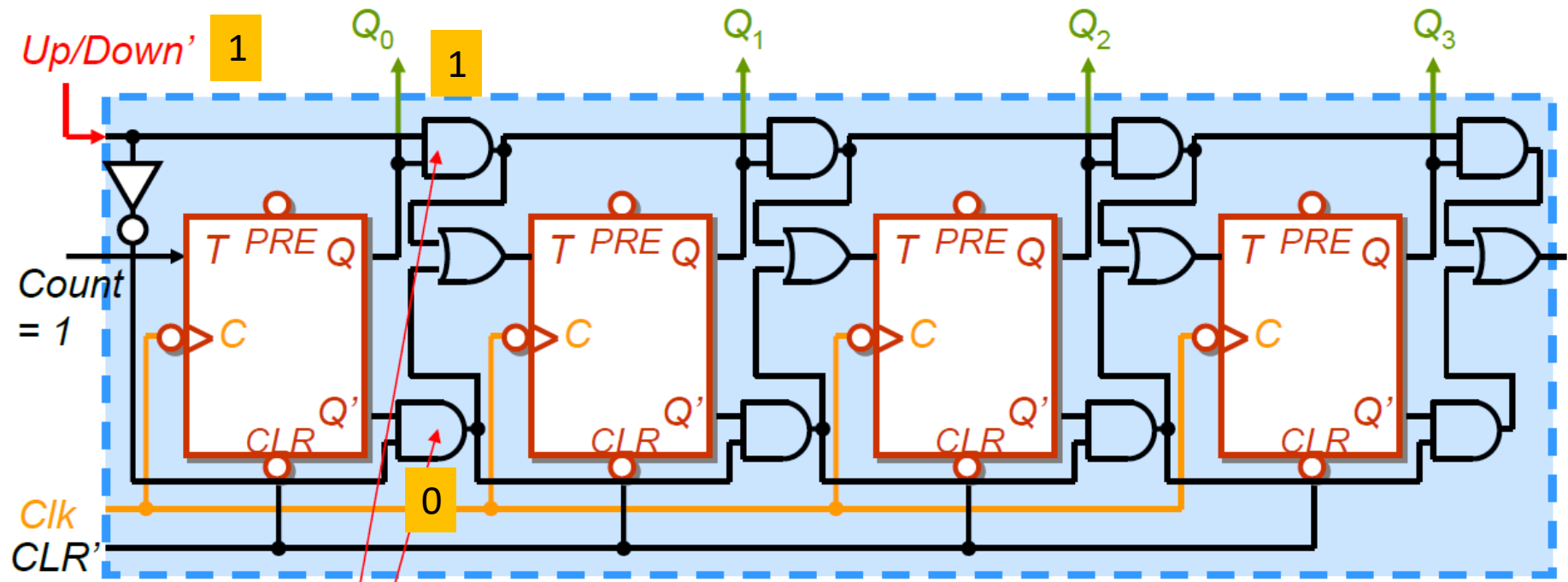

How Does It Work?


 


Down counter

 

How Does It Work?

Down counter

 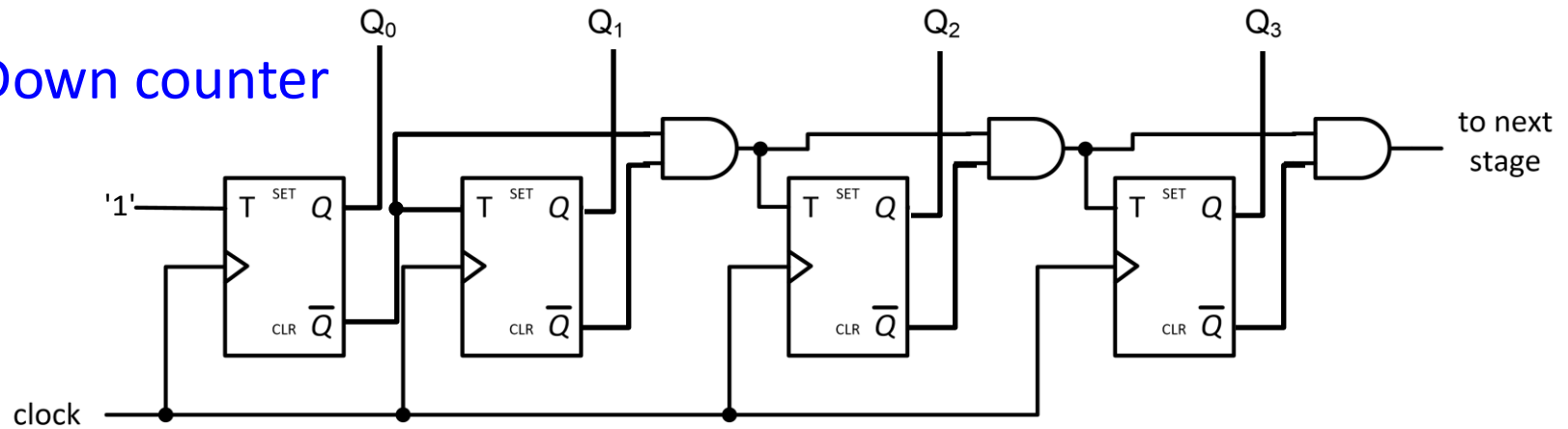


Synchronous Up/Down Counter

Upward Counting Sequence			
Q_3	Q_2	Q_1	Q_0
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	0	1
1	0	1	0
1	0	1	1
1	1	0	0
1	1	0	1
1	1	1	0
1	1	1	1

Downward Counting Sequence			
Q_3	Q_2	Q_1	Q_0
1	1	1	1
1	1	1	0
1	1	0	1
1	1	0	0
1	0	1	1
1	0	1	0
1	0	0	1
1	0	0	0
0	1	1	1
0	1	1	0
0	1	0	1
0	1	0	0
0	0	1	1
0	0	1	0
0	0	0	1
0	0	0	0


Binary Counter

 

- **LOAD**: to load inputs ($I_3I_2I_1I_0$) to outputs ($Q_3Q_2Q_1Q_0$) with signal '1'
- **CLR**: to clear the counter ($Q_3Q_2Q_1Q_0 = "0000"$) with signal '1'
- **Count**: +1 with signal '1' (e.g., from "0010" to "0011")
- **LOAD/CLR**: can be active high/low and async/sync


Modulo Counter

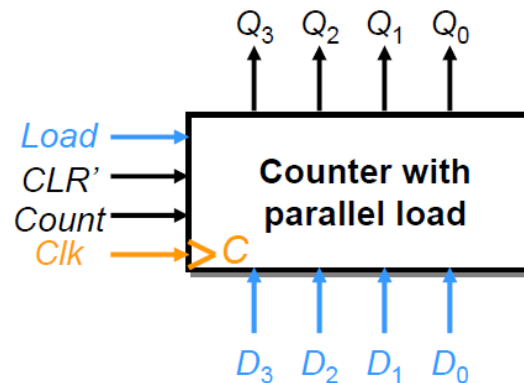- A modulo- N (abbreviated mod- N) counter is a counter that goes through a repeated sequence of N counts.
 - 0, 1, 2, 3, 0, 1... \rightarrow mod-4 counter
- Counter + Parallel Load



Parallel load the data into the counter when $Load = 1$ and Clk is in active transition


Modulo Counter (Example)

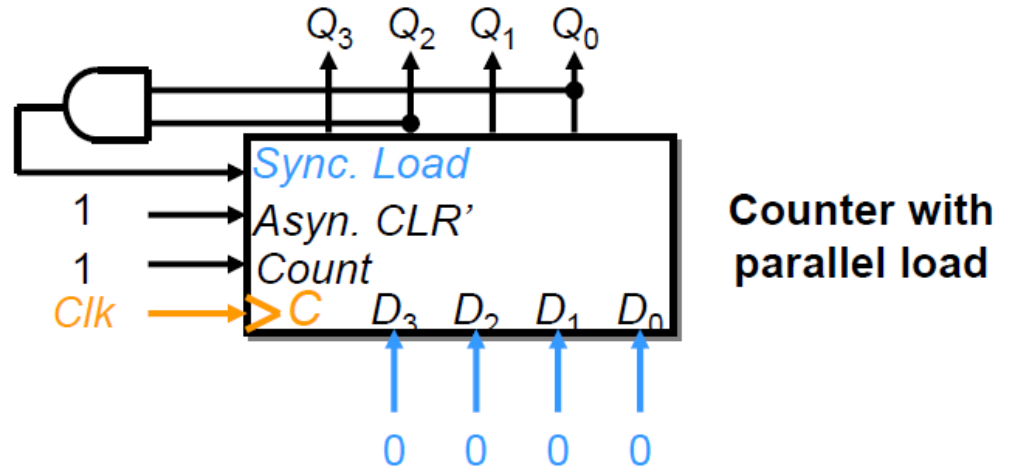


- Initial input: 0000
- Synchronous Load Bit: Q_2Q_0
→ Reset to 0000 after x1x1
- Counter: 0000 → 0001 → 0010 → 0011 → 0100 → 0101 → 0000
- Mod-6 counter

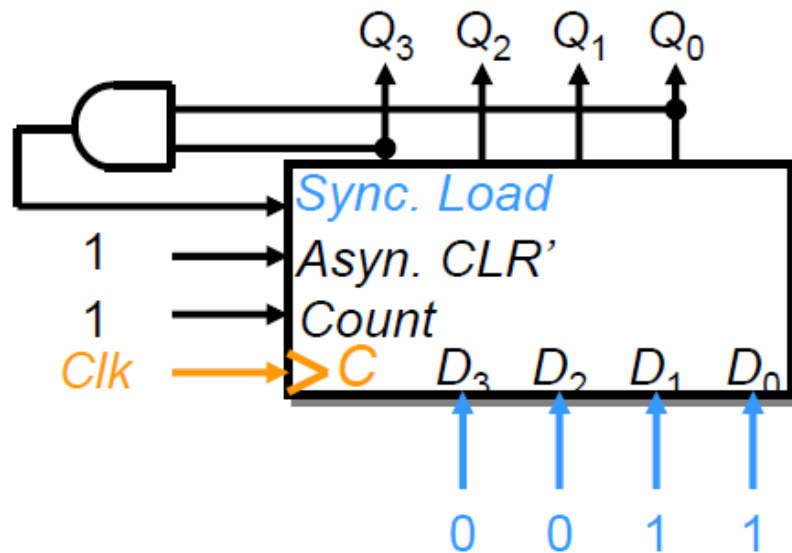Exercise

Determine the number sequence generated by the counter.




Exercise

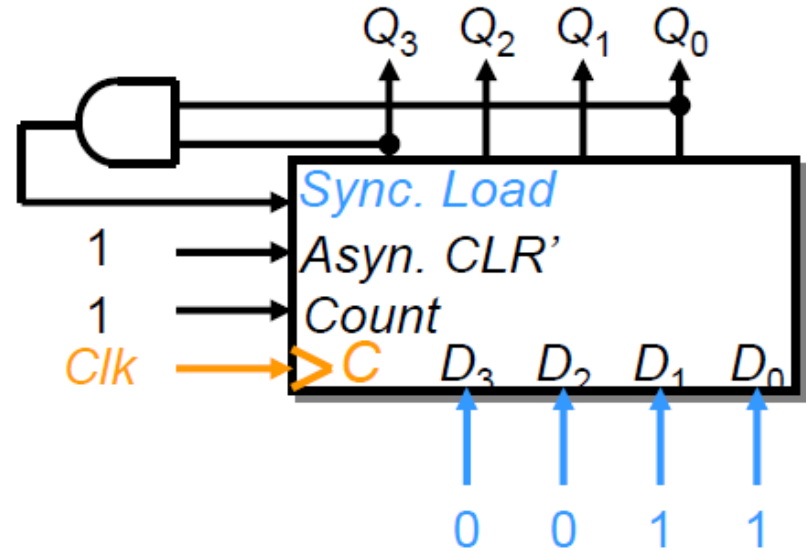



- Initial input:
- Synchronous Load Bit:
→ Reset to after
- Counter:
- Mod- counter

Asynchronous Load

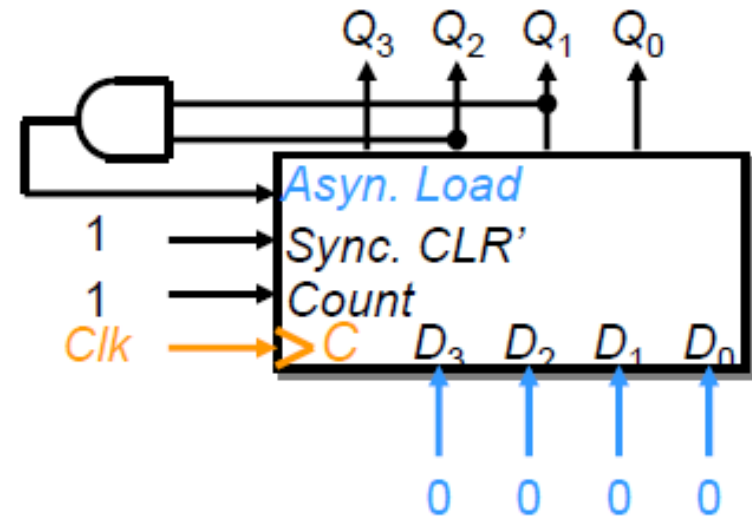


- Initial input: 0000
- Asynchronous Load Bit: Q_2Q_1
→ Reset to 0000 once x11x is detected
- Counter: 0000 → 0001 → 0010 → 0011 → 0100 → 0101 → 0**11**0/**0000**
- 0110 only appear for a negligible period and the counter is reset

Use CLEAR without Input

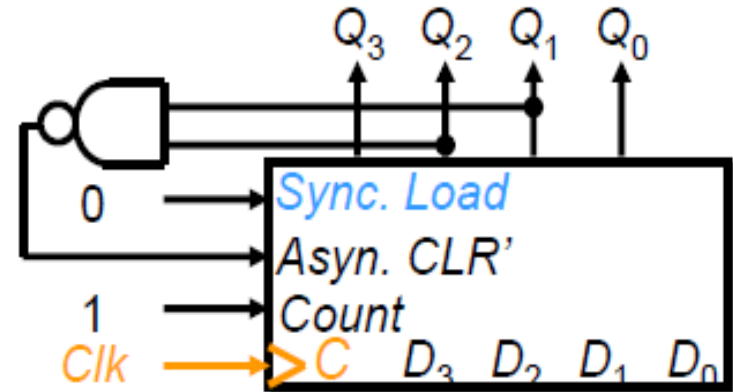 


- Simpler design without inputs (Start with “0000”)
- Synchronous CLR: Counter reset at the next Clk (0101)
- Asynchronous CLR: Counter reset instantly when 0110 is detected

Examples

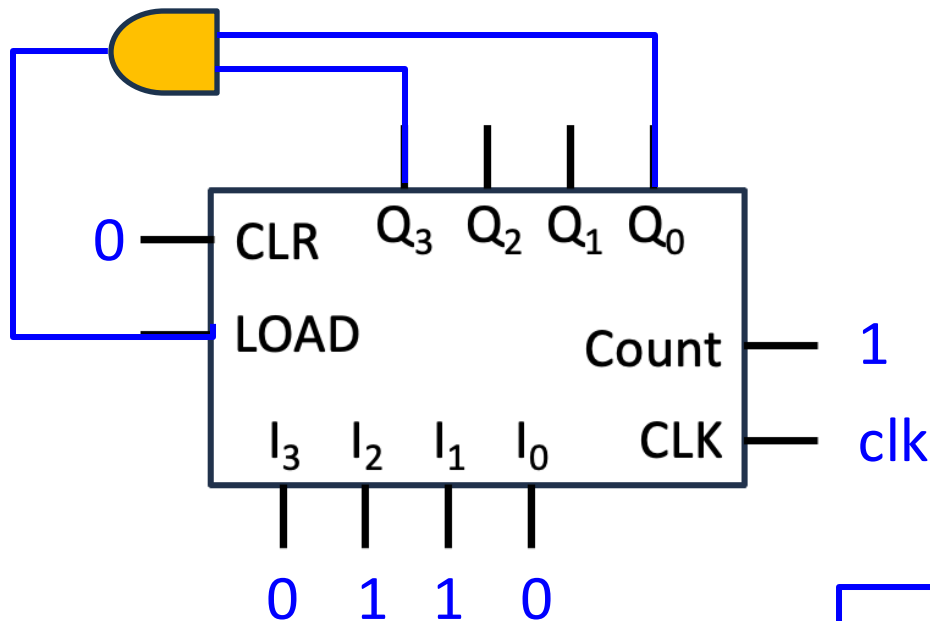


Counter: 0110 \rightarrow 0111 \rightarrow
1000 \rightarrow 1001 \rightarrow 0110

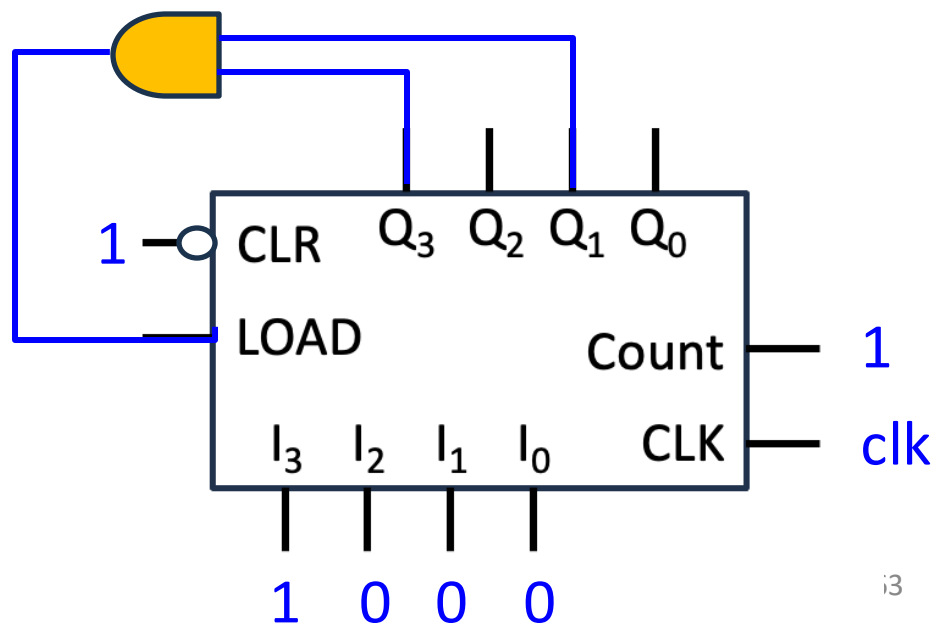Counter: 1000 \rightarrow 1001 \rightarrow
1010 \rightarrow 1000




Exercises

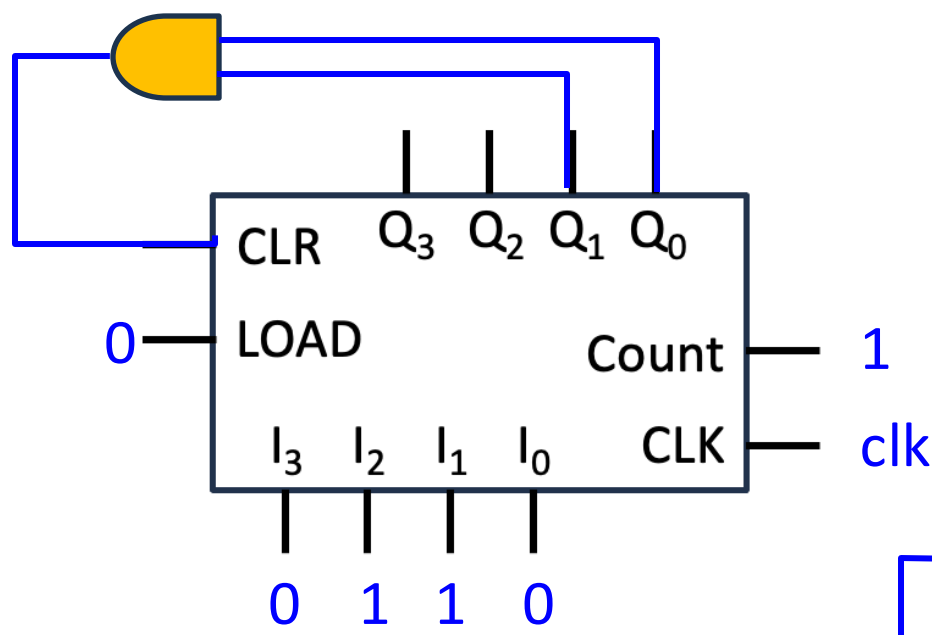


Counter:

Counter:

 


Ring Counter

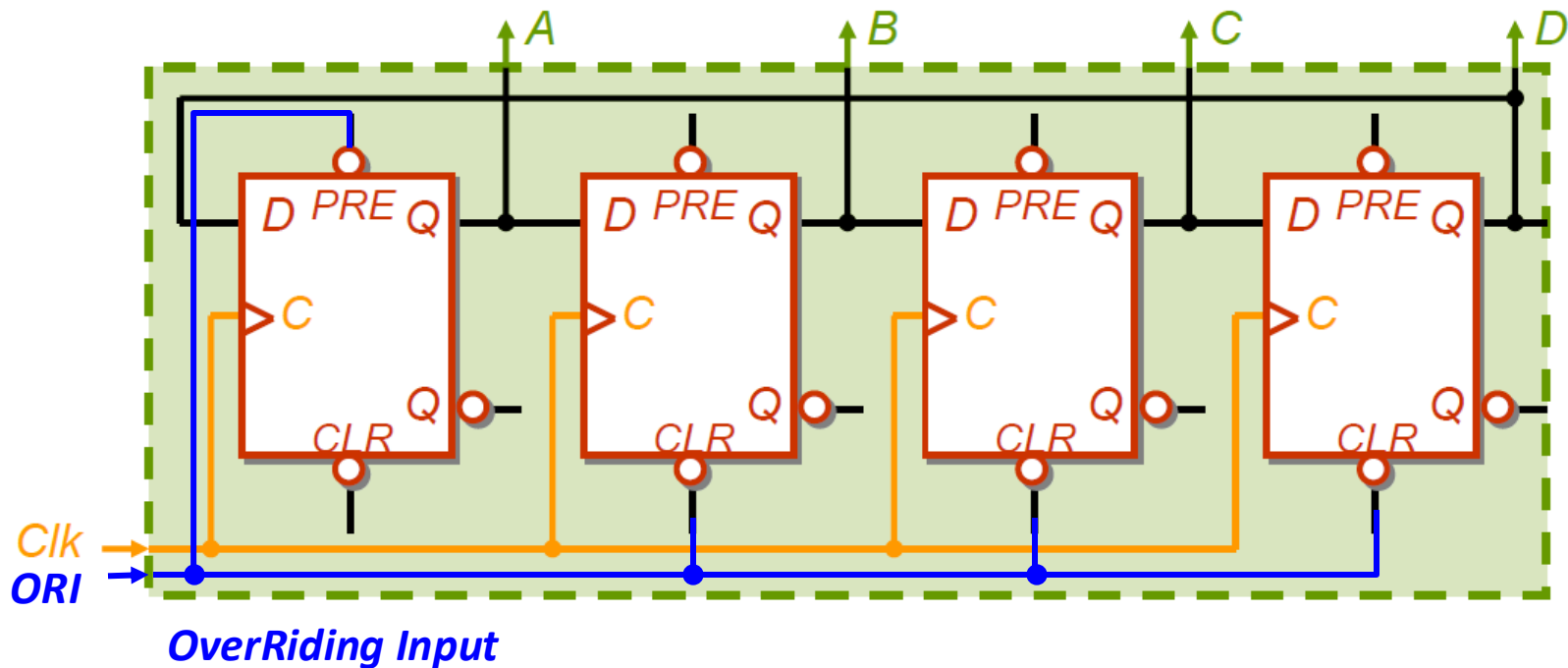- Circular shift counter: Output of last stage (FF) is connected to input of first stage (FF)
- Initial state: A is '1', others are '0'
- Only one FF is set to '1' at all time (One hot counter)




Ring Counter

 

Time	<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>Decoded Output</i>
1 st clock period	1	0	0	0	<i>A</i>
2 nd clock period	0	1	0	0	<i>B</i>
3 rd clock period	0	0	1	0	<i>C</i>
4 th clock period	0	0	0	1	<i>D</i>
5 th clock period	1	0	0	0	<i>A</i>
...

- The '1' will be rotated through the registers
- ***N***-stage counter = ***N*** FFs = ***N*** states
- Useful in time division multiplexing applications
 - Enable ONLY one output/device/user at a time

VHDL Codes for Ring Counter

 

A	B	C	D	Decoded Output
1	0	0	0	A
0	1	0	0	B
0	0	1	0	C
0	0	0	1	D

VHDL Code for 4 bit Ring Counter


```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Ring_counter is
    Port ( CLOCK : in  STD_LOGIC;
          RESET : in  STD_LOGIC;
          Q : out  STD_LOGIC_VECTOR (3 downto 0));
end Ring_counter;


architecture Behavioral of Ring_counter is
    signal q_tmp: std_logic_vector(3 downto 0):= "0000";
begin
    process(CLOCK,RESET)
    begin
        if RESET = '1' then
            q_tmp <= "1000";
        elsif Rising_edge(CLOCK) then
            q_tmp(3) <= q_tmp(0);
            q_tmp(2) <= q_tmp(3);
            q_tmp(1) <= q_tmp(2);
            q_tmp(0) <= q_tmp(1);
        end if;
    end process;
    Q <= q_tmp;
end Behavioral;
```

Twisted Ring Counter (Johnson)

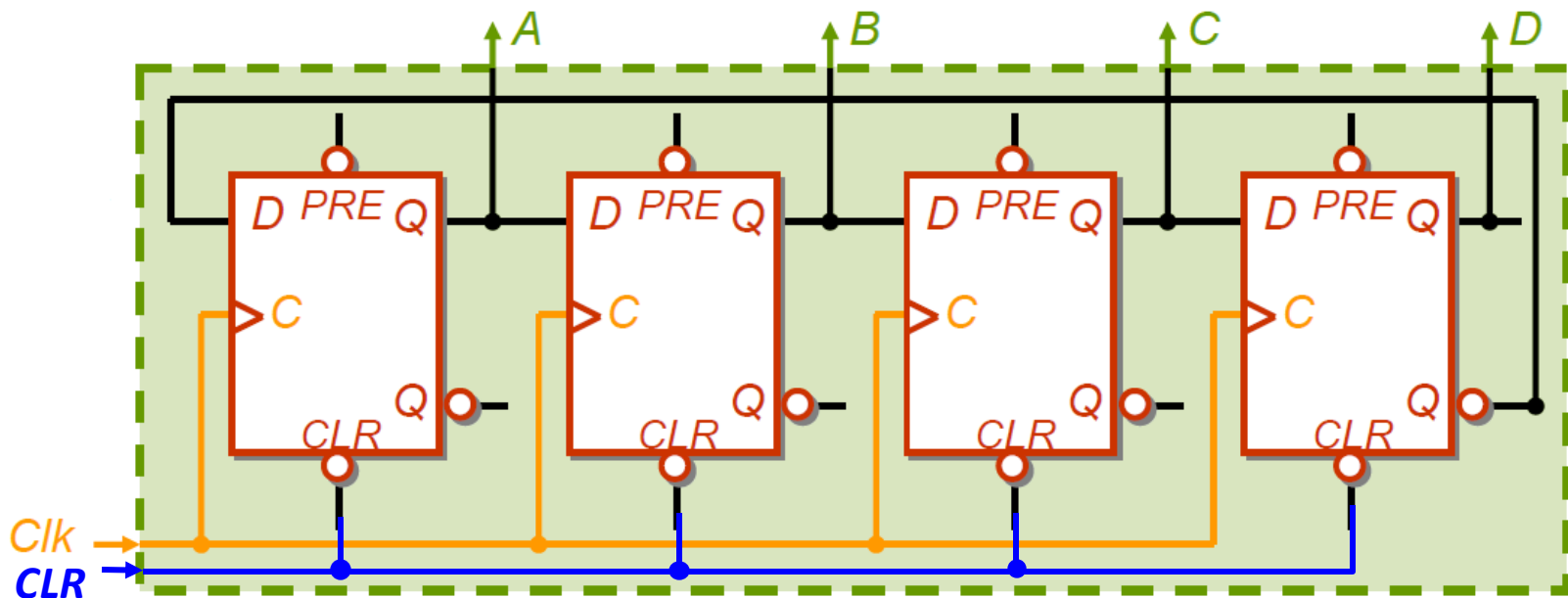- Circular shift counter: **Complement** output of last stage (FF) is connected to input of first stage
- Initial state: All are '0'



Johnson Ring Counter

 


A	B	C	D
0	0	0	0
1	0	0	0
1	1	0	0
1	1	1	0
1	1	1	1
0	1	1	1
0	0	1	1
0	0	0	1

- Count UP and then DOWN
- Adjacent States differ only by 1 bit, as in Gray Code
- N -stage counter = N FFs = $2N$ states

Johnson Ring Counter




A	B	C	D	Decoded Output
0	0	0	0	$\overline{A} \overline{D}$
1	0	0	0	$A \overline{B}$
1	1	0	0	$B \overline{C}$
1	1	1	0	$C \overline{D}$
1	1	1	1	$A D$
0	1	1	1	$\overline{A} B$
0	0	1	1	$\overline{B} C$
0	0	0	1	$\overline{C} D$

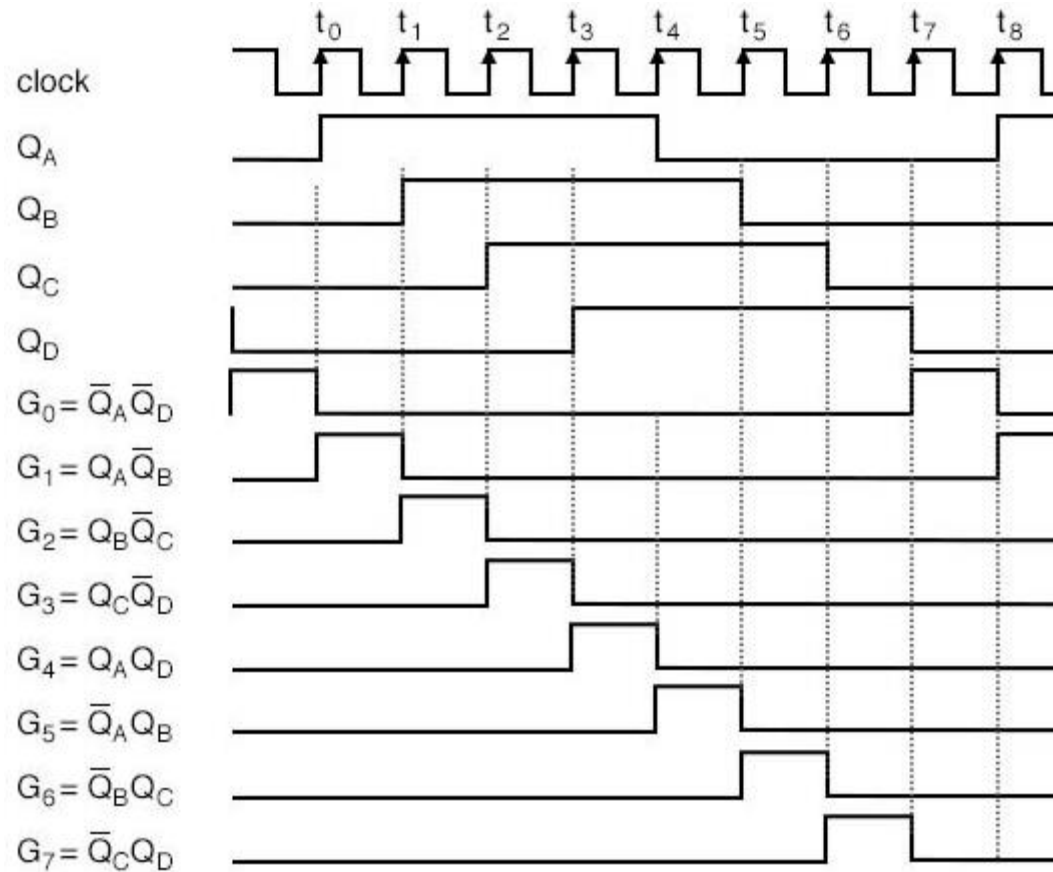


- Only two input gates are needed to decode each state for any N-stage Johnson ring counter

   Example (3-phase wave generator)

Phase difference: Fraction of a period difference between the signals expressed in deg






Example (3-phase wave generator)

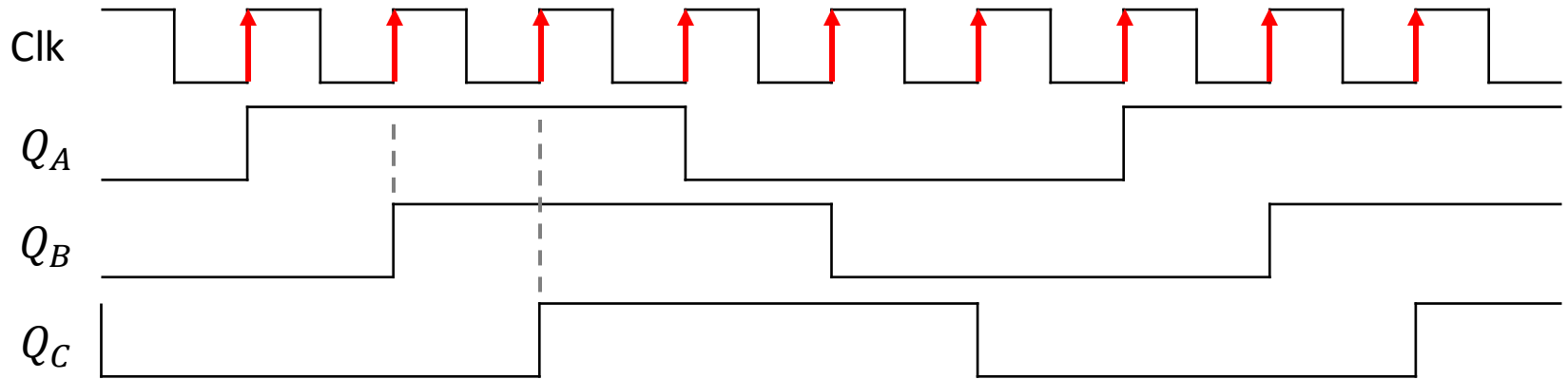

- 3-stage Johnson Ring Counter
- Phase difference
 - Q_A and Q_B : 60°
 - Q_B and Q_C : 60°
 - Q_A and Q_C : 120°

Example (3-phase wave generator)

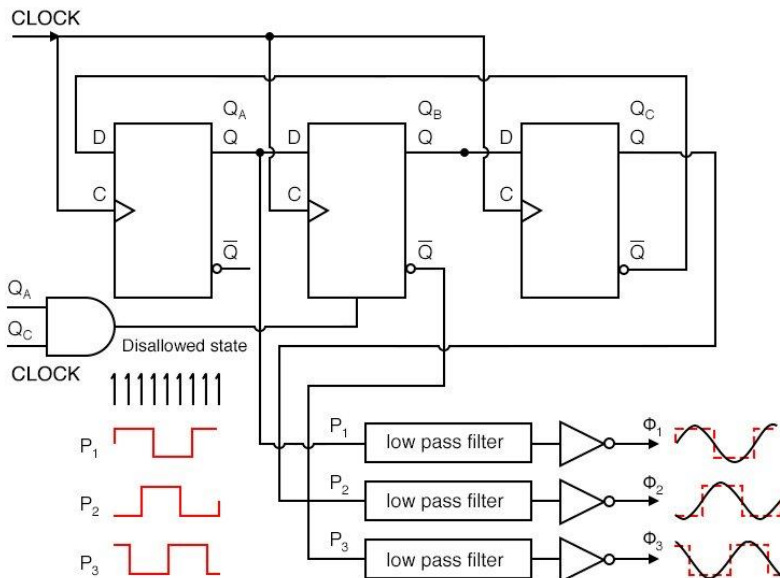  

- 3-phase alternating power supply
- 120° phase difference
- Low-pass filter → sine waves