
 


EE2000 Logic Circuit Design


Lecture 7 – Latch and Flip-Flop Circuits

 

PAL16R6




27 mm × 7.6 mm

 


9 mm × 9 mm

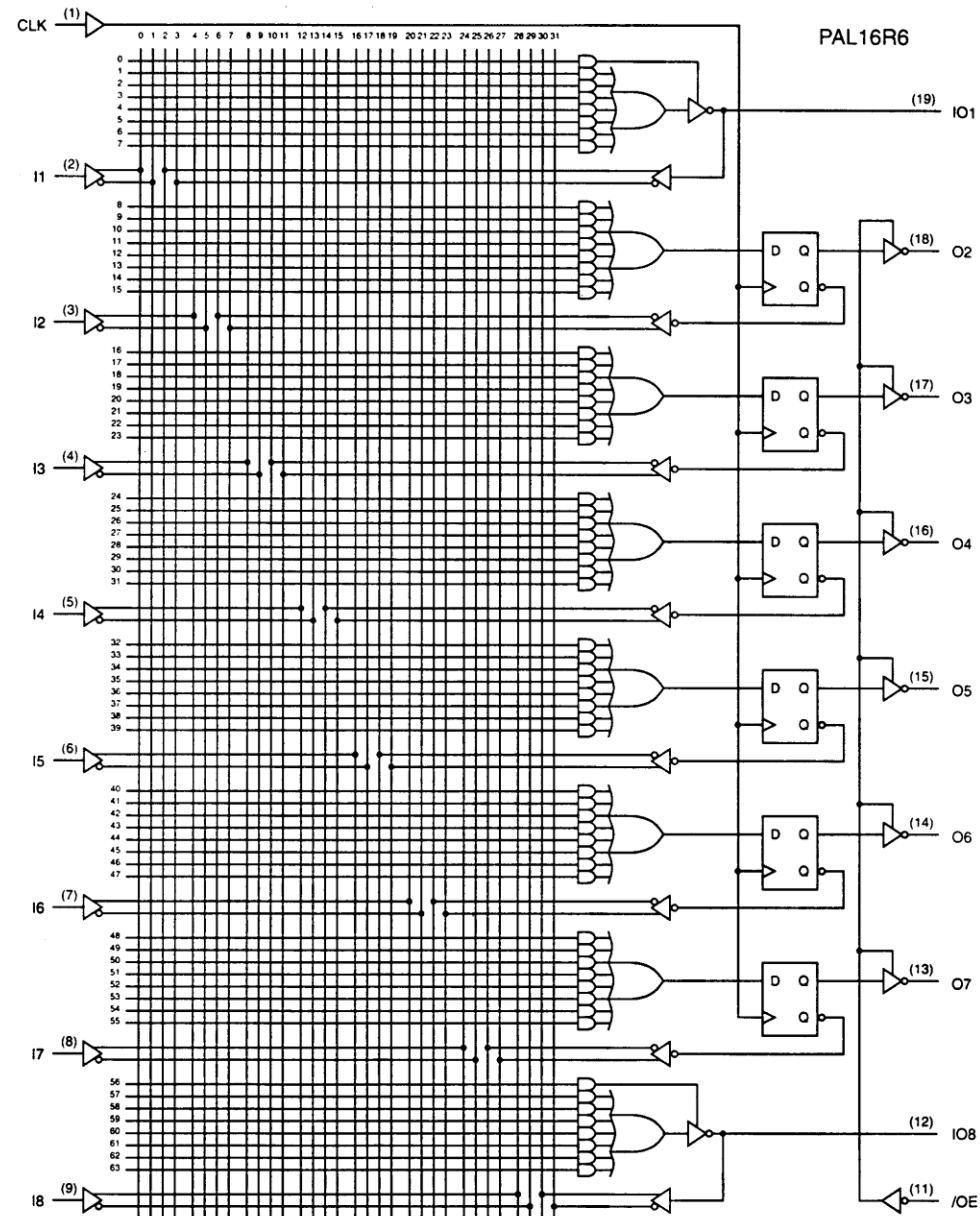- A PAL device with **16** inputs, **6** outputs with **D-latch** (1-bit memory device), and 2 un-buffered outputs
- **8** inputs are feedback from outputs
- This device can be used for designing a sequential circuit (Lecture 7)



Configurable Logic Block

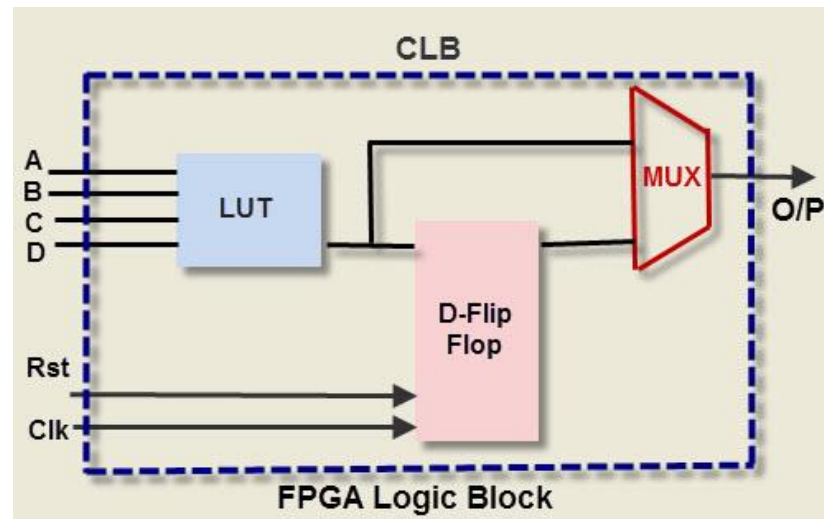- A configurable logic block (CLB) consists of a **look-up-table (LUT)**
- The LUT is for implementing the **truth table** of a logic function (*e.g.*, 4-input Boolean function)
- Additional elements are for control or other functions: D-FF (store output), MUX (select output)



What will you learn?

- 7.1 Learn different latches – Active High & Active Low
- 7.2 Learn different Flip-Flop (FF) – SR-, D-, JK-, T-FFs
- 7.3 Learn the operation of a Master-Slave FF
- 7.4 Learn the operation of an Edge-Triggered FF
- 7.5 Learn the operation of Synchronous and Asynchronous Inputs

Two Classes of Logic Circuits


Combinational logic circuit

Output depends only on the inputs (As discussed in previous lectures)


Sequential logic circuit

Output depends on **present input** + **past history**


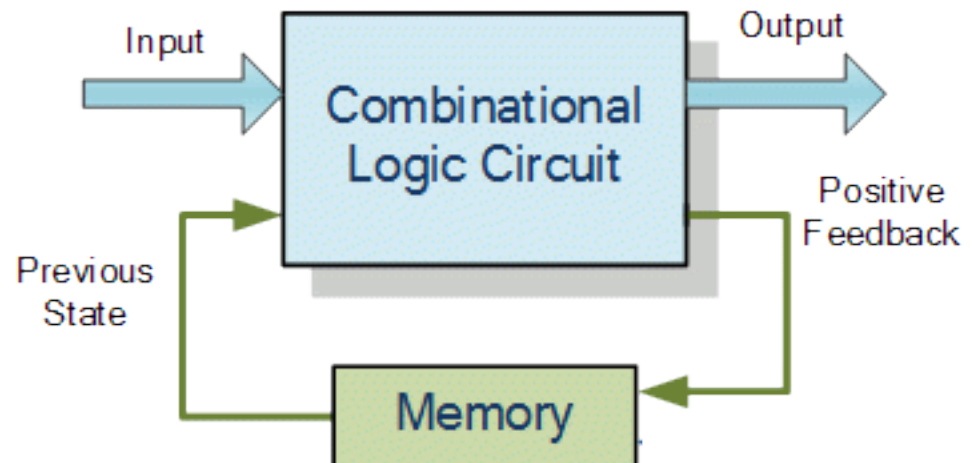
Memory circuit (to store previous STATE information) is required




Sequential Logic Circuit

 

 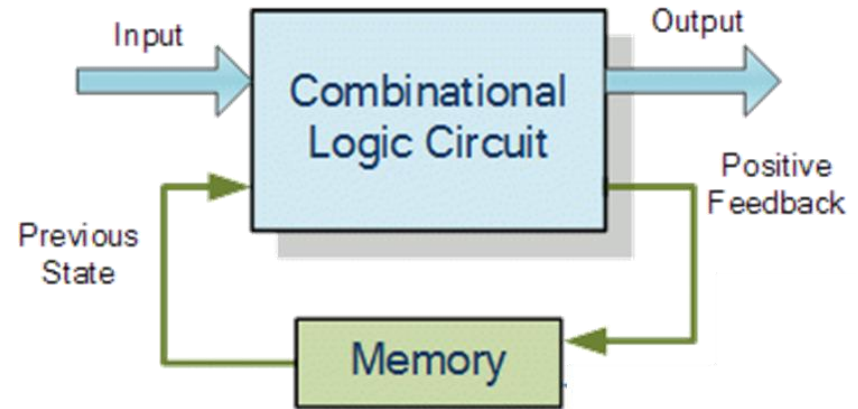Vending Machine
Food/ drink / MTR tickets



Digital counter / clock

 


Traffic light controller


Latches and **Flip-Flops** are building blocks of sequential logic circuit

 7.1 Latches

- Latch: A binary storage device, composed of logic gates with feedback
- The output state is controlled by its excitation input signals
- Two inputs: R stands for reset, S stands for set
- Two Outputs: Q stores the state of the latch (binary value)
- Bistable circuit: Two states




Active High Latch

 

$$Q = (R + P)'$$

$$P = (S + Q)'$$

 

- When S and R are 0,

$$Q = P' \quad \text{and} \quad P = Q' = \bar{Q}$$

The latch can store either

$$0 \quad (Q = 0, \bar{Q} = 1) \quad \text{or}$$

$$1 \quad (Q = 1, \bar{Q} = 0)$$

- When $S = 1, R = 0$

$$Q = 1, \bar{Q} = 0$$


- When $S = 0, R = 1$

$$Q = 0, \bar{Q} = 1$$

- When S and R are 1,

$$Q = 0, \bar{Q} = 0$$


Active High Latch

 

S	R	Next state of Q		State
		Q_{t+1}	Q'_{t+1}	
0	0	Q_t	Q'_t	Hold state
0	1	0	1	Reset state
1	0	1	0	Set state
1	1	0	0	Undefined state

t	1	2	3	4	5	6	7	8	9
S	1	0	0	0	0	1	1	1	0
R	0	0	1	0	0	0	1	0	0
Q	1	1	0	0	0	1	0	1	1
\bar{Q}	0	0	1	1	1	0	0	0	0
State	S	H	R	H	H	S	U	S	H

Active Low Latch

 


S'	R'	Q _{t+1}	Q' _{t+1}	State
1	1	Q _t	Q' _t	Hold state
1	0	0	1	Reset state
0	1	1	0	Set state
0	0	1	1	Undefined state


t	1	2	3	4	5	6	7	8	9
S̄	1	1	0	1	1	1	0	1	1
R̄	0	1	1	1	1	0	0	0	1
Q	0	0	1	1	1	0	1	0	0
Q̄	1	1	0	0	0	1	1	1	1
State	R	H	S	H	H	R	U	R	H

Summary

 Note that the input is active high for NOR gate implementation, whereas the input is active low for NAND gate implementation





Require a signal "1" to change its state

 

Require a signal "0" to change its state

Application – Key Debouncing Circuit

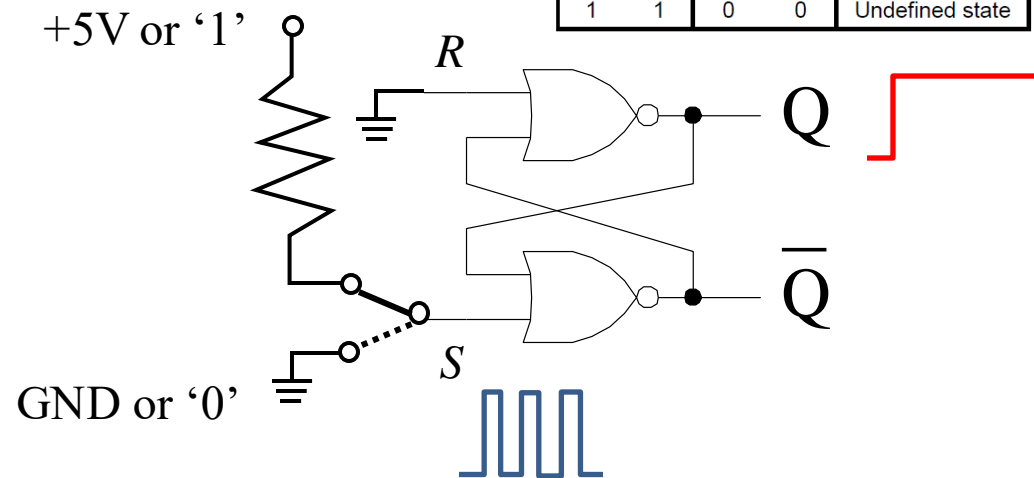 When pressing a key or switch, its internal spring may cause the contact point to vibrate for a short period of time, causing a series of “ON” and “OFF” state before settling down




Next state of Q

S	R	Q_{t+1}	Q'_{t+1}	State
0	0	Q_t	Q'_t	Hold state
0	1	0	1	Reset state
1	0	1	0	Set state
1	1	0	0	Undefined state

Drawback - Noise

If inputs S , R are unstable (or noise), output produces an unstable short pulse

Solution: Gated Latch!

 


E	S	R	Q_{t+1}	$\overline{Q_{t+1}}$	State
0	x	x	Q_t	$\overline{Q_t}$	Hold
1	0	0	Q_t	$\overline{Q_t}$	Hold
1	0	1	0	1	Reset
1	1	0	1	0	Set
1	1	1	0	0	Undefined

Drawback – Undefined State

The latches will enter **undefined state** for some inputs (e.g. $R = S = 1$)

Solution: **D Latch!**

 

E	D	Q_{t+1}	$\overline{Q_{t+1}}$	State
0	x	Q_t	$\overline{Q_t}$	Hold
1	1	1	0	Set
1	0	0	1	Reset

Remember in this way:


The value of D is transferred to the Q output

7.2 Flip-Flops



- Flip-Flop: A **clocked** binary storage device that the change of output state is controlled by the clock signal (synchronized)
- We will discuss the following four types of FF
 - Set-Reset FF (SR FF)
 - Data/Delay FF (D FF)
 - Jack Kilby FF (JK FF)
 - Toggle FF (T FF)

Set-Reset FF

 A clocked signal is connected to the Enable input of a gated latch




C	S	R	Q_{t+1}	\overline{Q}_{t+1}	State
0	x	x	Q_t	\overline{Q}_t	Hold
1	0	0	Q_t	\overline{Q}_t	Hold
1	0	1	0	1	Reset
1	1	0	1	0	Set
1	1	1	0	0	Undefined

  


Logic
symbol

Data/Delay FF

 A clocked signal is connected to the Enable input of a D latch





C	D	Q_{t+1}	$\overline{Q_{t+1}}$	State
0	x	Q_t	$\overline{Q_t}$	Hold
1	1	1	0	Set
1	0	0	1	Reset

 

Logic
symbol

Jack-Kilby FF

  Refined SR FF whereby the undetermined state of SR FF is defined; ***J*** is set and ***K*** is reset



Logic
symbol



C	J	K	Q_{t+1}	$\overline{Q_{t+1}}$	State
0	x	x	Q_t	$\overline{Q_t}$	Hold
1	0	0	Q_t	$\overline{Q_t}$	Hold
1	0	1	0	1	Reset
1	1	0	1	0	Set
1	1	1	$\overline{Q_t}$	Q_t	Toggle



C	J	K	Q_t	$\overline{Q_t}$	Q_{t+1}	$\overline{Q_{t+1}}$
1	1	1	0	1	1	0
1	1	1	1	0	0	1

Toggle FF

  Output state changes for each clock pulse when ***T*** is in its active state



Logic
symbol

C	T	Q_{t+1}	\bar{Q}_{t+1}	State
0	x	Q_t	\bar{Q}_t	Hold
1	0	Q_t	\bar{Q}_t	Hold
1	1	\bar{Q}_t	Q_t	Toggle



C	T	Q_t	\bar{Q}_t	Q_{t+1}	\bar{Q}_{t+1}
1	1	0	1	1	0
1	1	1	0	0	1

Summary

 
 
 
 


Table Given (Test and Exam)



S	R	Q_{t+1}	$\overline{Q_{t+1}}$	State
0	0	Q_t	$\overline{Q_t}$	Hold
0	1	0	1	Reset
1	0	1	0	Set
1	1	1	1	Undefined

J	K	Q_{t+1}	$\overline{Q_{t+1}}$	State
0	0	Q_t	$\overline{Q_t}$	Hold
0	1	0	1	Reset
1	0	1	0	Set
1	1	$\overline{Q_t}$	Q_t	Toggle



D	Q_{t+1}	$\overline{Q_{t+1}}$	State
1	1	0	Set
0	0	1	Reset

T	Q_{t+1}	$\overline{Q_{t+1}}$	State
0	Q_t	$\overline{Q_t}$	Hold
1	$\overline{Q_t}$	Q_t	Toggle

Exercise

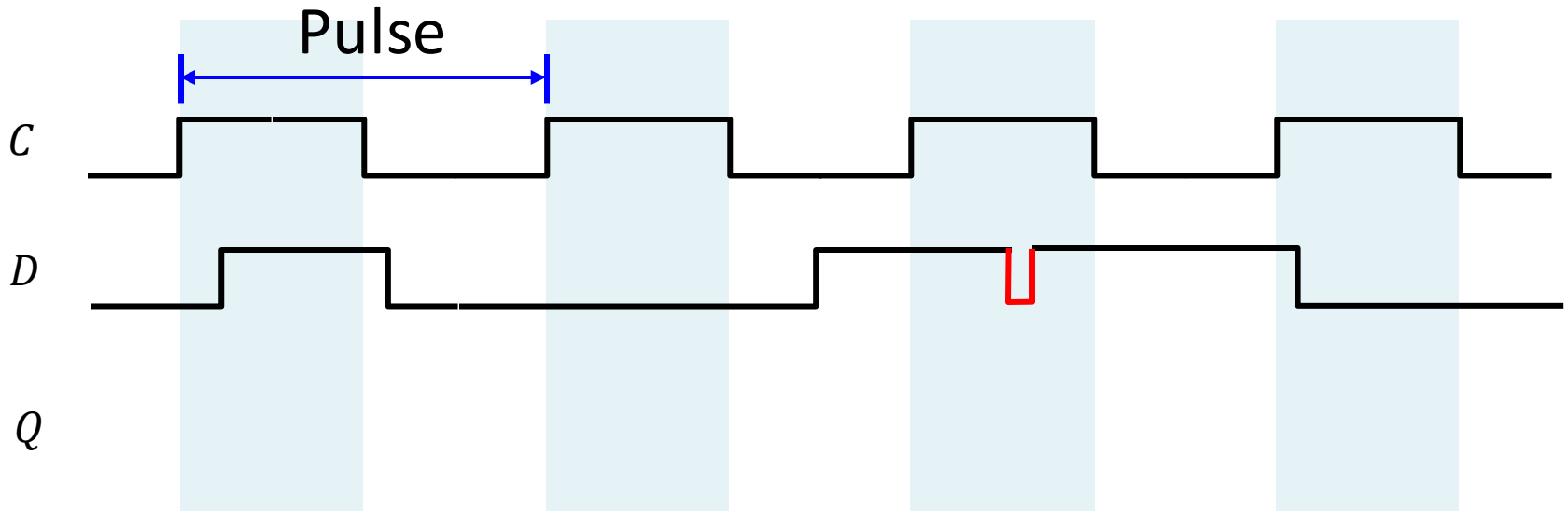
 


Exercise

 
 


  7.3 Master-Slave Flip-Flop

- A combination of two flip-flops together in a series configuration
- At any time, only one flip-flop is enabled




How Does It Work?

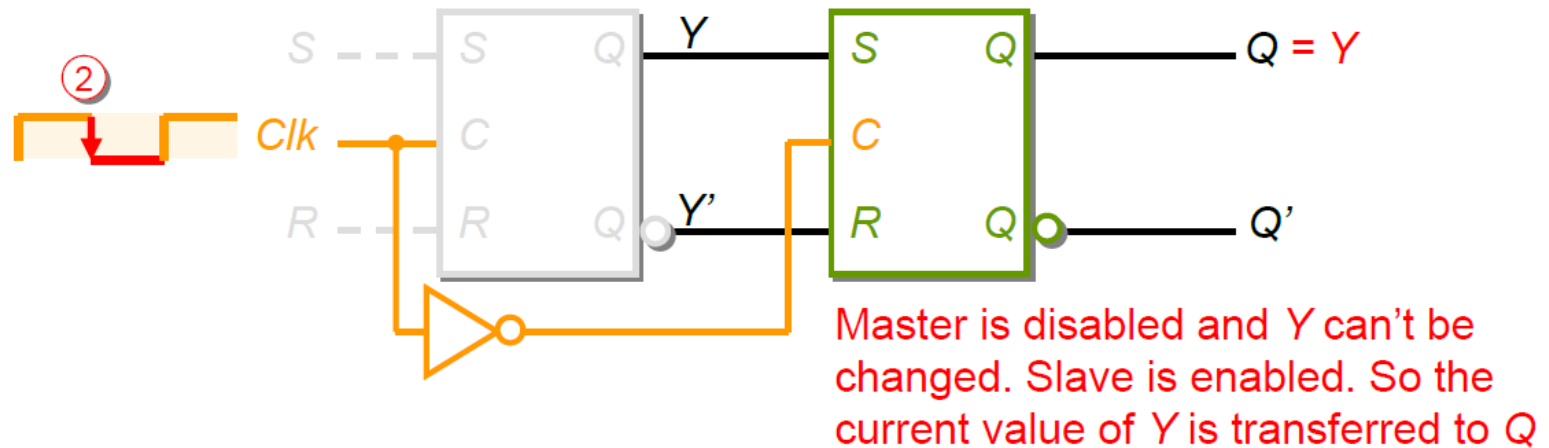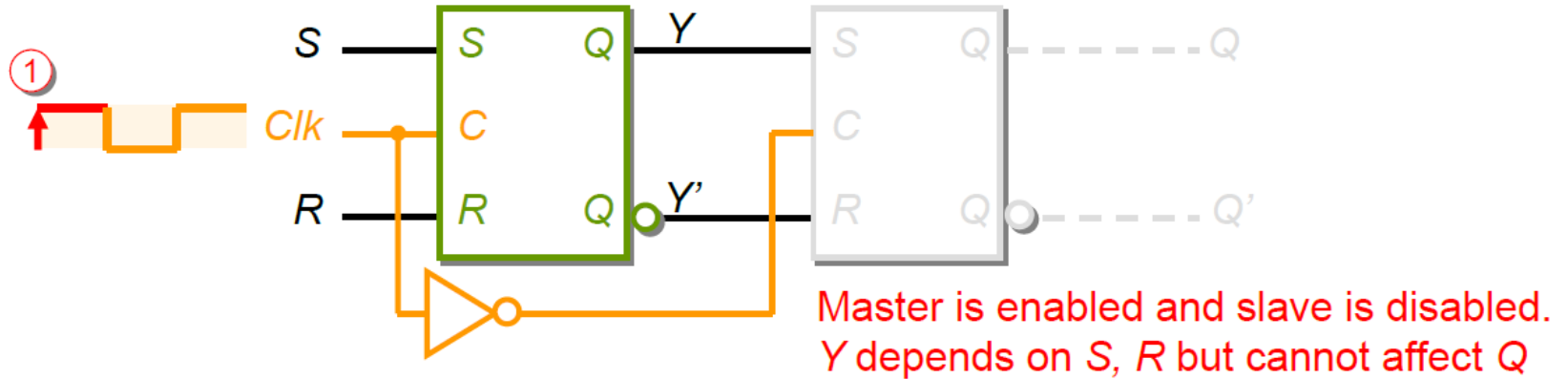

Timing Diagram

Initial inputs: S and R are LOW

Initial state of Y and Q unknown

 

- ① Clk switches to 1; master FF enabled; $S = 1, R = 0, \therefore Y = 1$
- ② Clk switches to 0; slave FF enabled; $Y = 1, \therefore Q = 1$
- ③ Clk switches to 1; master FF enabled; $S = 0, R = 0$, HOLD
- ④ $S = 0, R = 1, \therefore Y = 0$ ⑤ Clk switches to 0; slave FF enabled; $Y = 0, \therefore Q = 0$
- ⑥ Clk is 0; master FF disabled; no change on Y .
- ⑦ Clk switches to 1; master FF enabled; $S = 1, R = 0, \therefore Y = 1$
- ⑧ Clk switches to 0; slave FF enabled; $Y = 1, \therefore Q = 1$

Characteristics





- Y is updated when Clk goes to and remains at 1
- Q is updated when Clk goes to 0 and remains unchanged until the next pulse



Therefore,


- For each clock pulse, Q only changes state at most **once**
- State change only occurs **during the transition** of Clk **from 1 to 0**

Master-Slave D Flip-Flop

 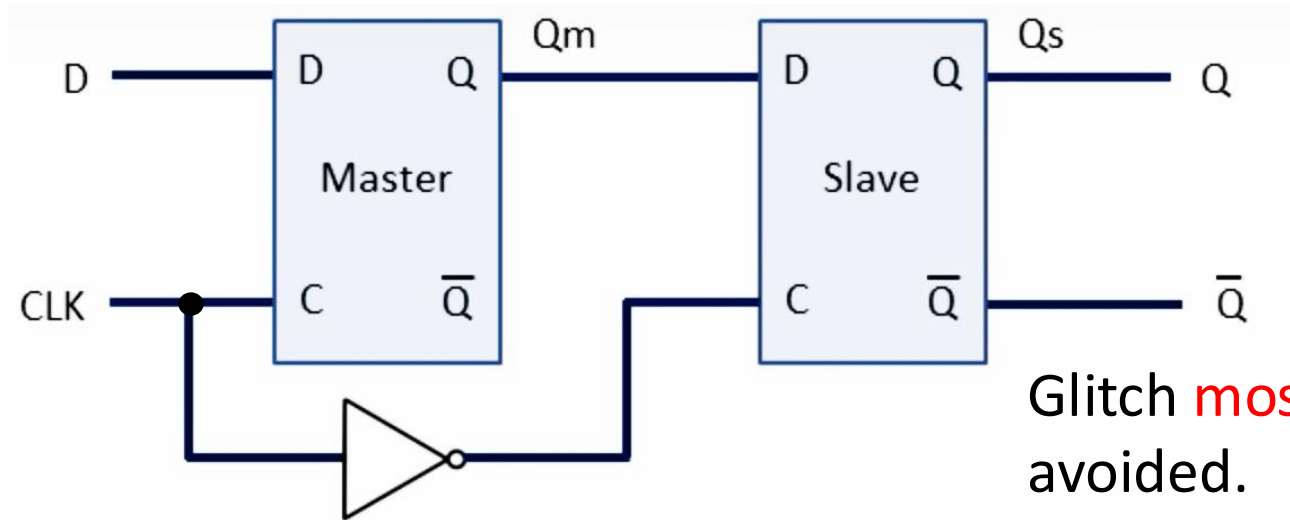


Master-Slave D Flip-Flop

  



Inputs		Outputs		
<i>D</i>	<i>Clk</i>	Next <i>Q</i>	Next <i>Q'</i>	Meaning
x	0	<i>Q</i>	<i>Q'</i>	Hold
x		<i>D</i>	<i>D'</i>	Set / Reset

Master-Slave JK Flip-Flop

 

- Two JK FFs connected in series
- Outputs are fed back to Master's inputs $Q \rightarrow K$ & $\bar{Q} \rightarrow J$
- J is SET and K is RESET
- Y is connected to SET of slave FF

Master-Slave JK Flip-Flop

  

$$\textcircled{1} J = 1, K = 0,$$



$$S_m = \bar{Q} = 1, R_m = 0 \text{ (SET)}$$

$$\therefore Y = 1$$

$$\textcircled{2} Y(S_s) = 1, \bar{Y}(R_s) = 0 \text{ (SET)}$$

$$\therefore Q = 1$$



Master-Slave JK Flip-Flop

  

③ $J = 0, K = 0$ (HOLD)
 $\therefore Y = 1$

④ $Y(S_s) = 1, \bar{Y}(R_s) = 0$ (SET)
 $\therefore Q = 1$



Master-Slave JK Flip-Flop

  

⑤ $J = 0, K = 1$ (RESET)
 $\therefore Y = 0$

⑥ $Y(S_s) = 0, \bar{Y}(R_s) = 1$
 (RESET)
 $\therefore Q = 0$

Master-Slave JK Flip-Flop

  

⑦ $J = 1, K = 1$


$S_m = \bar{Q} = 1, R_m = 0$ (SET)

$\therefore Y = 1$ at the point $C \rightarrow 0$

⑧ $Y(S_s) = 1, \bar{Y}(R_s) = 0$
(SET)


$\therefore Q = 1$

Master-Slave JK Flip-Flop

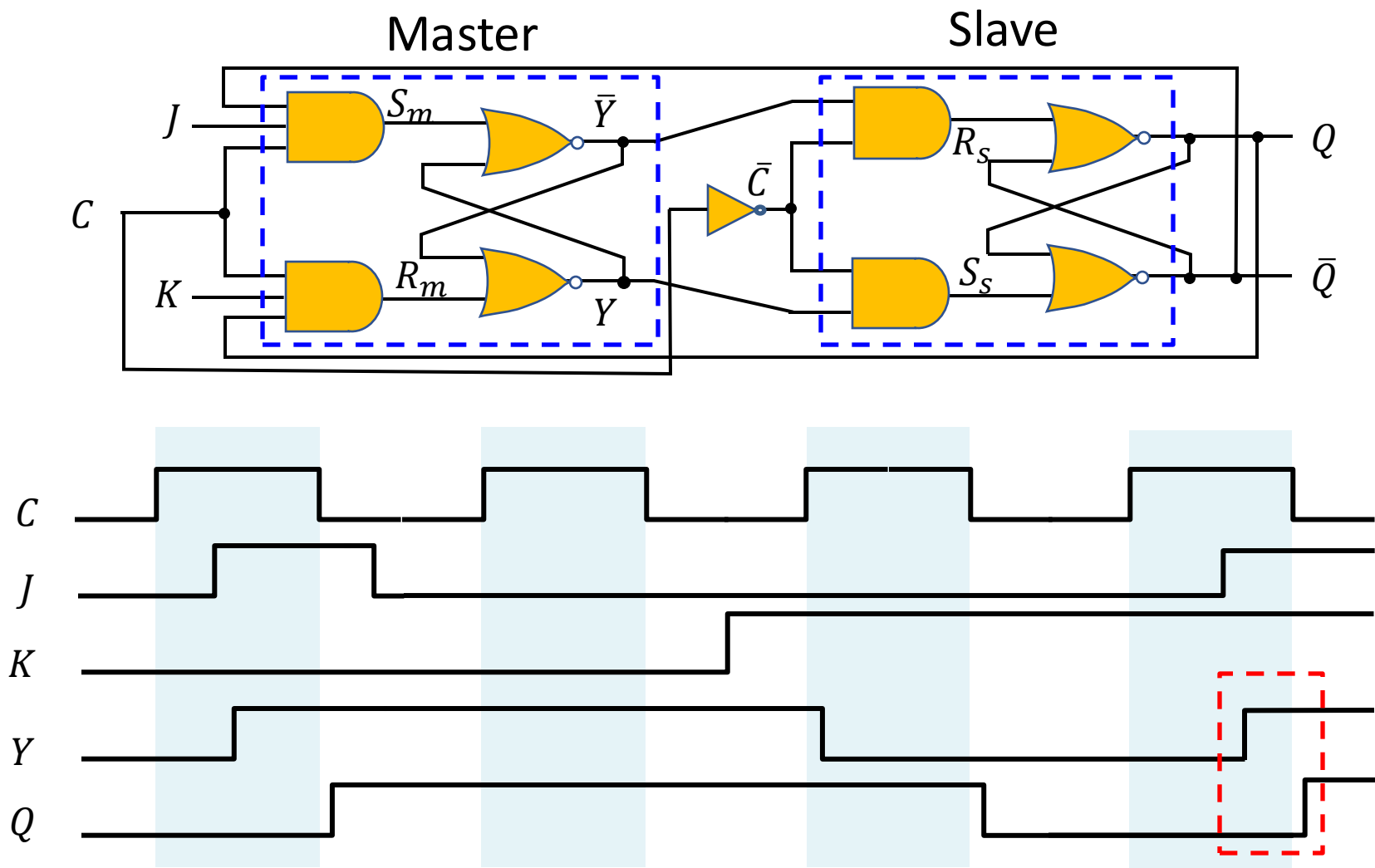



 

No racing!

Master-Slave JK Flip-Flop



Symbol

Inputs			Outputs		
<i>J</i>	<i>K</i>	<i>Clk</i>	Next <i>Q</i>	Next <i>Q'</i>	Meaning
x	x	0	<i>Q</i>	<i>Q'</i>	Hold
0	0		<i>Q</i>	<i>Q'</i>	Hold
0	1		0	1	Reset
1	0		1	0	Set
1	1		<i>Q'</i>	<i>Q</i>	Toggle

The same behaviors as master-slave *SR* flip-flop

Eliminated the undefined state

Problem

- For the presented MSFF, master is enabled during the period when the clock pulse is 1 (Level triggered)
- Undesired behavior produced when inputs values of S and R (or J , K , D , T) change at that period, especially just before the clock pulse changes to 0
- Undesired output due to glitch could not be fully avoided
- Better solution: Edge-triggered FFs

7.4 Edge-triggered Flip-Flop

- Use one of the edges of the clock signal to read the input values
 - either positive or negative transition
 - **triggering edge**
- The response to the triggering edge at the output of the flip-flop is almost immediate
- The flip-flops remains **unresponsive** to the input change until the next triggering edge

Triggering edge

- Triggered only during a signal transition from 0 to 1 (or from 1 to 0) on the **clock**

- Positive (rising, leading) edge-triggering: 0-to-1 transition




- Negative (falling, trailing) edge-triggering: 1-to-0 transition



- Additional circuit is included to ensure it will only response to the input at the transition edge of the clock pulse


Positive-Edge-Triggered D-FF

 

S	R	Q_{t+1}	$\overline{Q_{t+1}}$
1	1	Q_t	$\overline{Q_t}$
1	0	0	1
0	1	1	0
0	0	1	1

Inputs		Outputs		
D	Clk	Next Q	Next Q'	State
x	$\downarrow, 0, 1$	Q	Q'	Hold
x	\uparrow	D	D'	Set / Reset


When $C = 0$

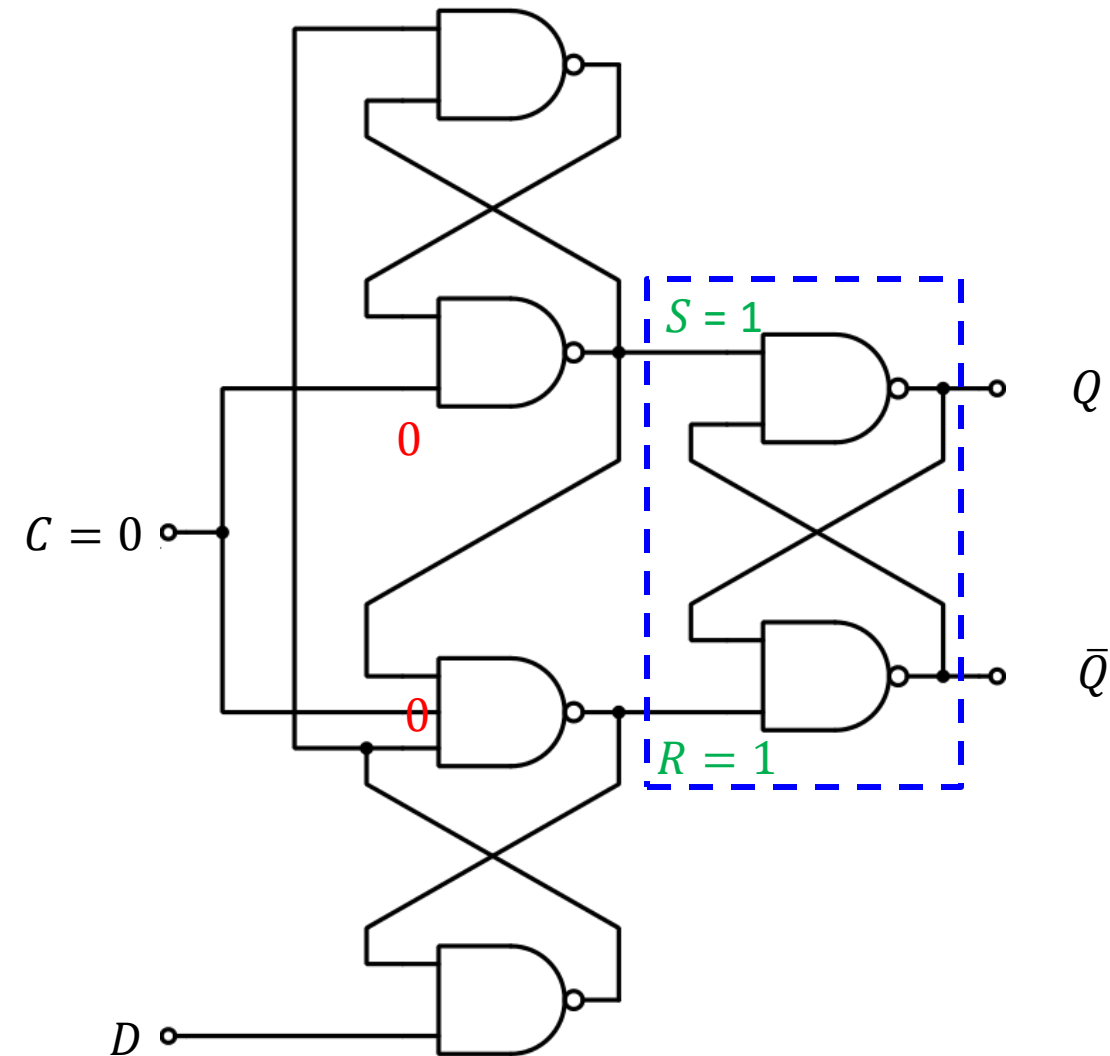

S	R	Q_{t+1}	$\overline{Q_{t+1}}$
1	1	Q_t	$\overline{Q_t}$
1	0	0	1
0	1	1	0
0	0	1	1

HOLD!

When $C = 0 \rightarrow 1$ & $D = 0$

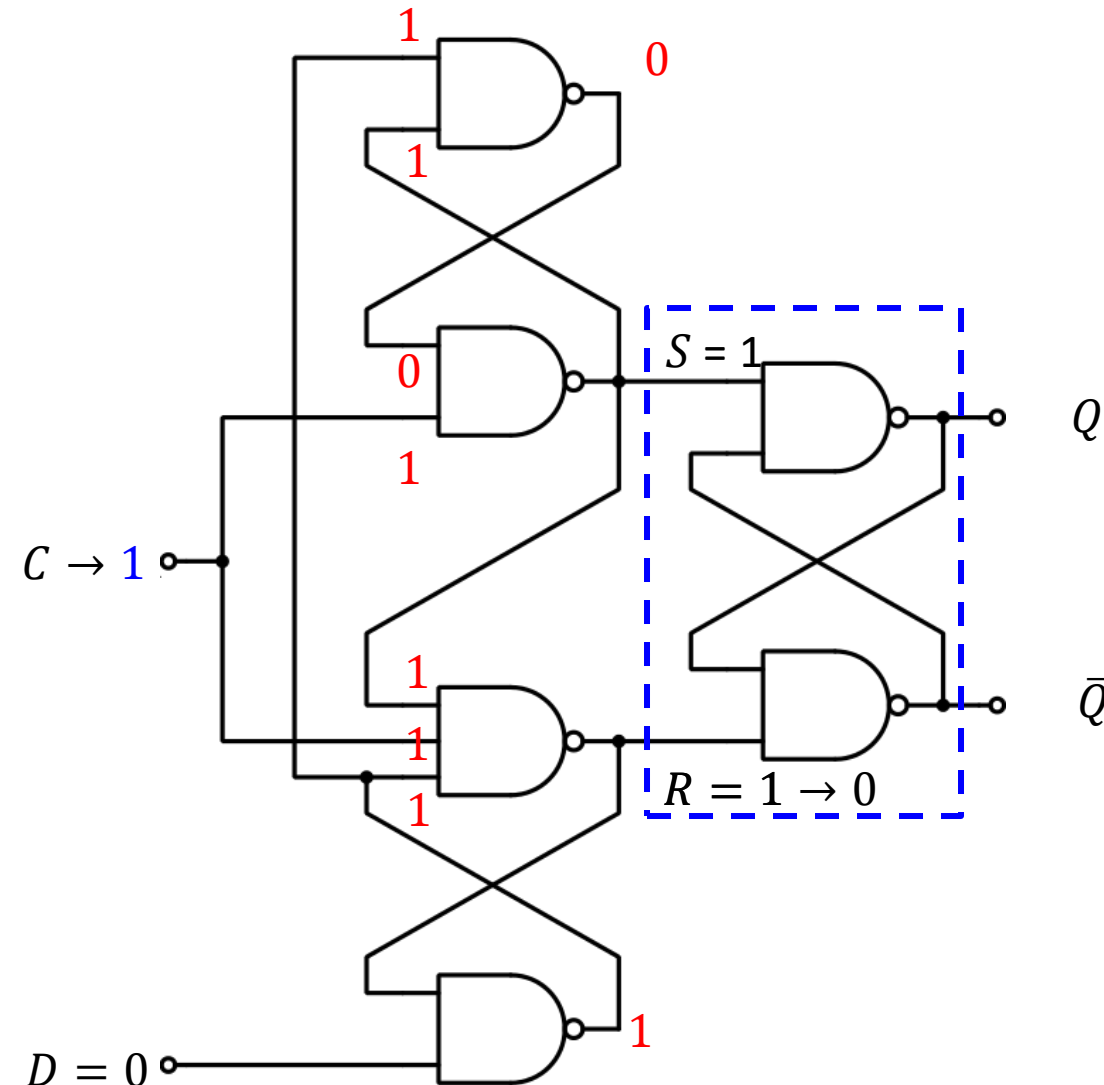


S	R	Q_{t+1}	$\overline{Q_{t+1}}$
1	1	Q_t	$\overline{Q_t}$
1	0	0	1
0	1	1	0
0	0	1	1

HOLD \rightarrow RESET

When $C = 0 \rightarrow 1$ & $D = 0$, $Q \rightarrow 0$

When $C = 0 \rightarrow 1$ & $D = 1$

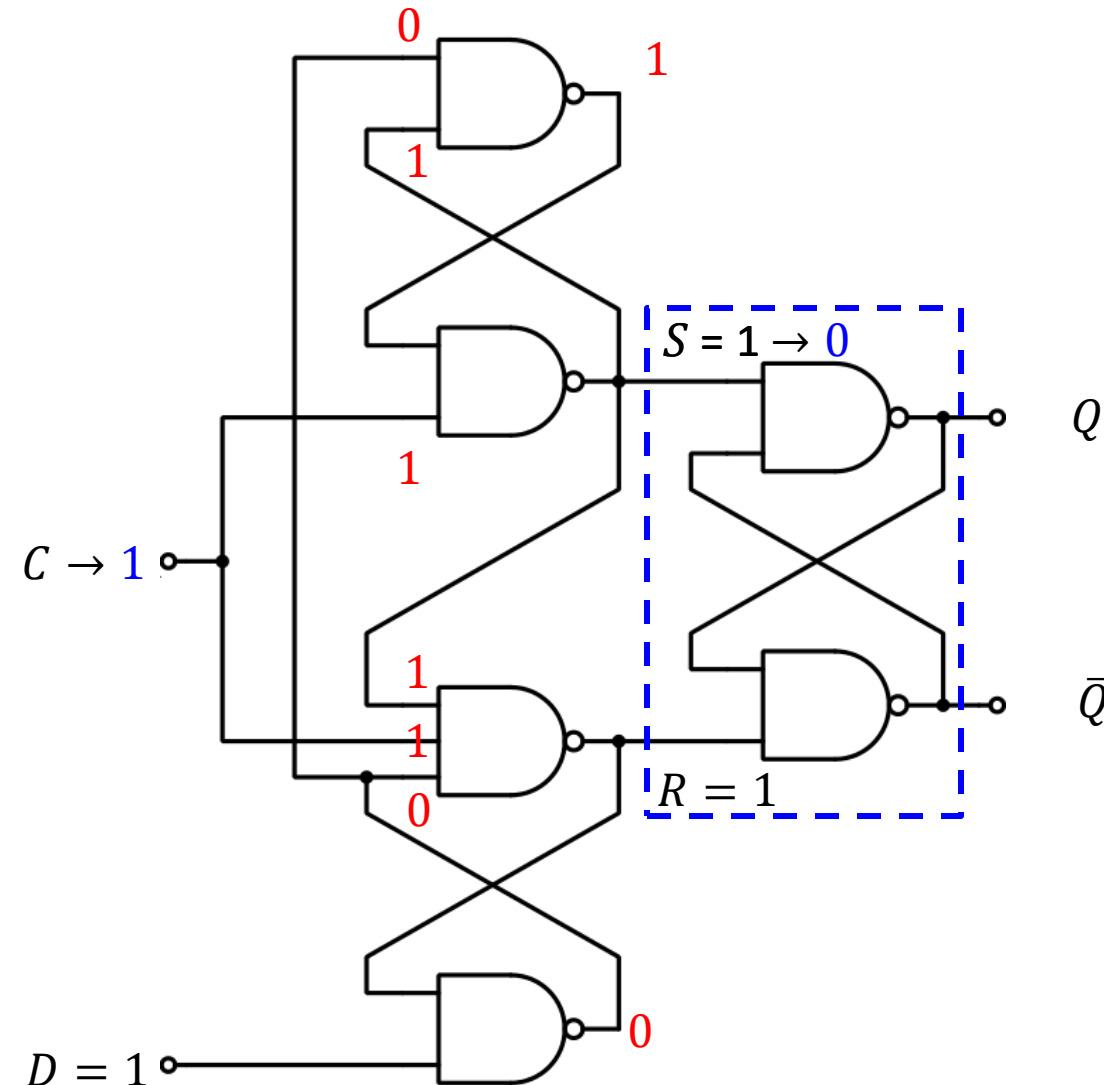


S	R	Q_{t+1}	$\overline{Q_{t+1}}$
1	1	Q_t	$\overline{Q_t}$
1	0	0	1
0	1	1	0
0	0	1	1

HOLD \rightarrow SET

When $C = 0 \rightarrow 1$ & $D = 1$, $Q \rightarrow 1$

When $C = 1$ & $D = 0 \rightarrow 1$

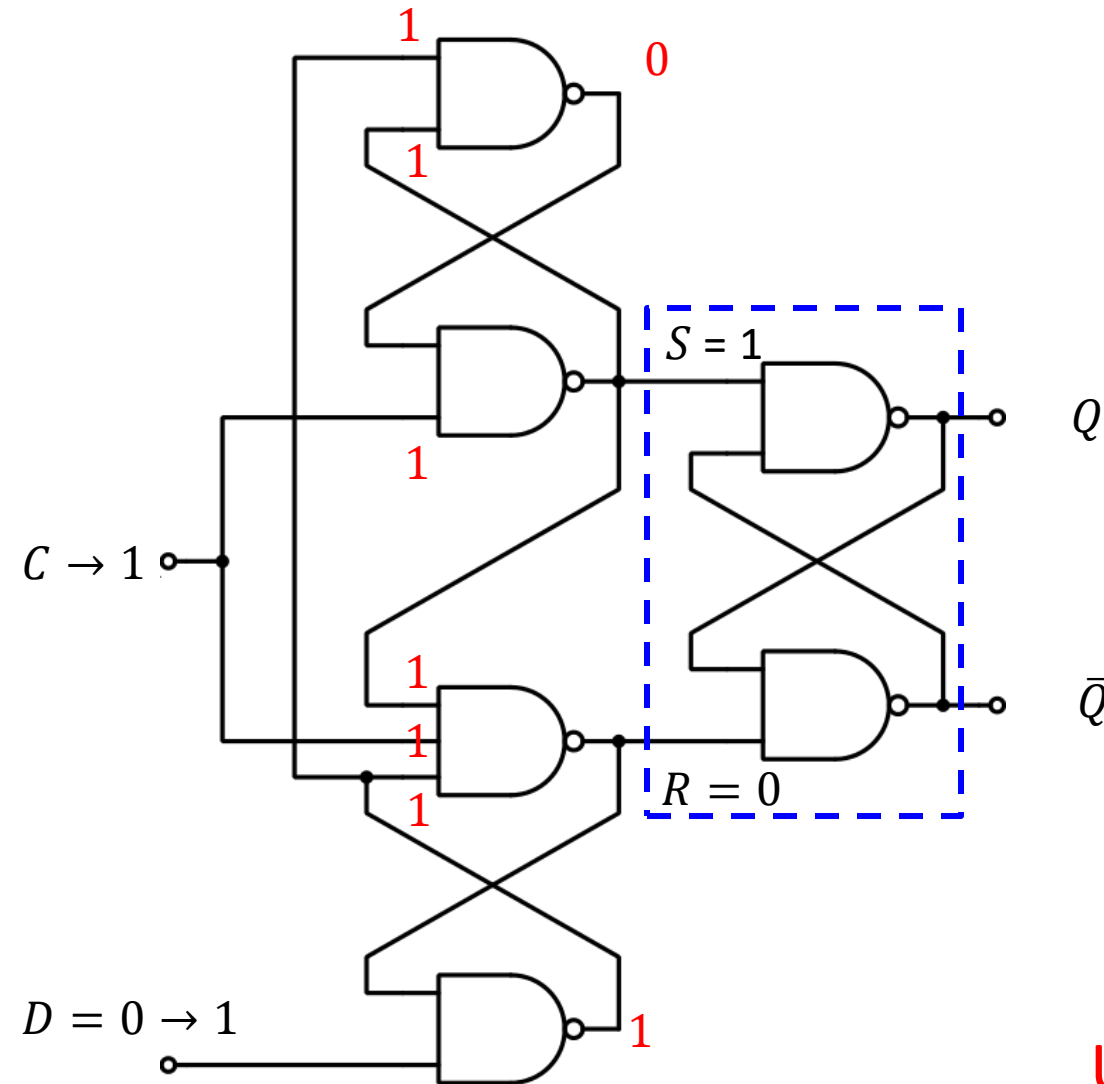


S	R	Q_{t+1}	$\overline{Q_{t+1}}$
1	1	Q_t	$\overline{Q_t}$
1	0	0	1
0	1	1	0
0	0	1	1

RESET \rightarrow RESET

When $C = 1$ & $D = 0$
 $\rightarrow 1, Q = 0$

Unresponsive!

When $C = 1$ & $D = 1 \rightarrow 0$

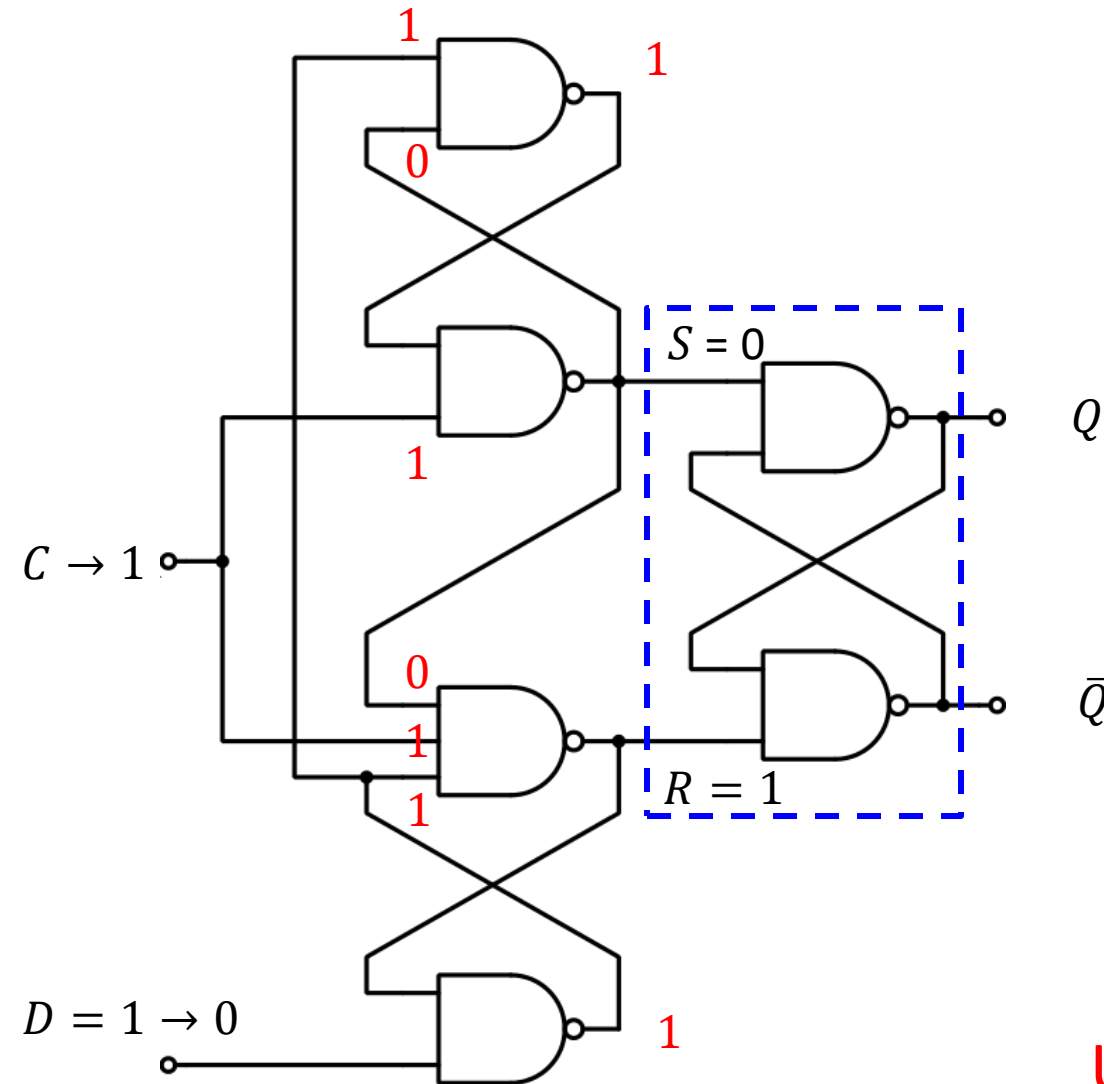



S	R	Q_{t+1}	$\overline{Q_{t+1}}$
1	1	Q_t	$\overline{Q_t}$
1	0	0	1
0	1	1	0
0	0	1	1

SET \rightarrow SET

When $C = 1$ & $D = 1$
 $\rightarrow 0$, $Q = 1$

Unresponsive!

Positive-Edge-Triggered D-FF

 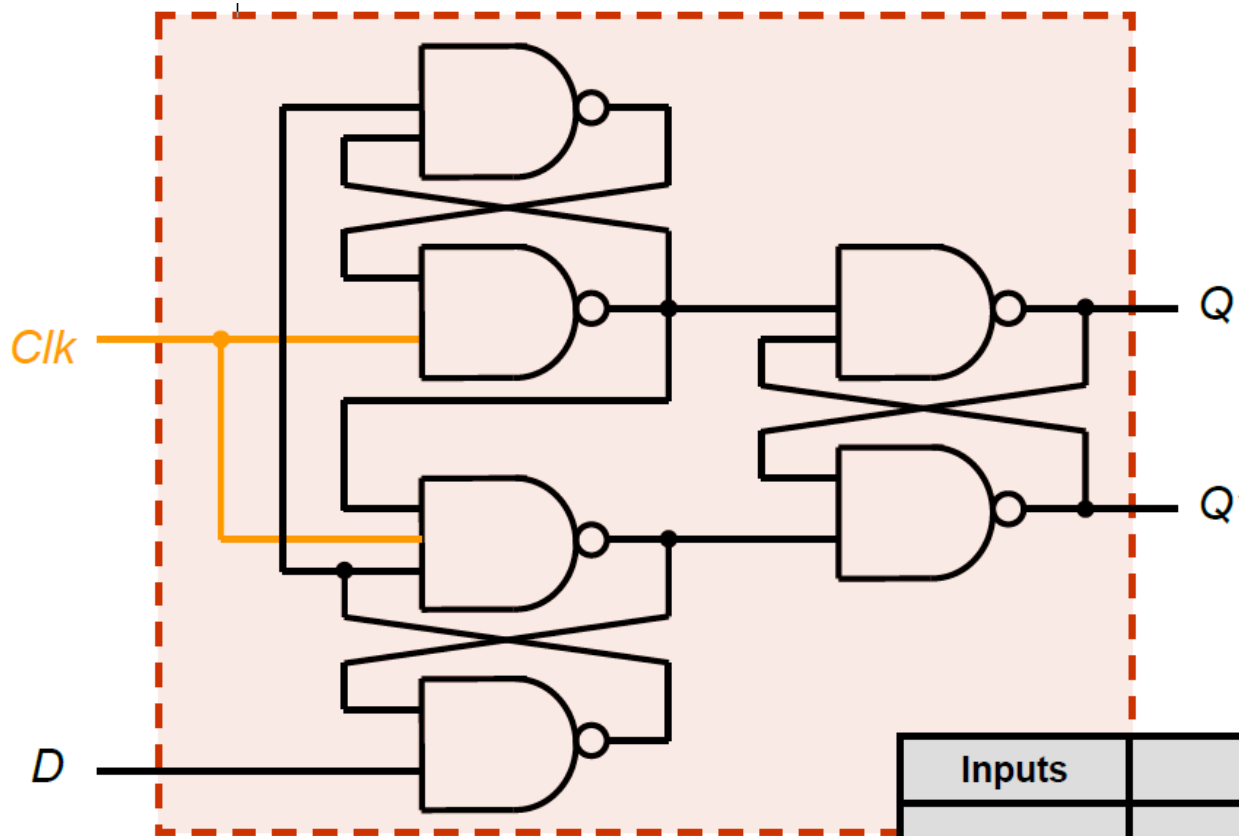


Remember the symbol only!

Note: ↓ (negative edge 1 to 0); '0' (value 0); '1' (value 1);
↑ (positive edge 0 to 1)


Inputs		Outputs		
D	Clk	Next Q	Next Q'	State
x	↓, 0, 1	Q	Q'	Hold
x	↑	D	D'	Set / Reset

Timing Diagram

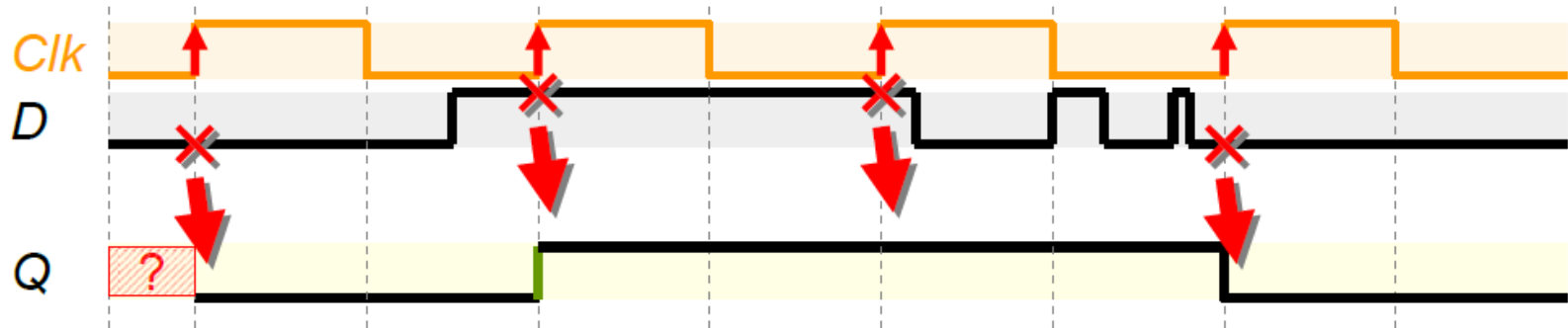Timing Diagram of PET D FF (if no output delay)




Timing Diagram of PET D FF

 

Thought


- How to build a negative-edge triggered D-FF?

Negative-Edge-Triggered D-FF

 


S	R	Q_{t+1}	$\overline{Q_{t+1}}$
1	1	Q_t	$\overline{Q_t}$
1	0	0	1
0	1	1	0
0	0	1	1

Negative-Edge-Triggered D-FF

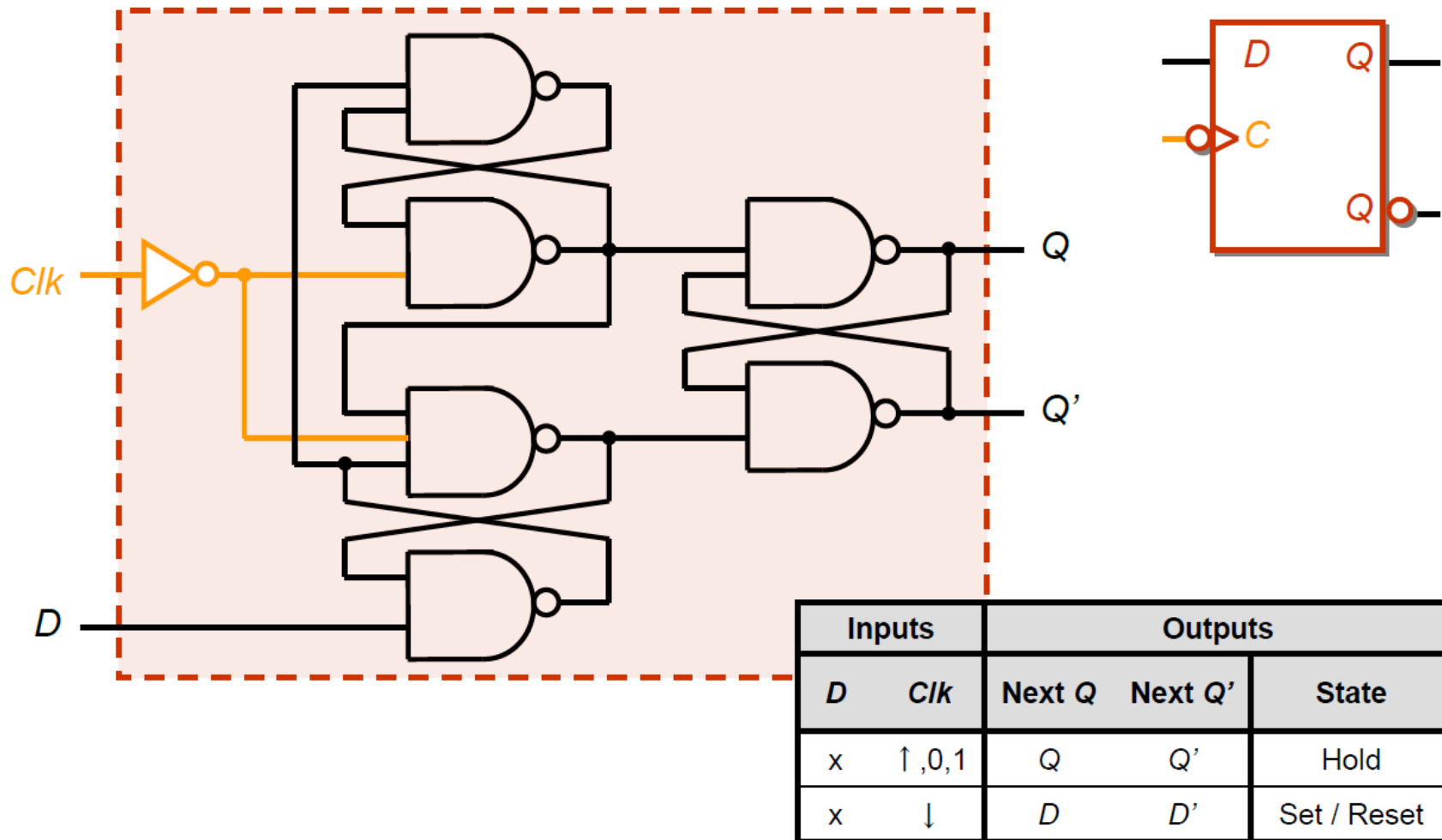


Timing Diagram

 
Timing Diagram of NET D FF (if no output delay)



Timing Diagram of NET D FF

 


Edge-Triggered JK-FF

 

$$D = Q\bar{K} + J\bar{Q}$$

J	K	D	STATE
0	0	Q	HOLD
0	1	0	RESET
1	0	$Q + \bar{Q} = 1$	SET
1	1	\bar{Q}	TOGGLE


Edge-Triggered JK-FF

 

$$D = Q\bar{K} + J\bar{Q}$$

Inputs			Outputs		
J	K	Clk	Next Q	Next Q'	State
x	x	$\downarrow, 0, 1$	Q	Q'	Hold
0	0	\uparrow	Q	Q'	Hold
0	1	\uparrow	0	1	Reset
1	0	\uparrow	1	0	Set
1	1	\uparrow	Q'	Q	Toggle

Edge-Triggered T-FF

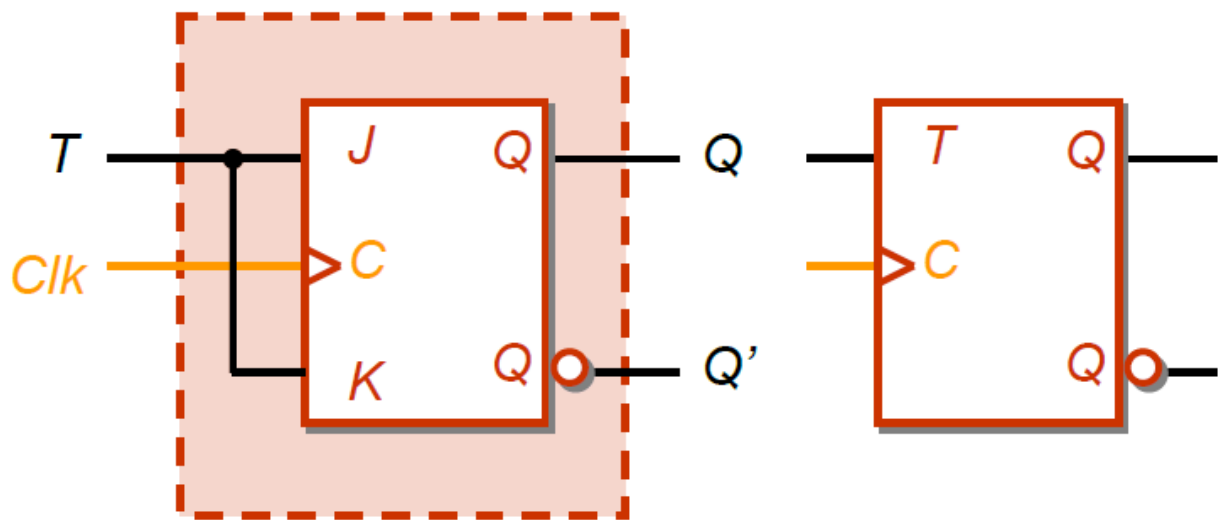


T	J	K	Q_{t+1}	STATE
0	0	0	Q_t	HOLD
1	1	1	$\overline{Q_t}$	TOGGLE


Inputs		Outputs		
T	Clk	Next Q	Next Q'	State
x	$\downarrow, 0, 1$	Q	Q'	Hold
0	\uparrow	Q	Q'	Hold
1	\uparrow	Q'	Q	Toggle

Timing Diagram

 Timing Diagram of PET JK FF (if no output delay)




 Timing Diagram of PET T FF (if no output delay)




Logic Symbols


Positive-Edge

 


RS flip-flop

 

D flip-flop

 


JK flip-flop

 


T flip-flop


Negative-Edge

 


RS flip-flop

 

D flip-flop

 


JK flip-flop

 

T flip-flop

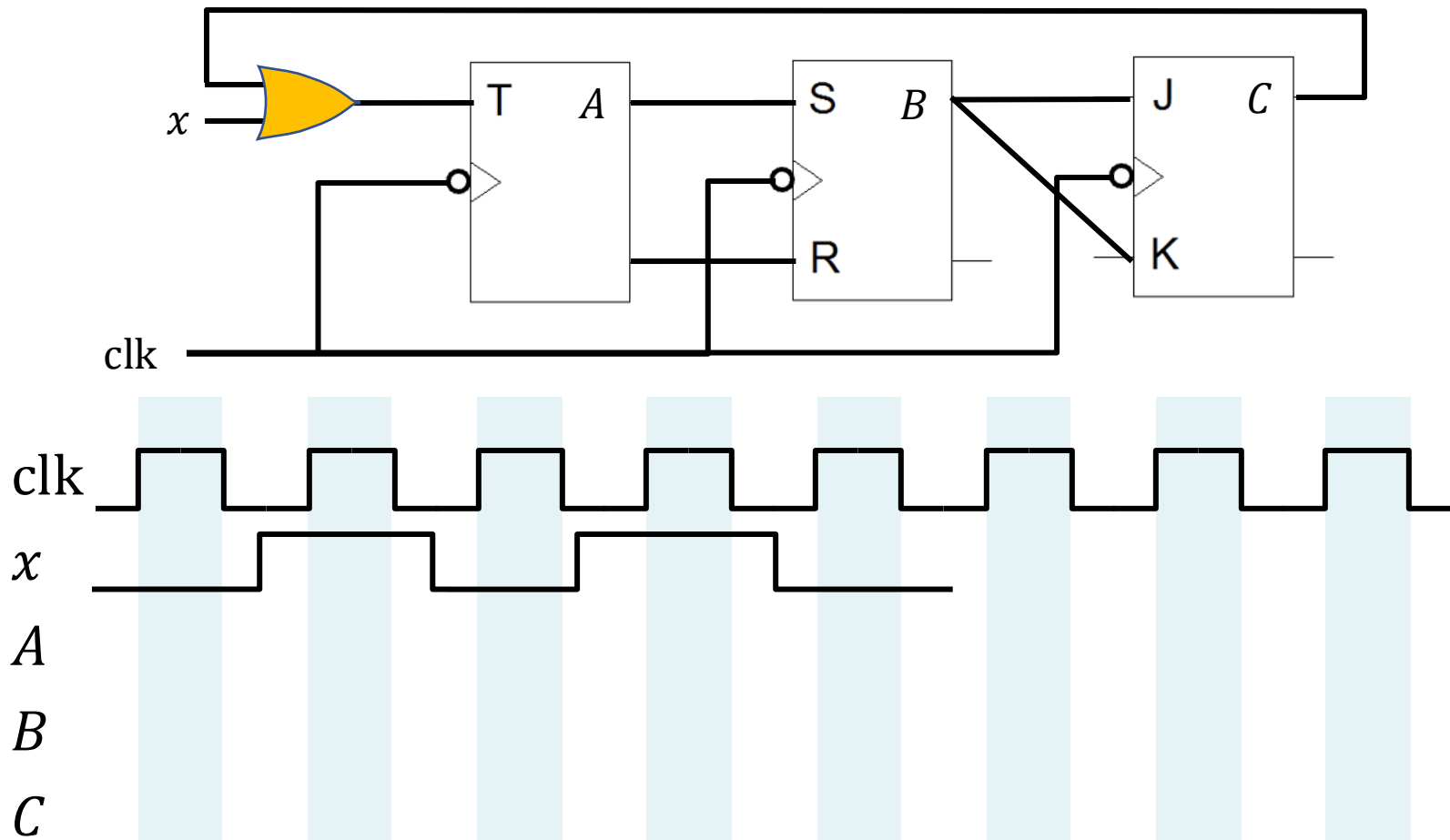Exercise

Assume all FFs are initially 0 and no propagation delay, work out the timing diagram of the output of each FF (A , B , C).



7.5 Synchronous & Asynchronous Inputs

- Inputs of flip-flops are categorized into two types
- **Synchronous:** Only affect the output in conjunction with a clock pulse (all inputs to FFs presented so far)
- **Asynchronous:** Inputs that can affect the output state independent of the clock pulse

Asynchronous Inputs

- The output will respond to the sync. inputs only if all async. inputs are inactive
- Particularly useful for bringing an FF into a desired initial state before normal clocked operation
- **Preset** (denoted by *PRE*) and **Clear** (denoted *CLR*) - Used to forcibly set and reset the state of flip-flop


Example

The corresponding function table

Inputs				Outputs		
PRE'	CLR'	Clk	D	Next Q	Next Q'	Meaning
0	1	x	x	1	0	Preset
1	0	x	x	0	1	Clear
0	0	x	x	1*	1*	Undefined
1	1	\uparrow	x	D	D'	Set / Reset
1	1	$\downarrow, 0, 1$	x	Q	Q'	Hold

*Unpredictable behavior will result if both PRE' and CLR' set to 0 simultaneously

} The same behaviors as D flip-flops

 


The logic symbol

Example

The function table of an negative-edge-triggered JK flip-flop with asynchronous preset and clear inputs

Inputs					Outputs		
PRE'	CLR'	Clk	J	K	Next Q	Next Q'	Meaning
L	H	x	x	x	H	L	Preset
H	L	x	x	x	L	H	Clear
L	L	x	x	x	H*	H*	Undefined
H	H	\downarrow	L	L	Q	Q'	Hold
H	H	\downarrow	H	L	H	L	Set
H	H	\downarrow	L	H	L	H	Reset
H	H	\downarrow	H	H	Q'	Q	Toggle
H	H	$\uparrow, 0, 1$	x	x	Q	Q'	Hold


The logic symbol

 

The same behaviors as JK flip-flops


Timing Diagram

 Timing Diagram of PET T FF with asynchronous preset and clear inputs
(if no output delay)



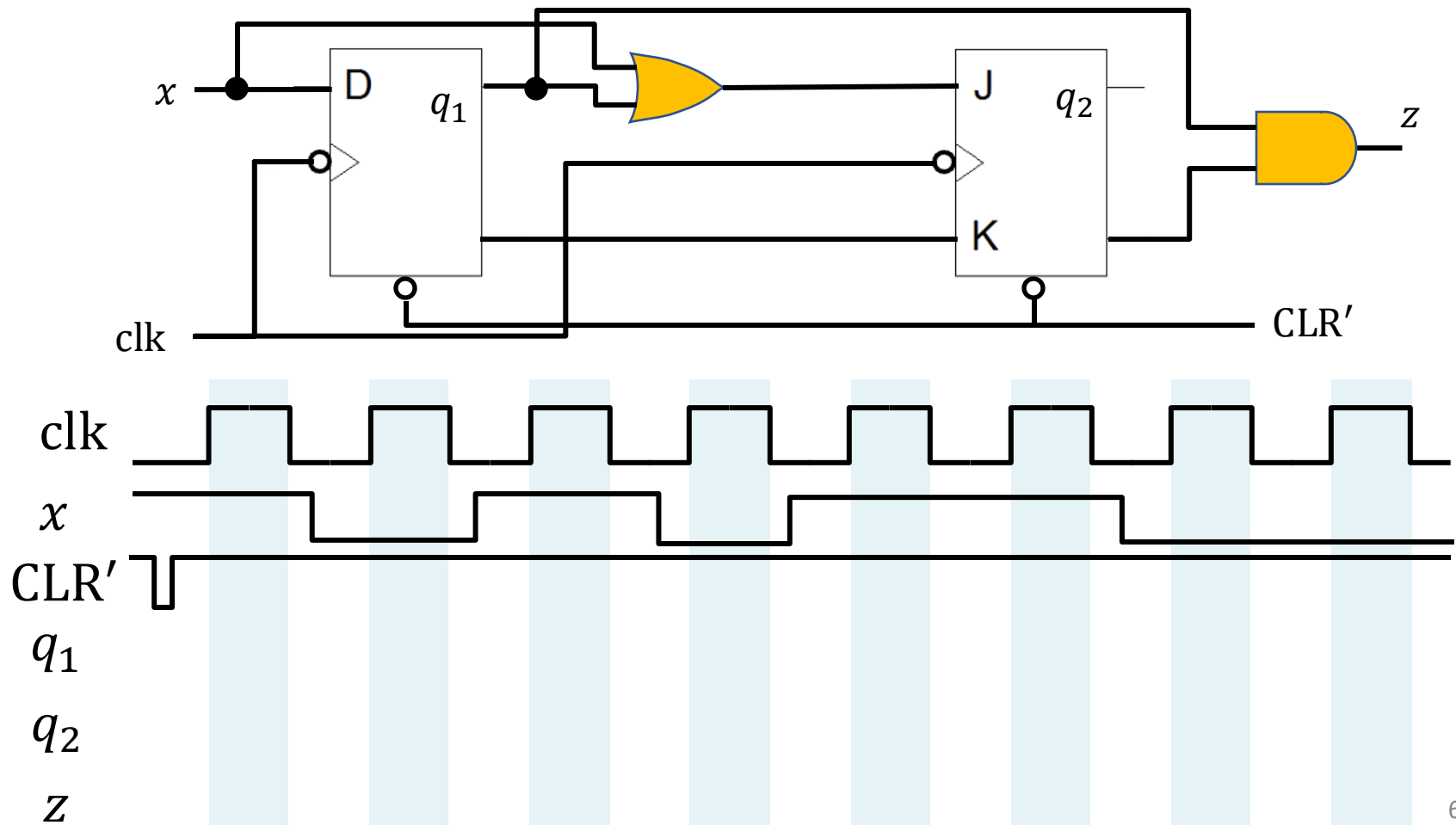
Exercise

Work out the timing diagram for the state of each flip-flop and the output (q_1 , q_2 , z). (Ignore delay)



 Exercise

Work out the timing diagram for the state of each flip-flop and the output (q_1 , q_2 , z). (Ignore delay)



Summary

- Latches & Flip-Flops: Basic building block (Memory) of Sequential system
- Flip-Flop (FF): One FF can store 1-bit data
 - Types: SR, D, JK, T, Master-Slave
 - Control inputs to change, set, reset or hold the value of Q
 - Triggering: Pulse vs Edge
 - Asynchronous inputs