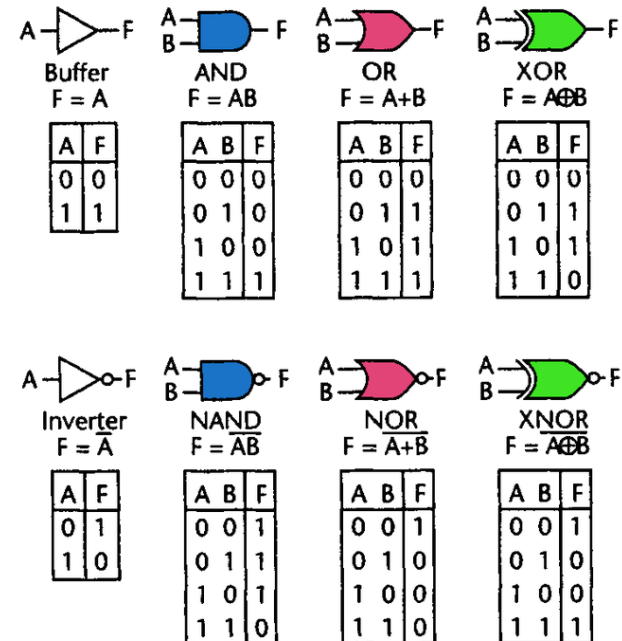



# EE2000 Logic Circuit Design

---

## Lecture 1 – Logic Function and Boolean Algebra



# Exercise

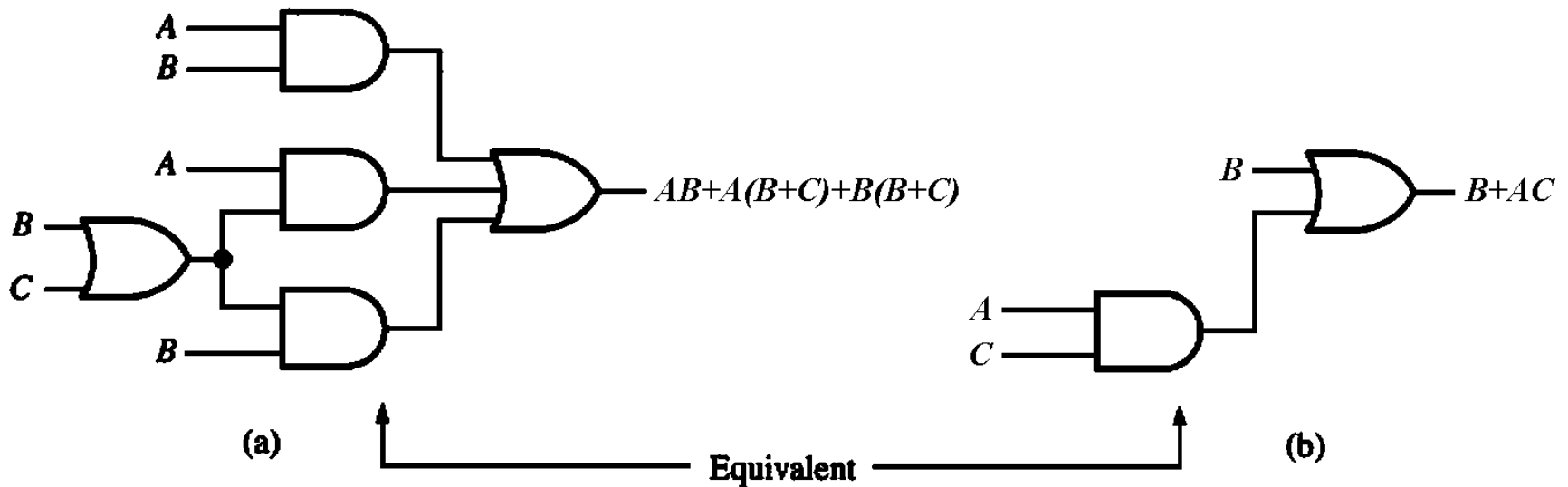

Prove that the above Circuit (a) is equivalent to Circuit (b).

*Solution by Boolean Algebra Simplification*

$$AB + A(B + C) + B(B + C)$$

$$AB + AB + AC + BB + BC$$

$$AB + AB + AC + B + BC$$

$$AB + AC + B + BC$$

$$AB + AC + B$$

$$B + AC$$

$$BB = B$$

$$AB + AB = AB$$

$$B + BC = B$$

$$AB + B = B$$

*Idempotent*

*Idempotent*

*Absorption*

*Absorption*

# Exercise

Simplify the following function.

$$f(w, x, y, z) = wxy' + w'y'z + wx'y' + xy'z + w'z$$

# Exercise


$$\begin{aligned}f(w, x, y, z) &= wxy' + w'y'z + wx'y' + xy'z + w'z \\&= wxy' + wx'y' + xy'z + w'z && \text{adsorption} \\&= wy' + w'z + xy'z && \text{adjacency}\end{aligned}$$

Term 1	Term 2	Consensus Term
$wy'$	$w'z$	$y'z$

$$\begin{aligned}&= wy' + w'z + xy'z + y'z && \text{Add the consensus term} \\&= wy' + w'z + y'z && \text{adsorption} \\&= wy' + w'z && \text{Remove the consensus term}\end{aligned}$$

# Exercise

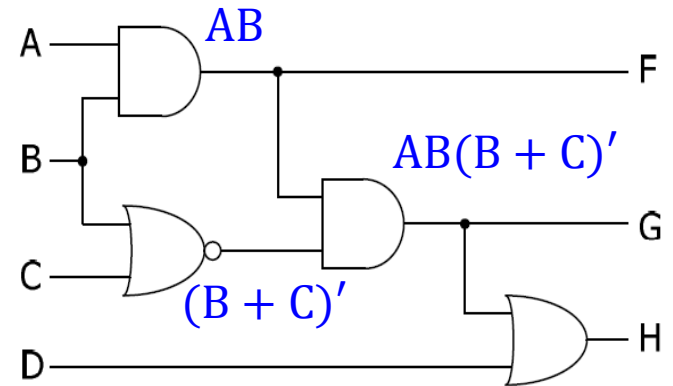1. Derive the Boolean functions to describe the operations of the logic circuit as shown.
2. Simplify the functions and draw the circuit.




$$F = AB$$

$$G = AB(B + C)'$$

$$= ABB'C' \quad \text{deMorgan}$$


$$= 0 \quad \text{Complement}$$

$$H = AB(B + C)' + D = D$$

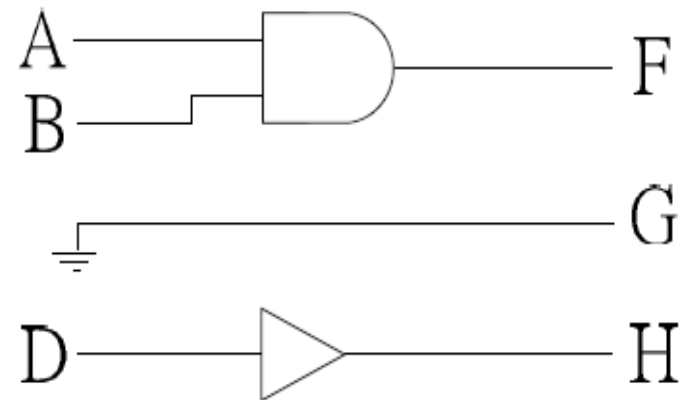
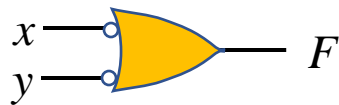
# Exercise


Work out the Boolean functions of the following circuits. Which standard logic gate does each of them represent?




$$F = x' + y' = (xy)'$$




$$F = (xx)' = x'$$

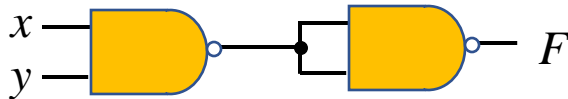

$$F = [(xy)']' = xy$$

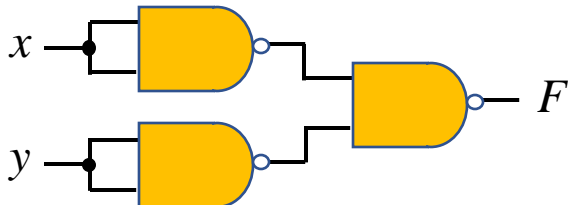

$$F = (x'y')' = x'' + y'' = x + y$$

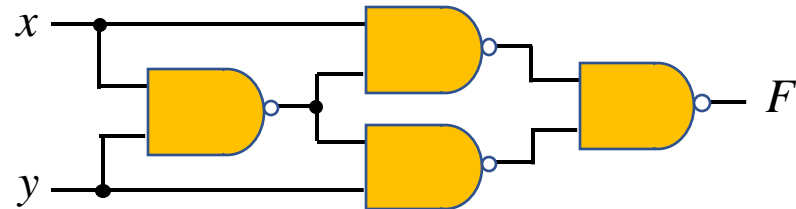

$$\begin{aligned} F &= \{[x(xy)']'[y(xy)']'\}' \\ &= [x(xy)']'' + [y(xy)']'' \\ &= x(xy)' + y(xy)' \\ &= x(x' + y') + y(x' + y') \\ &= xy' + yx' = x \oplus y \end{aligned}$$

# Exercise

Inputs			Output
$x$	$y$	$z$	$f(x, y, z)$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

$$f(x, y, z) = \sum m(1, 3, 6, 7) = \prod M(0, 2, 4, 5)$$

$$f(x, y, z) = x'y'z + x'yz + xyz' + xyz$$

$$= x'z + xy$$

