

EE 2000 Logic Circuit Design
Semester A 2024/25

Tutorial 4

1. What are the mistakes for this VHDL?

```
Library ieee;  
use IEEE.std-logic_1164.all;  
  
ENTITY and_gate IS  
    port (a&b : in STD_LOGIC;  
          S: out STD_LOGIC;);  
end;  
  
architecture CKT of and_Gate IS  
begin  
    s <= a AND b;  
end ckt;
```

```
Library ieee;  
use IEEE.std_logic_1164.all;  
  
ENTITY and_gate IS  
    port (a, b : in STD_LOGIC;  
          S: out STD_LOGIC);  
End and_gate;  
  
architecture CKT of and_Gate IS  
begin  
    s <= a AND b;  
end ckt;
```

2. Using VHDL to write the library and entity declarations for a logic design entity named MoZone that has the following inputs and outputs.
- (a) A1 is an array of 8-bit std_logic data with the highest index number holding the most significant bit.
 - (b) A2 is a 5-bit bit vector with the lowest index number holding the most significant bit
 - (c) O1 is a 1-bit std_logic output

```
library ieee;  
use IEEE.std_logic_1164.all;  
  
ENTITY mozone is  
    port (A1 : in std_logic_vector(7 downto 0);  
          A2 : in bit_vector(0 to 4);  
          O1 : out std_logic);  
End mozone;
```

3. Write a complete VHDL design module (with entity and architecture) to implement a circuit with the following Boolean expressions. Use concurrent statements and without NAND and NOR operators in your design.

- $x1 = A'B'C + A(BC)'$
- $x2 = (A'B + C')(BC' + A)'$
- $x3 = (A(BC)' + A'C')'$

```
ENTITY Prob_3 is
    port (A, B, C : in bit;
          x1, x2, x3 : out bit);
End Prob_3;

architecture behavior of Prob_3 is
begin
    x1 <= (NOT A AND NOT B AND C) OR (A AND NOT (B AND C));
    x2 <= (NOT A AND B OR NOT C) AND NOT (B AND NOT C OR A);
    x3 <= NOT ((A AND NOT (B AND C)) OR (NOT A AND NOT C));
end behavior;
```


4. Write a complete VHDL design module to implement a circuit with the following Boolean expressions. Assign a signal name sigW1 to represent the common logic term in your design. Use concurrent statements without NAND and NOR operators in your design.

- $A = (XY'Z')' + XZ$
- $B = (XY'Z')'(X + Z)$
- $C = ((XY'Z')' + X')'$

```
ENTITY Prob_4 is
    port (X, Y, Z : in bit;
          A, B, C : out bit);
End Prob_4;

architecture behavior of Prob_4 is
    signal sigW1 : bit;
begin
    sigW1 <= NOT (X AND NOT Y AND NOT Z);
    A <= sigW1 OR (X AND Z);
    B <= sigW1 AND (X OR Z);
    C <= NOT (sigW1 OR NOT X);
end behavior;
```

 5. Write a complete VHDL design module to implement the combinational circuit shown. Assign signals for intermediate outputs. Use concurrent statements (i) without NAND and NOR operators in your design; and (ii) with NAND and NOR operators.



```

ENTITY Prob_5 is
    port (w, x, y, z : in bit;
          F, G : out bit);
End Prob_5;

architecture behavior of Prob_5 is
    signal s1, s2, s3 : bit;
begin
    s1 <= w OR x;
    F <= NOT (NOT x OR s1);
    s2 <= NOT (w AND y);
    s3 <= s1 AND s2;
    G <= NOT (s3 AND z);
end behavior;
  
```

```

ENTITY Prob_5 is
    port (w, x, y, z : in bit;
          F, G : out bit);
End Prob_5;

architecture behavior of Prob_5 is
    signal s1, s2, s3 : bit;
begin
    s1 <= w OR x;
    F <= NOT x NOR s1;
    s2 <= w NAND y;
    s3 <= s1 AND s2;
    G <= s3 NAND z;
end behavior;
  
```