 


EE2000 Logic Circuit Design

Lecture 8– VHDL 2




What will you learn?

- 8.1 Use Component and instantiation
- 8.2 Understand the Conditional signal assignment
- 8.3 Understand the Selected signal assignment
- 8.4 Understand the Sequential statements
- 8.5 Understand various Decoder designs
 - Using Boolean Operators
 - Using Case statement
 - Using IF statement
 - With ENable Signal
- 8.6 Other examples – Encoder, MUX, DMUX, Flip-Flop

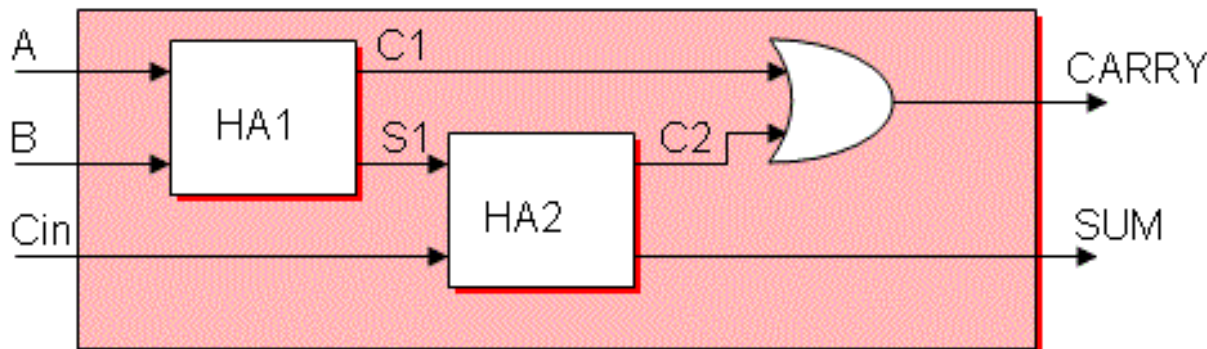8.1 Components and Instantiation

- **Structural modeling**: Modular design of a complex project
- When designing a complex project, we can split it into two or more simple designs (sub-modules/sub-circuits/**components**)
- Example: A full adder (FA) contains of 2 half adders (HAs); Half adder can be modeled by a **component**



Structural Modeling

- **Structural modeling** or modular design allows us to pack low-level functionalities into modules
- Allows a designed module to be **reused** without the need to reinvent and re-test the same functions/modules every time
- To include a **component** into a **module**, we need to
 - (1) **declare** the component
 - (2) **instantiate** the componentin **architecture**

Component Declaration

- An architecture may contain multiple components and they must be declared first

```
architecture [name] ...  
[signal]
```

```
component XX  
...  
end component;
```

-- Component declaration

```
component YY  
...  
end component;
```

-- Component declaration

```
begin  
... -- Component instantiation  
end [name];
```

Half Adder

Create the sub-module of half adder first

$$\text{sum} = a \oplus b \quad \text{carry} = a \cdot b = ab$$


Inputs		Outputs	
<i>a</i>	<i>b</i>	<i>c</i>	<i>s</i>
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

```
--sub module(half adder) entity declaration
entity halfadder is
port (a : in   STD_LOGIC;
       b : in   STD_LOGIC;
       sum : out  STD_LOGIC;
       carry : out  STD_LOGIC
       );
end halfadder;

architecture Behavioral of halfadder is
begin
  sum <= a xor b;
  carry <= a and b;
end Behavioral;
```

Full Adder

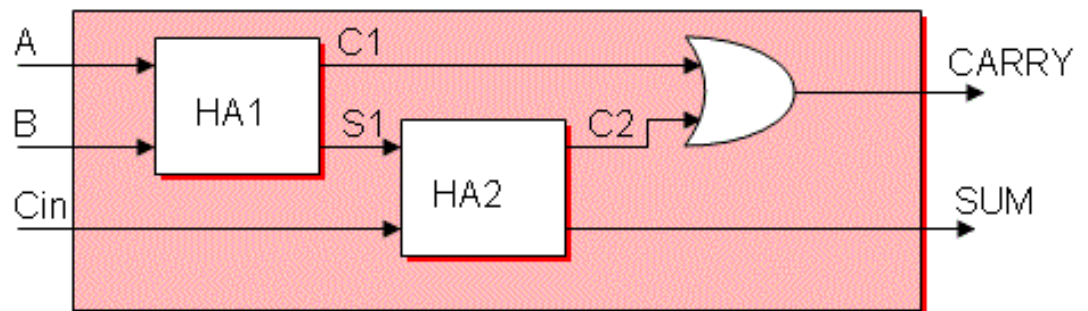- Create the component entity **halfadder**
- Create the module entity **fulladder**
- Determine the number of **components** (i.e. **2 halfadder** in this case) used in the design
- Define signals for inter-connections between **halfadder**
- Provide each component a different name
- Then instantiates the declared component



Full Adder

```
--top module(full adder) entity declaration
entity fulladder is
    port (a : in std_logic;
          b : in std_logic;
          cin : in std_logic;
          sum : out std_logic;
          carry : out std_logic
        );
end fulladder;
```

```
--top module architecture declaration
architecture behavior of fulladder is
```

```
    component halfadder
    port(
        a : in std_logic;
        b : in std_logic;
        sum : out std_logic;
        carry : out std_logic
    );
    end component;
```


--sub-module(half adder) is
declared as a component
before the keyword "begin"

Component Instantiation

Differences between a **component** and an **entity** declaration:

- **Entity** declaration declares a circuit model containing one or multiple architectures
- **Component** declaration declares a **virtual circuit** template, which must be **instantiated** to take effect during the design
- **Instantiation** – To map the signals in the entity with the input/output of the component
- **Port map** is required for component **instantiation**

Full Adder

 

- Two HAs are needed
- Internal signals **s1,c1,c2** are used to connect the two Has
- In HA, we define **port (a:in STD_LOGIC; b:in STD_LOGIC; sum:out STD_LOGIC; carry:out STD_LOGIC);**

```
signal s1,c1,c2 : std_logic:='0';  --declare internal signal

begin

--Provide a different name for each half adder.
--instantiate and do port map for the half adders.

HA1 : halfadder port map (a,b,s1,c1);
HA2 : halfadder port map (s1,cin,sum,c2);
carry <= c1 or c2;  --final carry calculation

end;
```

Component Instantiation

For creating connections between components and ports,
3 steps in VHDL instantiation:

- Label: identify a unique **instance** of component
- Component type: select a targeted declared **component**
- Port Map: Connect **component to signals**

```
HA1 : halfadder port map (a,b,s1,c1);  
HA2 : halfadder port map (s1,cin,sum,c2);
```

↑
Label

↑
Component

↑
Port Map

Signals must be of the **same data type** for the connecting pins

Component Instantiation

```
signal s1,c1,c2 : std_logic:='0';  --declare internal signal

begin

--Provide a different name for each half adder.
--instantiate and do port map for the half adders.

HA1 : halfadder port map (a,b,s1,c1);
HA2 : halfadder port map (
    a => s1,
    b => cin,
    sum => sum,
    carry => c2
);
carry <= c1 or c2;  --final carry calculation

end;
```

Port Map

```
entity halfadder is
Port ( a : in  STD_LOGIC;
      b : in  STD_LOGIC;
      sum : out STD_LOGIC;
      carry : out STD_LOGIC
    );
end halfadder;
```


Port name of Halfadder (a,b,sum,carry)

```
begin


--Provide a different name for each half adder.
--instantiate and do port map for the half adders.

HA1 : halfadder port map (a,b,s1,c1);
HA2 : halfadder port map (s1, cin,sum,c2);
carry <= c1 or c2;  --final carry calculation


end;
```

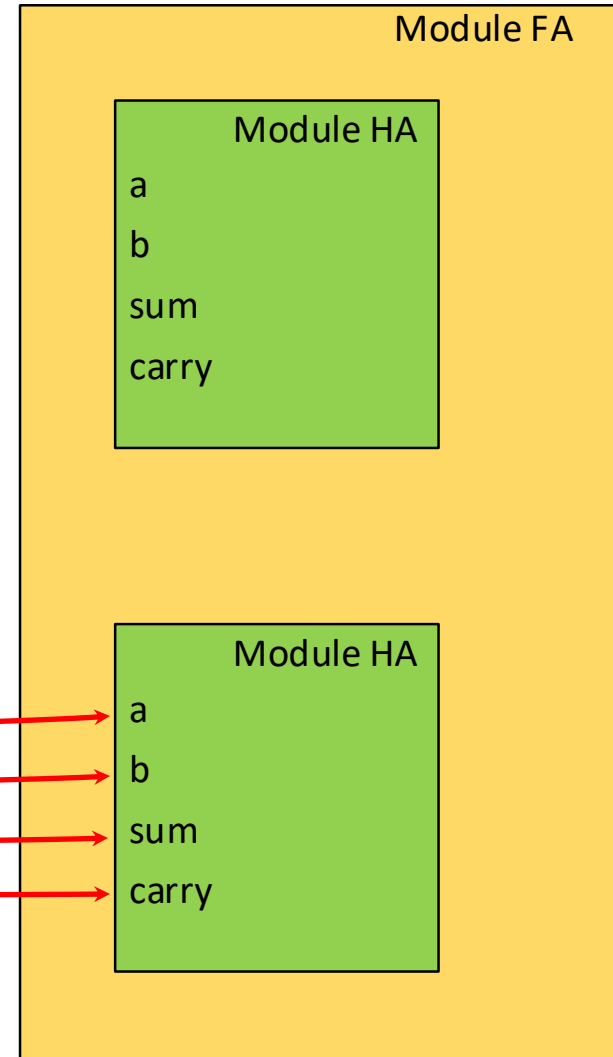


Half-Adder 1

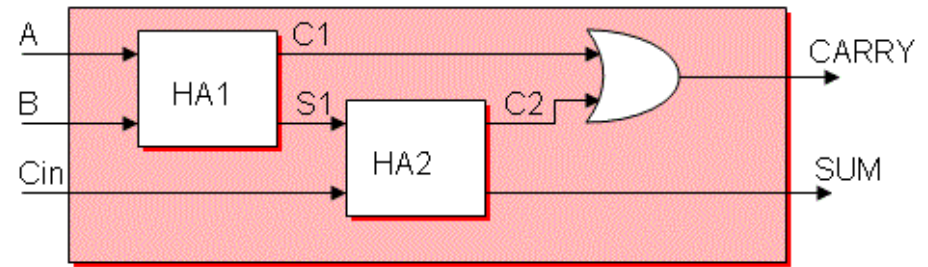

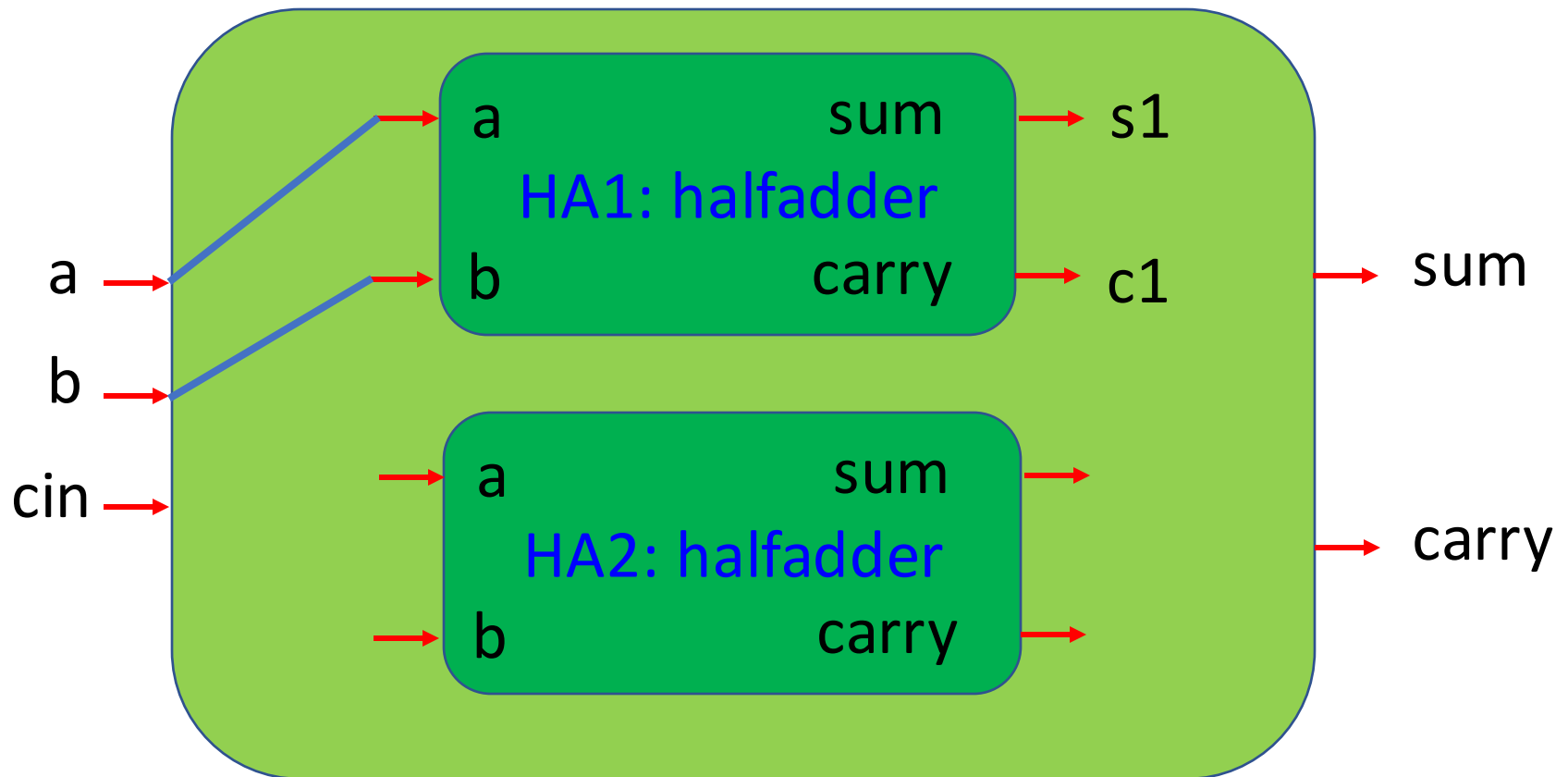
HA1 : halfadder **port map** (a,b,s1,c1) ;



Half-Adder 2

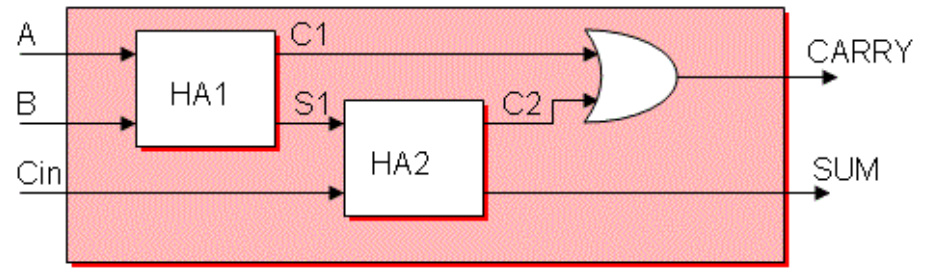
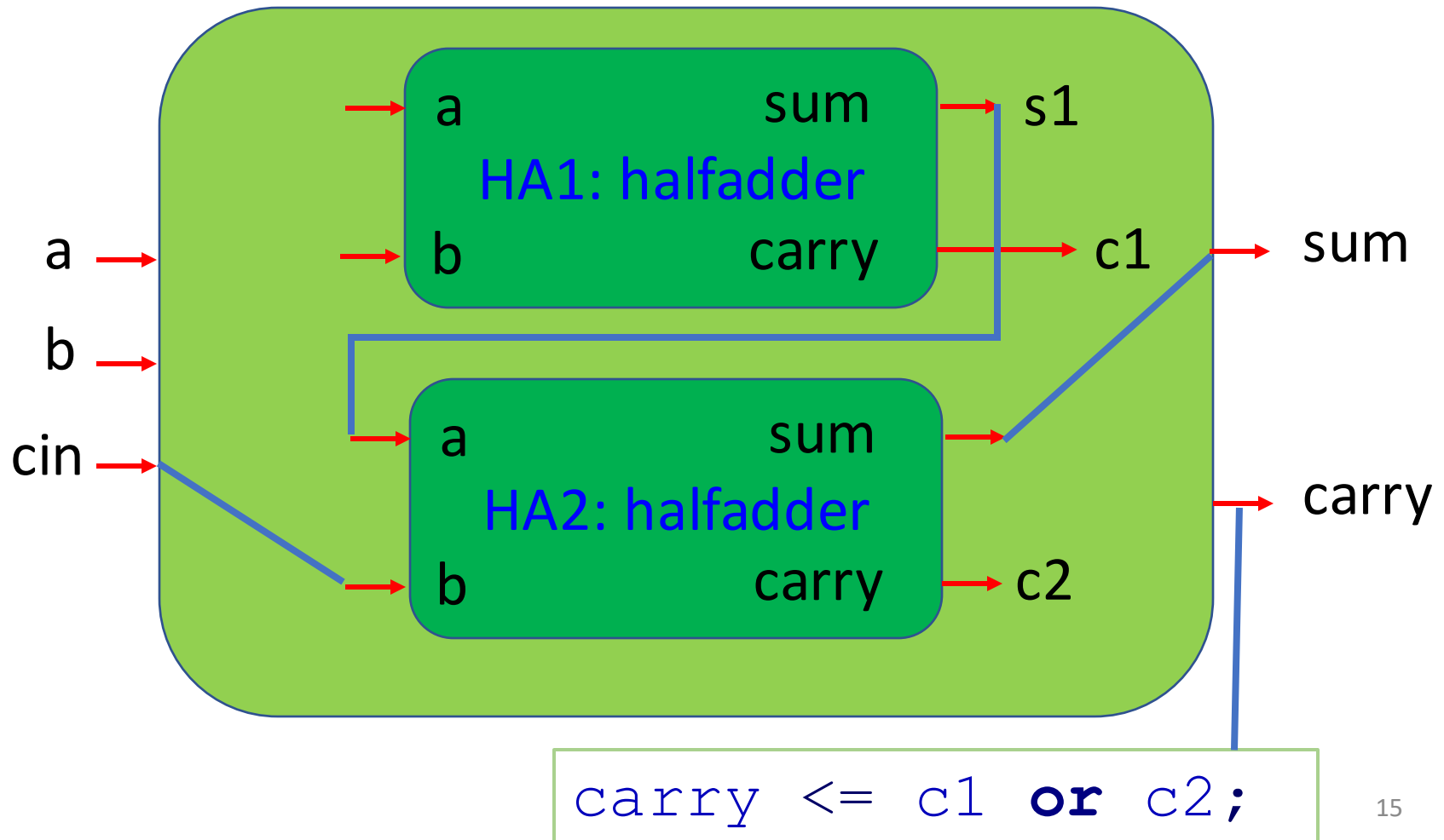
```
HA2 : halfadder port map (s1,cin,sum,c2);
```



8.2 Conditional Signal Assignment

```
signal_name <= expression1 when condition1 else  
                expression2 when condition2 else  
                [expressionN];
```


- Concurrent statement
- Conditions are evaluated successively until a true condition is found
- Conditions could be based on different signals

```
d <= a when b = '1' else  
    c when d = '0' else  
    e;
```

This means

1. When **b = '1'** then **d = a** or else
2. When **d = '0'** then **d = c** else
3. **d = e**

Example 4-to-1 MUX

 

```
OUT1 <= a when (s1 = '0' and s0 = '0') else  
      b when (s1 = '0' and s0 = '1') else  
      c when (s1 = '1' and s0 = '0') else  
      d;
```

8.3 Selected Signal Assignment

```
with expression_s select  
  signal_s <= expression1 [after delay-time] when choice1,  
    expression2 [after delay-time] when choice2,  
    ...  
    expression_n [after delay-time] when others];
```

- Concurrent statement
- Each line ends with ‘,’ and the last line with ‘;’
- “when others” is used to handle the default case, and also the don’t care cases
- No priority and based on a single signal

Examples

```
with d select
  Y <= '0' when "000",
    '1' when "001",
    '1' when "010",
    '0' when "011",
    '1' when "100",
    '0' when "101",
    '1' when "110",
    '1' when "111",
  NULL when others;
```

This means

1. When **d = '000'** then **Y = '0'** or else
2. When **d = '001'** then **Y = '1'** or else
3. When **d = '010'** then **Y = '1'** or else
-
9. For **other cases (don't care)**, then **Y = NULL**


Example 4-to-1 MUX

```
signal sel: integer;
```

```
sel <= 0 when (s1 = '0' and  
s0 = '0') else  
      1 when (s1 = '0' and  
s0 = '1') else  
      2 when (s1 = '1' and  
s0 = '0') else  
      3;
```

```
with sel select
```
 
```
  OUT1 <= a when 0,  
          b when 1,  
          c when 2,  
          d when others;
```



This means

1. When **sel = '0'** (00) then **OUT1 = a** or else
2. When **sel = '1'** (01) then **OUT1 = b** or else
3. When **sel = '2'** (10) then **OUT1 = c** or else
4. **OUT1 = d**

Conditional

```
d <= a when b = '1' else  
      c when d = '0' else  
      e;
```

- Can be based on different signals
- Evaluated successively until a true condition is found

Selected

```
with d select  
Y <= '0' when "000",  
      '0' when "011",  
      '0' when "101",  
      '1' when others;
```

- Based on a single signal only
- Only one condition is TRUE

Question: Which one will you use for the priority encoder?


8.4 Sequential Statements

- **Process statement** is used to enclose sequential statements that are executed in order
- **Sequential statements** are used in processes to specify how signals are assigned
- After all the sequential statements in the process are executed, the signals are assigned to their new values

```
[name:] process [(sensitivity_list)]  
begin  
    sequential statements  
end process;
```

Multiple Process Statements

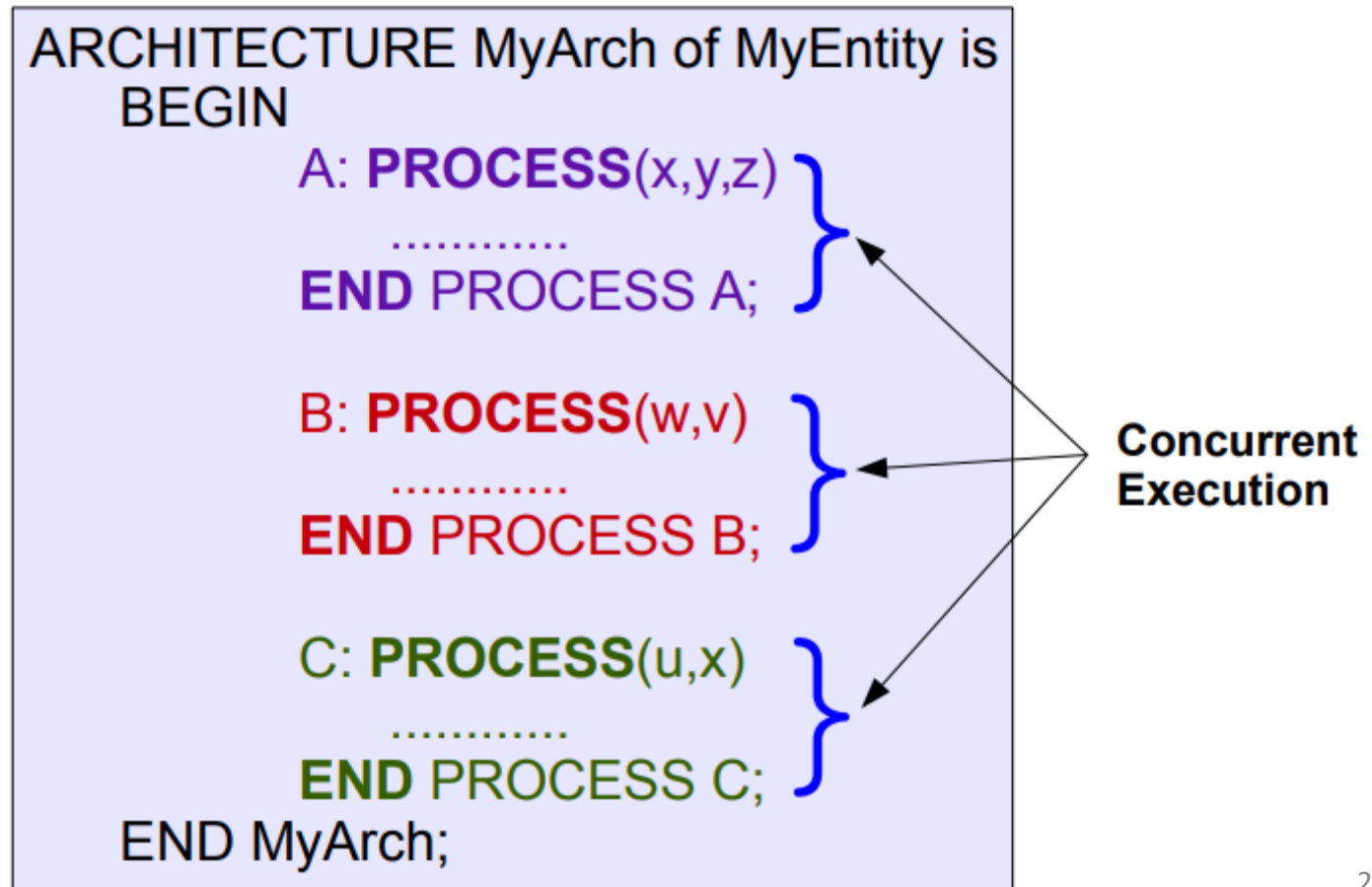Process statement is concurrent statement and can have more than one Process statements in an architecture



Recap from Lab Session 1

```
simgen: process          -- no sensitivity list
begin
    SW <= '0';
    wait for 50 ns;
    SW <= '1';
    wait for 100 ns;
    SW <= '0';
    wait for 50 ns
end process;
```



- **Without** the sensitivity list, the process will be run **continuously**
- **With** the sensitivity list, the process will be executed once when a **new event (change value)** occurs on any of the signals in the list

Sensitivity List

```
proc1: process (a, b, c)
begin
    x <= a and b and c;
end process;
```

When either a, b or c changes from '1' to '0' or vice versa, the process will run one time to update the value of x

```
proc1: process
begin
    x <= a and b and c;
    wait on a, b, c;
end process;
```

Wait Statement Forms

```
wait for 50 ns;
```

```
wait on a, b, c;
```

```
wait until signal = value;
```

```
wait until clk = '1';
```

The process will pause until clk changes to '1'

WHILE Loop Statement

```
[label:] while condition loop  
    sequential statements  
end loop [label];
```

- Conditional loop statement
- Condition is tested before the execution of the loop
- Terminate when the condition tested becomes false

```
while i < 10 loop  
    while j < 20 loop  
        ...  
        j <= j + 1;  
    end loop;  
    i <= i + 1;  
end loop;
```

FOR Loop Statement

```
[label:] for counter in range loop  
    sequential statements  
end loop [label];
```

- For the repeated execution of a sequence of statements a fixed number of times
- An iteration counter and a range are specified
- After an iteration, the counter is assigned the next value from the range
- Ascending order use **to**; descending order use **downto**

FOR Loop Statement

Compute the squares of integer values between 1 and 10 and stores them into the i_square array

```
for i in 1 to 10 loop  
    i_square (i) <= i * i;  
end loop;
```

i starts with 1, after computing i_square (1)

i becomes 2 (i = 2).....

Until i = 10.

FOR Loop Statement

```
entity match_bits is  
  port (a, b: in bit_vector (7 downto 0);  
        matches: out bit_vector (7 downto 0));  
end match_bits
```

```
architecture functional of match_bits is  
begin  
  process (a, b)  
  begin  
    for i in 7 downto 0 loop  
      matches (i) <= not (a(i) xor b(i));  
    end loop;  
end process;  
end functional;
```

what is the function?

FOR Loop Statement

- A set of **1-bit comparators** to compare the bits of the same order of vectors **a** and **b**
- Result is stored into the **matches** vector, which will contain '1' wherever the bits of the two vectors match and '0' otherwise

```
entity match_bits is
  port (a, b: in bit_vector (7 downto 0);
        matches: out bit_vector (7 downto 0));
end match_bits

architecture functional of match_bits is
begin
  process (a, b)
  begin
    for i in 7 downto 0 loop
      matches (i) <= not (a(i) xor b(i));
    end loop;
  end process;
end functional;
```


NEXT Statement

```
next [label:] [when condition];
```

The execution of the current iteration is skipped and the control is passed to the beginning of the loop statement

```
for i in 1 to 10 loop  
    next when v(i) = '0';  
    count <= count + 1;  
end loop;
```


8.5 Decoder Designs (2-to-4 decoder)

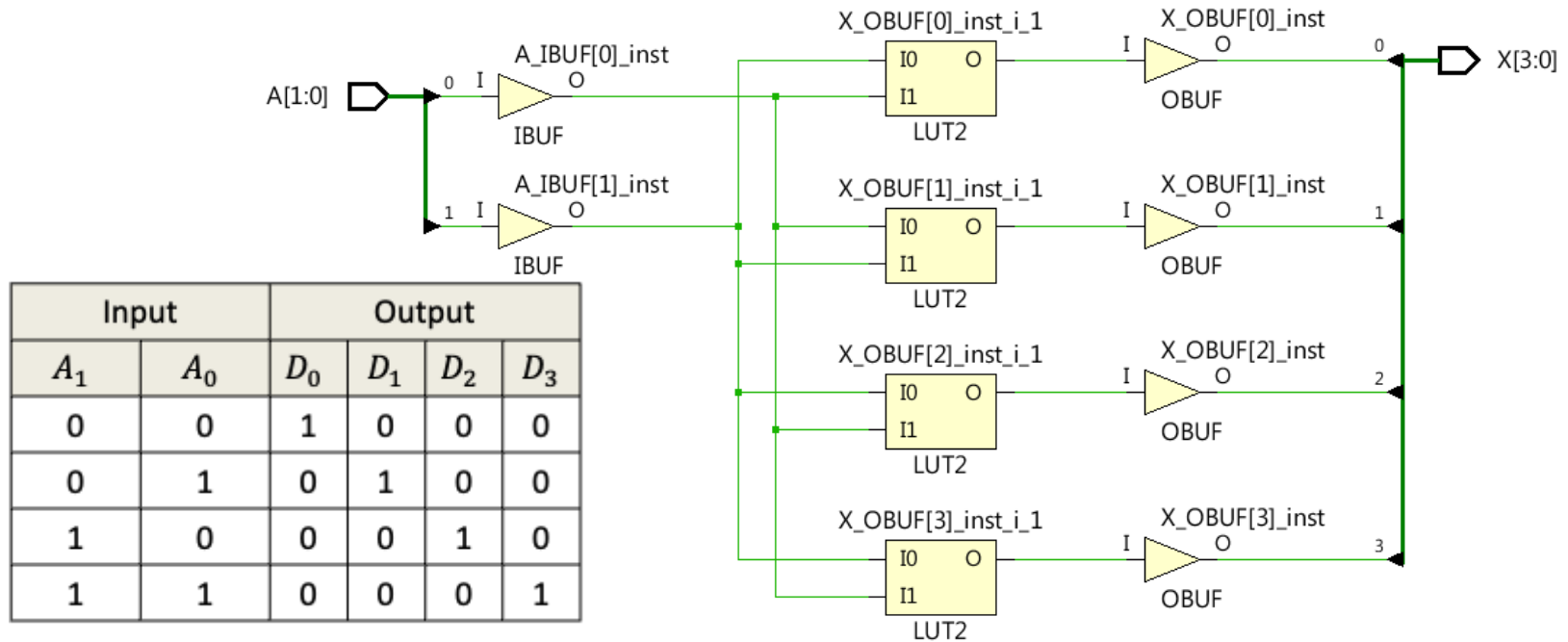

- Input A (2 bits)
- Output X (4 bits)

Using Boolean Operators

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity decoder is
port(
    A : in STD_LOGIC_VECTOR(1 downto 0);
    X : out STD_LOGIC_VECTOR(3 downto 0)
);
end decoder;

architecture Structral of decoder is
begin
    X(0) <= not A(0) and not A(1);
    X(1) <= A(0) and not A(1);
    X(2) <= not A(0) and A(1);
    X(3) <= A(0) and A(1);
end Structral;
```

Input		Output			
A_1	A_0	D_0	D_1	D_2	D_3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

Using CASE statement (Sequential)

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity decoder is
port(
    A : in STD_LOGIC_VECTOR(1 downto 0);
    X : out STD_LOGIC_VECTOR(3 downto 0)
);
end decoder;

architecture Behavioral of decoder is
begin

    process(a)
    begin
        case A is
            when "00" => X <= "0001";
            when "01" => X <= "0010";
            when "10" => X <= "0100";
            when "11" => X <= "1000";
        end case;
    end process;
end Behavioral;
```

case expression is
 when option1 =>
statement;
 when option2 =>
statement;
 ...
 [**when others** =>
statement;]
end case;

When A is "00" X <= "0001"

Input		Output			
A ₁	A ₀	D ₀	D ₁	D ₂	D ₃
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

Using IF statement (Sequential)

```
entity decoder is
port(
    A : in STD_LOGIC_VECTOR(1 downto 0);
    X : out STD_LOGIC_VECTOR(3 downto 0)
);
end decoder;

architecture Behavioral of decoder is
begin
    process(a)
    begin
        if (A="00") then
            X <= "0001";
        elsif (A="01") then
            X <= "0010";
        elsif (A="10") then
            X <= "0100";
        else
            X <= "1000";
        end if;
    end process;
end Behavioral;
```

if condition **then**
statement;
[**elsif** condition **then**
statement;]
...
[**else** statement;]
end if;

If A is "00" X <= "0001"

Input		Output			
A ₁	A ₀	D ₀	D ₁	D ₂	D ₃
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

With Enable Input

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity decode_2to4_top is
    Port ( A : in  STD_LOGIC_VECTOR (1 downto 0);    -- 2-bit input
          X : out STD_LOGIC_VECTOR (3 downto 0);    -- 4-bit output
          EN : in  STD_LOGIC);                      -- enable input
end decode_2to4_top;


architecture Behavioral of decode_2to4_top is
begin
    process (A, EN)
    begin
        X <= "1111";    -- default output value
        if (EN = '1') then -- active high enable pin
            case A is
                when "00" => X(0) <= '0';
                when "01" => X(1) <= '0';
                when "10" => X(2) <= '0';
                when "11" => X(3) <= '0';
                when others => X <= "1111";
            end case;
        end if;
    end process;
end Behavioral;
```

Active Low

 8.6 Other Examples

```
entity encoder is
  port(
    a : in STD_LOGIC_VECTOR(3 downto 0);
    b : out STD_LOGIC_VECTOR(1 downto 0)
  );
end encoder;
```

```
architecture Behavioral of encoder is
begin
  process(a)
  begin
    case a is
      when "1000" => b <= "00";
      when "0100" => b <= "01";
      when "0010" => b <= "10";
      when "0001" => b <= "11";
      when others => b <= "ZZ";
    end case;
  end process;
end Behavioral;
```



Input				Output	
A_3	A_2	A_1	A_0	B_1	B_0
1	0	0	0	0	0
0	1	0	0	0	1
0	0	1	0	1	0
0	0	0	1	1	1

Simulation


Input				Output	
A_3	A_2	A_1	A_0	B_1	B_0
1	0	0	0	0	0
0	1	0	0	0	1
0	0	1	0	1	0
0	0	0	1	1	1

```
entity encoder is
    port(
        a : in STD_LOGIC_VECTOR(3 downto 0);
        b : out STD_LOGIC_VECTOR(1 downto 0)
    );
end encoder;

architecture Behavioral of encoder is
begin
    process(a)
    begin
        case a is
            when "1000" => b <= "00";
            when "0100" => b <= "01";
            when "0010" => b <= "10";
            when "0001" => b <= "11";
            when others => b <= "ZZ";
        end case;
    end process;
end Behavioral;
```



```
ENTITY tb_encoder IS
END tb_encoder;

ARCHITECTURE behavior OF tb_encoder IS
    COMPONENT encoder
        PORT(
            a : IN std_logic_vector(3 downto 0);
            b : OUT std_logic_vector(1 downto 0)
        );
    END COMPONENT;
    signal a : std_logic_vector(3 downto 0) := (others => '0');
    signal b : std_logic_vector(1 downto 0);
    BEGIN
        uut: encoder PORT MAP (a => a, b => b);
        stim_proc: process
        begin
            -- hold reset state for 100 ns.
            wait for 100 ns;
            a <= "0000";
            wait for 100 ns;
            a <= "0001";
            wait for 100 ns;
            a <= "0010";
            wait for 100 ns;
            a <= "0100";
            wait for 100 ns;
            a <= "1000";
            wait;
        end process;
    END;
```

 

Recap (Decimal-to-BCD Encoder)

Inputs										Outputs			
0	1	2	3	4	5	6	7	8	9	A_3	A_2	A_1	A_0
1	0	0	0	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	0	0	0	1	0	0
0	0	0	0	0	1	0	0	0	0	0	1	0	1
0	0	0	0	0	0	1	0	0	0	0	1	1	0
0	0	0	0	0	0	0	1	0	0	0	1	1	1
0	0	0	0	0	0	0	0	1	0	1	0	0	0
0	0	0	0	0	0	0	0	0	1	1	0	0	1

  

Encoder (Decimal-to-BCD Encoder)

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

```
entity ENC3 is
```

```
    Port ( Q : in std_logic;
```

```
          R : in std_logic;
```

```
          S : in std_logic;
```

```
          T : in std_logic;
```

```
          U : in std_logic;
```

```
          V : in std_logic;
```

```
          W : in std_logic;
```

```
          X : in std_logic;
```

```
          Y : in std_logic;
```

```
          Z : in std_logic;
```

```
          OUT0 : out std_logic;
```

```
          OUT1 : out std_logic;
```

```
          OUT2 : out std_logic;
```

```
          OUT3 : out std_logic);
```

```
end ENC3;
```

```
architecture Behavioral of ENC3 is
```

```
begin
```


```
    process (Q,R,S,T,U,V,W,X,Y,Z)
```

```
    begin
```


Enter your codes here

```
    end process;
```

```
end Behavioral;
```

 

Multiplexer

 

Input		output
S1	S0	Z
0	0	A
0	1	B
1	0	C
1	1	D

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity mux_4to1 is
    port(
        A,B,C,D : in STD_LOGIC;
        S0,S1: in STD_LOGIC;
        Z: out STD_LOGIC
    );
end mux_4to1;

architecture bhv of mux_4to1 is
begin
    process (A,B,C,D,S0,S1) is
    begin
        if (S0 = '0' and S1 = '0') then
            Z <= A;
        elsif (S0 = '1' and S1 = '0') then
            Z <= B;
        elsif (S0 = '0' and S1 = '1') then
            Z <= C;
        else
            Z <= D;
        end if;
    end process;
end bhv;
```

Simulation

```
ENTITY tb_mux IS
END tb_mux;

ARCHITECTURE behavior OF tb_mux IS
  COMPONENT mux_4to1
  PORT (
    A : IN  std_logic;
    B : IN  std_logic;
    C : IN  std_logic;
    D : IN  std_logic;
    S0 : IN  std_logic;
    S1 : IN  std_logic;
    Z : OUT std_logic
  );
END COMPONENT;

signal A, B, C, D, S0, S1 : std_logic := '0';
signal Z : std_logic;


BEGIN

  uut: mux_4to1 PORT MAP (A => A, B => B, C => C, D => D, S0 => S0, S1 => S1, Z => Z);


  stim_proc: process
  begin
    -- hold reset state for 100 ns.
    wait for 100 ns;
    A <= '1';
    B <= '0';
    C <= '1';
    D <= '0';
    S0 <= '0'; S1 <= '0';
    wait for 100 ns;
    S0 <= '1'; S1 <= '0';
    wait for 100 ns;
    S0 <= '0'; S1 <= '1';
    wait for 100 ns;
    S0 <= '0'; S1 <= '1';
    wait for 100 ns;
    end process;

END;
```

Input		output
S1	S0	Z
0	0	A
0	1	B
1	0	C
1	1	D

 

Demultiplexer

 


Input	Selection line		Output			
F	S1	S0	D	C	B	A
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	1	0	0	1	0	0
1	1	1	1	0	0	0
0	X	X	0	0	0	0

```

entity demux_1to4 is
    port(
        F : in STD_LOGIC;
        S0,S1: in STD_LOGIC;
        A,B,C,D: out STD_LOGIC
    );
end demux_1to4;

architecture bhv of demux_1to4 is
begin
    process (F,S0,S1) is
    begin
        if (S0 = '0' and S1 = '0') then
            A <= F;
        elsif (S0 = '1' and S1 = '0') then
            B <= F;
        elsif (S0 = '0' and S1 = '1') then
            C <= F;
        else
            D <= F;
        end if;
    end process;
end bhv;
    
```

D-Flip Flop

 

Inputs		Outputs		
<i>D</i>	<i>Clk</i>	Next <i>Q</i>	Next <i>Q'</i>	State
x	↓,0,1	<i>Q</i>	<i>Q'</i>	Hold
x	↑	<i>D</i>	<i>D'</i>	Set / Reset

Inputs		Outputs		
<i>D</i>	<i>Clk</i>	Next <i>Q</i>	Next <i>Q'</i>	State
x	↑,0,1	<i>Q</i>	<i>Q'</i>	Hold
x	↓	<i>D</i>	<i>D'</i>	Set / Reset

Rising-edge triggered

```
process (clk)
begin
    if rising_edge (clk)
then
    q <= d;
    end if;
end process;
```

Falling-edge triggered

```
process (clk)
begin
    if falling_edge (clk)
then
    q <= d;
    end if;
end process;
```

D-Flip Flop with RESET

Edge condition comes before reset

Syn active “high” reset

Rising edge FF

```
process (clk)
begin
  if rising_edge (clk)
  then
    if sreset = '1' then
      q <= '0';
    else
      q <= d;
    end if;
  end if;
end process;
```

Syn active “low” reset

Falling edge FF

```
process (clk)
begin
  if falling_edge (clk)
  then
    if sreset = '0' then
      q <= '0';
    else
      q <= d;
    end if;
  end if;
end process;
```

D-Flip Flop with RESET

Reset condition comes before edge

Asyn active “high” reset

Rising edge FF

```
process(clk, areset)
begin
    if areset = '1' then
        q <= '0';
    elsif rising_edge(clk) then
        q <= d;
    end if;
end process;
```

Asyn active “low” reset

Falling edge FF

```
process(clk, areset)
begin
    if areset = '0' then
        q <= '0';
    elsif falling_edge(clk) then
        q <= d;
    end if;
end process;
```

D-Flip Flop with RESET

```
library ieee;  
use ieee.std_logic_1164.all;  
  
entity DFF is  
port( din: in std_logic;  
      clk: in std_logic;  
      rst: in std_logic;  
      dout: out std_logic);  
end DFF;
```

```
architecture behavioral of DFF is  
begin  
  process(rst,clk,din)  
  begin  
    if (rst='1') then  
      dout<='0';  
    elsif(rising_edge(clk)) then  
      dout<= din;  
    end if;  
  end process;  
  
end behavioral;
```


D-Flip Flop with SET and RESET

Asyn **set** active “high” , **reset** active “low”

Rising edge FF

```
process(clk, areset, aset)
begin
    if aset = '1' then
        q <= '1';
    elsif areset = '0' then
        q <= '0';
    elsif rising_edge(clk)
    then
        q <= d;
    end if;
end process;
```

Note: **set** has higher priority than **reset**

T-Flip Flop with RESET

Rising edge FF

Asyn Active High Reset

C	T	Q_{t+1}	$\overline{Q_{t+1}}$	State
0	x	Q_t	$\overline{Q_t}$	Hold
1	0	Q_t	$\overline{Q_t}$	Hold
1	1	$\overline{Q_t}$	Q_t	Toggle


```
library ieee;
use ieee.std_logic_1164.all;

entity TFF is
port(  T: in std_logic;
      clk: in std_logic;
      areset: in std_logic;
      Q: out std_logic;
end TFF;
```

```
architecture behavioral of TFF is
signal tmp : std_logic;
begin
process (clk, areset)
begin

end process;
end behavioral;
```

Simulation

 

Lab Session 3

Objectives

- To practice **designing combinational logic circuit**
- To reuse the materials and knowledge from previous labs
- To learn how to perform **type conversion** in VHDL Code
- To apply **bit slicing** and **bit concatenation** technique in VHDL
- To learn how to use a **logic analyzer** to trace the digital signals

Lab Session 3

- An arithmetic logic unit (ALU) is to perform arithmetic and bitwise operation on integer binary numbers
- In this experiment, you will implement a simple 3- bit ALU
- Given two 3-bit operands **A**, **B** and the 2-bit operator **op**, the result is shown in the table

op	Result	carry
00	A ADD B	It depends
01	A AND B	0
10	A XOR B	0
11	A << 1	0

100 + 011 = 111

100 AND 111 = 100

100 XOR 111 = 011

Left shift A 011 -> 110

VHDL Codes

```
Library IEEE;
```

```
Use IEEE.STD_LOGIC_1164.ALL;
```

```
USE IEEE.STD_LOGIC_UNSIGNED.ALL;
```

Entity ALU is

Port (

A: in STD_LOGIC_VECTOR (2 DOWNT0 0);

B: in STD_LOGIC_VECTOR (2 DOWNT0 0);

op: in STD_LOGIC_VECTOR (1 DOWNT0 0);

result: out STD_LOGIC_VECTOR (2 DOWNT0 0);

carry: out STD_LOGIC;

--dup_result and dup_carry are used for observation using Logic Analyzer

dup_result: out STD_LOGIC_VECTOR (2 DOWNT0 0);

dup_carry: out STD_LOGIC

);

end ALU;

VHDL Codes

Architecture Behavioral of ALU is

```
SIGNAL result_t: STD_LOGIC_VECTOR (2 DOWNT0 0);
```

```
SIGNAL carry_t: STD_LOGIC;
```

--You can add your declaration here.

Begin

```
dup_result <= result_t;
```

```
dup_carry <= carry_t;
```

```
result <= result_t;
```

```
carry <= carry_t;
```

--Write your own code to implement this ALU.

```
end Behavioral;
```

Type Conversion

(1) In VHDL, if the type is `STD_LOGIC_VECTOR`, you can directly use the following operators.

<code>A + B</code>	-- Addition
<code>A AND B</code>	-- Logical and
<code>A OR B</code>	-- Logical or
<code>A XOR B</code>	-- Logical xor

(2) VHDL has logical shift operator **sll** (shift left) and **srl** (shift right), but they are for `BIT_VECTOR`. If A and result are both `STD_LOGIC_VECTOR`, then type conversion is needed.

<code>result <= to_stdlogicvector(to_bitvector(A) sll 1);</code>

Expand to 4 Bits

- (3) You can get the sum and carry of two 3-bit inputs by expanding inputs to 4-bit, that is

```
tmp <= ('0' & A) + ('0' & B);
```

```
-- A and B are both 3-bit inputs
```

```
-- tmp is a 4-bit result and tmp(2 downto 0) is the sum and tmp(3) is the  
carry value
```

A: 100

B: 100

Result: 1000

A: 0100

B: 0100

Result: 1000

Sum output: "000"

Carry out: "1"


Selected Signal Assignment

op	Result	carry
00	A ADD B	It depends
01	A AND B	0
10	A XOR B	0
11	A << 1	0

(4) Now you can learn how to use the **WHEN** statement. Here is a simple example for you. It is a simple decoder from SIGNAL sel to SIGNAL result_out. Note the use of ‘,’ and ‘;’ carefully.

```
WITH sel SELECT
    result_out <= "0001" WHEN "00",
                "0010" WHEN "01",
                "0100" WHEN "10",
                "1000" WHEN "11",
                "ZZZ" WHEN others;
```

RTL Analysis

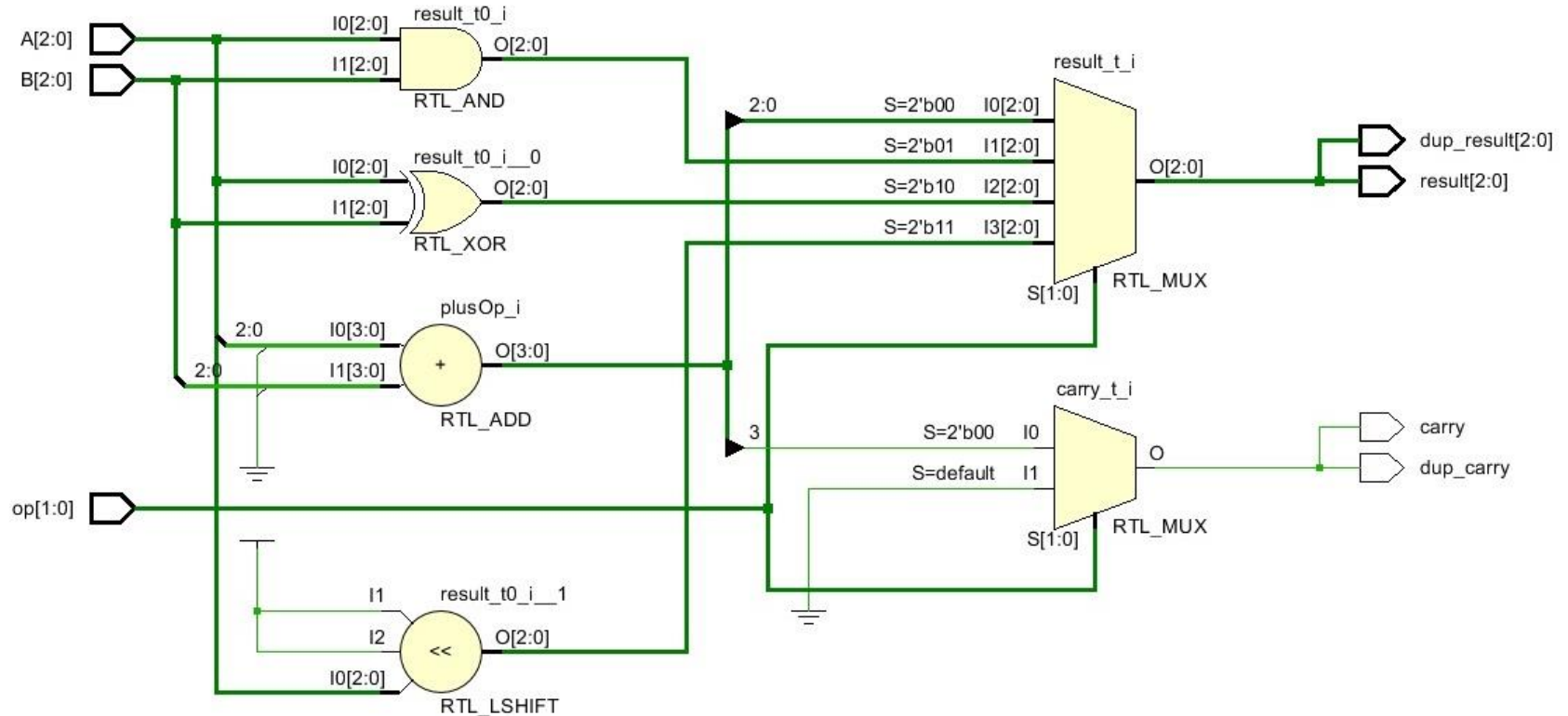

As the design is different from one another, the schematic may not be the same

Logic Analyzer

