 


**EE 2000 Logic Circuit Design**  
**Semester A 2024/25**

Tutorial 10

1. Using JK FFs and with the minimum number of states to design a counter with counting sequence: 0,4,2,1,6 and repeat. State whether the circuit is a self started circuit.
2. Design a sequential circuit with two JK FFs,  $A$  &  $B$ , and two inputs,  $x$  &  $E$ . if  $E=0$ , the circuit remains in the same state regardless of the value of  $x$ . When  $E = 1$  and  $x = 1$ , the circuit goes through the state transitions from 00 to 01 to 10 to 11 back to 00, and repeats. When  $E = 1$  and  $x = 0$ , the circuit goes through the state transitions from 00 to 11 to 10 to 01 back to 00, and repeats.
3. Using a synchronous binary counter as shown, design and draw a counter to generate the following repeating sequences 2 to 9 repeatedly for a free running clock.



4. Given the following VHDL code, Specify which functional block is being implemented and its function in detail.

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity func1 is
port ( clk: in std_logic;
      rst: in std_logic;
      Q: out std_logic_vector (3 downto 0));
end func1;

architecture Behavioral of func1 is
signal temp: std_logic_vector(3 downto 0) := "0000";
begin
    process(clk, rst)
        if rst = '1' then
            temp <= "0000";
        elsif rising_edge(clk) then
            temp(2) <= temp(3);
            temp(1) <= temp(2);
            temp(0) <= temp(1);
            temp(3) <= not temp(0);
        end if;
    end process;
    Q <= temp;
end Behavioral;
```