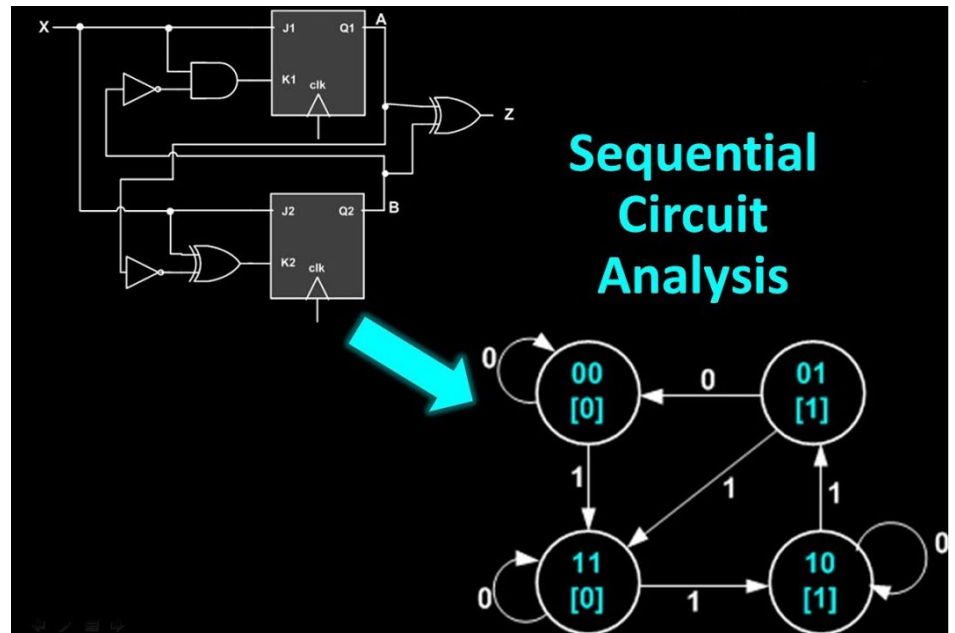


# EE2000 Logic Circuit Design

---

## Lecture 9 – Sequential Logic Circuit Design



# Exercise (Sequence Detector)

Design a Mealy machine to detect the sequence “111”  
(Overlapping)

In other words,

Design a system with one input  $x$  and one output  $z$  such that  $z = 1$  if  $x$  has been 1 for at least three consecutive clock times.

$x$	0	1	1	0	1	1	1	0	1	1	1	1	1	0
$z$	0	0	0	0	0	0	1	0	0	0	1	1	1	0

# Exercise (Sequence Detector)

$x$	0	1	1	0	1	1	1	0	1	1	1	1	1	0
$z$	0	0	0	0	0	0	1	0	0	0	1	1	1	0

**STEP 1:** Determine what needs to be stored in memory and how to store them.

A: input is '0'      \*if next input is 0, remains at A else B

B: one '1' is detected      \*if next input is 0, back to A else C

C: two '1's are detected

                         \* if next input is 0, back to A and output '0',  
else remains at C and output '1'

# Exercise (Sequence Detector)


## STEP 2: Work out the State Diagram

A: Input is '0'      \*if next input is 0, remains at A else B

B: one '1' is detected      \*if next input is 0, back to A else C

C: two '1's are detected

 
\* if next input is 0, back to A and output '0',  
else remains at C and output '1'


 
# Exercise (Sequence Detector)

**STEP 3:** Work out the analysis table with assigned FFs

3 states  $\rightarrow$  2 FFs (We use D-FFs in this example)



Assign State A:

$Q_1 \rightarrow 0$  and  $Q_2 \rightarrow 0$  etc

Present State ( $Q_1 Q_2$ )	Input $X$	Next stage		Output $Z$
		$Q_1^*$	$Q_2^*$	
A (0 0)	0			
A (0 0)	1			
B (0 1)	0			
B (0 1)	1			
(1 0)	X			
C (1 1)	0			
C (1 1)	1			

# Exercise (Sequence Detector)

**STEP 4:** Work out  $D_1$  and  $D_2$

Present State ( $Q_1Q_2$ )	Input $X$	Next State $Q_1^* \quad Q_2^*$		Output $Z$
A (0 0)	0	0	0	0
A (0 0)	1	0	1	0
B (0 1)	0	0	0	0
B (0 1)	1	1	1	0
(1 0)	x	x	x	x
C (1 1)	0	0	0	0
C (1 1)	1	1	1	1

$Q_1^*$

		$Q_1Q_2$			
		00	01	11	10
$x$	0	0	0	0	x
	1	0	1	1	x

$$D_1 = Q_1^* = xQ_2$$

$Q_2^*$

		$Q_1Q_2$			
		00	01	11	10
$x$	0	0	0	0	x
	1	1	1	1	x

$$D_2 = Q_2^* = x$$

# Exercise (Sequence Detector)

## STEP 5: Work out $z$

Present State ( $Q_1Q_2$ )	Input $X$	Next State $Q_1^* \quad Q_2^*$		Output $Z$
A (0 0)	0	0	0	0
A (0 0)	1	0	1	0
B (0 1)	0	0	0	0
B (0 1)	1	1	1	0
(1 0)	x	x	x	x
C (1 1)	0	0	0	0
C (1 1)	1	1	1	1

$Q_1Q_2$		00	01	11	10
$x$	0	0	0	0	x
	1	0	0	1	x

$$z = xQ_1$$


# Exercise (Sequence Detector)

**STEP 6:** Draw the sequential logic circuits

$$D_1 = xQ_2$$

$$D_2 = x$$

$$z = xQ_1$$

 



# Exercise (Sequence Detector)

Use T FFs to design a Mealy machine to detect the sequence “111” (Overlapping)

Present State ( $Q_1 Q_2$ )	Input $X$	Next State		Flip-Flops		Output $Z$
		$Q_1^*$	$Q_2^*$	$T_1$	$T_2$	
A (0 0)	0	0	0	0	0	0
A (0 0)	1	0	1	0	1	0
B (0 1)	0	0	0	0	1	0
B (0 1)	1	1	1	1	0	0
(1 0)	x	x	x	x	x	x
C (1 1)	0	0	0	1	1	0
C (1 1)	1	1	1	0	0	1

$T$	$Q_{t+1}$	$\overline{Q_{t+1}}$	State
0	$Q_t$	$\overline{Q_t}$	Hold
1	$\overline{Q_t}$	$Q_t$	Toggle

# Exercise (Sequence Detector)

Present State ( $Q_1Q_2$ )	Input $X$	Flip-Flops	
		$T_1$	$T_2$
A (0 0)	0	0	0
A (0 0)	1	0	1
B (0 1)	0	0	1
B (0 1)	1	1	0
(1 0)	x	x	x
C (1 1)	0	1	1
C (1 1)	1	0	0

$T_1$

$x$	$Q_1Q_2$			
	00	01	11	10
0	0	0	1	x
1	0	1	0	x

$$T_1 = xQ_1'Q_2 + x'Q_1$$


$T_2$

$x$	$Q_1Q_2$			
	00	01	11	10
0	0	1	1	x
1	1	0	0	x

$$T_2 = xQ_2' + x'Q_2$$
 
# Exercise (Sequence Detector)


$$T_1 = xQ_1'Q_2 + x'Q_1 \quad T_2 = xQ_2' + x'Q_2 = x \oplus Q_2 \quad z = xQ_1$$



# Exercise (Sequence Detector)

Use JK FFs to design a Mealy machine to detect the sequence “111” (Overlapping)

Present State ( $Q_1Q_2$ )	Input $X$	Next State		Flip-Flops				Output $Z$
		$Q_1^*$	$Q_2^*$	$J_1$	$K_1$	$J_2$	$K_2$	
A (0 0)	0	0	0					0
A (0 0)	1	0	1					0
B (0 1)	0	0	0					0
B (0 1)	1	1	1					0
(1 0)	x	x	x					x
C (1 1)	0	0	0					0
C (1 1)	1	1	1					1

 

Present State ( $Q_1Q_2$ )	Input $X$	Flip-Flops			
		$J_1$	$K_1$	$J_2$	$K_2$
A (0 0)	0				
A (0 0)	1				
B (0 1)	0				
B (0 1)	1				
(1 0)	x				
C (1 1)	0				
C (1 1)	1				

$J_1$

$Q_1Q_2$		00	01	11	10
$x$	0				
	1				

$J_1 =$

$K_1$

$Q_1Q_2$		00	01	11	10
$x$	0				
	1				

$K_1 =$

Present State ( $Q_1Q_2$ )	Input $X$	Flip-Flops			
		$J_1$	$K_1$	$J_2$	$K_2$
A (0 0)	0				
A (0 0)	1				
B (0 1)	0				
B (0 1)	1				
(1 0)	x				
C (1 1)	0				
C (1 1)	1				

$J_2$

$Q_1Q_2$		00	01	11	10
$x$	0				
	1				

$J_2 =$

$K_2$

$Q_1Q_2$		00	01	11	10
$x$	0				
	1				

$K_2 =$

# Mealy vs Moore Machines

Mealy machine

Present State	Input X	
	0	1
A	A/0	B/0
B	A/0	C/0
C	A/0	C/1

Moore machine

Present State	Input X		Present Output Z
	0	1	
A	A	B	0
B	A	C	0
C	A	D	0
D	A	D	1




## Moore machine

- Typically more states, more complex logic circuits

## Mealy machine




- + Typically fewer states, simpler logic circuits

# Example (Timing Diagram)

   






# Example (Timing Diagram)

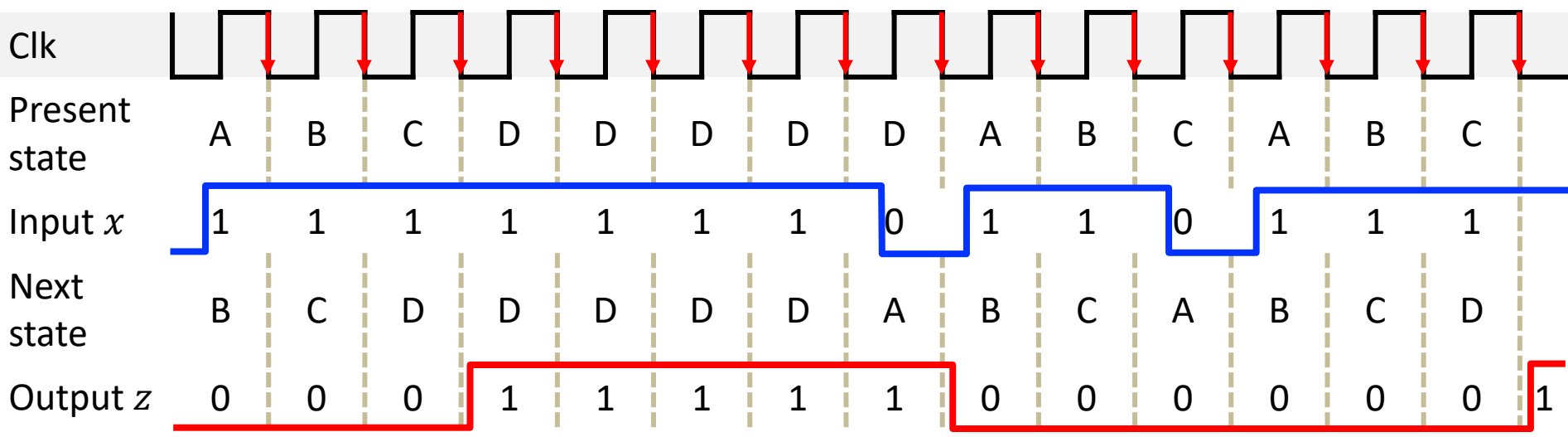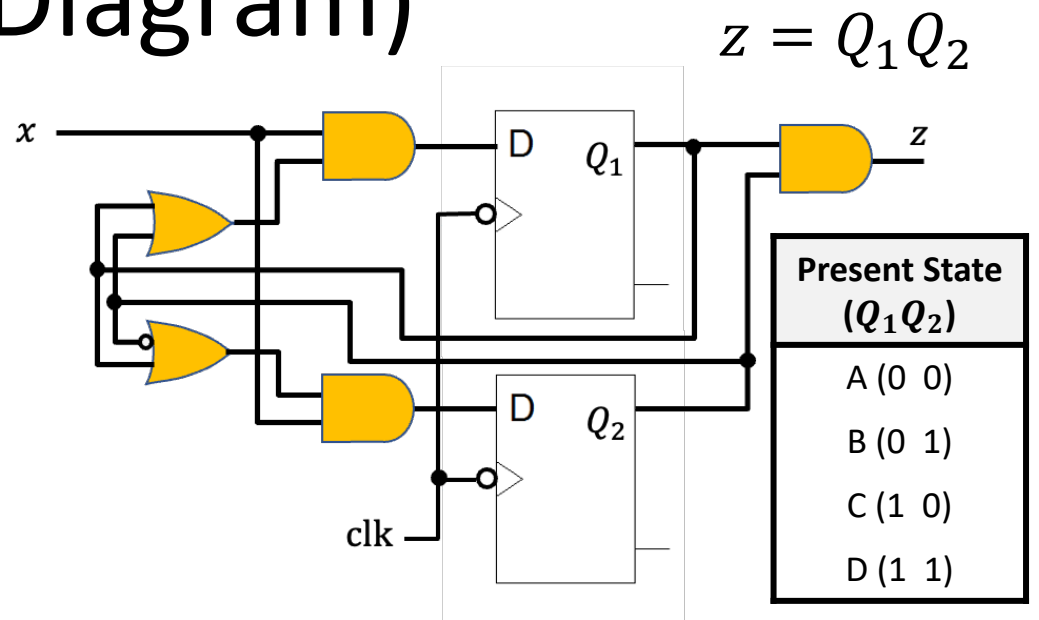 


# Exercise (Timing Diagram)

$$z = xQ_1$$

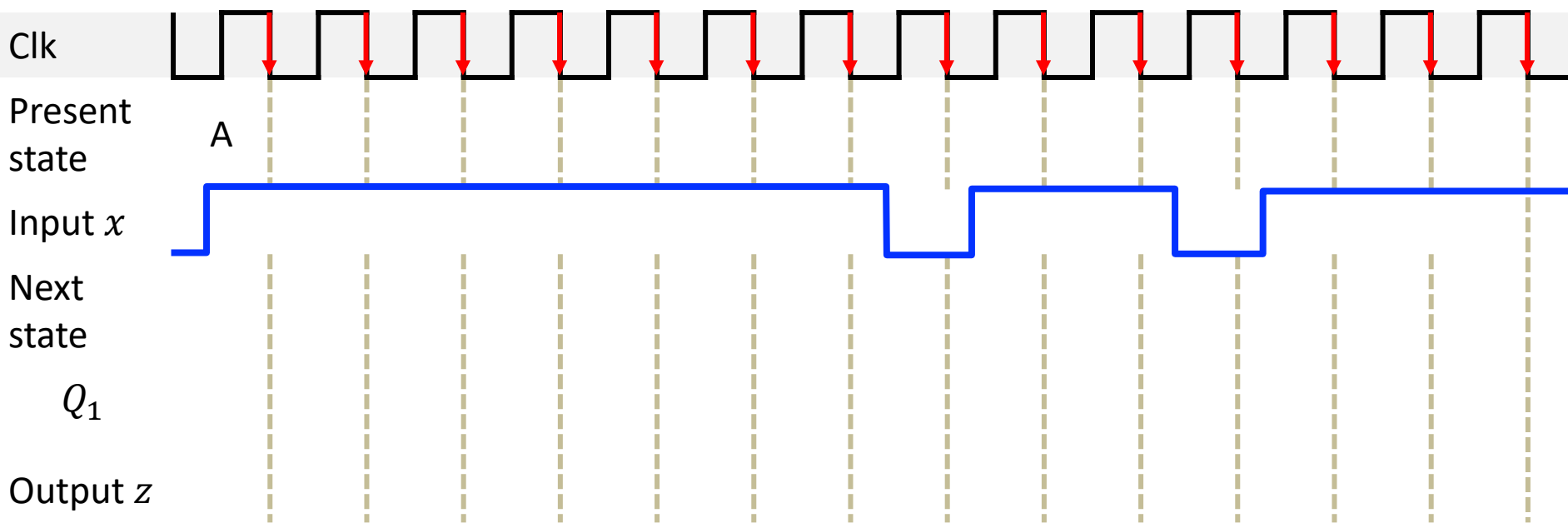  

# Mealy vs Moore Machines

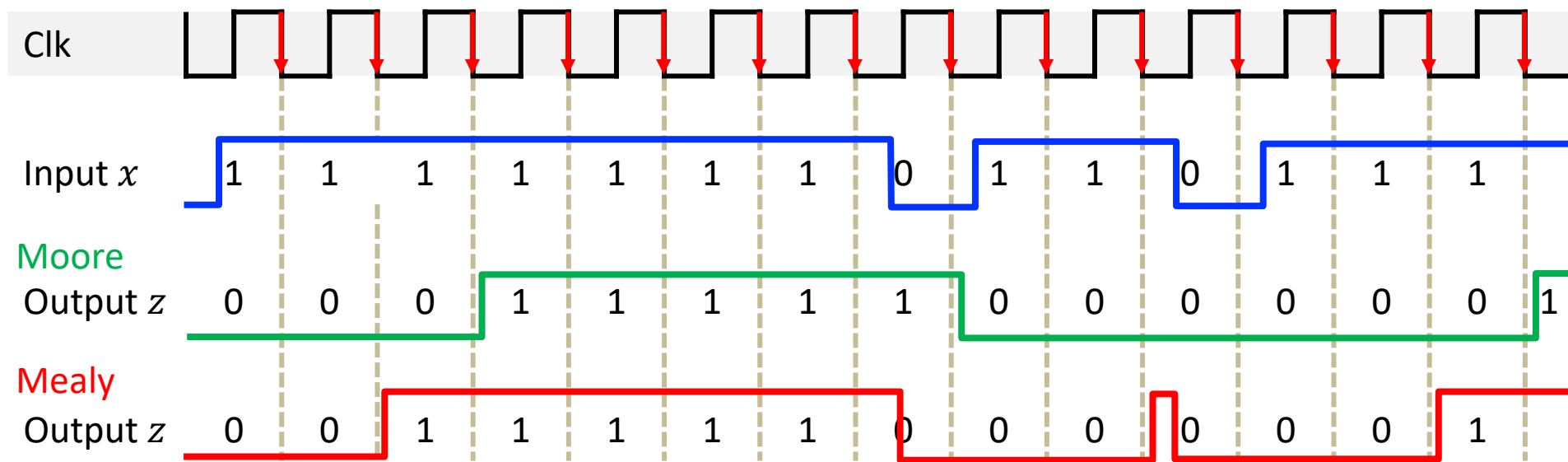

## Observation


- Moore: Output changes occur only after clk edge
- Mealy: Output changes occur whenever input changes
- Mealy: Faster response but glitch might occurs

# Mealy vs Moore Machines

Mealy machine	Moore machine
Output depends on inputs and present state	Output depends only on present state
Typically fewer states, simpler logic circuits	Typically more states, more complex logic circuits
React faster to inputs	React one clock cycle later
Asynchronous	Synchronous
Glitches might present	No glitch

Better solution?

Synchronous Mealy machine

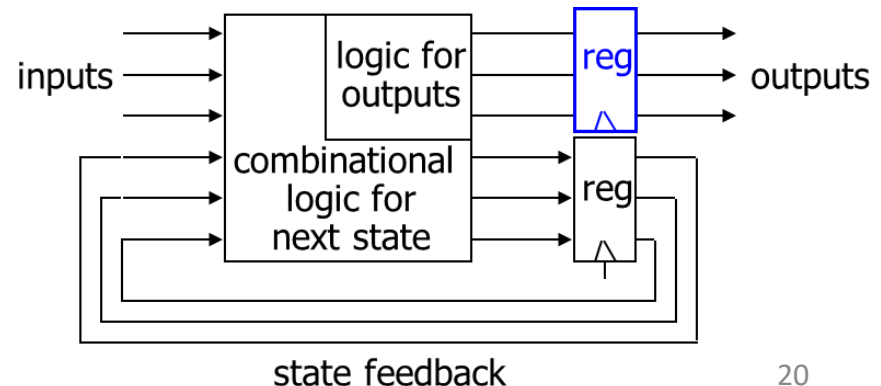

# Exercise (Sequence Detector)

Design a Moore machine to detect the sequence “11” or “000” (Overlapping)

In other words,

Design a system with one input  $x$  and one output  $z$  such that  $z = 1$  if  $x$  has been 1 for at least two consecutive clock times or 0 for at least three consecutive clock times.

$x$	0	0	0	0	1	0	1	1	0	0	1	1	1	0
$z$	?	?	?	1	1	0	0	0	1	0	0	0	1	1

# Exercise (Sequence Detector)

$x$	0	0	0	0	1	0	1	1	0	0	1	1	1	0
$z$	?	?	?	1	1	0	0	0	1	0	0	0	1	1

(Hint: 5 states)

# Exercise (Sequence Detector)

Design a Mealy machine to detect the sequence “00110”  
(No overlapping)

In other words,

Design a system with one input  $x$  and one output  $z$  such that  $z = 1$  if  $x$  has been 0 for two consecutive clock times, follows by two 1's and then a 0.

$x$	0	0	1	1	0	0	1	1	0	0	1	1	0	1
$z$	0	0	0	0	1	0	0	0	0	0	0	0	1	0

# Exercise (Sequence Detector)


$x$	0	0	1	1	0	0	1	1	0	0	1	1	0	1
$z$	0	0	0	0	1	0	0	0	0	0	0	0	1	0

(Hint: 5 states)


 
# State Minimization

- No of FFs  $\propto$  No of states
- Combinational logic complexity  $\propto$  No of states
- More FFs, more complex logic circuits  $\rightarrow$  higher COST!
- Solution: Aims to remove redundant states



# State Minimization

- Direct observation

Identify same output combinations and same state

	0	1
A	A/0	E/1
B	E/1	C/0
C	A/1	D/1
D	F/0	G/1
E	B/1	C/0
F	F/0	E/1
G	A/1	D/1

	0	1
A	A/0	E/1
B	E/1	C/0
C	A/1	D/1
D	F/0	G/1
E	B/1	C/0
F	F/0	E/1
G	A/1	D/1

	0	1
A	A/0	E/1
B	E/1	C/0
C	A/1	D/1
D	F/0	G/1
E	B/1	C/0
F	F/0	E/1
G	A/1	D/1

	0	1
A	A/0	E/1
B	E/1	C/0
C	A/1	D/1
D	F/0	G/1
E	B/1	C/0
F	F/0	E/1
G	A/1	D/1



	0	1
A=F	A/0	B/1
B=E	B/1	C/0
C=G	A/1	D/1
D	A/0	C/1

# Partitioning Method

	0	1
A	A/0	E/1
B	E/1	C/0
C	A/1	D/1
D	F/0	G/1
E	B/1	C/0
F	F/0	E/1
G	A/1	D/1

- Separate states with different outputs to different partitions

$$P_0 = (A \ B \ C \ D \ E \ F \ G)$$

- A, D and F have outputs (0 1); B and E have outputs (1 0); C and G have outputs (1 1)

$$P_1 = (A \ D \ F)(B \ E)(C \ G)$$

# Partitioning Method

P		0	1
1	A	A/0	E/1
	D	F/0	G/1
	F	F/0	E/1
2	B	E/1	C/0
	E	B/1	C/0
3	C	A/1	D/1
	G	A/1	D/1

$$P_1 = (A \ D \ F)(B \ E)(C \ G)$$

- Next check the next state of each state in each partition

$$- A(0) \rightarrow A \ (P1) \quad A(1) \rightarrow E \ (P2)$$

$$- D(0) \rightarrow F \ (P1) \quad D(1) \rightarrow G \ (P3)$$

$$- F(0) \rightarrow F \ (P1) \quad F(1) \rightarrow E \ (P2)$$

$\therefore$  A and F same partitions; D is different

$$P_2 = (A \ F)(D)(B \ E)(C \ G)$$

# Partitioning Method

P		0	1
1	A	A/0	E/1
	F	F/0	E/1
2	B	E/1	C/0
	E	B/1	C/0
3	C	A/1	D/1
	G	A/1	D/1
4	D	F/0	G/1

$$P_2 = (A F)(D)(B E)(C G)$$

This is the final with no more changes!

	I	J
A=F	A/0	B/1
B=E	B/1	C/0
C=G	A/1	D/1
D	A/0	C/1

# Exercise

Present State	Input $X$		Present Output $Z$
	0	1	
A	I	C	0
B	B	I	0
C	C	G	0
D	I	C	1
E	D	E	1
F	I	C	1
G	E	F	1
H	H	A	0
I	A	C	0

Reduce the state table using partitioning method

$$P_0 = (A\ B\ C\ D\ E\ F\ G\ H\ I)$$

Group states based on same output

# Exercise

Present State	Input $X$		Present Output $Z$
	0	1	

Reduce the state table using partitioning method

$$P_1 =$$

# Exercise

Present State	Input <i>X</i>		Present Output <i>Z</i>
	0	1	

Reduce the state table using partitioning method

$$P_2 =$$



# Exercise

Present State	Input <i>X</i>		Present Output <i>Z</i>
	0	1	

Reduce the state table using partitioning method

$P_3 =$


# Exercise

Present State	Input X		Present Output Z
	0	1	


Reduce the state table using partitioning method

$$P_3 =$$


# VHDL for Finite State Machine

 

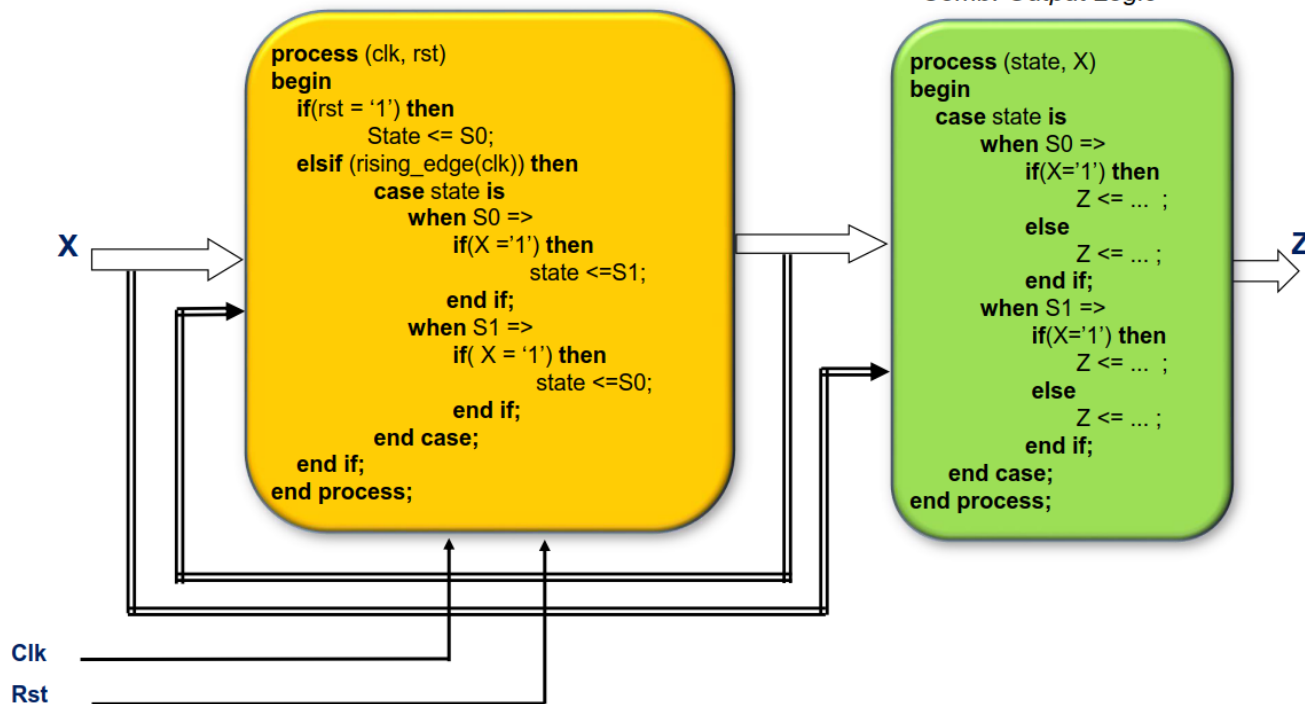*Seq. Present State and Next State Logic*




# Example

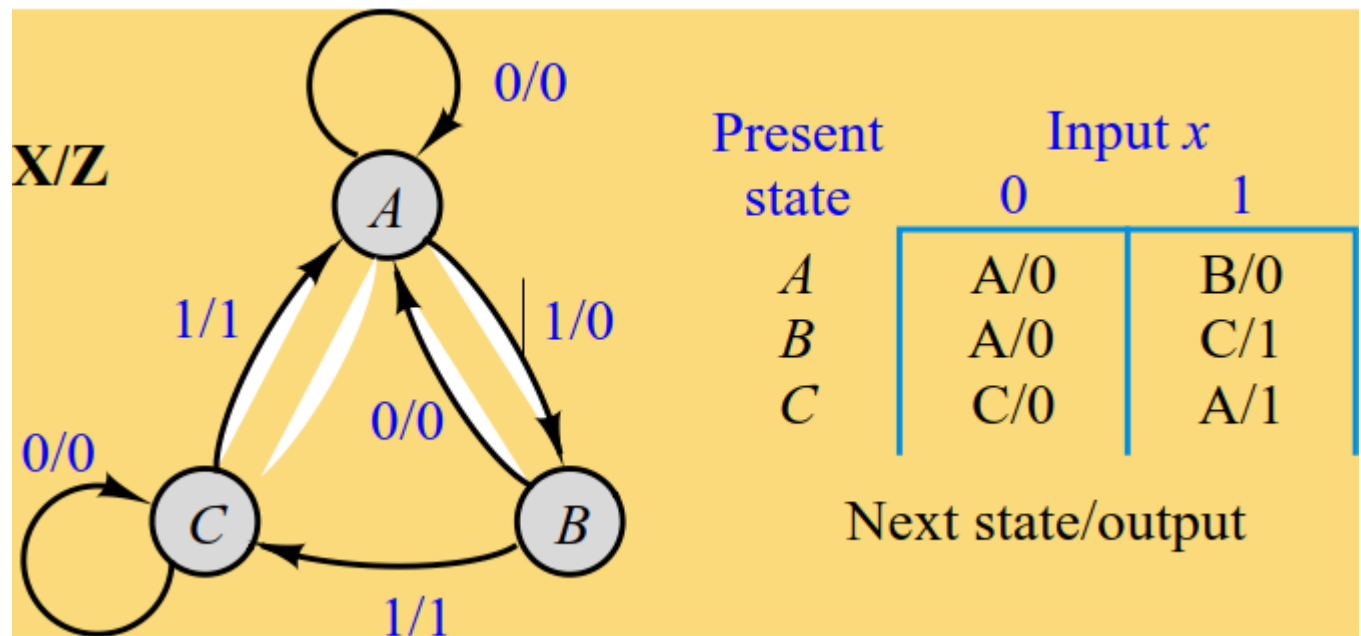

```
entity seqckt is  
port (  
    x: in std_logic; -- FSM input  
    z: out std_logic; -- FSM output  
    clk: in std_logic ); -- clock  
end seqckt;
```

# Output Logic

 

**architecture** behave **of** seqckt **is**

```

type states is (A,B,C);    -- symbolic state names (enumerate)
signal state: states;      --state variable
  
```

Begin

**-- Output Logic**

```


z <= '1' when ((state = B) and (x = '1'))    --all conditions
              or ((state = C) and (x = '1'))  --for which z = 1
              else '0';                       --otherwise z = 0
  
```

# Next State Logic

```


process (clk) - Present & next states logic
begin
  if rising_edge(clk) then -- clock edge
    case state is
      when A => if (x = '0') then
        state <= A;
      else
        state <= B; -- x = '1'
      end if;
      when B => if (x='0') then
        state <= A;
      else
        state <= C; -- x = '1'
      end if;
      when C => if (x='0') then
        state <= C;
      else
        state <= A; -- x = '1'
      end if;
    end case;
  end if;
end process;
end behave;

```

 
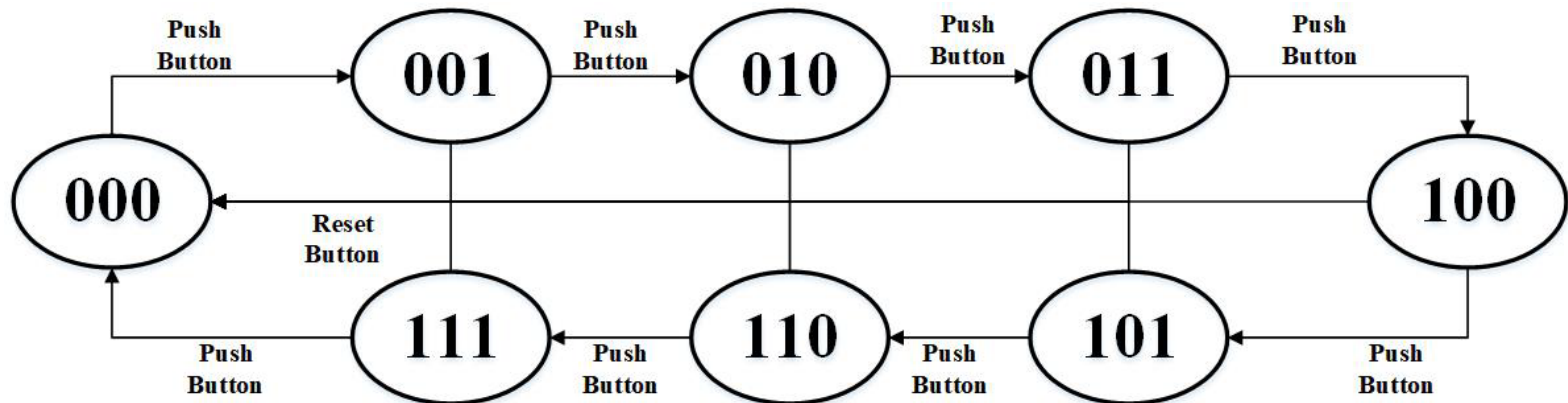
# Lab Session 4

- Implement a **simple finite-state machine** with a good coding style
- Implement **two buttons** to control the state change of the FSM
- Display the state transition with the **LEDs** on the BASYS3 board



# VHDL Codes

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity fsm is
Port (
clk: in STD_LOGIC;
rst: in STD_LOGIC;
ctrlButton: in STD_LOGIC;
led: out STD_LOGIC_VECTOR (7 DOWNTO 0)
);
end fsm;
```

## Inputs

- clock signal (clk)
- Master reset button (rst)
- Control button (ctrlButton)


## Output

- 8 LEDS for 8 states


 
# Key Debouncing

When pressing a key or switch, its internal spring may cause the contact point to vibrate for a short period of time, causing a series of “ON” and “OFF” state before settling down



## Inputs

- clock signal (clk)
- Master reset button (rst)
- **Control button (ctrlButton)**

## Output

- 8 LEDS for 8 states

# VHDL Codes

Constant TIME\_10ms: integer := 1000000;

Signal key\_counter: integer range 0 to 1000001;

Signal btnDetection: boolean;

begin

Key\_detection: process (clk) begin

if rising\_edge(clk) then

if (ctrlButton='1') then

key\_counter <= 0;

elsif (ctrlButton='0') and (key\_counter <= TIME\_10MS) then

key\_counter <= key\_counter + 1;

end if; end if;

end process;

btnDetection <= (key\_counter = TIME\_10ms);

When control button is pushed, **key\_counter** will set to 0. Then, the timer will start counting and if the stable time reach to **TIME\_10ms**, **btnDetection** sets to true for that cycle.

# VHDL Codes

## Internal signals


- data types: states
- present\_state
- next\_state

Architecture Behavioral of fsm is

```
type states is (zero, one, two, three, four, five, six, seven);
```

```
signal present_state, next_state: states;
```

# VHDL Codes

 

The sequential logic of our FSM is very simple. Every time the *btnDetection* is true, the FSM will jump to the next state. We define a type called *states* enumerating all possible states. Then we define two signals *present\_state* and *next\_state* which are both *states* type. Every time the *btnDetection* is true, the value of *next\_state* will be provided to *present\_state* (meaning the state jumps to the next state). The assignment of *next\_state* will be introduced in the next section

```
state_transition: process (rst, clk)
begin
    if (rst='1') then
        --Write your code here to describe state transition.
    elsif (rising_edge(clk) and btnDetection = true ) then
        --Write your code here to describe state transition.
    end if;
end process;
```

# VHDL Codes

present_state	LED Output
zero	00000001
one	00000010
two	00000100

three	00001000
four	00010000
five	00100000
six	01000000
seven	10000000

The corresponding VHDL template and you can complete the following code.

```
decoder: process (present_state)
begin
    case present_state is
        --Write your code here to assign LED and next_state
    end case;
end process;
end Behavioral;
```