

# EE2000 Logic Circuit Design

---

## Lecture 5 – Combinational Functional Blocks



# What will you learn?

5.1 What is an equality comparator and how to implement it using a modular design

5.2 Learn various arithmetic functional blocks

- Half adder, Full adder, Ripple carry adder
- Half and Full subtractors, Ripple borrow subtractor
- Carry-look-ahead adder

5.3 Learn various logical functional blocks

- Decoder
- Encoder
- Multiplexer
- Demultiplexer

# 5.1 Equality Comparator

- A circuit to compare two binary numbers to determine whether they are equal or not
- The inputs consist of two variables:  $A$  and  $B$
- The output of the circuit is a variable  $E$
- $E$  is equal to 1 if  $A$  and  $B$  are equal
- $E$  is equal to 0 if  $A$  and  $B$  are different

# 1-bit Equality Comparator

## ■ Formulation:

Inputs		Output
$A_0$	$B_0$	$E$
0	0	1
0	1	0
1	0	0
1	1	1


## ■ Optimization:

■  $E(A_0, B_0) = \sum m(0, 3)$


■  $= A_0' B_0' + A_0 B_0$

■  $= A_0 \otimes B_0$

## ■ Final logic diagram:

 

or

 

# 2-bit Equality Comparator

Inputs				Output
$A_1$	$A_0$	$B_1$	$B_0$	$E$
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

$$\begin{aligned}E(A_1, A_0, B_1, B_0) &= \sum m(0, 5, 10, 15) \\&= A_1'A_0'B_1'B_0' + \\&A_1'A_0B_1'B_0 + A_1A_0'B_1B_0' \\&+ A_1A_0B_1B_0\end{aligned}$$

# 4-bit Equality Comparator

## ■ Formulation:

- How many inputs?
- How many outputs?
- How many rows?

## Problem:

Not easy to design

Difficult in simplification

K-map? QM ?

## Solution:


Modular design

Functional circuit blocks

Inputs								Output
$A_3$	$A_2$	$A_1$	$A_0$	$B_3$	$B_2$	$B_1$	$B_0$	$E$
0	0	0	0	0	0	0	0	1
0	0	0	0	0	0	0	1	0
0	0	0	0	0	0	1	0	0
0	0	0	0	0	0	1	1	0
0	0	0	0	0	1	0	0	0
0	0	0	0	0	1	0	1	0
0	0	0	0	0	1	1	0	0
0	0	0	0	0	1	1	1	0
0	0	0	0	1	0	0	0	0
0	0	0	0	1	0	0	1	0
0	0	0	0	1	0	1	0	0
0	0	0	0	1	0	1	1	0
0	0	0	0	1	1	0	0	0
1	1	1	1	1	1	1	1	1
 
# Modular Design

- Modular design
  - Decompose the problem into four 1-bit comparison
  - Compare bit by bit, then combine all results
- Logic diagram



Functional Blocks:



1-bit Comparator Block




Equality Block

# Modular Design
 
## ■ 1-bit Comparator Block


- The output is 1 if the inputs are the same
- The output is 0 if the inputs are different
- i.e. 1-bit equality comparator  $N_i = A_i \oplus B_i$


 
## ■ Equality Block

- The output  $E$  is 1 if all  $N_i$  values are 1
- The output  $E$  is 0 if not all  $N_i$  values are 1


■  $E = N_3 \cdot N_2 \cdot N_1 \cdot N_0$






# Modular Design


- Final logic diagram

 


Functional Blocks:

 

Block X:

 

Block Y:

 

# Summary

- Instead of designing a complex  $n$ -bit equality comparator circuit
- Design only a 1-bit comparator block and a simple equality block
- Re-use the 1-bit comparator block for  $n$  times
- Reusable small circuits are called **combinational functional blocks**

## 5.2 Arithmetic Functional Blocks

- Special class of functional blocks that perform arithmetic operations
- Operate on binary numbers (input) and produce binary numbers (output)
- Each bit position has the same **sub-function**
- Design a **functional block** for the **sub-function** and use **repeatedly** for each bit position
- Example arithmetic functional blocks
  - Adders, subtractors

# Addition

■ Compute the sum of  $(0110)_2$  and  $(0111)_2$

■  $(0110)_2 = (6)_{10}$

■  $(0111)_2 = (7)_{10}$

Carries		0		1 0		1 1 0		1 1 0		
Augend		0	1	1	0	0	1	1	0	
Addend		+	0	1	1	+	0	1	1	1
Sum										

Sum the LSBs first:  $0 + 1 = 1$

Sum the 2<sup>nd</sup> LSBs and the carry bit:  $0 + (1 + 1) = 0 + 10 = 10$

The final result is  $1101_2$  ( $13_{10}$ )

# Half Adder (1-bit Adder)

Operation: 1-bit binary addition (the addition of two numbers,  $x$  and  $y$ )

Inputs:  $x$  and  $y$

Outputs:  $s$  (sum) and  $c$  (carry-out)

0 $x$			
(+)	0	$y$	
<hr/>			
	0	0	
	$c$	$s$	

0 $x$			
(+)	1	$y$	
<hr/>			
	0	1	
	$c$	$s$	


1 $x$			
(+)	0	$y$	
<hr/>			
	0	1	
	$c$	$s$	

1 $x$			
(+)	1	$y$	
<hr/>			
	1	0	
	$c$	$s$	

Inputs		Outputs	
$x$	$y$	$c$	$s$
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$s = x \oplus y$$

$$c = x \cdot y = xy$$

 

# Full Adder

Operation: 1-bit binary addition (the addition of two numbers,  $x$  and  $y$ ; and a carry-in bit,  $c_{in}$ )

Inputs:  $x$ ,  $y$  and  $c_{in}$       Outputs:  $s$  (sum) and  $c_o$  (carry-out)

$\begin{array}{r} 0 \ x \\ 0 \ y \\ (+) \ 0 \ c_{in} \\ \hline 0 \ 0 \\ c_o \ s \end{array}$	$\begin{array}{r} 0 \ x \\ 1 \ y \\ (+) \ 0 \ c_{in} \\ \hline 0 \ 1 \\ c_o \ s \end{array}$	$\begin{array}{r} 1 \ x \\ 0 \ y \\ (+) \ 0 \ c_{in} \\ \hline 0 \ 1 \\ c_o \ s \end{array}$	$\begin{array}{r} 1 \ x \\ 1 \ y \\ (+) \ 0 \ c_{in} \\ \hline 1 \ 0 \\ c_o \ s \end{array}$
$\begin{array}{r} 0 \ x \\ 0 \ y \\ (+) \ 1 \ c_{in} \\ \hline 0 \ 1 \\ c_o \ s \end{array}$	$\begin{array}{r} 0 \ x \\ 1 \ y \\ (+) \ 1 \ c_{in} \\ \hline 1 \ 0 \\ c_o \ s \end{array}$	$\begin{array}{r} 1 \ x \\ 0 \ y \\ (+) \ 1 \ c_{in} \\ \hline 1 \ 0 \\ c_o \ s \end{array}$	$\begin{array}{r} 1 \ x \\ 1 \ y \\ (+) \ 1 \ c_{in} \\ \hline 1 \ 1 \\ c_o \ s \end{array}$

Inputs			Outputs	
$x$	$y$	$c_{in}$	$c_o$	$s$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

# Example

$\begin{array}{r} 0 \ x \\ 0 \ y \\ (+) \ 0 \ c_{in} \\ \hline 0 \ 0 \\ c_o \ s \end{array}$	$\begin{array}{r} 0 \ x \\ 1 \ y \\ (+) \ 0 \ c_{in} \\ \hline 0 \ 1 \\ c_o \ s \end{array}$	$\begin{array}{r} 1 \ x \\ 0 \ y \\ (+) \ 0 \ c_{in} \\ \hline 0 \ 1 \\ c_o \ s \end{array}$	$\begin{array}{r} 1 \ x \\ 1 \ y \\ (+) \ 0 \ c_{in} \\ \hline 1 \ 0 \\ c_o \ s \end{array}$
$\begin{array}{r} 0 \ x \\ 0 \ y \\ (+) \ 1 \ c_{in} \\ \hline 0 \ 1 \\ c_o \ s \end{array}$	$\begin{array}{r} 0 \ x \\ 1 \ y \\ (+) \ 1 \ c_{in} \\ \hline 1 \ 0 \\ c_o \ s \end{array}$	$\begin{array}{r} 1 \ x \\ 0 \ y \\ (+) \ 1 \ c_{in} \\ \hline 1 \ 0 \\ c_o \ s \end{array}$	$\begin{array}{r} 1 \ x \\ 1 \ y \\ (+) \ 1 \ c_{in} \\ \hline 1 \ 1 \\ c_o \ s \end{array}$

Inputs			Outputs	
$x$	$y$	$c_{in}$	$c_o$	$s$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

- Work out the algebraic functions of  $s$  and  $c_o$  using K-map
- Draw the logic circuit diagram of full adder

	$c$	$ab$	00	01	11	10
0		$m_0$	$m_2$	$m_6$	$m_4$	
1		$m_1$	$m_3$	$m_7$	$m_5$	

# Example

$c_o$		$c_{in}$			
		$xy$			
		00	01	11	10
$c_{in}$	0			1	
	1		1	1	1

$$\begin{aligned}
 c_o &= xy + xc_{in} + yc_{in} = xy + c_{in}(x + y) \\
 &= xy + c_{in}(xy' + x'y + xy) \\
 &= xy(1 + c_{in}) + c_{in}(xy' + x'y) \\
 &= xy + c_{in}(x \oplus y)
 \end{aligned}$$

$s$		$c_{in}$			
		$xy$			
		00	01	11	10
$c_{in}$	0		1		1
	1	1		1	


$$\begin{aligned}
 s &= x'y'c_{in} + xyc_{in} + x'y'c'_{in} + xy'c'_{in} \\
 &= c_{in}(x'y' + xy) + c'_{in}(x'y + xy') \\
 &= c_{in}(x \oplus y)' + c'_{in}(x \oplus y) \\
 &= c_{in} \oplus (x \oplus y)
 \end{aligned}$$



# Example


c \ ab	00	01	11	10
	0	1	1	0
0	$m_0$	$m_2$	$m_6$	$m_4$
1	$m_1$	$m_3$	$m_7$	$m_5$
 
$$c_o = xy + c_{in}(x \oplus y) \quad s = c_{in} \oplus (x \oplus y)$$




# Half Adder and Full Adder


■ Logic circuit diagram

 


■ Logic circuit diagram

 

■ Symbol

 


■ Symbol

 

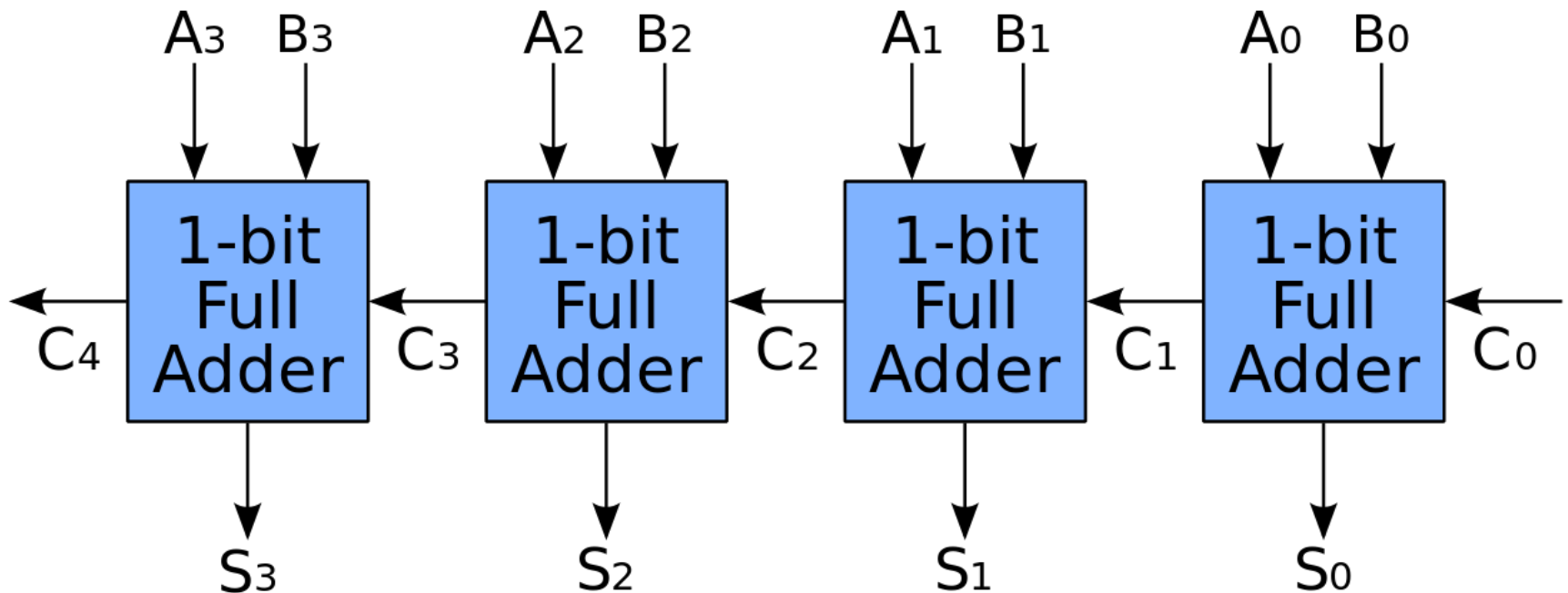
# Ripple Carry Adder

- Connect  $n$  1-bit adders to build an  $n$ -bit adder



# Example (0011 + 1011)

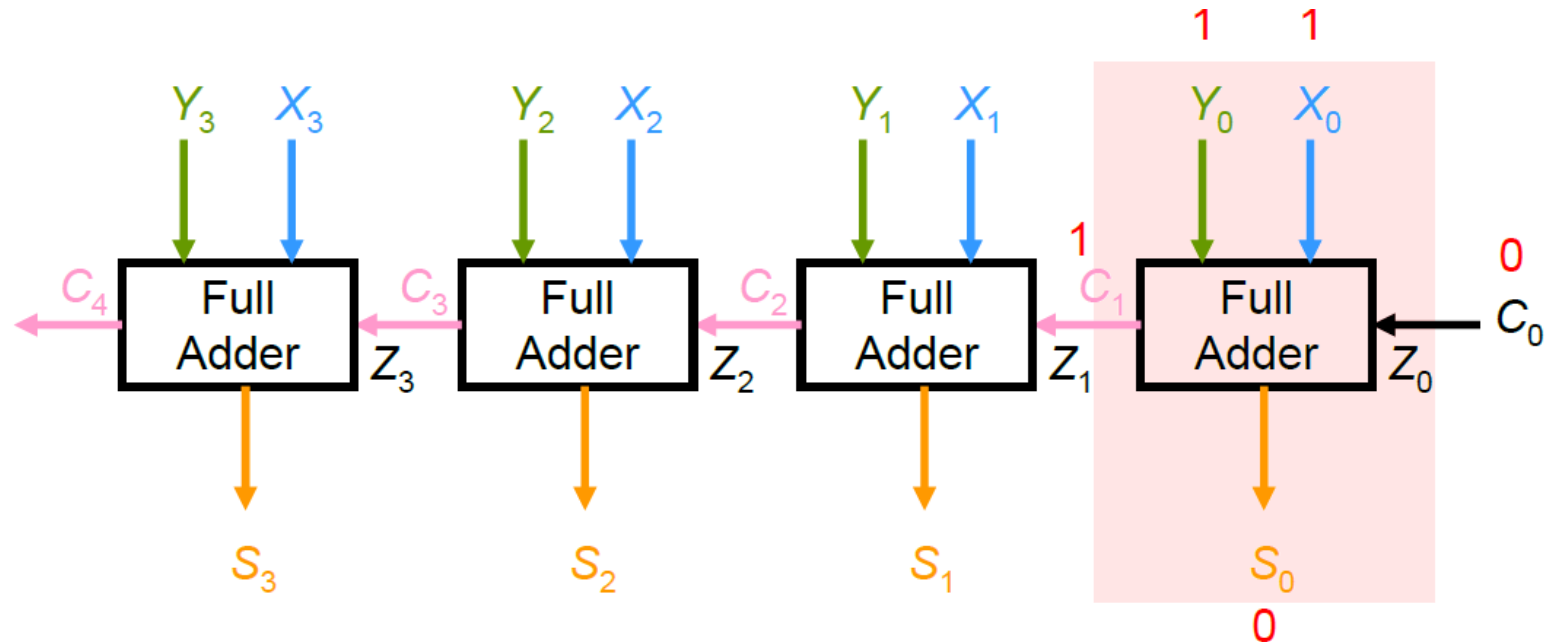


Carry-in ( $Z_i$ )

Augend ( $X_i$ )

Addend ( $Y_i$ )


Sum ( $S_i$ )

Carry-out ( $C_i$ )

 

Carry out connect to the carry input of next full adder

# Example

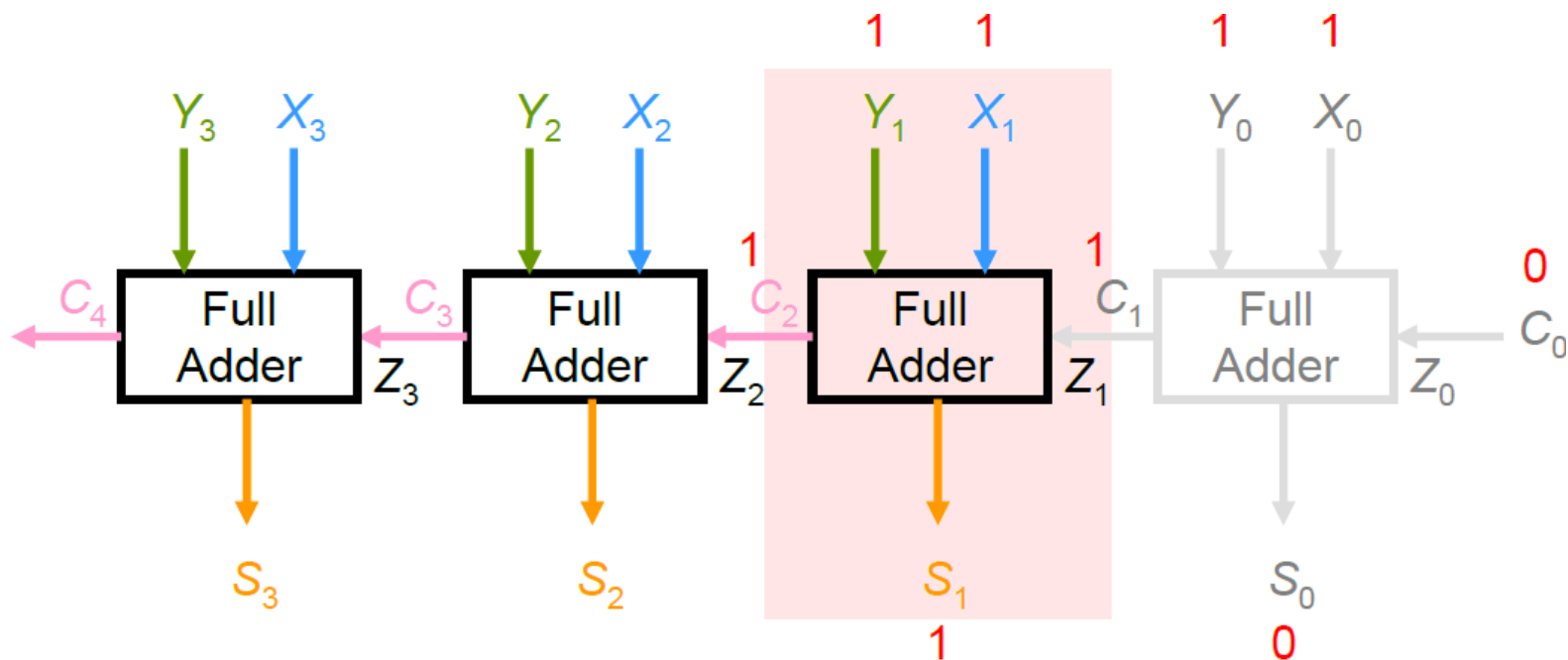


Carry-in ( $Z_i$ )

Augend ( $X_i$ )


Addend ( $Y_i$ )

Sum ( $S_i$ )


Carry-out ( $C_i$ )

 

# Example

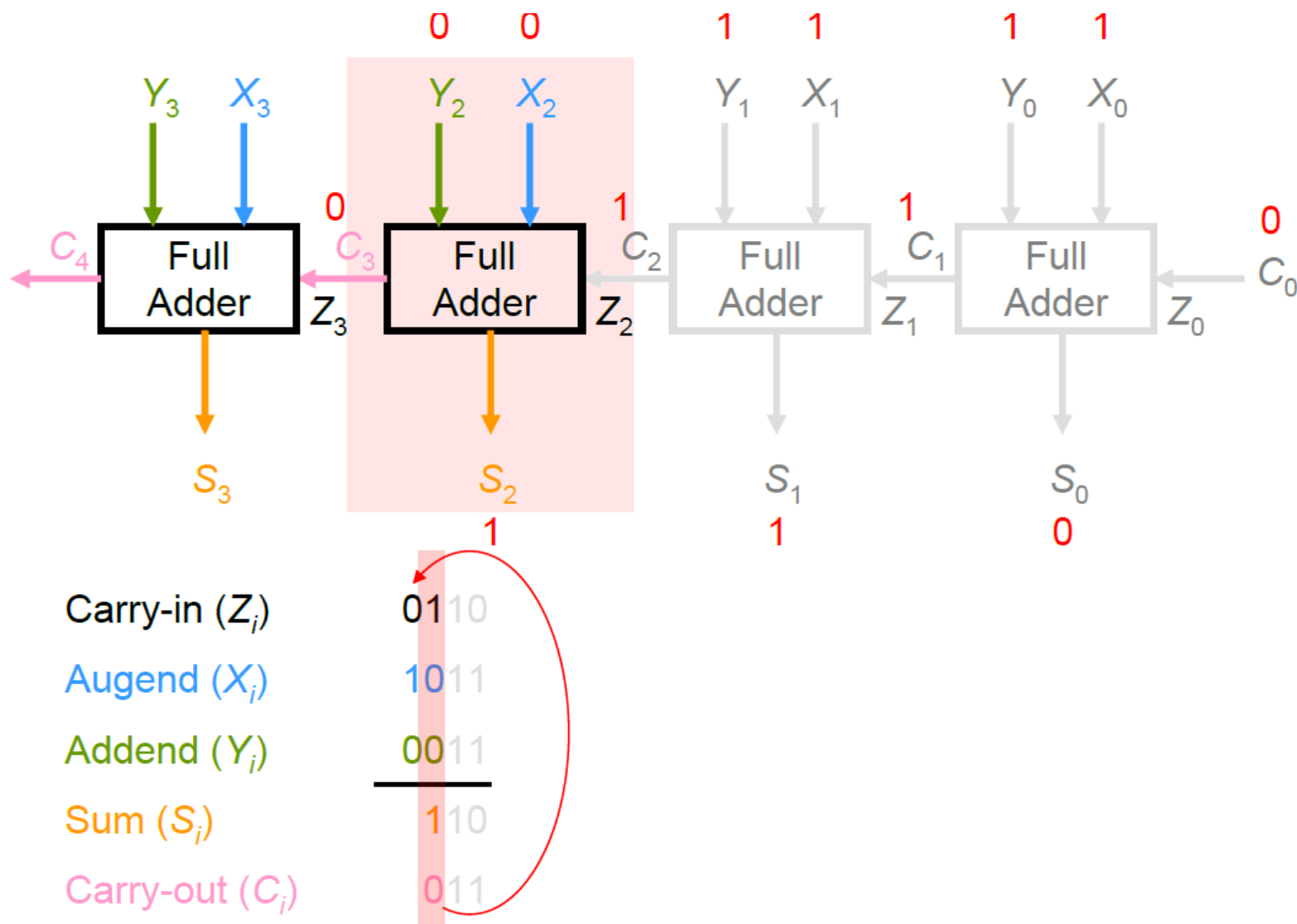

# Example

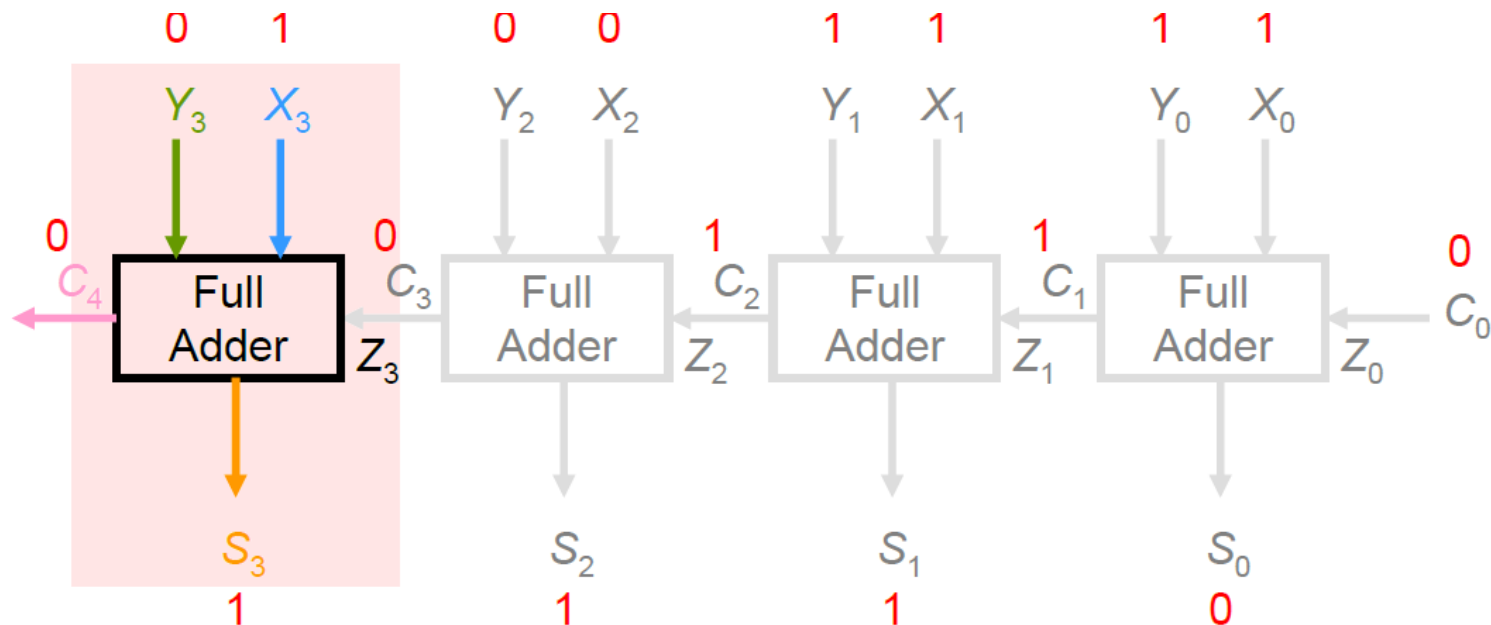

Carry-in ( $Z_i$ )

Augend ( $X_i$ )

Addend ( $Y_i$ )

Sum ( $S_i$ )

Carry-out ( $C_i$ )


0110

1011

0011

1110

0011

 

# HA vs FA vs RCA

Augend (X)		1
Addend (Y)	+) 0	
		<hr/>
Sum (S)		1

HA: performs simple two single-bit addition

Carry-in ( $Z_i$ )		0
Augend ( $X_i$ )		1
Addend ( $Y_i$ )	+) 1	
		<hr/>
Sum ( $S_i$ )		0

FA: performs simple three single-bit addition

Carry-in ( $Z_i$ )		0	1	1	0
Augend ( $X_i$ )		1	0	1	1
Addend ( $Y_i$ )	+) 0	0	1	1	
		<hr/>			
Sum ( $S_i$ )		1	1	1	0

RCA: performs real two  $n$ -bit addition



# Subtractors

$$\begin{array}{r} \text{Minuend (X)} \quad 1 \\ \text{Subtrahend (Y) } -) \quad 0 \\ \hline \text{Difference (D)} \quad 1 \end{array}$$

Half Subtractor:  
perform simple two  
single-bit subtraction

$$\begin{array}{r} \text{Borrow-in (Z}_i\text{)} \quad 0 \\ \text{Minuend (X}_i\text{)} \quad 1 \\ \text{Subtrahend (Y}_i\text{) } -) \quad 1 \\ \hline \text{Difference (D}_i\text{)} \quad 0 \end{array}$$

Full Subtractor:  
perform simple three  
single-bit subtraction

$$\begin{array}{r} \text{Borrow-in (Z}_i\text{)} \quad ? \ ? \ ? \ ? \\ \text{Minuend (X}_i\text{)} \quad 1 \ 0 \ 1 \ 1 \\ \text{Subtrahend (Y}_i\text{) } -) \ 0 \ 0 \ 1 \ 1 \\ \hline \text{Difference (D}_i\text{)} \quad ? \ ? \ ? \ ? \end{array}$$

Ripple Borrow Subtractor:  
perform real two *n*-bit  
subtraction

# Half Subtractor

Operation: 1-bit binary subtraction ( $x - y$ )

Inputs:  $x$  and  $y$       Outputs:  $d$  (difference) and  $b$  (Borrow-out)

$b$	0	0	$x$	$b$	1	0	$x$
(-)		0	$y$	(-)		1	$y$
<hr/>				<hr/>			
		0				1	
		$d$				$d$	


  

$b$	0	1	$x$	$b$	0	1	$x$
(-)		0	$y$	(-)		1	$y$
<hr/>				<hr/>			
		1				0	
		$d$				$d$	

Inputs		Outputs	
$x$	$y$	$b$	$d$
0	0	0	0
0	1	1	1
1	0	0	1
1	1	0	0

$$d = x \oplus y$$

$$b = x' \cdot y = x'y$$

 

# Full Subtractor

Operation: 1-bit binary subtraction ( $x - y - b_{in}$ )

Inputs:  $x$ ,  $y$  and  $b_{in}$       Outputs:  $d$  and  $b_o$

$b_o$ 0 0 $x$ (-) 0 $y$ (-) 0 $b_{in}$ <hr/> 0 $d$	$b_o$ 1 0 $x$ (-) 1 $y$ (-) 0 $b_{in}$ <hr/> 1 $d$	$b_o$ 0 1 $x$ (-) 0 $y$ (-) 0 $b_{in}$ <hr/> 1 $d$	$b_o$ 0 1 $x$ (-) 1 $y$ (-) 0 $b_{in}$ <hr/> 0 $d$
$b_o$ 1 0 $x$ (-) 0 $y$ (-) 1 $b_{in}$ <hr/> 1 $d$	$b_o$ 1 0 $x$ (-) 1 $y$ (-) 1 $b_{in}$ <hr/> 0 $d$	$b_o$ 0 1 $x$ (-) 0 $y$ (-) 1 $b_{in}$ <hr/> 0 $d$	$b_o$ 1 1 $x$ (-) 1 $y$ (-) 1 $b_{in}$ <hr/> 1 $d$

Inputs			Outputs	
$x$	$y$	$b_{in}$	$b_o$	$d$
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	1	0
1	0	0	0	1
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

# Exercise

$\begin{array}{rrrr} b_o & 0 & 0 & x \\ (-) & & 0 & y \\ (-) & & 0 & b_{in} \\ \hline & 0 & & \\ & d & & \end{array}$	$\begin{array}{rrrr} b_o & 1 & 0 & x \\ (-) & & 1 & y \\ (-) & & 0 & b_{in} \\ \hline & 1 & & \\ & d & & \end{array}$	$\begin{array}{rrrr} b_o & 0 & 1 & x \\ (-) & & 0 & y \\ (-) & & 0 & b_{in} \\ \hline & 1 & & \\ & d & & \end{array}$	$\begin{array}{rrrr} b_o & 0 & 1 & x \\ (-) & & 1 & y \\ (-) & & 0 & b_{in} \\ \hline & 0 & & \\ & d & & \end{array}$
$\begin{array}{rrrr} b_o & 1 & 0 & x \\ (-) & & 0 & y \\ (-) & & 1 & b_{in} \\ \hline & 1 & & \\ & d & & \end{array}$	$\begin{array}{rrrr} b_o & 1 & 0 & x \\ (-) & & 1 & y \\ (-) & & 1 & b_{in} \\ \hline & 0 & & \\ & d & & \end{array}$	$\begin{array}{rrrr} b_o & 0 & 1 & x \\ (-) & & 0 & y \\ (-) & & 1 & b_{in} \\ \hline & 0 & & \\ & d & & \end{array}$	$\begin{array}{rrrr} b_o & 1 & 1 & x \\ (-) & & 1 & y \\ (-) & & 1 & b_{in} \\ \hline & 1 & & \\ & d & & \end{array}$

Inputs			Outputs	
$x$	$y$	$b_{in}$	$b_o$	$d$
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	1	0
1	0	0	0	1
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

- Work out the algebraic functions of  $d$  and  $b_o$  using K-map
- Draw the logic circuit diagram of full subtractor

	$ab$	00	01	11	10
0		$m_0$	$m_2$	$m_6$	$m_4$
1		$m_1$	$m_3$	$m_7$	$m_5$

# Exercise

		<i>ab</i>			
<i>c</i>		00	01	11	10
	0	$m_0$	$m_2$	$m_6$	$m_4$
	1	$m_1$	$m_3$	$m_7$	$m_5$

		<i>xy</i>			
$b_o$	$b_{in}$	00	01	11	10
	0		1		
	1	1	1	1	

$$b_o = x'y + x'b_{in} + yb_{in}$$

		<i>xy</i>			
$d$	$b_{in}$	00	01	11	10
	0		1		1
	1	1		1	

$$d = x'y'b_{in} + xyb_{in} + x'yb'_{in} + xy'b'_{in}$$

# Exercise

		<i>ab</i>			
		00	01	11	10
<i>c</i>	0	$m_0$	$m_2$	$m_6$	$m_4$
	1	$m_1$	$m_3$	$m_7$	$m_5$

$x$

$y$


$d$

$b_{in}$


$b_o$
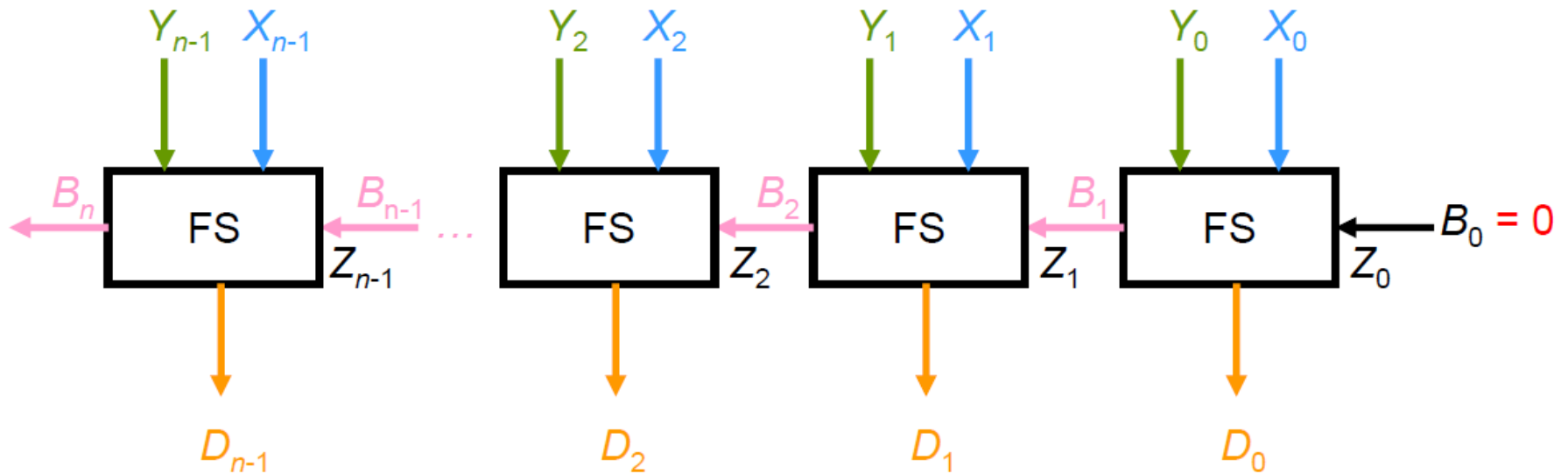
# Ripple Borrow Subtractor

- Connect  $n$  1-bit subtractors to build an  $n$ -bit subtractor



# Propagation Delay in RCA

 

$$c_{out} = xy + c_{in}(x \oplus y)$$

$$s = c_{in} \oplus (x \oplus y)$$

- The carry output of each full-adder stage is connected to the carry input of the next stage
- Assume that the delay for generating the carry output is  $\Delta\tau$ , for  $n$ -bit adder, the total delay is  $n \Delta\tau$
- Serious delay problem if  $n$  is a large number
- **Solution:** Calculate the carry bits beforehand, then construct the carry-look-ahead adder



# Carry Bits Calculation


- $G_i$  is defined as the generate bit

$$G_i = x_i y_i$$

- $P_i$  is defined as the propagate bit

$$P_i = x_i \oplus y_i$$

$$c_{out} = xy + c_{in}(x \oplus y)$$

 


$$c_i = x_{i-1}y_{i-1} + c_{i-1}(x_{i-1} \oplus y_{i-1}) = G_{i-1} + c_{i-1}(P_{i-1})$$

$i$	$G_i$	$P_i$	$c_i$
0	$G_0 = x_0 y_0$	$P_0 = (x_0 \oplus y_0)$	$c_0$
1	$G_1 = x_1 y_1$	$P_1 = (x_1 \oplus y_1)$	$c_1 = G_0 + c_0 P_0$
2	$G_2 = x_2 y_2$	$P_2 = (x_2 \oplus y_2)$	$c_2 = G_1 + c_1 P_1 = G_1 + P_1 (G_0 + c_0 P_0)$ $= G_1 + P_1 G_0 + c_0 P_0 P_1$
3	$G_3 = x_3 y_3$	$P_3 = (x_3 \oplus y_3)$	$c_3 = G_2 + c_2 P_2 = G_2 + P_2 G_1 + P_2 P_1 G_0 + c_0 P_0 P_1 P_2$

# 4-Bit Carry-Look-Ahead Adder


Carry-look-ahead Generator

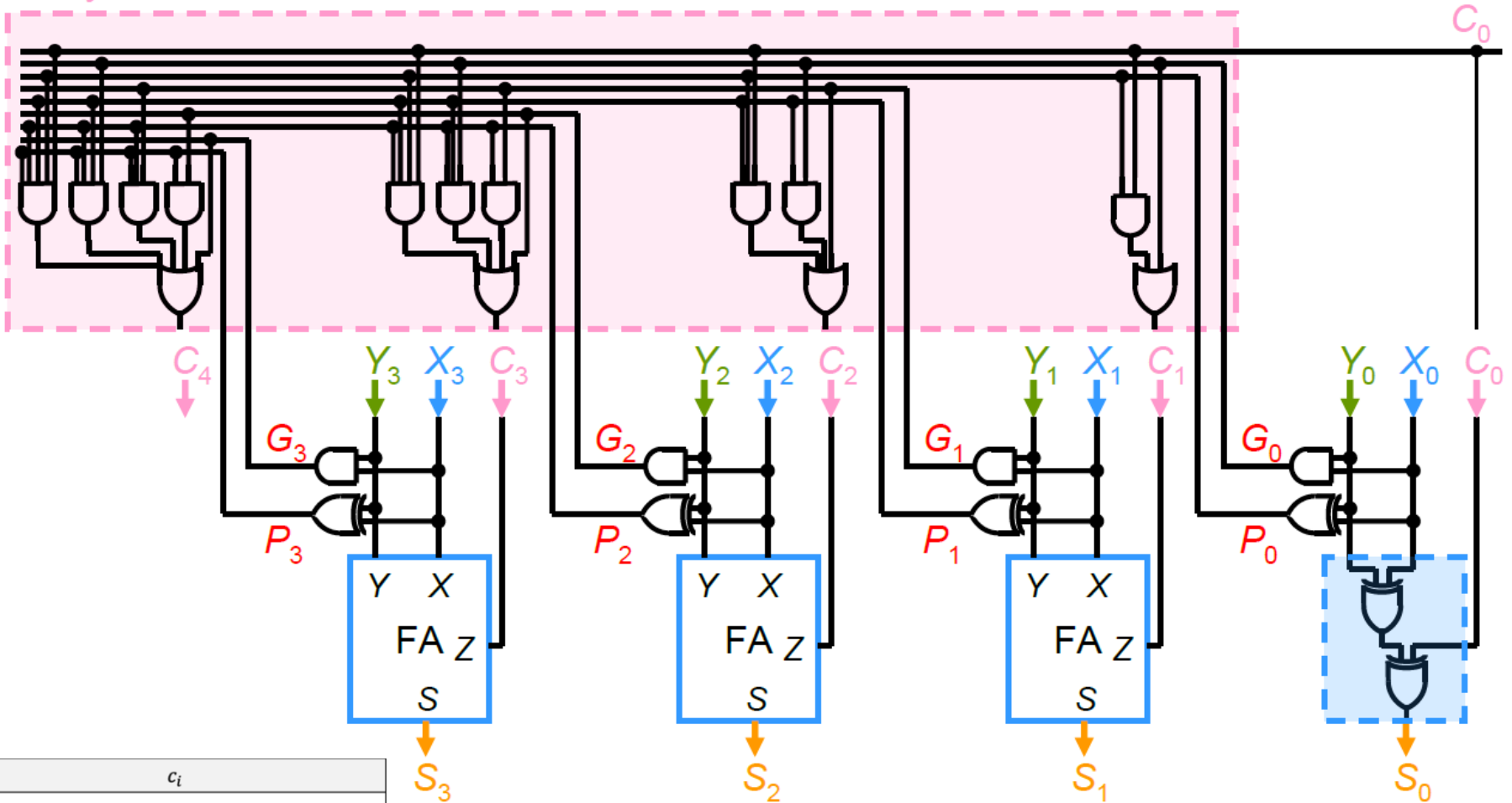

$c_i$
$c_0$
$G_0 + c_0 P_0$
$G_1 + c_1 P_1 = G_1 + P_1 (G_0 + c_0 P_0)$ $= G_1 + P_1 G_0 + c_0 P_0 P_1$
$G_2 + c_2 P_2 = G_2 + P_2 G_1 + P_2 P_1 G_0 + c_0 P_0 P_1 P_2$

$$s = c_{in} \oplus (x \oplus y)$$


# Summary

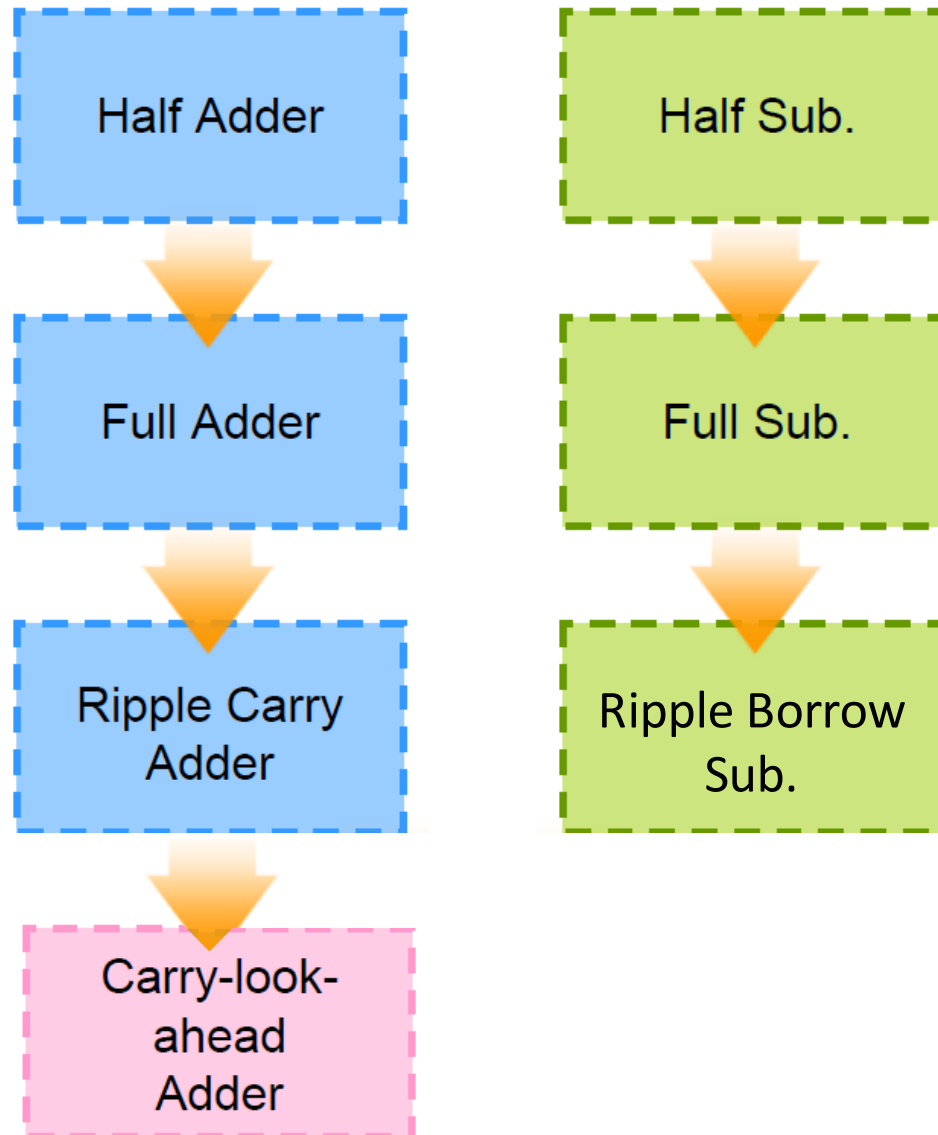

# 5.3 Logical Functional Blocks
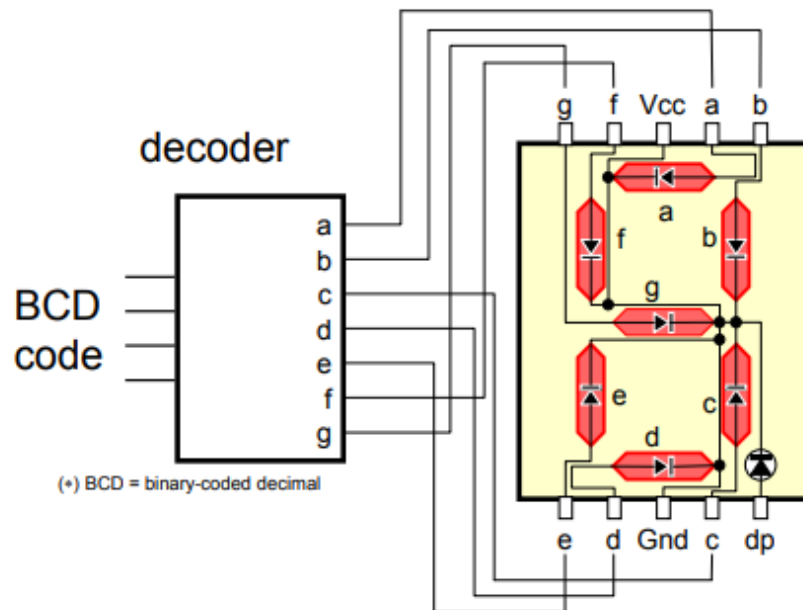
## Decoder


- A decoder is a combinational circuit that converts coded inputs into coded outputs.
- Each input produces a different output (1-to-1 mapping)




# Binary Decoder

- Accept an  $n$ -bit binary input code and activate only one of the  $2^n$  outputs
- Outputs  $m \leq 2^n$ , but usually  $m = 2^n$
- A very important functional blocks.
  - Select different banks of memory
  - Select different devices
  - Enable different functional units
  - ...

e.g. Input  $A = (0 \dots 00)$

 

e.g. Input  $A = (0 \dots 01)$

 



# 1-to-2 Decoder

- Input: 1-bit ( $A_0$ )
- Output: 2-bit ( $D_0$  &  $D_1$ )

Input	Output	
$A_0$	$D_1$	$D_0$
0	0	1
1	1	0

$$D_0 = A_0' = m_0$$

$$D_1 = A_0 = m_1$$

  



# 2-to-4 Decoder

- Input: 2-bit ( $A_0$  &  $A_1$ )
- Output: 4-bit ( $D_0, D_1, D_2, D_3$ )

Input		Output			
$A_1$	$A_0$	$D_3$	$D_2$	$D_1$	$D_0$
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

$$D_0 = A_1' A_0' = m_0 \quad D_2 = A_1 A_0' = m_2$$

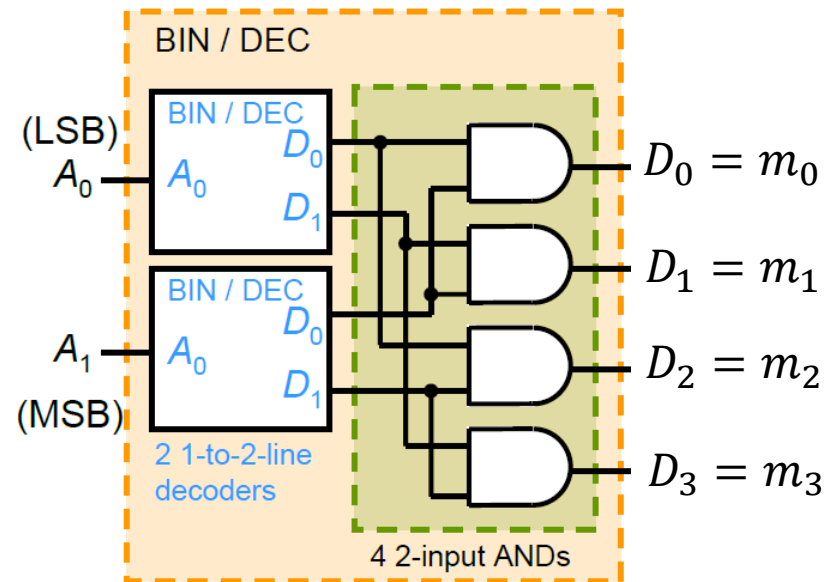 
$$D_1 = A_1' A_0 = m_1 \quad D_3 = A_1 A_0 = m_3$$



Active high decoder!
 
# 2-to-4 Decoder (Active Low decoder)

- Input: 2-bit ( $A_0$  &  $A_1$ )
- Output: 4-bit ( $D_0, D_1, D_2, D_3$ )





Input		Output			
$A_1$	$A_0$	$D_3$	$D_2$	$D_1$	$D_0$
0	0	1	1	1	0
0	1	1	1	0	1
1	0	1	0	1	1
1	1	0	1	1	1

$$D_0 = (A_1' A_0')'$$

$$D_1 = (A_1' A_0)'$$

$$D_2 = (A_1 A_0')'$$

$$D_3 = (A_1 A_0)'$$

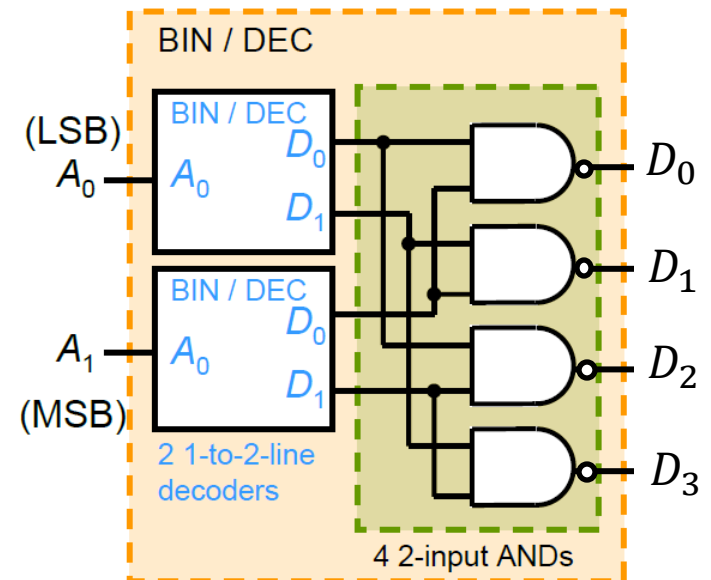 




# 3-to-8 Decoder

Input			Output							
$A_2$	$A_1$	$A_0$	$D_7$	$D_6$	$D_5$	$D_4$	$D_3$	$D_2$	$D_1$	$D_0$
0	0	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	1	0	0	0	0	0	0	1	0	0
0	1	1	0	0	0	0	1	0	0	0
1	0	0	0	0	0	1	0	0	0	0
1	0	1	0	0	1	0	0	0	0	0
1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0

Use simpler block to build higher order decoder

$$D_{2-4-0} = A_1' A_0' \quad D_{2-4-2} = A_1 A_0'$$
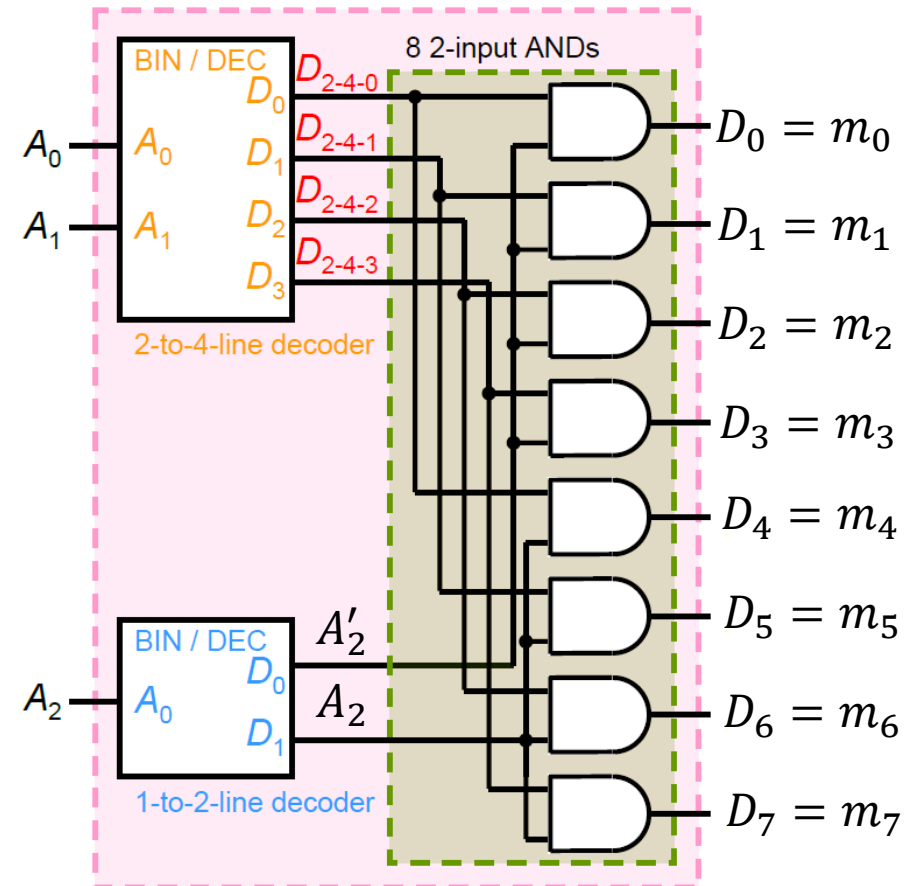
$$D_{2-4-1} = A_1' A_0 \quad D_{2-4-3} = A_1 A_0$$




# Decoder with Enable Input (2-to-4)

- Input: 3-bit ( $A_0, A_1, EN$ )
- Output: 4-bit ( $D_0, D_1, D_2, D_3$ )
- Decoder is activated only when  $EN = 1$


Input			Output			
$EN$	$A_1$	$A_0$	$D_3$	$D_2$	$D_1$	$D_0$
0	x	x	0	0	0	0
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	1	0	0	1	0	0
1	1	1	1	0	0	0

# Decoder with Enable Input (2-to-4)

$$\blacksquare D_i = EN \cdot m_i$$

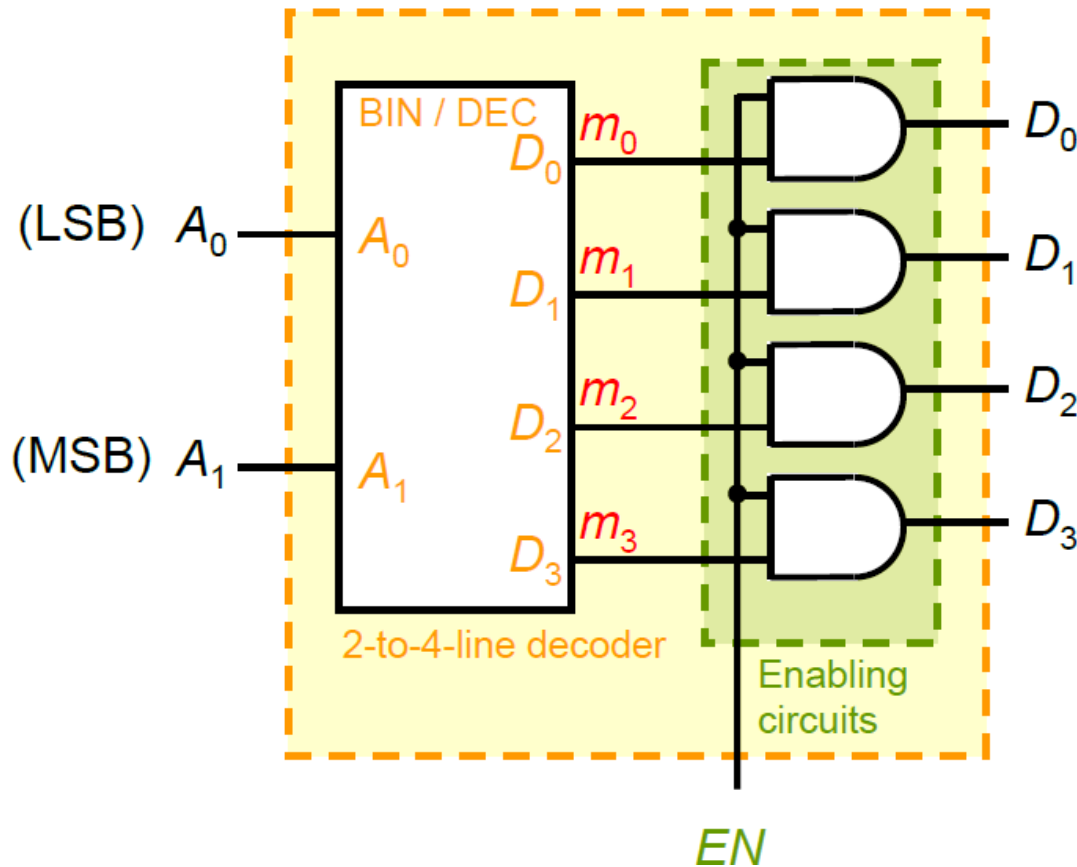


 
The corresponding symbol of 2-to-4-line decoder with enabling



# Decoder with Enable Input (2-to-4)

Input			Output			
$EN'$	$A_1$	$A_0$	$D_3$	$D_2$	$D_1$	$D_0$
1	x	x	0	0	0	0
0	0	0	0	0	0	1
0	0	1	0	0	1	0
0	1	0	0	1	0	0
0	1	1	1	0	0	0

Input			Output			
$EN'$	$A_1$	$A_0$	$D_3$	$D_2$	$D_1$	$D_0$
1	x	x	1	1	1	1
0	0	0	1	1	1	0
0	0	1	1	1	0	1
0	1	0	1	0	1	1
0	1	1	0	1	1	1

  

# Example





Given that

$$f(a, b, c) = \sum m(0, 2, 3, 7)$$

$$g(a, b, c) = \sum m(1, 3, 4, 6)$$

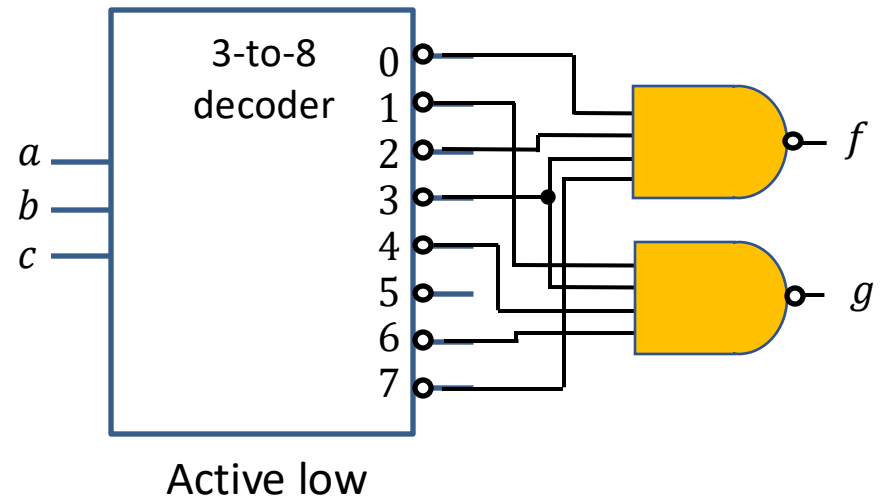 
Use (a) active high, and (b) active low 3-to-8 decoder to realize the functions.


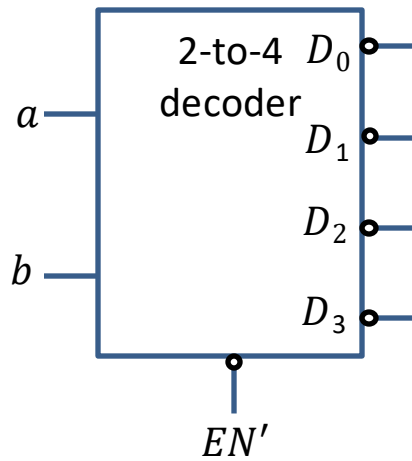
# Example


Build a 16-bit decoder using Active Low 2-to-4 decoders and mapped all the minterms.

- 16-bit = 16 outputs = 4 decoders
- Use 2 bits to control the 4 decoders via EN input





Input			Output			
$EN'$	$a$	$b$	$D_3$	$D_2$	$D_1$	$D_0$
1	x	x	1	1	1	1
0	0	0	1	1	1	0
0	0	1	1	1	0	1
0	1	0	1	0	1	1
0	1	1	0	1	1	1

# Example (4-variable K-map)

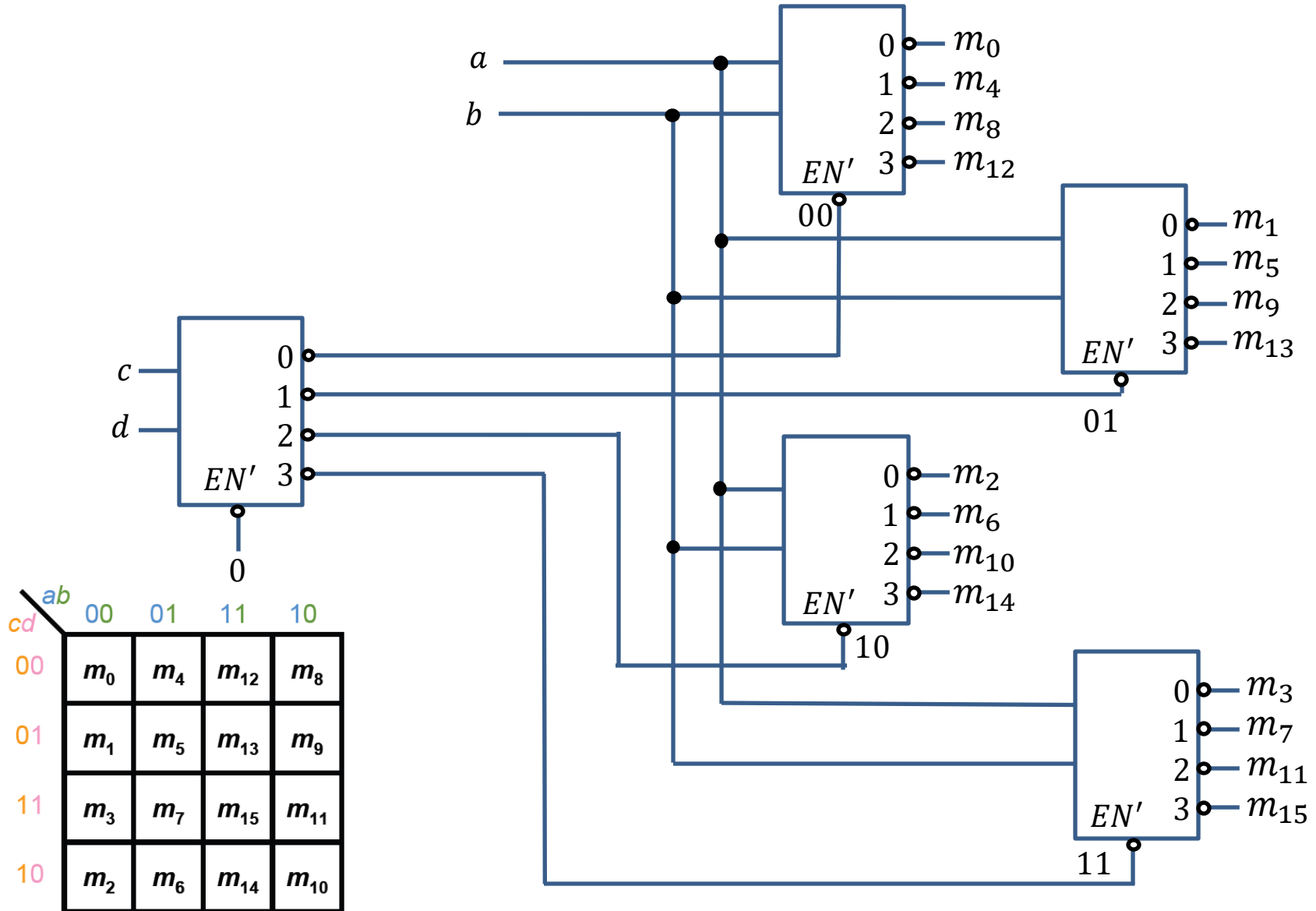
  
# Binary Encoder


- A functional block that performs the inverse operation of a decoder
- $m$  inputs and  $n$  outputs
- $m \leq 2^n$ , but usually  $m = 2^n$
- Only one input can be '1' at a time.




 
# Example (Octal-to-Binary Encoder)

- 8 inputs and 3 outputs
- Only one input can be '1' at a time



No	Input								Output		
	$D_7$	$D_6$	$D_5$	$D_4$	$D_3$	$D_2$	$D_1$	$D_0$	$A_2$	$A_1$	$A_0$
0	0	0	0	0	0	0	0	1	0	0	0
1	0	0	0	0	0	0	1	0	0	0	1
2	0	0	0	0	0	1	0	0	0	1	0
3	0	0	0	0	1	0	0	0	0	1	1
4	0	0	0	1	0	0	0	0	1	0	0
5	0	0	1	0	0	0	0	0	1	0	1
6	0	1	0	0	0	0	0	0	1	1	0
7	1	0	0	0	0	0	0	0	1	1	1


# Example (Octal-to-Binary Encoder)

No	Input								Output		
	$D_7$	$D_6$	$D_5$	$D_4$	$D_3$	$D_2$	$D_1$	$D_0$	$A_2$	$A_1$	$A_0$
0	0	0	0	0	0	0	0	1	0	0	0
1	0	0	0	0	0	0	1	0	0	0	1
2	0	0	0	0	0	1	0	0	0	1	0
3	0	0	0	0	1	0	0	0	0	1	1
4	0	0	0	1	0	0	0	0	1	0	0
5	0	0	1	0	0	0	0	0	1	0	1
6	0	1	0	0	0	0	0	0	1	1	0
7	1	0	0	0	0	0	0	0	1	1	1


$$A_0 = D_1 + D_3 + D_5 + D_7$$

$$A_1 = D_2 + D_3 + D_6 + D_7$$

$$A_2 = D_4 + D_5 + D_6 + D_7$$

 


# Exercise (Decimal-to-Binary Encoder)

 

Inputs										Outputs			
0	1	2	3	4	5	6	7	8	9	$A_3$	$A_2$	$A_1$	$A_0$
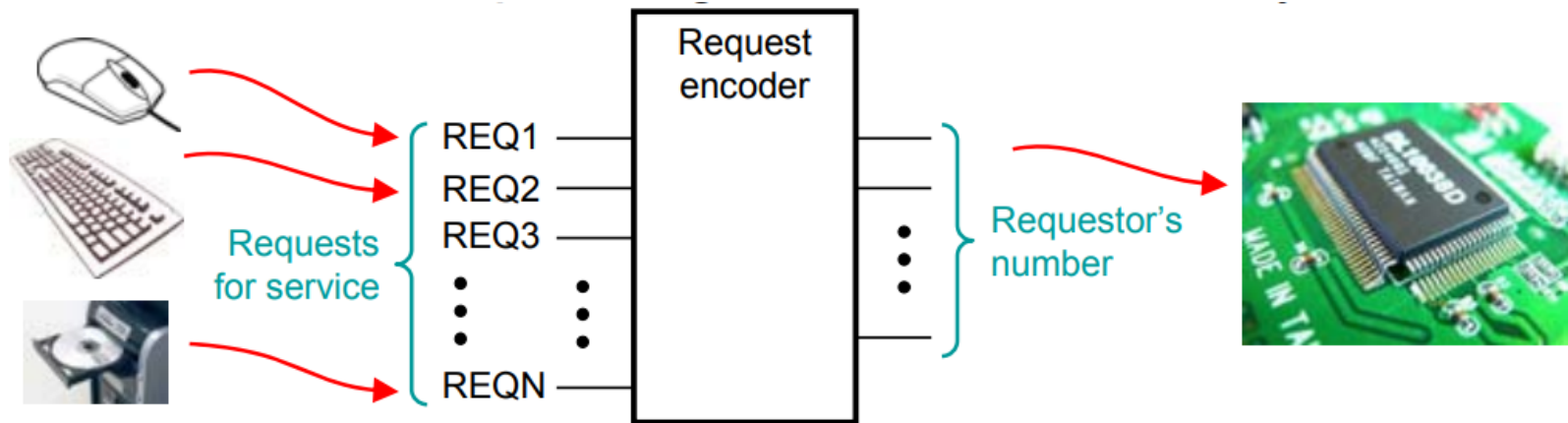
# Limitation

- Only one input can be active (*i.e.*, 1)
- If two or more inputs active simultaneously, the output produces an incorrect combination



# Solution – Priority Encoder

- Only one input can be active (*i.e.*, 1)
- If two or more inputs are active simultaneously, the output produces an incorrect combination
- **Solution:**
  - To resolve this ambiguity, introduce an **input priority**
  - Each input pin has a different priority
  - If two or more inputs are 1 at the same time, only consider input that has a higher priority
  - This kind of encoder is called a **priority encoder**


# Example (4-input Priority Encoder)

- Design a 4-input priority encoder whereby inputs with higher subscript numbers has higher priority.
- Add an extra output **V** stands for valid output.
- If all inputs are 0, **V** is 0; else **V** is 1.

Input				Output		
$D_3$	$D_2$	$D_1$	$D_0$	$A_1$	$A_0$	$V$
0	0	0	0	X	X	0
0	0	0	1	0	0	1
0	0	1	X	0	1	1
0	1	X	X	1	0	1
1	X	X	X	1	1	1


# Example (4-input Priority Encoder)

Input				Output		
$D_3$	$D_2$	$D_1$	$D_0$	$A_1$	$A_0$	$V$
0	0	0	0	X	X	0
0	0	0	1	0	0	1
0	0	1	X	0	1	1
0	1	X	X	1	0	1
1	X	X	X	1	1	1

 


$$A_1(D_3, D_2, D_1, D_0) = D_3 + D_2$$
 
$$A_0(D_3, D_2, D_1, D_0) = D_3 + D_2' D_1$$



$$V' = D_3' D_2' D_1' D_0'$$


$$V = D_3 + D_2 + D_1 + D_0$$

 

# Exercise (Active Low)


- Design an Active Low 4-input priority encoder whereby inputs with higher subscript numbers has higher priority.
- Output IDLE is High when all inputs are high.

Input				Output		
$I_3$	$I_2$	$I_1$	$I_0$	$A_1$	$A_0$	IDLE

 





# Exercise (Active Low)

 
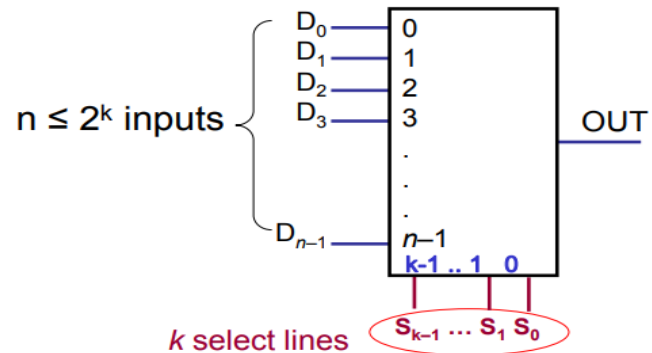 
# Multiplexer (MUX)



- Basically a digital switch
- Pass one of the inputs to the output
- Selected by the control input.




- $k$  control inputs
- $n$  data inputs,  $n \leq 2^k$
- 1 output
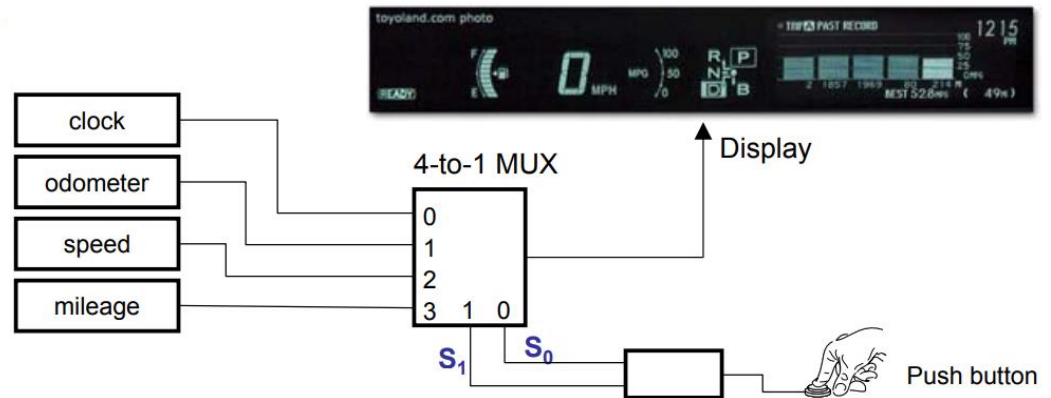 
# Applications

- In computers, select signals
- To implement different functions
- Trip controller in a car to choose different displays
- ...




# 2-to-1 Multiplexer (MUX)

 

Input			Output
$S$	$D_1$	$D_0$	
0	x	x	$D_0$
1	x	x	$D_1$

$$OUT = S'D_0 + SD_1$$

 

# 4-to-1 Multiplexer (MUX)

## ■ Specification:

■  $m = 4$


■  $n = \log_2 m = 2$

## ■ Formulation:

Inputs						Output
$I_0$	$I_1$	$I_2$	$I_3$	$S_1$	$S_0$	$Y$
x	x	x	x	0	0	$I_0$
x	x	x	x	0	1	$I_1$
x	x	x	x	1	0	$I_2$
x	x	x	x	1	1	$I_3$
 
## ■ Optimization:

■  $Y(I_0, I_1, I_2, I_3, S_1, S_0) =$   
 $S_1' S_0' I_0 + S_1' S_0 I_1 +$   
 $S_1 S_0' I_2 + S_1 S_0 I_3$



# Example

Realize the function  $f(w, x, y, z) = \sum m(1, 2, 5, 7, 9, 11, 13)$  using a 4-to-1 MUX

STEP 1: Plot the K-map

		$yz$			
		00	01	11	10
$wx$	00		1		1
	01		1	1	
	11		1		
	10		1	1	

# Example

STEP 2: Since 4-to-1 MUX has 2 control inputs, choose two variables for these inputs

$$w = S_1 \quad x = S_0$$

$w \backslash x$	$yz$ 00	01	11	10
00		1		1
01		1	1	
11		1		
10		1	1	

STEP 3:

$$f(w = 0, x = 0) = y'z + yz'$$

$$f(w = 0, x = 1) = z$$

$$f(w = 1, x = 1) = y'z$$

$$f(w = 1, x = 0) = z$$

# Example


$$w = S_1 \quad x = S_0$$

$$f(w = 0, x = 0) = y'z + yz'$$

$$f(w = 0, x = 1) = z$$

$$f(w = 1, x = 1) = y'z$$

$$f(w = 1, x = 0) = z$$

 

**Question:** How can we realize the function using 2-to-1 muxs?



# Exercise

Realize the function  $f(w, x, y, z) = \sum m(1, 2, 5, 7, 9, 11, 13)$  using a 2-to-1 MUX

$wx \backslash yz$	00	01	11	10
00				
01				
11				
10				

# Exercise

Realize the function  $f(w, x, y, z) = \sum m(1, 2, 5, 7, 9, 11, 13)$  using an 8-to-1 MUX


$wxyz$	$F$
0000	0
0001	1
0010	1
0011	0
0100	0
0101	1
0110	0
0111	1

$wxyz$	$F$
1000	0
1001	1
1010	0
1011	1
1100	0
1101	1
1110	0
1111	0



# Summary

With		2-to-1 Mux	4-to-1 Mux	8-to-1 Mux
wxyz	F	$S_0=w$	$S_1=w, S_0=x$	$S_2=w, S_1=x, S_0=y$
0000	0	$I_0=xz+y'z+x'yz'$	$I_0=y \oplus z$	$I_0=z$
0001	1			$I_1=z'$
0010	1			
0011	0			
0100	0		$I_1=z$	$I_2=z$
0101	1			
0110	0			$I_3=z$
0111	1			
1000	0	$I_1=x'z+y'z$	$I_2=z$	$I_4=z$
1001	1			
1010	0			$I_5=z$
1011	1			
1100	0		$I_3=y'z$	$I_6=z$
1101	1			
1110	0			$I_7=0$
1111	0			

# Cascading Multiplexers

 


Inputs						Output
$I_0$	$I_1$	$I_2$	$I_3$	$S_1$	$S_0$	$Y$
x	x	x	x	0	0	$I_0$
x	x	x	x	0	1	$I_1$
x	x	x	x	1	0	$I_2$
x	x	x	x	1	1	$I_3$

  

 
# Demultiplexer (DMUX)

- Reverse the function of MUX
- Route a single input to one of the many outputs
- Selected by the control input.


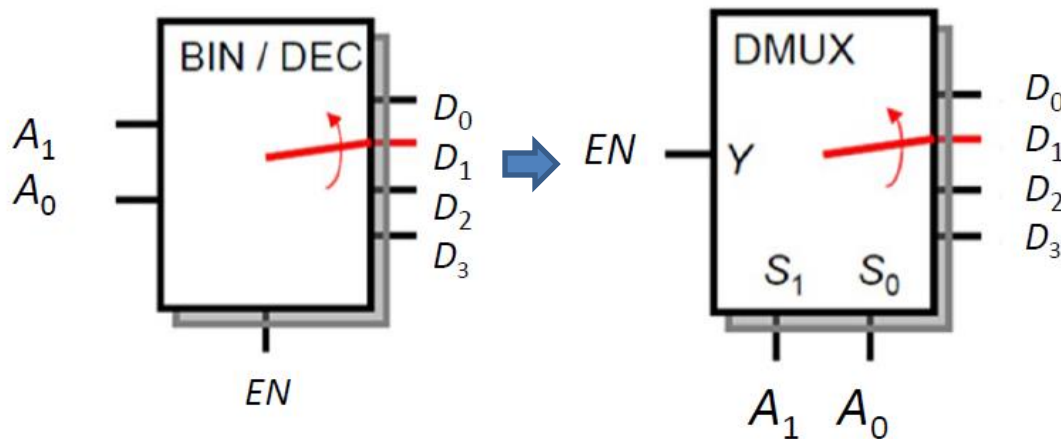
# Demultiplexer (DMUX)


- Remember the decoder with Enable?
- The decoder can perform demultiplexer if we take EN as the input line,  $A_i$  (input lines of decoder) as the selection inputs



Input	Select lines		Output			
$EN$	$A_1$	$A_0$	$D_3$	$D_2$	$D_1$	$D_0$
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	1	0	0	1	0	0
1	1	1	1	0	0	0
0	X	X	0	0	0	0

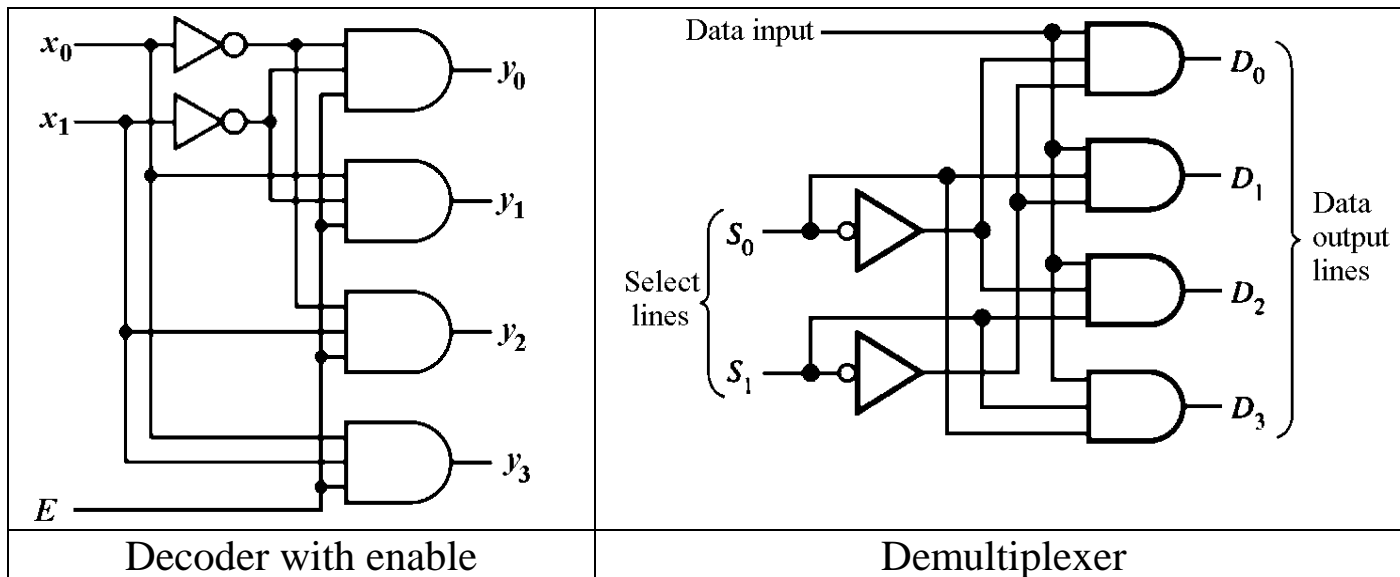
# Demultiplexer (DMUX)

- Can be realized using decoder with enable input
- Input lines -> Select/Control lines
- Enable -> Data input


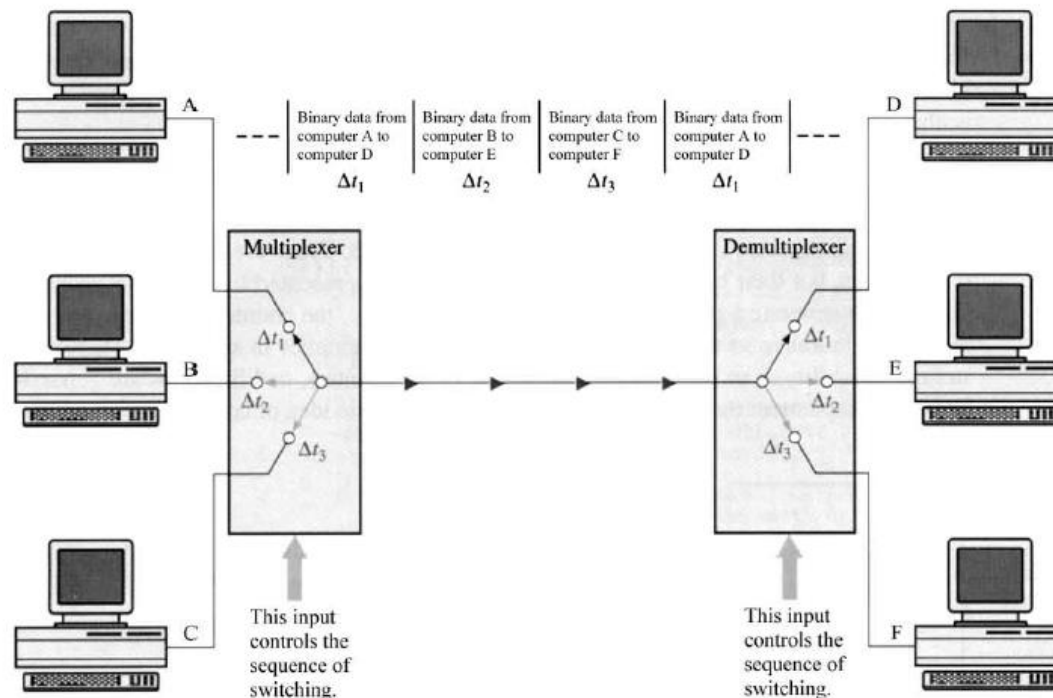
# Example of MUX & DMUX Application


- A MUX allows digital information from several sources to be routed onto a single line for transmission over that line to a common destination
- A DMUX basically reverses the multiplexing function






# Summary

Only 1 output is '1'

 


Binary Decoder

 


MUX

Only 1 input is '1'

 

Binary Encoder

1 input

 

DMUX

# Supplementary Information (For your own interest)

# Signed Numbers

- In ordinary arithmetic, a plus(+)/minus(-) sign is used to represent positive or negative numbers (+4 or -4)
- In digital electronic circuits, everything is represented with a bit (0 or 1)
- There are several ways to represent the signed binary numbers using a bit
- **Sign magnitude representation**: The **MSB** is a sign bit

e.g.      01101 = +13      11101 = -13  
            00000 = +0      10000 = -0

Disadvantages: (1) **2 patterns represent 0**,  
(2) **handle sign bit separately**

# One's Complement

- Positive numbers and the corresponding negative numbers **complement** each other
- Complement of 0 is 1; 1 is 0

e.g.      01101 = +13

10010 = -13

00000 = +0

11111 = -0

- Advantage: **Symmetry and easy**
- Disadvantage: **2 patterns to represent 0**

# Two's Complement

- Positive numbers and negative numbers are their corresponding **1's complement number + 1**

e.g.      $01101 = +13$

$10010 + 1 = 10011 = -13$

$00000 = +0$

$11111 + 1 = 00000 = +0$

- Advantages: **(1) Only 1 pattern represents 0**  
**(2) Handle sign bit as other bits**

# Value of a Two's Complement Number

- For an  $n$ -bit Two's Complement number  $a_{n-1}a_{n-2} \dots a_1 a_0$ , it has a value of

$$N = (-1)a_{n-1} \times 2^{n-1} + a_{n-2} \times 2^{n-2} + \dots + a_1 \times 2^1 + a_0 \times 2^0$$

e.g.  $-9_{10}$   
 $+9 =$  01001  
Invert bits: 10110  
Plus 1: 10111 =  $-9_{10}$   
Check:  $-16 + 0 + 4 + 2 + 1 = \underline{-9}$

# Binary Addition

- Two's complement numbers can be added in ordinary binary addition
- Any carry beyond the MSB will be discarded/ignored

$$\begin{array}{r} +3 \\ + +4 \\ \hline +7 \end{array} \quad \begin{array}{r} 0011 \\ + 0100 \\ \hline 0111 \end{array}$$

$$\begin{array}{r} +6 \\ + -3 \\ \hline +3 \end{array} \quad \begin{array}{r} 0110 \\ + 1101 \\ \hline 10011 \end{array}$$

$$\begin{array}{r} -2 \\ + -6 \\ \hline -8 \end{array} \quad \begin{array}{r} 1110 \\ + 1010 \\ \hline 11000 \end{array}$$

$$\begin{array}{r} +4 \\ + -7 \\ \hline -3 \end{array} \quad \begin{array}{r} 0100 \\ + 1001 \\ \hline 1101 \end{array}$$

# Range and Overflow

Unsigned	0000 → 1111	0 → 15
1's Complement	1000 → 1111	-7 → -0
	0000 → 0111	0 → 7
2's Complement	1000 → 1111	-8 → -1
	0000 → 0111	0 → 7

- For 4-bit binary, the range is
- Overflow occurs when the addition operation produces a result that exceed the range of the number system
- Overflow is detected when addition of 2 numbers with same signs produces a different sign

$$\begin{array}{r}
 -3 \quad 1101 \\
 + -6 \quad + 1010 \\
 \hline
 -9 \quad \textcolor{blue}{10111} = +7
 \end{array}$$

$$\begin{array}{r}
 +5 \quad 0101 \\
 + +6 \quad + 0110 \\
 \hline
 +11 \quad 1011 = -5
 \end{array}$$

$$\begin{array}{r}
 -8 \quad 1000 \\
 + -8 \quad + 1000 \\
 \hline
 -16 \quad \textcolor{blue}{10000} = +0
 \end{array}$$

$$\begin{array}{r}
 +7 \quad 0111 \\
 + +7 \quad + 0111 \\
 \hline
 +14 \quad 1110 = -2
 \end{array}$$




# Ripple Carry Subtractor

- How can we build an  $n$ -bit subtractor using  $n$  1-bit Full Adder?

$$(X_3X_2X_1X_0) + (-Y_3Y_2Y_1Y_0)$$

- How to represent negative binary number?

## 1) Sign-magnitude Format

 

## 2) Complement Format

# Sign-Magnitude Binary

- The MSB is a sign bit
  - 0 means positive “+”
  - 1 means negative “-”

For example:

4-bit system ( +5 = 0101; -5 = 1101)

Last 3 bits used for magnitude/value

# Problems

1) Incorrect result for the addition of negative number

e.g. Compute the sum of +5 and -3

$$+5 = 0101 \quad -3 = 1011$$

$$\text{Sum} = 10000 \text{ (???) not } 0010$$

2) Two zeros (0000 and 1000)

# Two-Complement (4-bit)

- 1) MSB (0 as positive and 1 as negative)
- 2) Negative number  $(-a) = 2^n - a = 16 - a$  for n-bit

Decimal	2's complement
0	0000
+1	0001
+2	0010
+3	0011
+4	0100
+5	0101
+6	0110
+7	0111

Decimal	2's complement
-1	1111
-2	1110
-3	1101
-4	1100
-5	1011
-6	1010
-7	1001
-8	1000

4-bit system

( +5 = 0101; -5= 1101) Sign-Magnitude Binary

( +5 = 0101; -5= 1011) Two's Complement Binary

# Easier Way to Find Negative Binary

- 1) Find the binary equivalent magnitude
- 2) Complement each bit
- 3) Add 1

	-5	-0
Step 1)	$5_{10} = 0101_2$	$0_{10} = 0000_2$
Step 2)	1010	1111
Step 3)	$\begin{array}{r} 1010 \\ +) \quad 1 \\ \hline 1011 \end{array}$	$\begin{array}{r} 1111 \\ +) \quad 1 \\ \hline \text{1} 0000 \end{array}$
Answer =	$1011_2$	$0000_2$

The carry bit  
can be ignored.

# 2-Complement Binary to Decimals

- 1) Complement each bit
- 2) Add 1 and find the magnitude
- 3) Add – to represent negative number

	1011 <sub>2</sub>
Step 1)	0100 <sub>2</sub>
Step 2)	$\begin{array}{r} 0100 \\ +) \quad 1 \\ \hline 0101 \end{array}$
Step 3)	0101 <sub>2</sub> = 5 <sub>10</sub>
Magnitude	5
Answer =	-5 <sub>10</sub>

# Addition using 2-Complement

■ (a)  $(-5) + 3$ , (b)  $(-5) + 7$

		(a)	(b)
Carries		0 1 1	1 1 1
Augend	- 5	1 0 1 1	- 5    1 0 1 1
Addend	<u>+ 3</u>	<u>0 0 1 1</u>	<u>+ 7</u> <u>0 1 1 1</u>
Sum	- 2	1 1 1 0	2 <del>1</del> 0 0 1 0

Carry out is ignored

The results are correct now!

# Binary Subtraction using 2-Complement

- $A - B = A + (-B) = A + (2\text{'s complement of } B)$   
e.g.  $5 - 7$

Input:  $5 = 0101$       and       $7 = 0111$

Step 1: Complement each bit       $7 = 1000$

Step 2: Add 1       $7 = 1001$

Step 3: Perform addition       $0101 + 1001 = 1110 (-2)$




# Ripple Carry Subtractor

- How can we build an  $n$ -bit subtractor using  $n$  1-bit Full Adder?

$$(X_3X_2X_1X_0) + (-Y_3Y_2Y_1Y_0)$$

Step1: Complement each bit

Step 2: Add 1

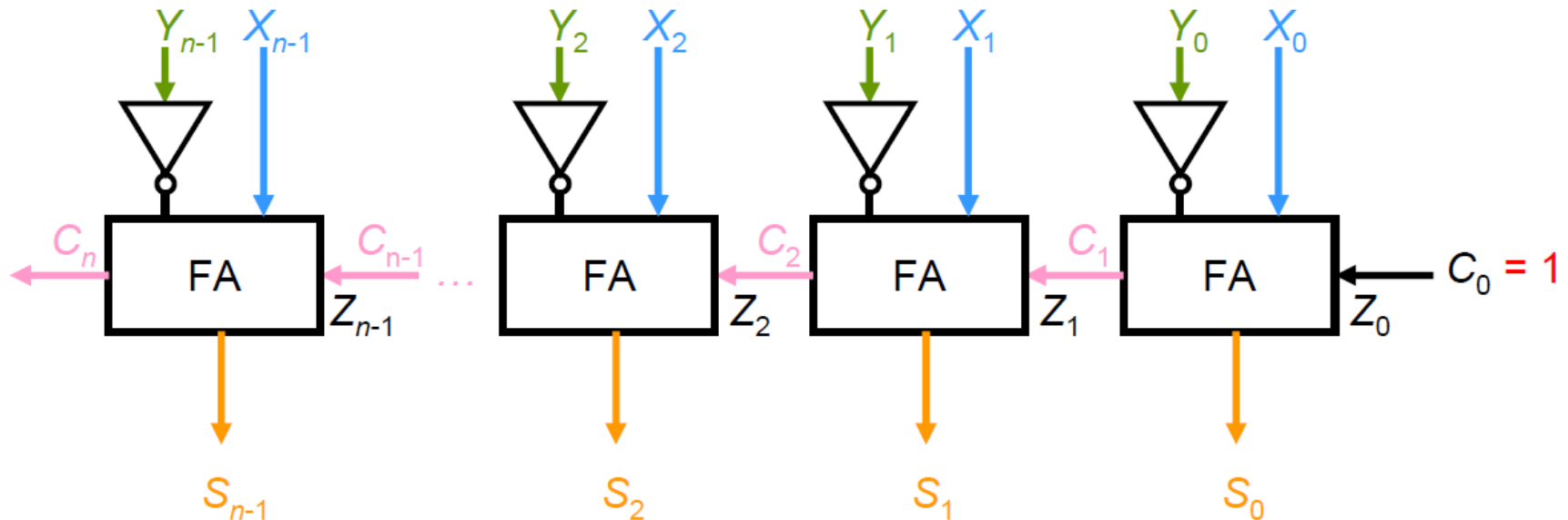

# Exercise

Build an  $n$ -bit adder + subtractor using  $n$  1-bit Full Adder, i.e. combine ripple carry adder and subtractor.


# Exercise

$y_i$	$M$	$f$
0	0	0
1	0	1
0	1	1
1	1	0

For addition,  $C_0 = 0$ ,  $Y_i = Y_i$

For subtraction,  $C_0 = 1$ ,  $Y_i = Y_i'$

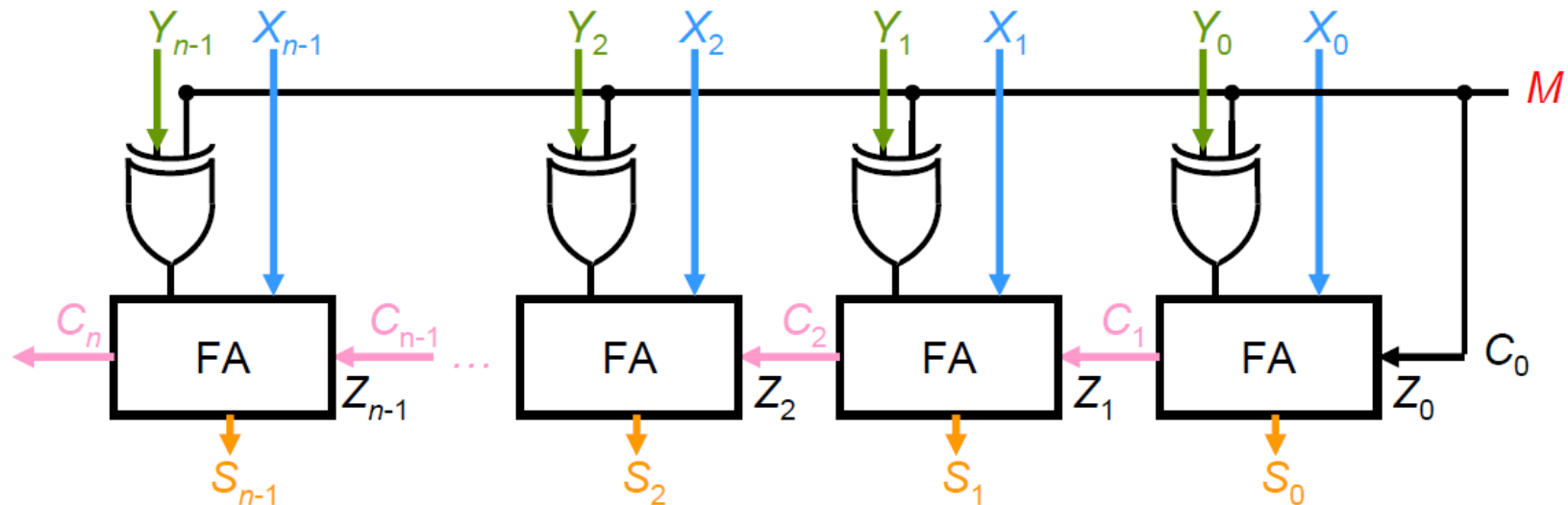- $M$  is the mode selection cable (0 means addition, 1 means subtraction)



- For addition ( $M = 0$ ),  $C_0 = 0$ ,  $Y_i = Y_i \oplus 0 = Y_i$
- For subtraction ( $M = 1$ ),  $C_0 = 1$ ,  $Y_i = Y_i \oplus 1 = Y_i'$