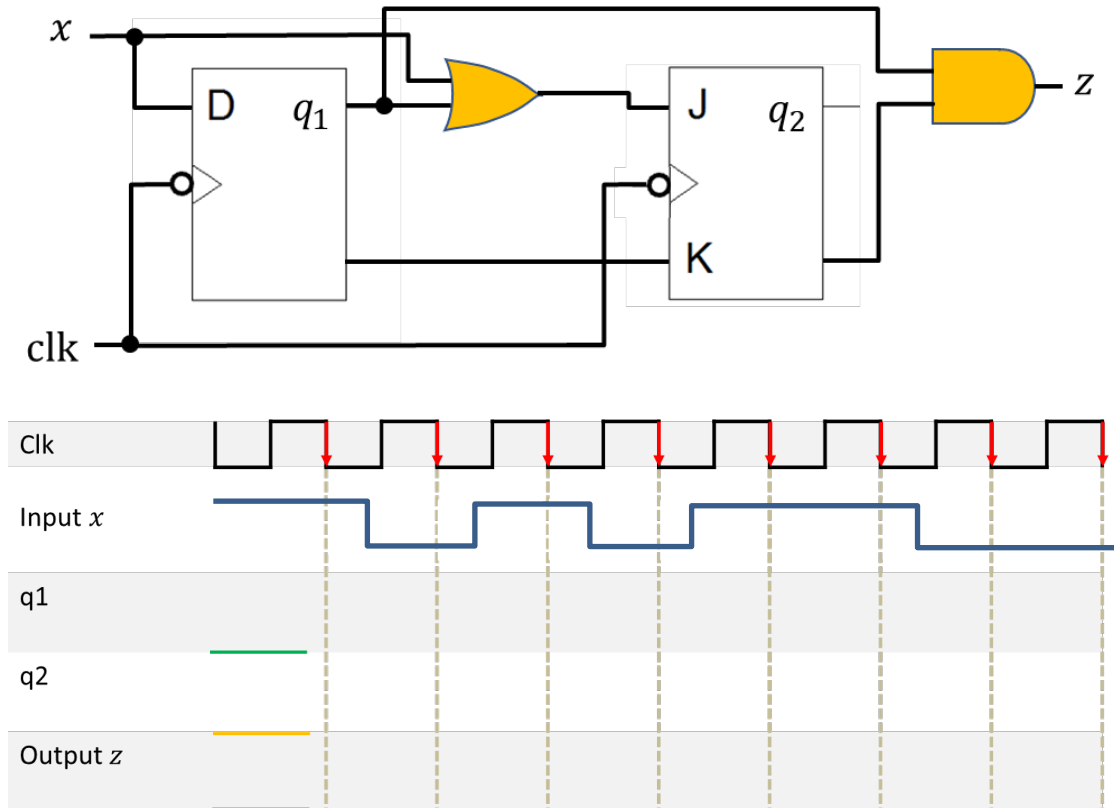


**EE 2000 Logic Circuit Design**  
Semester A 2024/25

Tutorial 9

1. For the following circuits, (a) determine the state table and state diagram (calling the states 00, 01, 10, 11), (b) complete the timing diagram as shown.



2. Design a Mealy system using D-FFs with one input  $x$  and one output  $z$  such that  $z = 1$  if  $x$  has been 1 for exactly two consecutive clock-times. A sample input/output trace for such a system is shown below.

$x$	0	1	1	1	1	0	1	1	0	0	1	0
$z$	0	0	0	0	0	0	0	0	1	0	0	0

3. Design a Moore system with one input  $x$  and one output  $z$  such that  $z = 1$  if a sequence of "101" has been detected (overlapping is allowed). A sample input/output trace for such a system is shown below.

$x$	0	1	0	1	1	0	1	0	1	0	0	0
$z$	0	0	0	0	1	0	0	1	0	1	0	0

4. Use the partitioning method to minimize the number of states in the state table shown.

Present state	Next state		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
A	F	B	0	0
B	D	C	0	0
C	F	E	0	0
D	G	A	1	0
E	D	C	0	0
F	F	B	1	1
G	G	H	0	1
H	G	A	1	0